
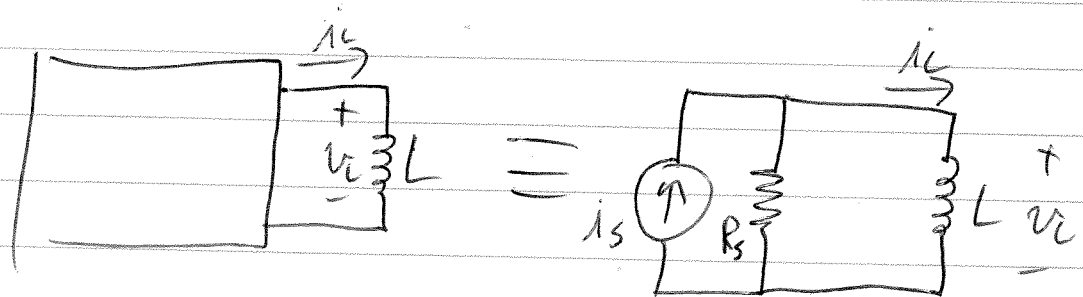


Read + Do examples + Exercises 6-13, 14, + 15.

We're going to move on to Ch. 7 -  
1<sup>st</sup> + 2<sup>nd</sup> order ckt's. Many things, even  
in the digital world today, still are  
governed or constrained by 1<sup>st</sup> + 2<sup>nd</sup> order  
phenomena, such as RC Time Constants, that  
limit our computer clock speed.

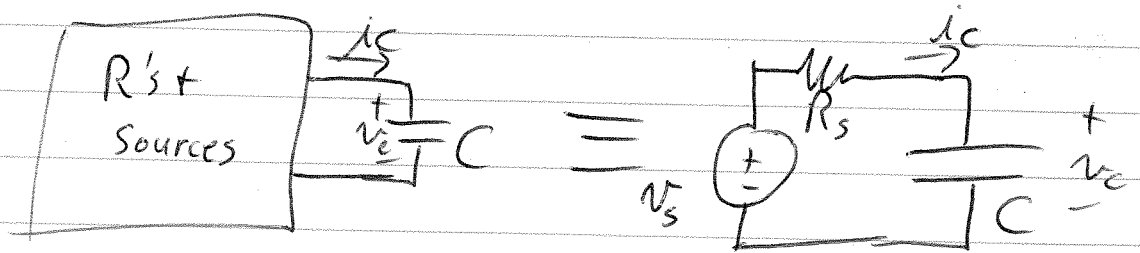First Order Ckts contain one C or one L,  
and an equivalent resistance:



This is one reason we spent so much time learning  
to find Thev + Norton Equivalents

Look at RC:

$$\text{KVL} + \Omega\text{'s Law: } R_s i_c + v_c - v_s = 0$$

$$R_s \left( C \frac{dv_c}{dt} \right) + v_c = v_s$$

$$R_s C \frac{dv_c}{dt} + v_c = v_s$$

$$\text{or } \frac{dv_c}{dt} + \frac{1}{R_s C} v_c = \frac{1}{R_s C} v_s \quad \text{in "standard form"}$$

Inhomogeneous, <sup>1<sup>st</sup></sup> order, <sup>Linear</sup> DE w/ constant coeff's.  $\tau = \text{Time Constant} = R_s C$

$v_c(t)$  is known as the "State Variable" because it determines the energy stored in the capacitor.

$v_s$  is the input +  $v_c$  is the response.

Look at RL:

$$-i_s(t) + \frac{v_L(t)}{R_s} + i_L(t) = 0$$

$$\frac{1}{R_s} L \frac{di_L}{dt} + i_L(t) = +i_s(t)$$

$$\frac{di_L(t)}{dt} + \frac{R_s}{L} i_L(t) = \frac{R_s}{L} i_s(t)$$

$$\frac{di_L}{dt}(t) + \frac{1}{L/R_s} i_L = \frac{1}{L/R_s} i_s(t)$$

$$\frac{di_L}{dt}(t) + \frac{1}{\tau} i_L(t) = \frac{1}{\tau} i_s(t) \quad \tau = L/R_s$$

Here  $i_s$  is the state variable.

$i_L$  is the response to  $i_s$  as the input.

~~Insert 207~~

To solve 1<sup>st</sup> order equations we need to ~~have~~ ~~known~~ know the response at at least one time, usually taken to be the Initial Value, or ~~Initial~~ Initial Condition, at  $t=0$  (or whenever we "start" the ckt by switching something on, or off, or to a different value.)

First, note that the RHS of these equations can be thought of as:

$$\frac{1}{R_s C} v_s(t) + 0$$

$$\text{or } \frac{R_s}{L} v_s(t) + 0$$

and we can think of the variables  $v_c$  &  $i_L$  as

$$v_c(t) = v_{cf}(t) + v_{cn}(t), \text{ called the natural and forced responses.}$$

and  $i_L(t) = i_{Lp}(t) + i_{Ln}(t)$

→ Insert (208a)

The derivatives and constants distribute over the sums, so we can separate them as:

$$\frac{dv_{cf}}{dt} + \frac{1}{\tau} v_{cf} = \frac{1}{\tau} v_{cs} + \frac{dv_{cn}}{dt} + \frac{1}{\tau} v_{cn} = 0$$

and  $\frac{di_{Lf}}{dt} + \frac{1}{\tau} i_{Lf} = \frac{1}{\tau} i_s + \frac{di_{Ln}}{dt} + \frac{1}{\tau} i_{Ln} = 0$

called the  
Forced Response

Homogeneous, 1<sup>st</sup> Order

DE's w/ Constant Coeff's.

called the Zero-Input Response, or  
Natural Response

Solutions are of form

$$v_{cn} = K e^{st}$$

$$\text{and } i_{Ln} = K e^{st}$$

$$\frac{dv_{cn}}{dt} = s K e^{st}$$

$$\frac{di_{Ln}}{dt} = s K e^{st}$$

Substitute:

$$s K e^{st} + \frac{1}{\tau} K e^{st} = 0 \quad \text{and} \quad s K e^{st} + \frac{1}{\tau} K e^{st} = 0$$

$$(s + \frac{1}{\tau}) K e^{st} = 0$$

$$(s + \frac{1}{\tau}) K e^{st} = 0$$

3 possibilities

same!

$K=0$  — trivial solution

$e^{st}=0$  impossible except for  $st=-\infty$

We can think of this like Super position, the output due to both is the sum of the response due to one plus the response due to the other. Further, the nature of the response due to an input is the same as the nature of the input (ie: a constant input leads to a constant output.) This is often called a "particular response."

(209)

or  $(s + \frac{1}{\tau}) = 0$  The characteristic equation

$$\boxed{s = -\frac{1}{\tau}}$$

So  $v_c = K e^{-t/\tau}$  or  $i_L = K e^{-t/\tau}$   
 $\tau = R_s C$   $\tau = L/R_s$

there is no forcing function  $v_s$  or  $i_s = 0$  ~~the and~~

If we ~~are~~ are given or can analyze the

ckt to find  $v_c(0)$  or  $i_L(0)$  (IC's of the State Variables)

then we can write:

$$\underline{v_c(0) = K e^{-0} = K} \quad \text{or} \quad \underline{i_L(0) = K e^{-0} = K}$$

So now we know

$$v_c(t) = v_c(0) e^{-t/\tau} \quad \text{or} \quad i_L(t) = i_L(0) e^{-t/\tau}$$

$\uparrow$  a constant usually called  $V_0$ 
 $\uparrow$  called  $I_0$

$$v_c(t) = V_0 e^{-t/\tau}$$

$$i_L = I_0 e^{-t/\tau}$$