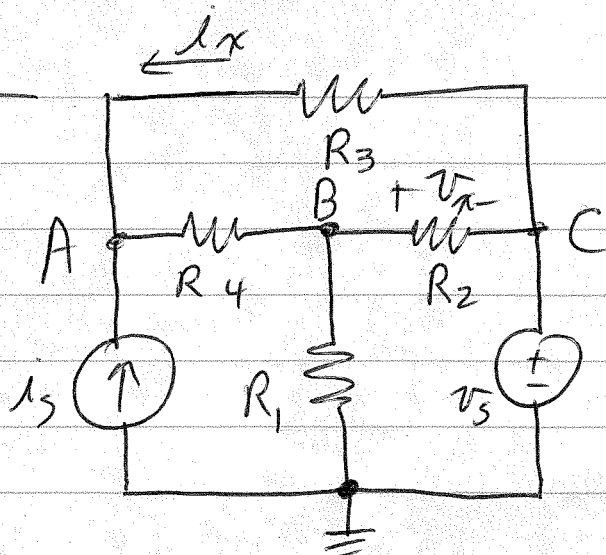


# 2014- HW 3 Solutions

(1)

3-6



a) Choose ground and write N-V equations.

Answer: Choose "bottom" node as ground  
to eliminate 1 eqn. Label nodes as  
shown.  $V_C = v_5$

$$(A) \quad \frac{V_A - V_B}{R_4} - i_s + \frac{V_A - V_C}{R_3} = 0$$

$$\left(\frac{1}{R_3} + \frac{1}{R_4}\right)V_A - \frac{1}{R_4}V_B = i_s + \frac{v_5}{R_3}$$

$$(B) \quad \frac{V_B - V_A}{R_4} + \frac{V_B}{R_1} + \frac{V_B - V_C}{R_2} = 0$$

$$-\frac{1}{R_4}V_A + \left(\frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2}\right)V_B = \frac{v_5}{R_2}$$

(2)

b.) Solve for  $v_x + i_x$  when  $R_1 = R_2 = R_3 = R_4 = 10k\Omega$ ,  
~~and~~  $v_s = 25V$ , and  $i_s = 1mA$ .

Answer: First, write  $v_x + i_x$  in terms of  $V$ 's:

$$v_x = V_B - V_C = \underline{V_B - v_s}$$

$$i_x = \frac{V_C - V_A}{R_3} = \underline{\frac{v_s - V_A}{R_3}}$$

So we need to solve for both  $V_A + V_B$ .

First let  $R_1 = R_2 = R_3 = R_4 = \underline{R}$  and simplify:

$$\textcircled{A} \quad \frac{2}{R}V_A - \frac{1}{R}V_B = i_s + \frac{v_s}{R}$$

$$2V_A - V_B = Ri_s + v_s$$

$$\textcircled{B} \quad -\frac{1}{R}V_A + \left(\frac{3}{R}\right)V_B = \frac{v_s}{R}$$

$$-V_A + 3V_B = v_s$$

$$3V_B = v_s + V_A$$

$$V_B = \frac{1}{3}(v_s + V_A)$$

$$2V_A - \left(\frac{1}{3}\right)(v_s + V_A) = Ri_s + v_s$$

$$2V_A - \frac{1}{3}V_A = Ri_s + v_s + \frac{1}{3}v_s$$

$$\frac{5}{3}V_A = Ri_s + \frac{4}{3}v_s$$

$$V_A = \frac{3}{5}Ri_s + \frac{4}{5}v_s$$

(3)

Now substitute values:


$$V_A = \frac{3}{5}(10k\Omega)1mA + \frac{4}{5}(25V) \\ = 6V + 20V = \underline{\underline{26V}}$$

$$V_B = \frac{1}{3}(25V + 26V) = \frac{51}{3}V = \underline{\underline{17V}}$$

$$\text{So } v_x = V_B - 25V = 17V - 25V = \underline{\underline{-8V}}$$

$$i_x = \frac{25V - 26V}{10k\Omega} = \frac{-1V}{10k\Omega} = \underline{\underline{-0.1mA}}$$

(4)

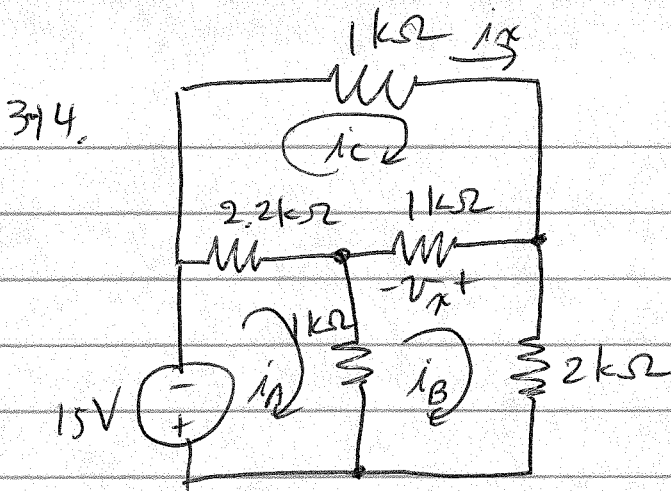

a) Formulate MC eqn's + put in matrix form.

$$\textcircled{A} \quad 2.2k\Omega(i_A - i_C) + 1k\Omega(i_A - i_B) + 15V = 0$$

$$3.2k\Omega i_A - 1k\Omega i_B - 2.2k\Omega i_C = -15V$$

$$\textcircled{B} \quad 1k\Omega(i_B - i_C) + 2k\Omega i_B + 1k\Omega(i_B - i_A) = 0$$

$$-1k\Omega i_A + 4k\Omega i_B - 1k\Omega i_C = 0$$

$$\textcircled{C} \quad 1k\Omega i_C + 1k\Omega(i_C - i_B) + 2.2k\Omega(i_C - i_A) = 0$$

$$-2.2k\Omega i_A - 1k\Omega i_B + (4.2k\Omega) i_C = 0$$

Matrix form:

$$\begin{pmatrix} 3.2k\Omega & -1k\Omega & -2.2k\Omega \\ -1k\Omega & 4k\Omega & -1k\Omega \\ -2.2k\Omega & -1k\Omega & 4.2k\Omega \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} -15V \\ 0 \\ 0 \end{pmatrix}$$

(5)

b) Solve by Cramer's Rule.

$\Delta$  = determinant of Resistance Matrix

$$= 3.2k \left( (4k)(4.2k) - (-1k)(-1k) \right)$$

$$- (-1k)(-1k)(4.2k) - (-2.2k)(1k)$$

$$+ (-2.2k)(-1k)(-1k) - (-2.2k)(4k)$$

$$\Delta = 3.2k(16.8k^2 - 1k^2) + 1k(-4.2k^2 - 2.2k^2) - 2.2k(1k^2 + 8.8k^2)$$

$$= 3.2k(15.8k^2) + 1k(-6.4k^2) - 2.2k(9.8k^2)$$

$$= 50.56 k^3 - 6.4k^3 - 21.56 k^3$$

$$\Delta = 22.6 k^3$$

$$\Delta_A = (-15V) \left[ (4k)(4.2k) - (-1k)(-1k) \right] - (-1k) \left[ 0 - 0 \right] + (-2.2k) \left[ 0 - 0 \right]$$

$$= -15V \left[ 16.8k^2 - 1k^2 \right] = -15V \left[ 15.8k^2 \right]$$

$$\Delta_B = 3.2k \left[ 0 - 0 \right] - (-15V) \left[ (-1k)(4.2k) - (-2.2k)(-1k) \right] + (-2.2k) \left[ 0 - 0 \right]$$

$$= 15V \left[ -4.2k^2 - 2.2k^2 \right] = 15V \left[ -6.4k^2 \right]$$

$$\Delta_C = 3.2k \left[ 0 - 0 \right] - (-1k) \left[ 0 - 0 \right] + (-15V) \left[ (-1k)(1k) - (-2.2k)(4k) \right]$$

$$= (-15V) \left[ -1k^2 + 8.8k^2 \right] = -15V \left[ 7.8k^2 \right]$$

$$\text{So } i_A = \frac{\Delta_A}{\Delta} = \frac{-15V \left[ 15.8k^2 \right]}{22.6 k^3 \Omega^3} = \frac{-15V}{k\Omega} \frac{15.8}{22.6} =$$

$$i_A = -10.5 \text{ mA}$$

(6)

$$i_B = \frac{A_B}{\Delta} = \frac{-15V(6.4k^2\Omega^2)}{22.6k^3\Omega^3}$$

$$\underline{i_B = -4.25 \text{ mA}}$$

$$i_C = \frac{A_C}{\Delta} = \frac{-15V(9.8k^2\Omega^2)}{22.6k^3\Omega^3}$$

$$\underline{i_C = -6.50 \text{ mA}}$$


c) Use these to find  $v_x + i_x$ :

$$\begin{aligned} \text{Answer: } v_x &= 1k\Omega(i_C - i_B) \\ &= 1k\Omega(-6.50\text{mA} - (-4.25\text{mA})) \end{aligned}$$

$$\underline{v_x = -2.25V}$$

$$\underline{i_x = i_C = -6.50 \text{ mA}}$$

3-16

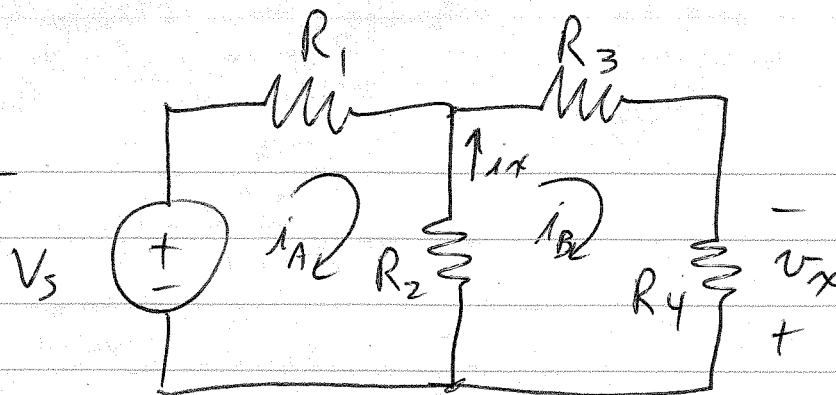

a) Formulate MC eqns + write as matrix.

Answer: (A)  $R_1 i_A + R_2 (i_A - i_B) - V_s = 0$   
 $(R_1 + R_2) i_A - R_2 i_B = V_s$

(B)  $R_3 i_B + R_4 i_B + R_2 (i_B - i_A) = 0$   
 $-R_2 i_A + (R_2 + R_3 + R_4) i_B = 0$

Matrix Form:

$$\begin{pmatrix} (R_1 + R_2) & -R_2 \\ -R_2 & (R_2 + R_3 + R_4) \end{pmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} V_s \\ 0 \end{pmatrix}$$

b) Use these to find  $v_x + i_x$ .

Solve for  $i_A + i_B$  by Cramer's Rule:

$$\begin{aligned} \Delta &= (R_1 + R_2)(R_2 + R_3 + R_4) - (-R_2)(-R_2) \\ &= (R_1 + R_2)(R_2 + R_3 + R_4) - R_2^2 \\ &= R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2^2 + R_2 R_3 + R_2 R_4 - R_2^2 \end{aligned}$$

(8)

$$\Delta_A = V_s(R_2 + R_3 + R_4) - \cancel{R_2}$$

$$= V_s(R_2 + R_3 + R_4)$$

$$\Delta_B = 0 - (-R_2)(V_s)$$

$$= R_2 V_s$$

$$i_A = \frac{\Delta_A}{\Delta} = \frac{(R_2 + R_3 + R_4)}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4} V_s$$

$$i_B = \frac{R_2}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4} V_s$$

$$v_x = R_4(-i_B) = -\frac{R_4(R_2 \cancel{R_3} \cancel{R_4})}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4} V_s$$


$$i_x = i_B - i_A$$

$$i_x = \frac{R_2 - (R_2 + R_3 + R_4)}{\Delta} V_s$$

$$i_x = \frac{-R_3 - R_4}{\Delta} V_s$$



(9)

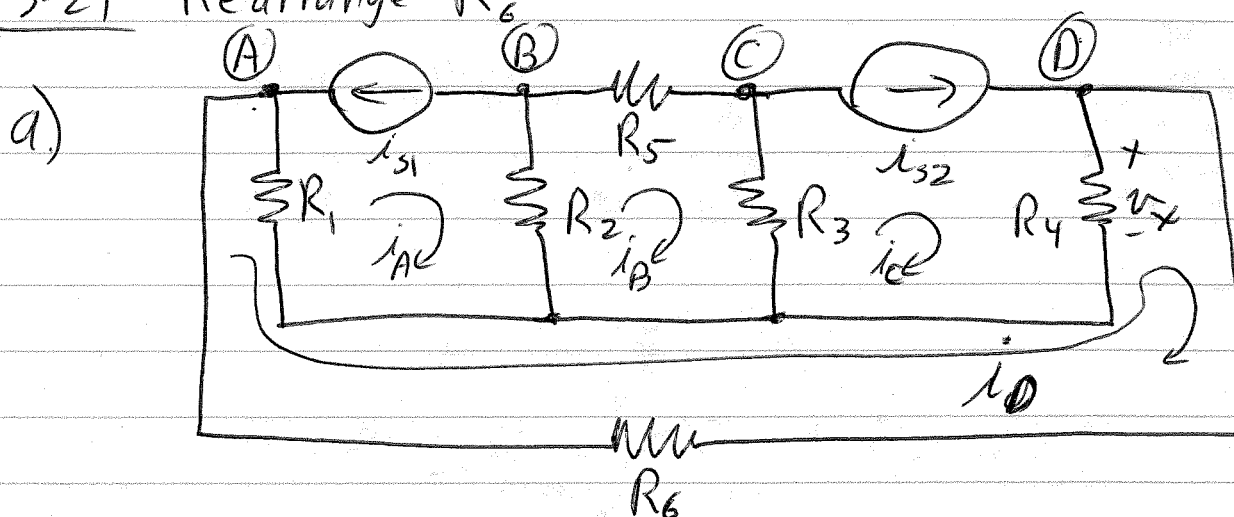3-21 Rearrange  $R_6$ :

b) Mesh-Current Eqn's:

$$\underline{i_A = -i_{s1}}$$

$$\underline{i_C = i_{s2}}$$

$$\textcircled{B} \quad R_5 i_B + R_3 (i_B - i_C) + R_2 (i_B - i_A) = 0$$

$$\underline{(R_5 + R_3 + R_2) i_B = R_3 i_C + R_2 i_A = R_3 i_{s2} - R_2 i_{s1}}$$

$$\textcircled{D} \quad R_1 (i_D - i_A) + R_4 (i_D - i_C) + R_6 i_D = 0$$

$$\underline{(R_1 + R_4 + R_6) i_D = R_1 i_A + R_4 i_C = -R_1 i_{s1} + R_4 i_{s2}}$$

c) Solve for  $v_x$  when  $R_1 = R_2 = R_3 = R_4 = 4\text{ k}\Omega$ ,  
 $R_5 = R_6 = 2\text{ k}\Omega$ ,  $i_{s1} = 80\text{ mA}$ ,  $i_{s2} = 40\text{ mA}$ .

$v_x = R_4(i_c - i_D)$  so we need to solve for  $i_D$ :


$$\begin{aligned}
 i_D &= \frac{-R_1 i_{s1} + R_4 i_{s2}}{R_1 + R_4 + R_6} \\
 &= \frac{-(4k)(80mA) + (4k)(40mA)}{4k + \cancel{4k} + 2k} \\
 &= \frac{-320V + 160V}{10k} = \frac{-160V}{10k\Omega} = \underline{\underline{-16mA}}
 \end{aligned}$$

$$\begin{aligned}
 \text{So } v_x &= 4k\Omega(40mA + \frac{16mA}{\cancel{12.8mA}}) \\
 &= 4k\Omega(\frac{56mA}{\cancel{12.8mA}}) = \underline{\underline{224V}}
 \end{aligned}$$

(Answer in back of book gives 224V.

I reviewed equations parts a & b are same  
~~different~~ simulated it in CircuitLab & got ~~224V~~  
 224.84V.)

(11)

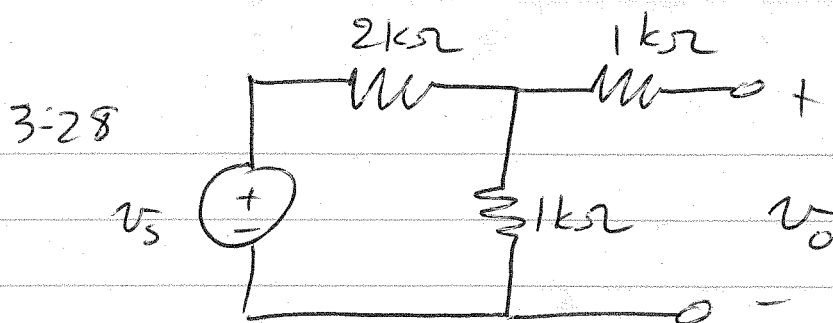


Find proportionality constant  $K = v_o/v_s$ .

Answer: No current thru  $1k\Omega$  on top, so  
no voltage drop, so

$$v_o = \frac{1k\Omega}{1k\Omega + 2k\Omega} v_s \text{ by Voltage Div.}$$


$$v_o = \frac{1}{3} v_s$$
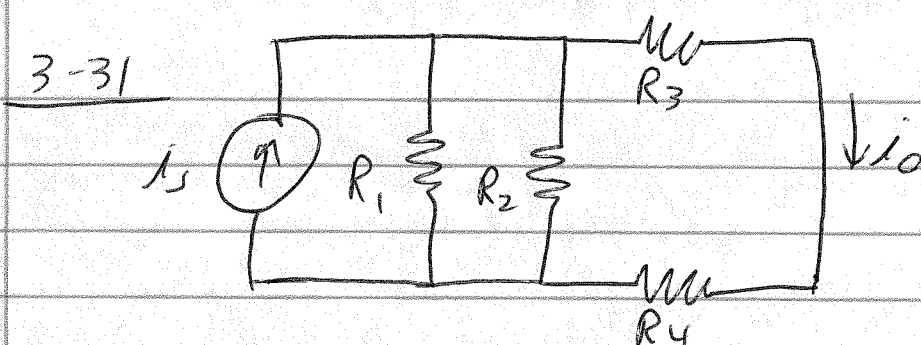
$$\text{or } \underline{\underline{K = \frac{1}{3}}}$$



Find  $k = \frac{i_o}{i_s}$  in this ckt.

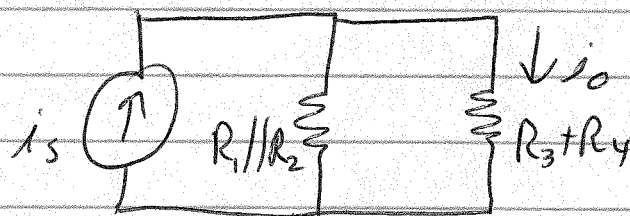Answer:  $i_o$  is current thru  $R_3 + R_4$  in series, Combine  $R_1 + R_2$  in parallel & get:




By Current Division,

$$i_o = \frac{R_1 // R_2}{R_1 // R_2 + (R_3 + R_4)} i_s$$

or

$$k = \frac{i_o}{i_s} = \frac{\frac{R_1 R_2}{R_1 + R_2}}{\frac{R_1 R_2}{R_1 + R_2} + (R_3 + R_4)}$$

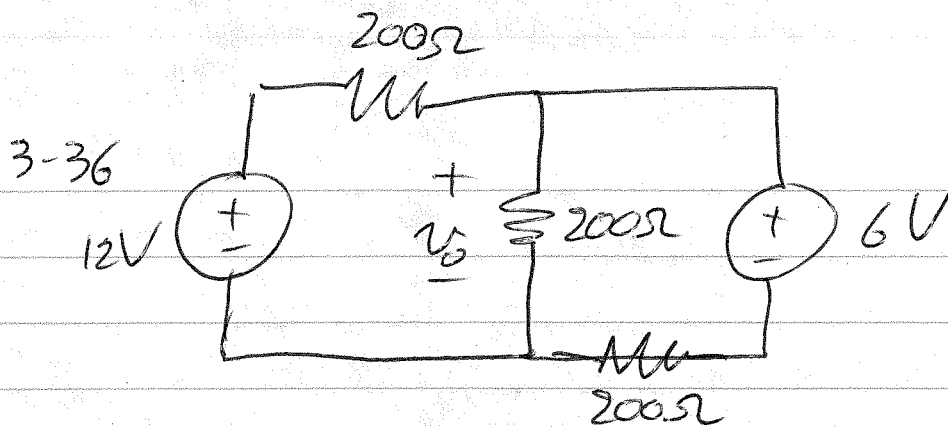
$$k = \frac{\frac{R_1 R_2}{(R_1 + R_2)}}{\frac{R_1 R_2 + (R_1 + R_2)(R_3 + R_4)}{(R_1 + R_2)}} = \frac{R_1 R_2}{R_1 R_2 + (R_1 + R_2)(R_3 + R_4)}$$



Use Superposition to find  $v_o$ .

Answer:

a) Turn off 6V src:

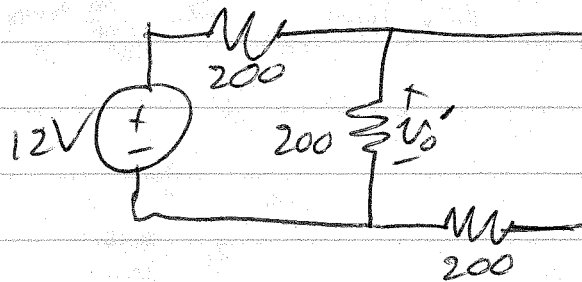


$v_o'$  is Voltage across parallel R's;  $R_{eq} = 100\Omega$

$$v_o' = \frac{100\Omega}{100\Omega + 200\Omega} 12V \text{ by Voltage Div.}$$

$$= \frac{1}{3} 12V = \underline{\underline{4V}}$$

Turn off 12V src:

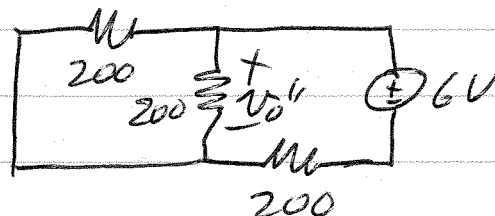

$$\text{Again: } v_o'' = \frac{100}{100 + 200} 6V = \frac{1}{3} (6V) = \underline{\underline{2V}}$$

$$\text{So } v_o = v_o' + v_o'' = 4V + 2V = \underline{\underline{6V}}$$