

Introduction to Audio and Music Engineering

Lecture 14

Topics:

- Complex number review
- Complex exponential function
- Phasors
- Capacitors
- RC circuits
- High-pass and Low-pass filters

Complex Numbers

The need for imaginary numbers ...

$$x^2 - 4 = 0 \quad \rightarrow \quad x^2 = 4, \quad \text{so } x = +2 \text{ and } x = -2 \text{ are solutions}$$

How about: $x^2 + 4 = 0$

$$x^2 = -4 = (-1)(4) \quad \text{so } x = \sqrt{-1} \sqrt{4} \quad x = \pm 2 \sqrt{-1} \quad x = \pm 2j$$

$$j = \sqrt{-1}$$

$$j^1 = j \quad j^2 = -1 \quad j^3 = -j \quad j^4 = 1 \quad j^5 = j \quad \dots$$

Complex Number: $z = x + j y$

↑
real
part

↑
imaginary
part

$$\text{Re}(z) = x$$

$$\text{Im}(z) = y$$

Complex Number Arithmetic


Addition: $(a + jb) + (c + jd) = (a+c) + j(b+d)$

Multiplication: $(a + jb) \times (c + jd) = (ac-bd) + j(bc+ad)$

Complex Conjugate: $(a + jb) \xrightarrow{cc} (a - jb)$ $z = a + jb$ $z^* = a - jb$

$$|z|^2 = z \times z^* = a^2 + b^2$$

Graphing Complex Numbers:

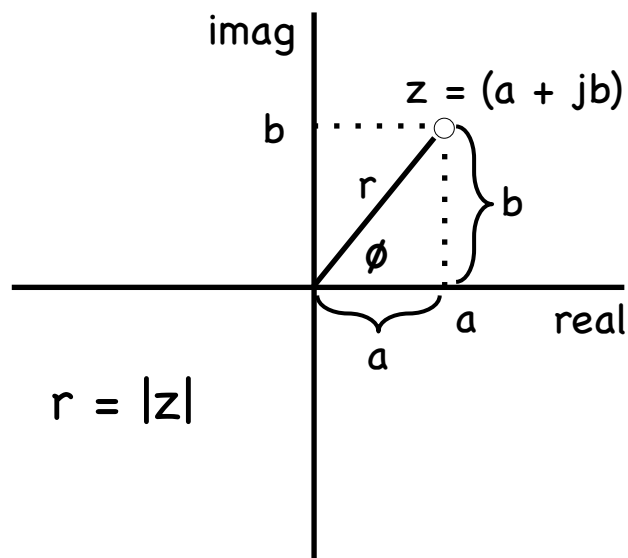

$$\sin \phi = \frac{b}{r}, \quad b = r \sin \phi$$

$$\cos \phi = \frac{a}{r}, \quad a = r \cos \phi$$

$$r^2 = a^2 + b^2, \quad r = \sqrt{a^2 + b^2}$$

$$\tan \phi = \frac{b}{a}, \quad \phi = \tan^{-1} \frac{b}{a}$$

Complex Exponential Function

Taylor Series Expansions

https://en.wikipedia.org/wiki/Taylor_series

$$n! = n(n-1)(n-2)\dots 1$$

$$\sin x = x - \frac{x^3}{3!} + \frac{x^5}{5!} - \frac{x^7}{7!} + \dots$$

$$\cos x = 1 - \frac{x^2}{2!} + \frac{x^4}{4!} - \frac{x^6}{6!} + \dots$$

$$e^x = 1 + \frac{x}{1!} + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \frac{x^5}{5!} + \dots$$

Consider ... $e^{j\phi}$

$$e^{j\phi} = 1 + \frac{j\phi}{1!} + \frac{(j\phi)^2}{2!} + \frac{(j\phi)^3}{3!} + \frac{(j\phi)^4}{4!} + \frac{(j\phi)^5}{5!} + \dots$$

$$e^{j\phi} = \left(1 - \frac{\phi^2}{2!} + \frac{\phi^4}{4!} - \dots \right) + j \left(\frac{\phi}{1!} - \frac{\phi^3}{3!} + \frac{\phi^5}{5!} - \dots \right)$$


$$e^{j\phi} = \cos \phi + j \sin \phi \quad \text{Euler's Formula}$$

A remarkable equation!

$$e^{j\pi} = \boxed{-1} + \boxed{0}$$

or equivalently $e^{j\pi} + 1 = 0$
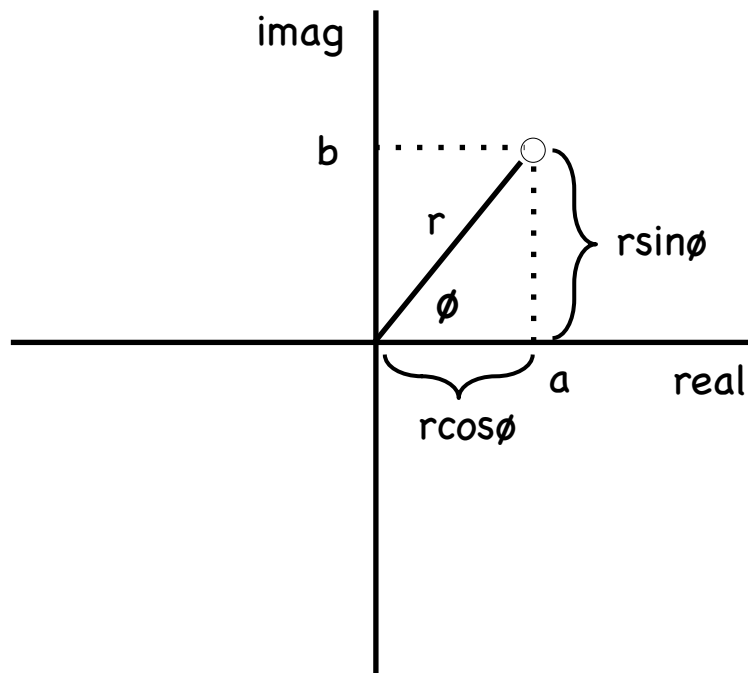
$$re^{j\phi} = r \cos \phi + jr \sin \phi$$




$$e^{j0} = \cos 0 + j \sin 0 = 1$$

$$e^{j\frac{\pi}{2}} = \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} = j$$

$$e^{j\pi} = \cos \pi + j \sin \pi = -1$$

$$e^{j\frac{3\pi}{2}} = \cos \frac{3\pi}{2} + j \sin \frac{3\pi}{2} = -j$$
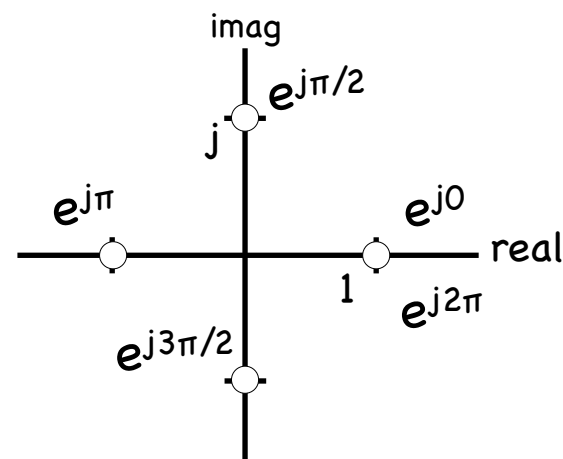
$$e^{j2\pi} = \cos 2\pi + j \sin 2\pi = 1$$



Complex Arithmetic revisited

Simplifications using complex exponential notation:

Multiplication: $r_1 e^{j\varphi_1} \times r_2 e^{j\varphi_2} = r_1 r_2 e^{j(\varphi_1 + \varphi_2)}$

Magnitude: $|re^{j\varphi}|^2 = r^2$
 $|re^{j\varphi}| = r$

Division: $\frac{r_1 e^{j\varphi_1}}{r_2 e^{j\varphi_2}} = \frac{r_1}{r_2} e^{j(\varphi_1 - \varphi_2)}$

Useful
Identities


$$\frac{e^{j\varphi} + e^{-j\varphi}}{2} = \cos \phi$$
$$\frac{e^{j\varphi} - e^{-j\varphi}}{2} = j \sin \phi$$

Complex phasors and sinusoidal oscillations

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

Circular motion in the complex plane

Capacitors

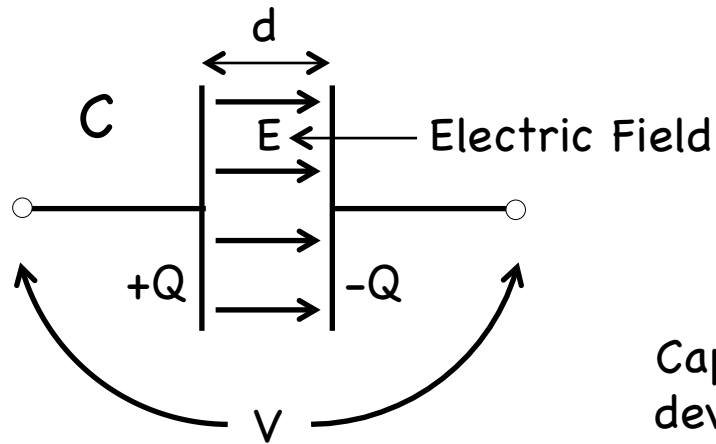

Energy is stored by the electric field in the capacitor.

$$E = V/d \quad \text{or} \quad V = E d$$


Capacitance is the capacity of the device to store charge ...

$$C = Q/V = \text{Coulomb/Volt (Farads)}$$

$$Q = C V \quad 1 \text{ Farad capacitor} \rightarrow 1 \text{ Volt} / 1 \text{ Coulomb}$$

Typical capacitor values: picoFarads (pF) to milliFarads (mF)

(10^{-12})

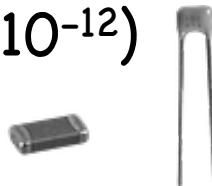

(10^{-3})




Current / Voltage relationship for a capacitor

$$Q = CV \quad I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

Assume that C has a fixed value,
it does not change in time

Transient behavior of RC circuit:

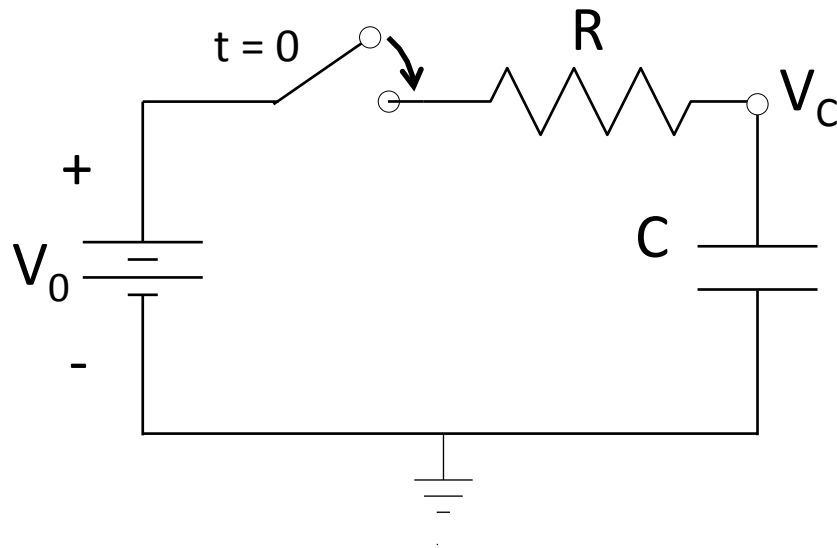

Find the charge $Q(t)$ and voltage $V_C(t)$ for
the capacitor as a function of time

Kirchhoff's voltage law:

$$V_0 - V_R - V_C = 0 \rightarrow V_R + V_C = V_0$$

$$R \frac{dQ}{dt} + \frac{1}{C} Q = V_0$$

Initial Condition: $Q(t=0) = 0$

Final State: $I = 0$ so $Q(t \rightarrow \infty) = CV_0$

Solution ...

$$R \frac{dQ}{dt} + \frac{1}{C} Q = V_0$$

Initial Condition: $Q(t=0) = 0$

First, write this as two equations ...

$$1) \quad \frac{dQ}{dt} + \frac{1}{RC} Q = \frac{V_0}{R}$$

$$2) \quad \frac{dQ}{dt} + \frac{1}{RC} Q = 0$$

Find any particular solution to (1), Q_p : $\frac{1}{RC} Q_p = \frac{V_0}{R} \rightarrow Q_p = CV_0$

Then add the general solution of (2), Q_g : $Q_g(t) = Ae^{-\frac{t}{RC}}$


$$Q(t) = Q_p + Q_g = CV_0 + Ae^{-\frac{t}{RC}}$$

but $Q(t) = 0$ at $t = 0$


$$\text{so } Q(t) = CV_0 \left(1 - e^{-\frac{t}{RC}} \right)$$

$$\text{and } V_c(t) = V_0 \left(1 - e^{-\frac{t}{RC}} \right)$$


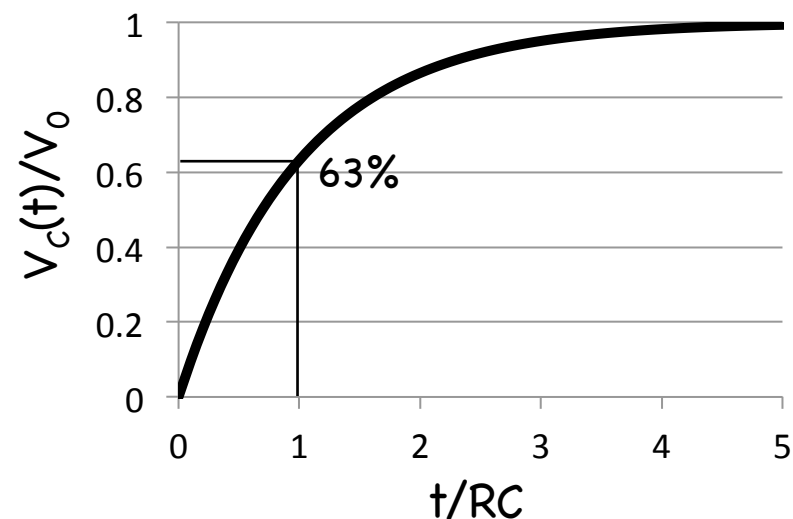
Final State: $V_c(t \rightarrow \infty) = V_0$



Two variations of the RC circuit ...

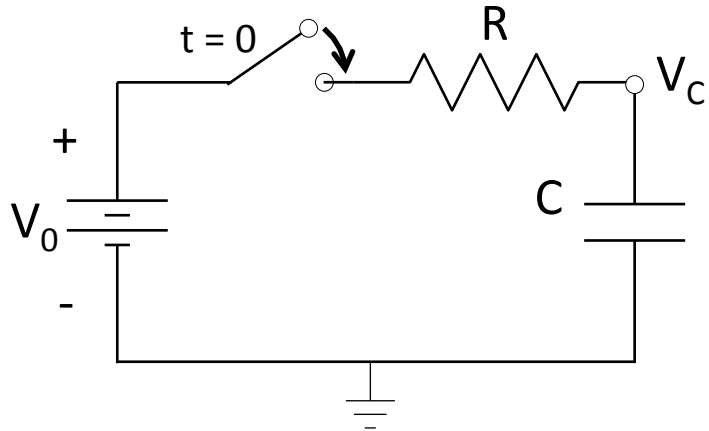

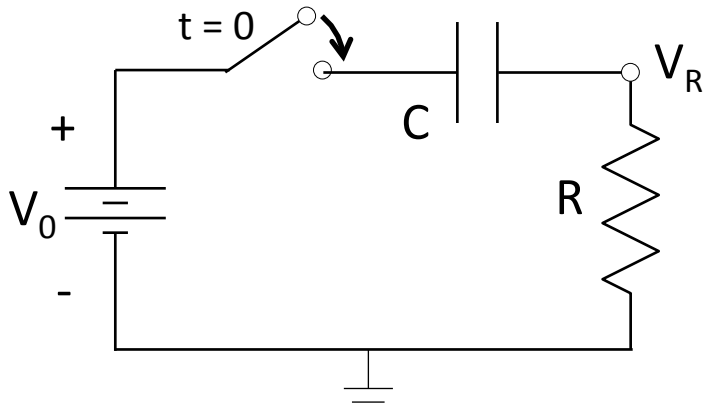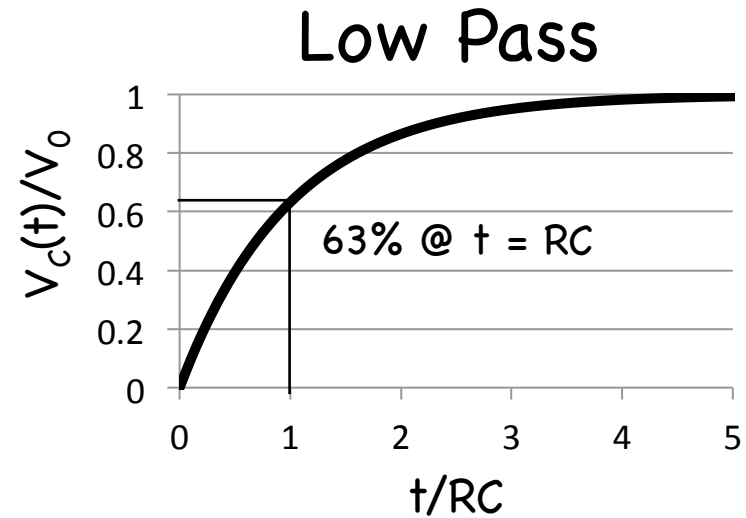Open and close switch repeatedly.
Rapidly: $V_C \approx 0$ Slowly: $V_C \approx V_0$



Open and close switch repeatedly.
Rapidly: $V_R \approx V_0$ Slowly: $V_R \approx 0$

