

Introduction to Audio and Music Engineering


Lecture 15

Topics:

- Inductors
- Transients in RL circuits
- Low-pass and high-pass RL filters
- Phasors in AC circuit analysis
- Impedance
- Summary of simple RC and RL filters

Inductors

Magnetic Flux

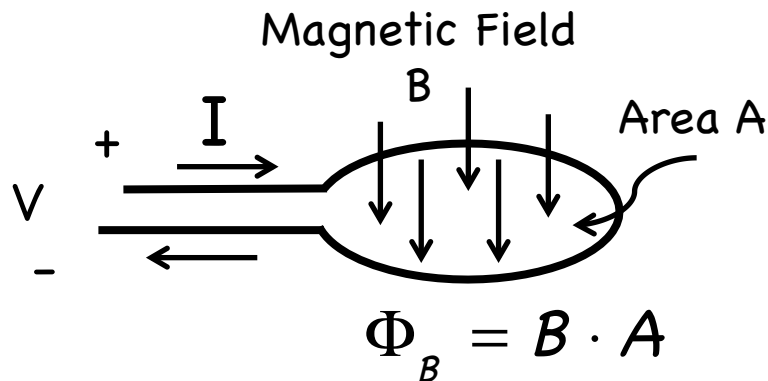


Faraday's Law

$$V = -N \frac{d\Phi_B}{dt} \quad N \text{ turns}$$

Lenz's Law - A change in magnetic flux generates a voltage, which in turn drives a current that produces a magnetic field that opposes the change.

Inductor

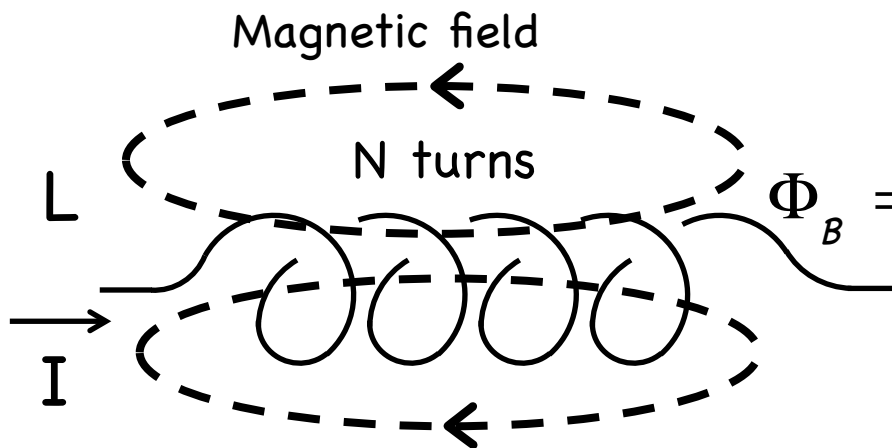

$$\Phi_B = L \cdot I$$

$$V = L \frac{dI}{dt}$$


$$L = \mu \frac{N^2 A}{l}$$

l is length of coil
 A is area of a coil
 $\mu = 4\pi \times 10^{-7} \text{ Henry/m}$

$$1 \text{ Volt} = 1 \text{ Henry} \times 1 \text{ Amp/sec}$$

Energy is stored by the magnetic field in the inductor.

Transient behavior of RL circuit

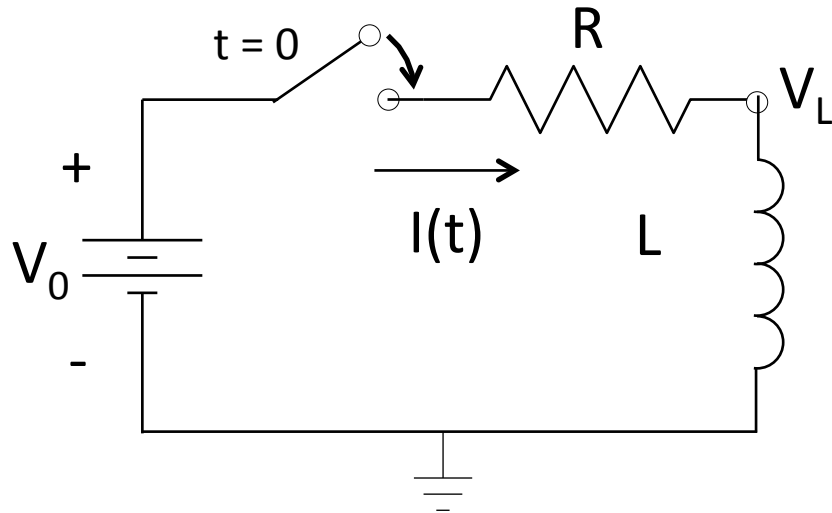

Kirchhoff's voltage law:

$$V_0 - V_R - V_L = 0 \rightarrow V_R + V_L = V_0$$

$$IR + L \frac{dI}{dt} = V_0$$

Initial Condition: $I(t=0) = 0$


Use solution method employed previously:

$$I_p = \frac{V_0}{R} \quad I_g(t) = Ae^{-\frac{R}{L}t}$$

$$I(t=0) = 0 \rightarrow A = -V_0/R$$

$$I(t) = \frac{V_0}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$

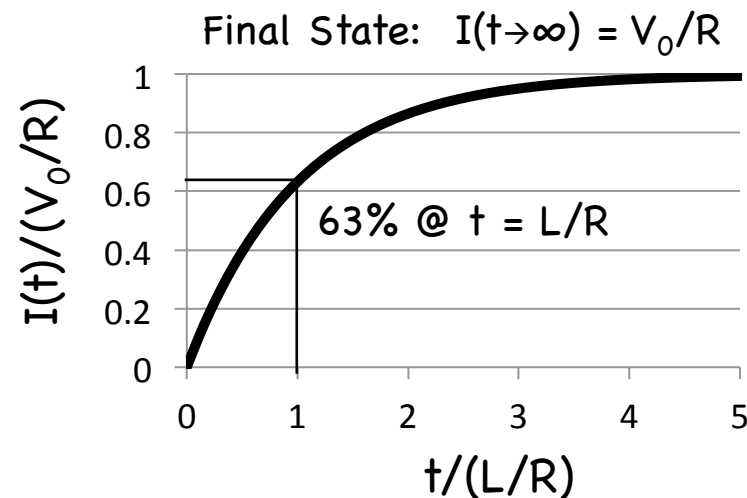
$$I(t) = I_p + I_g = \frac{V_0}{R} + Ae^{-\frac{R}{L}t}$$





Two variations of the RL circuit ...

$$I(t) = \frac{V_0}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$

High Pass

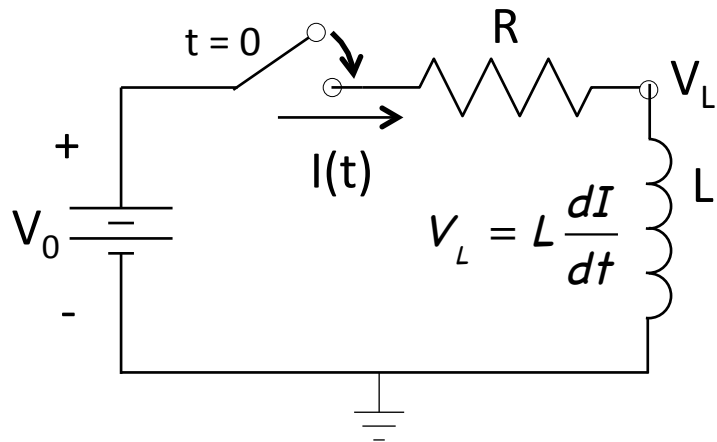


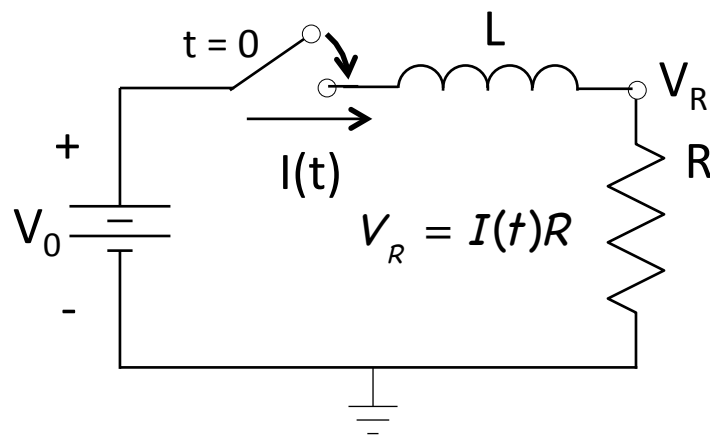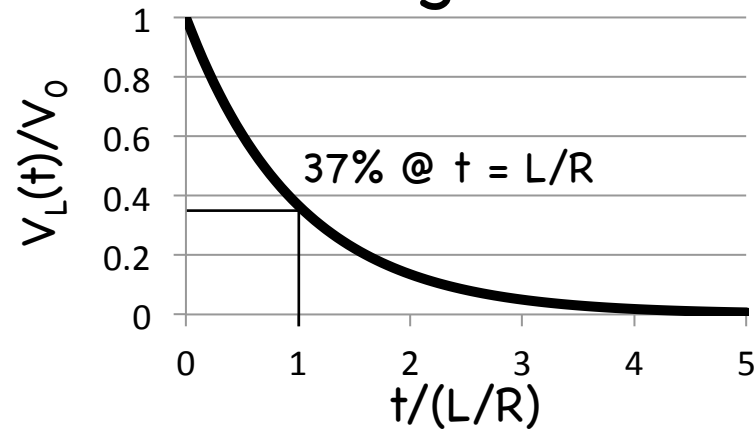Open and close switch repeatedly.
Rapidly: $V_L \approx V_0$ Slowly: $V_L \approx 0$



Open and close switch repeatedly.
Rapidly: $V_R \approx 0$ Slowly: $V_R \approx V_0$

Low Pass

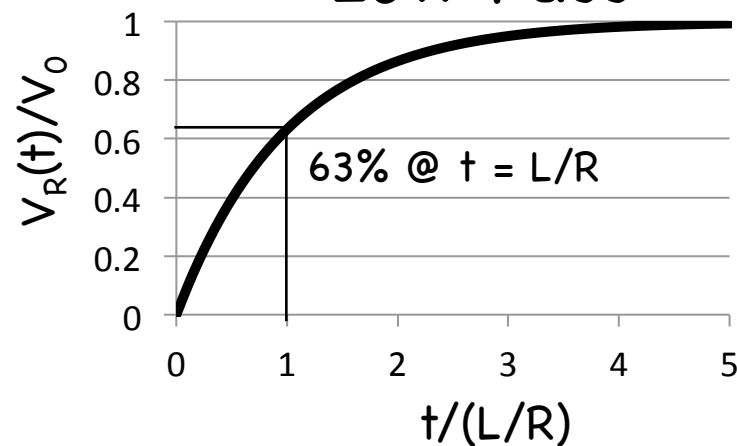


Using phasors in AC Circuit Analysis

Let... $I(t) = \tilde{I}(\omega)e^{j\omega t}$ $V(t) = \tilde{V}(\omega)e^{j\omega t}$

Phasors: $\tilde{I}(\omega)$, $\tilde{V}(\omega)$ Phasors: time independent, complex

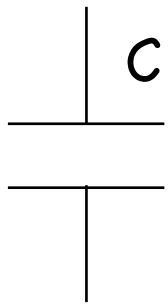Notation: drop ω , $\tilde{I}(\omega) \rightarrow \tilde{I}$, $\tilde{V}(\omega) \rightarrow \tilde{V}$



$$I = C \frac{dV}{dt} \quad \tilde{I}e^{j\omega t} = C \frac{d}{dt} (\tilde{V}e^{j\omega t}) = C\tilde{V}j\omega e^{j\omega t}$$

$$\tilde{I} = j\omega C \tilde{V} \quad \tilde{V} = \frac{1}{j\omega C} \tilde{I} \quad \text{Impedance: } \boxed{\frac{1}{j\omega C}}$$



$$V = L \frac{dI}{dt} \quad \tilde{V}e^{j\omega t} = L \frac{d}{dt} (\tilde{I}e^{j\omega t}) = L\tilde{I}j\omega e^{j\omega t}$$


$$\tilde{V} = j\omega L \tilde{I} \quad \text{Impedance: } \boxed{j\omega L}$$

Generalized Impedance


Electrical

V = voltage
I = current


Dissipation

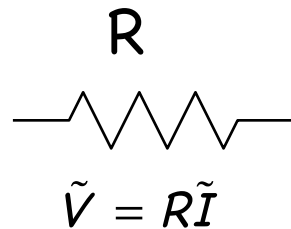

Spring
(potential)



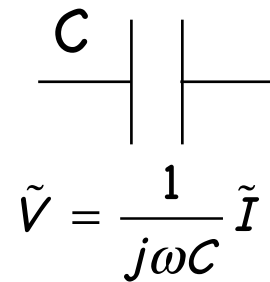


Inertia
(kinetic)

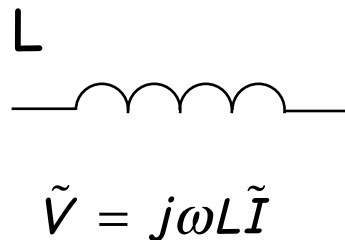




Mechanical

F = force
v = velocity

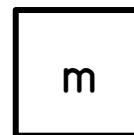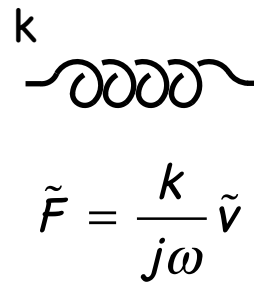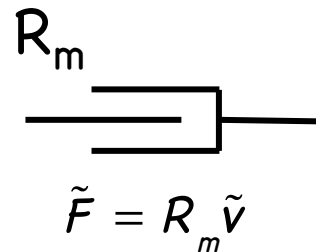


Acoustic

P = pressure
u = flow velocity

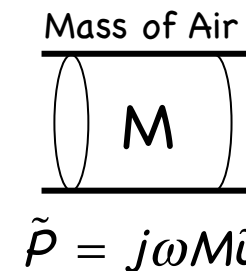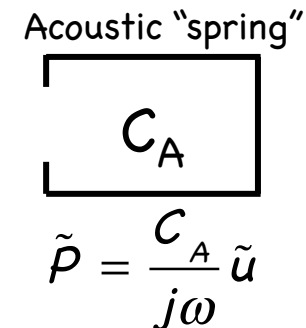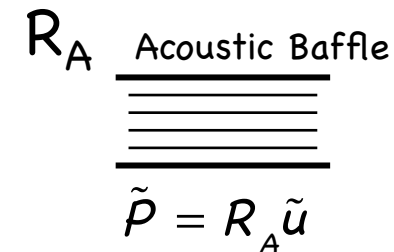

Circuit analysis example

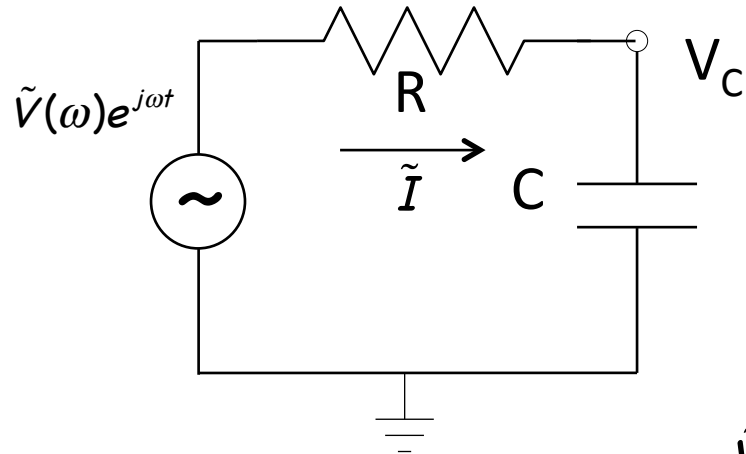

Find V_C

$$\text{KVL: } \tilde{V} - \tilde{I}R - \frac{1}{j\omega C} \tilde{I} = 0$$

$$\tilde{I} = \frac{\tilde{V}}{R + 1/j\omega C}$$

$$\tilde{V}_C = \frac{1}{j\omega C} \tilde{I} = \frac{1/j\omega C}{R + 1/j\omega C} \tilde{V} = \frac{1}{j\omega CR + 1} \tilde{V}$$

Compute magnitude of V_C


$$\frac{|\tilde{V}_C|}{|\tilde{V}|} = \left| \frac{1}{1 + j\omega CR} \right|$$

$$\frac{|\tilde{V}_C|}{|\tilde{V}|} = \left[\frac{1}{1 + j\omega CR} \cdot \frac{1}{1 - j\omega CR} \right]^{1/2}$$


$$\frac{|\tilde{V}_C|}{|\tilde{V}|} = \left[\frac{1}{1 + \omega^2 R^2 C^2} \right]^{1/2}$$

$$\text{when } \omega = \frac{1}{RC} \rightarrow \left[\frac{1}{1 + 1} \right]^{1/2} = 0.707$$

Low Pass

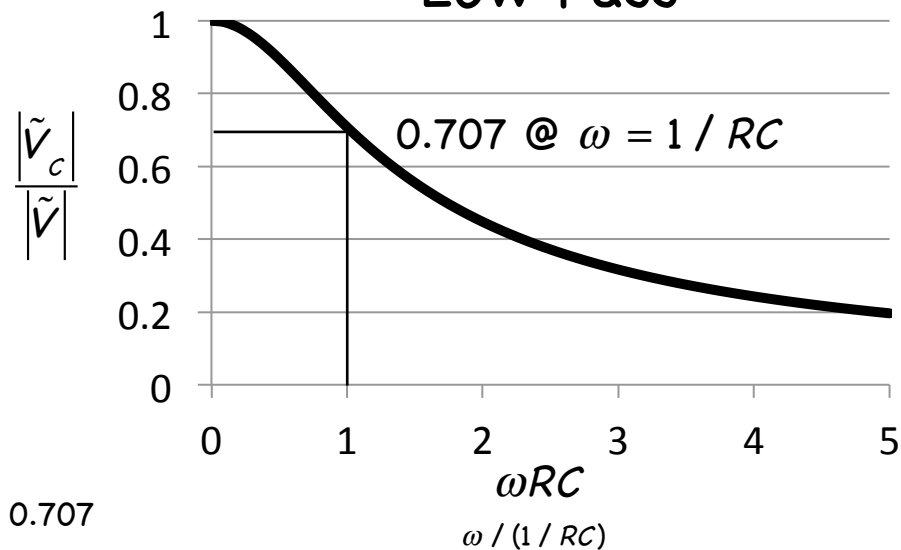

Another circuit analysis example

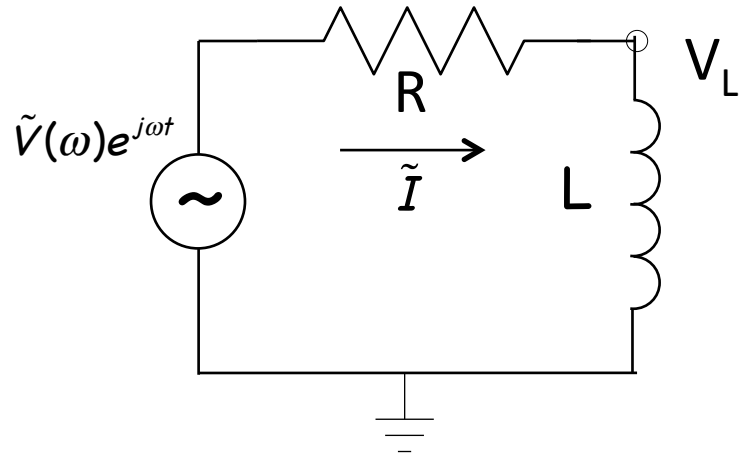

Find V_L

$$\text{KVL: } \tilde{V} - \tilde{I}R - j\omega L\tilde{I} = 0$$

$$\tilde{I} = \frac{\tilde{V}}{R + j\omega L}$$

$$\tilde{V}_L = j\omega L\tilde{I} = \frac{j\omega L}{R + j\omega L} \tilde{V} = \frac{j\omega L/R}{1 + j\omega L/R} \tilde{V}$$


Compute magnitude of V_L

$$\frac{|\tilde{V}_L|}{|\tilde{V}|} = \left| \frac{j\omega L/R}{1 + j\omega L/R} \right|$$



$$\frac{|\tilde{V}_L|}{|\tilde{V}|} = \left[\frac{j\omega L/R}{1 + j\omega L/R} \cdot \frac{-j\omega L/R}{1 - j\omega L/R} \right]^{1/2}$$

$$\frac{|\tilde{V}_L|}{|\tilde{V}|} = \left[\frac{\omega^2 L^2/R^2}{1 + \omega^2 L^2/R^2} \right]^{1/2}$$

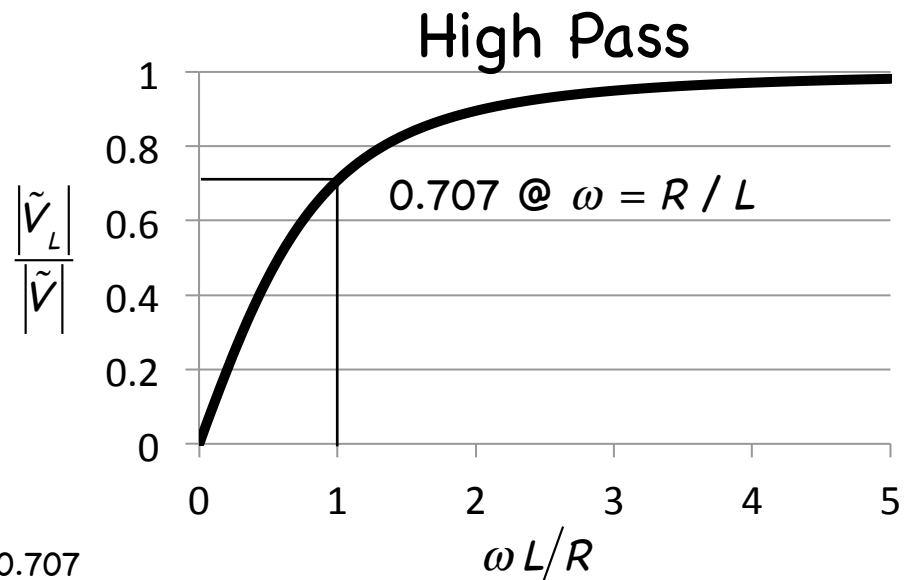
$$\text{when } \omega = \frac{R}{L} \rightarrow \left[\frac{1}{1+1} \right]^{1/2} = 0.707$$



Find the transfer functions ...

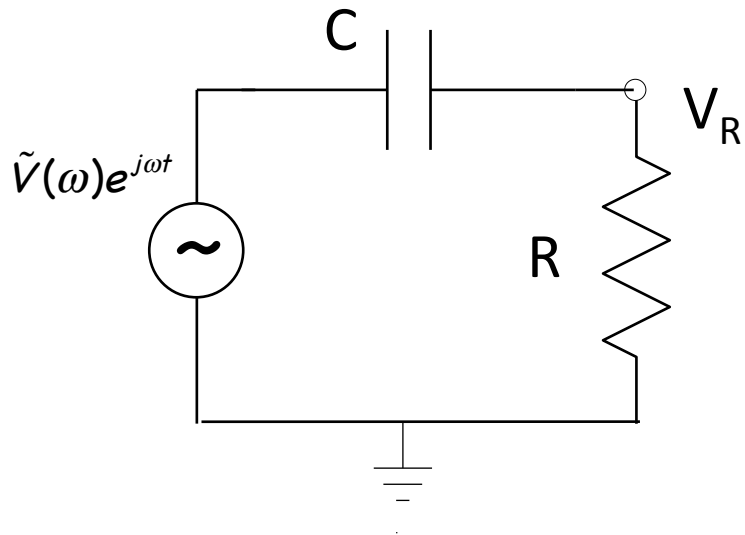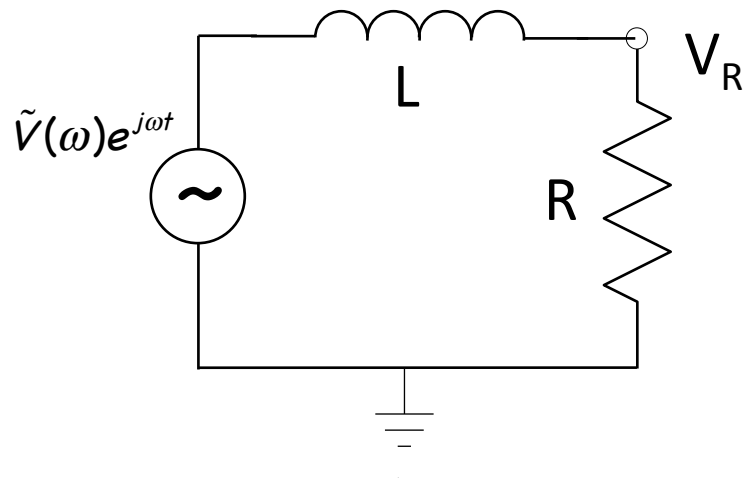

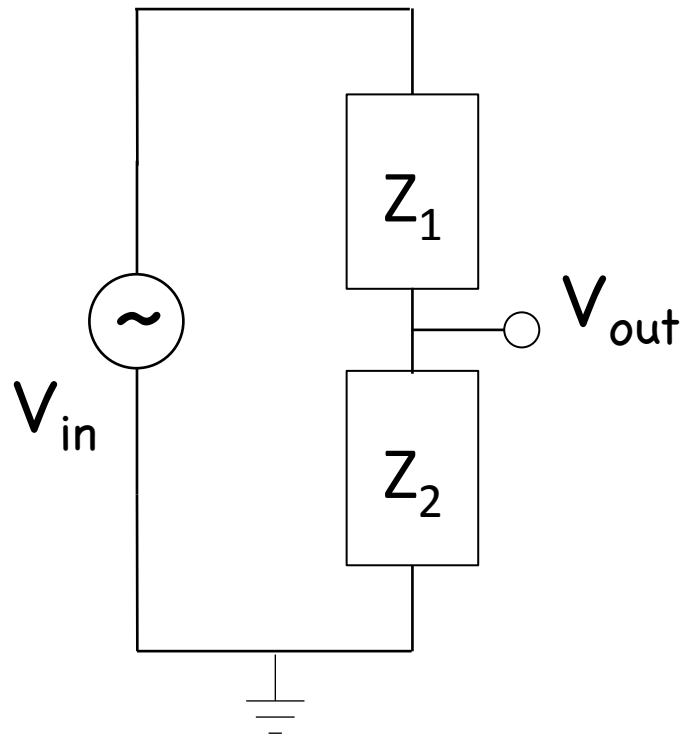Filters are simply
frequency dependent voltage dividers ...



$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{|Z_2|}{|Z_1 + Z_2|}$$

Z	Z	Filter type	Cutoff Freq
R	$\frac{1}{j\omega C}$	Low	$\frac{1}{2\pi RC}$
R	$j\omega L$	High	$\frac{1}{2\pi L}$
$\frac{1}{j\omega C}$	R	High	$\frac{1}{2\pi RC}$
$j\omega L$	R	Low	$\frac{1}{2\pi L}$