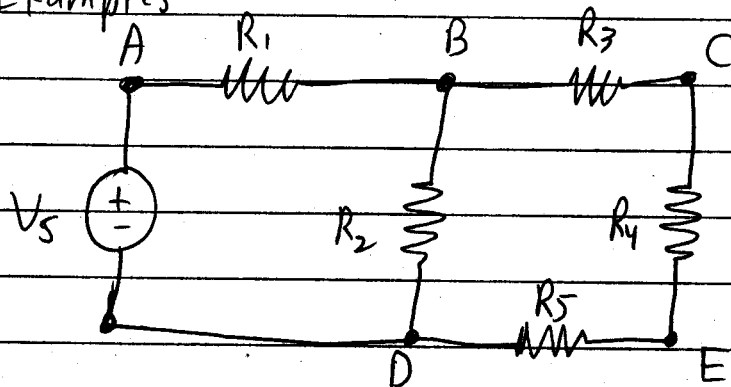


As stated in text:

KCL: If a ckt contains N nodes,
there are $N-1$ independent KCL
equations.

KVL: If a ckt contains E 2-terminal
elements and N nodes, there are
only $E-N+1$ independent KVL
equations.

Examples:



How many elements? — $6 = E$


How many nodes? — $5 = N$

KCL Equations: $N - 1 = 5 - 1 = \underline{4}$

KVL Equations: $E - (N - 1) = 6 - 4 = 2$

I have already told you about "series

connections":

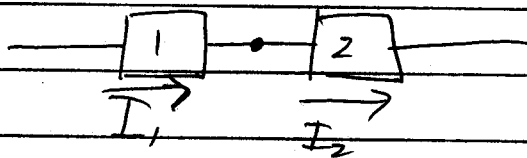


$$I_1 = I_2$$

* Connected to a "common node to which no

other element with current flowing


through it is connected," is how the

book says it.

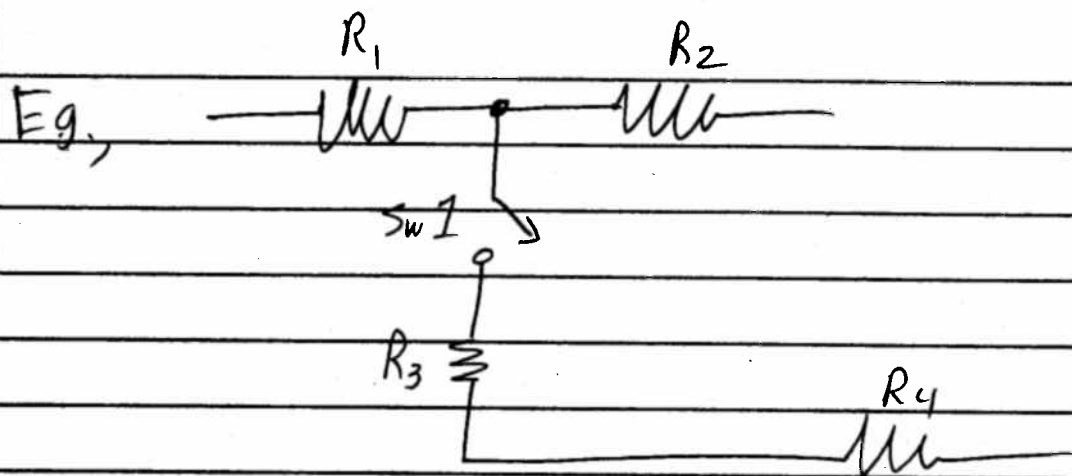


When SW1 is open, $R_1 + R_2$ are in series.

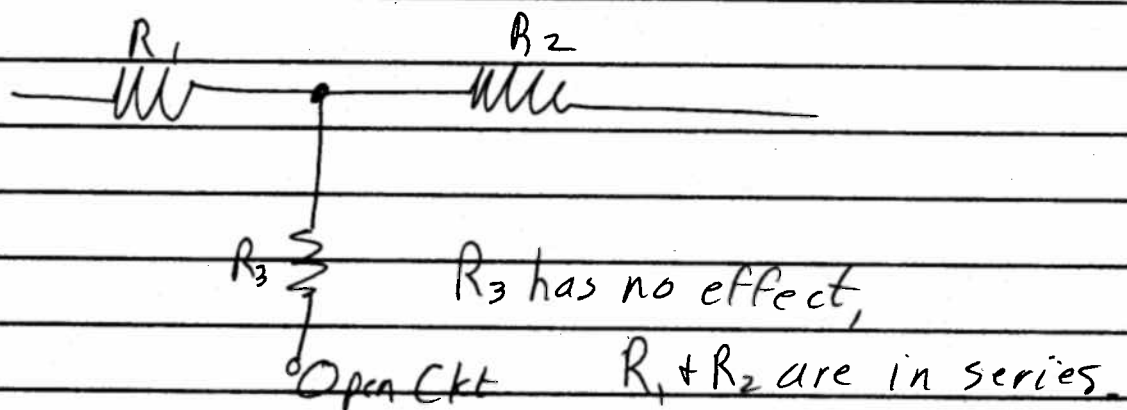When SW1 is closed, $R_1 + R_2$ are not in series.



~~From~~ We say that elements are in parallel

when they form a loop by themselves:

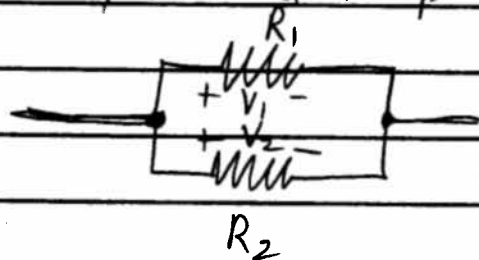


$$KVL: +V_1 - V_2 = 0$$

$$V_1 = V_2$$

Another way of saying this:

When both ends of 2 or more elements are


connected to the same 2 nodes:

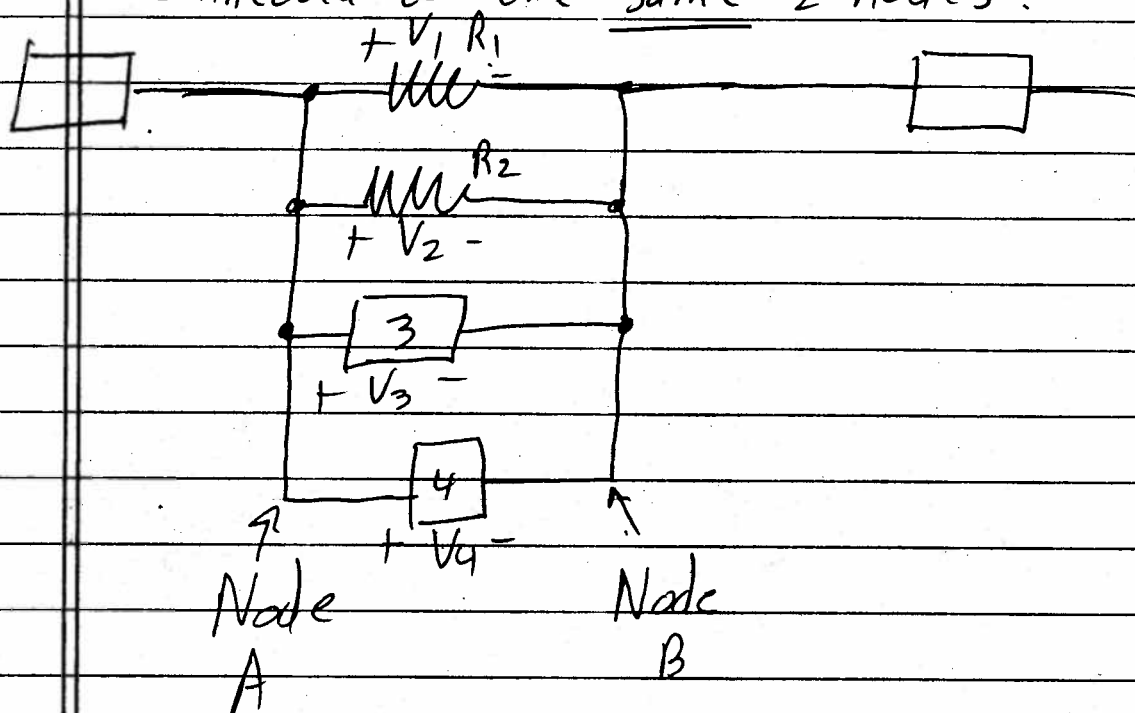

$R_1, R_2, 3, + 4$ are all in parallel:

$$V_1 = V_2 = V_3 = V_4$$


Sometimes they do not look like it:

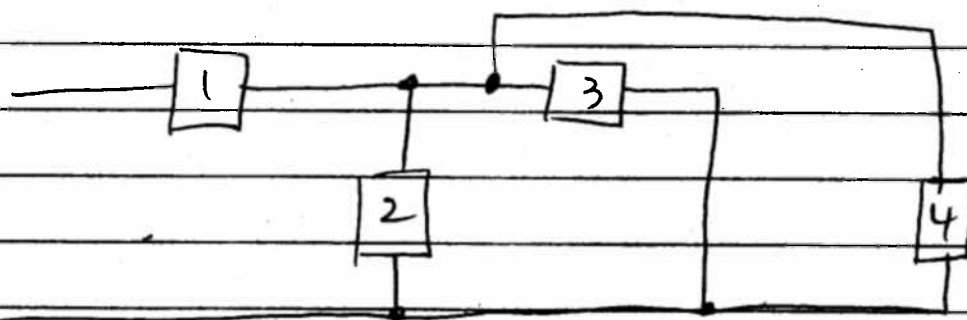


Sometime we will write this as

1 in series with $2 // 3 // 4$

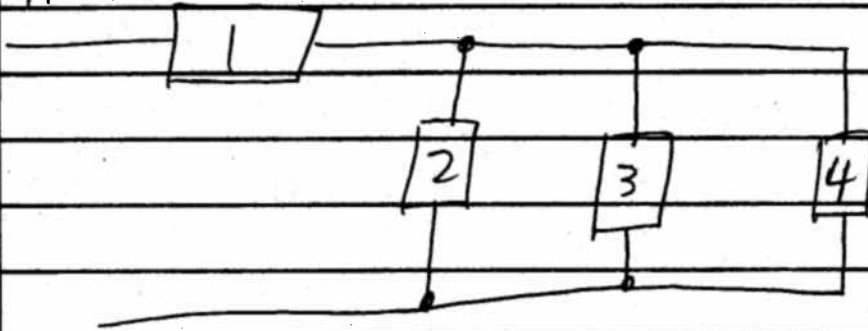
Note I can bend + stretch wires with
no effect, as long as the do not connect
to other things. Can also slide connections.
Previous ckt can be:



or

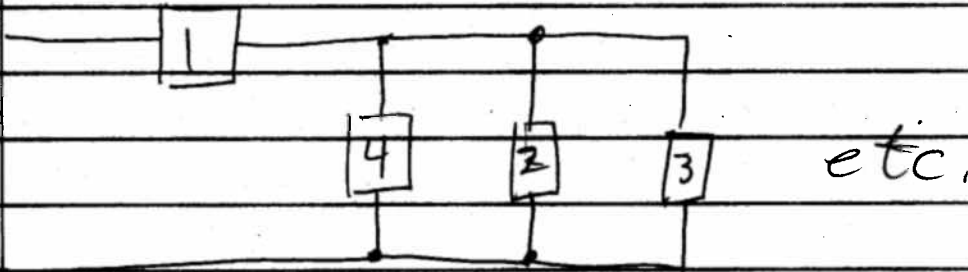

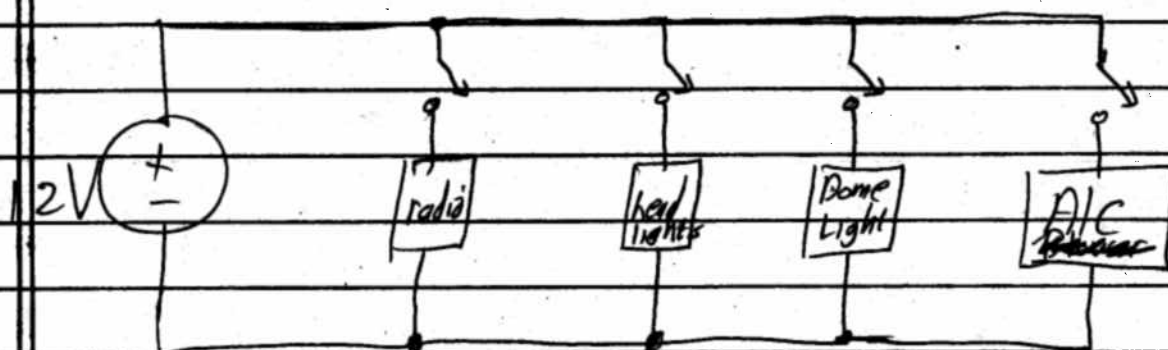
Parallel ckt's, in some ways, have minimal effect on each other, and so are used to good effect, say in your car:



You should do examples in text + H.W.

We will now combine Element + Ckt

Constraints to "solve" ckt's.

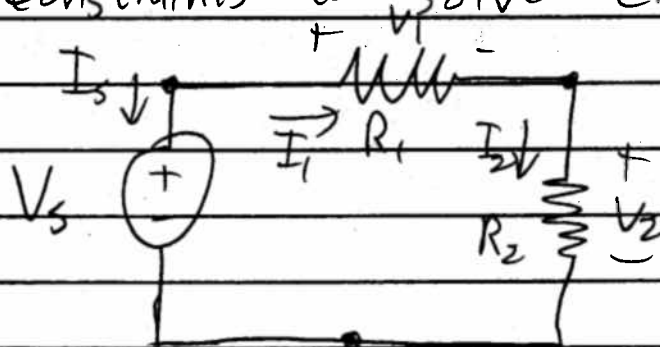

$$N=3 \quad KCL: 2$$

$$E=3 \quad KVL: 1$$

$R_1 + R_2$ are in series, so $I_1 = I_2$

$V_s + R_1$ are in series, but I_s is opposite in direction: $I_1 + I_s = 0$

Let $I_1 = I_2 = -I_s = I$ $I_s = -I$

Write KVL: $+V_1 + V_2 - V_s = 0$

$$V_1 + V_2 = V_s$$

Ckt Constraint

Ohm's Law

$$V_1 = R_1 I$$

$$+ V_2 = R_2 I$$

Element constraints

So

$$R_1 I + R_2 I = V_s$$

$$(R_1 + R_2) I = V_s$$

→ looks like Ohm's Law with $R_{eq} = R_1 + R_2$


$$I = \frac{V_s}{R_1 + R_2}$$

$$V_s = R_{eq} I$$

$$\text{Now } V_1 = R_1 I = R_1 \left(\frac{V_s}{R_1 + R_2} \right) = \frac{R_1}{R_1 + R_2} V_s$$

$$\text{and } V_2 = R_2 I = \frac{R_2}{R_1 + R_2} V_s$$

Example of Voltage Division:

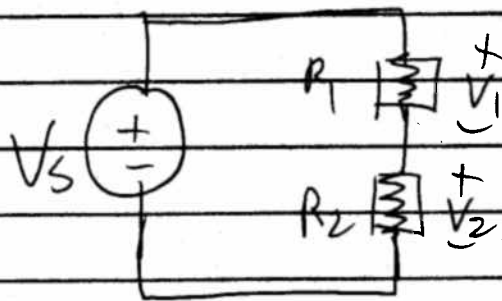


$$\text{KVL: } V_1 + V_2 = V_s$$

We divide the voltage source between the

2 ~~elements~~ Resistors

Similarly:

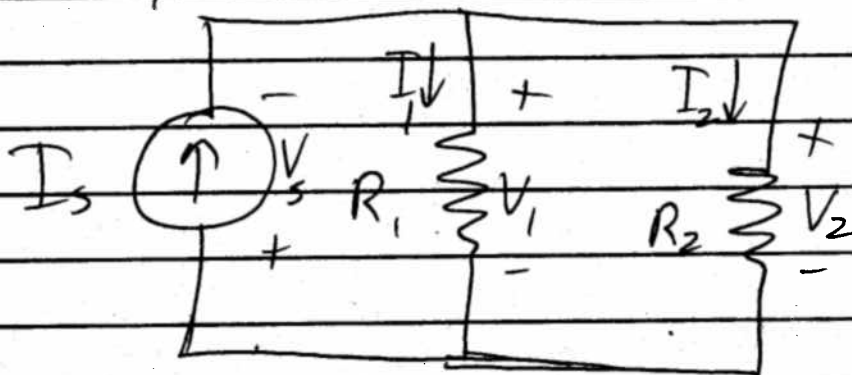

$$N=2, \text{KCL}=1$$

$$E=3, \text{KVL}=2$$

$$V_1 = V_2 = -V_s = V$$

$$\text{KCL @ top: } -I_s + I_1 + I_2 = 0$$

$$I_1 + I_2 = I_s$$

$$\frac{V}{R_1} + \frac{V}{R_2} = I_s$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V = I_s$$

$$\left(\frac{R_2 + R_1}{R_1 R_2}\right)V = I_s$$

$$V = \frac{R_1 R_2}{R_1 + R_2} I_s$$


looks like
Ohm's Law
With $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

$$I_1 = \frac{V}{R_1} = \frac{1}{R_1} \left[\frac{R_1 R_2}{R_1 + R_2} I_s \right] \text{ and } I_2 = \frac{V}{R_2}$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_s = \frac{R_1}{R_1 + R_2} I_s$$

This is called Current Division: Given a Current Source and 2 parallel resistors, how ~~much~~ is the Source Current divided between the 2 resistors?

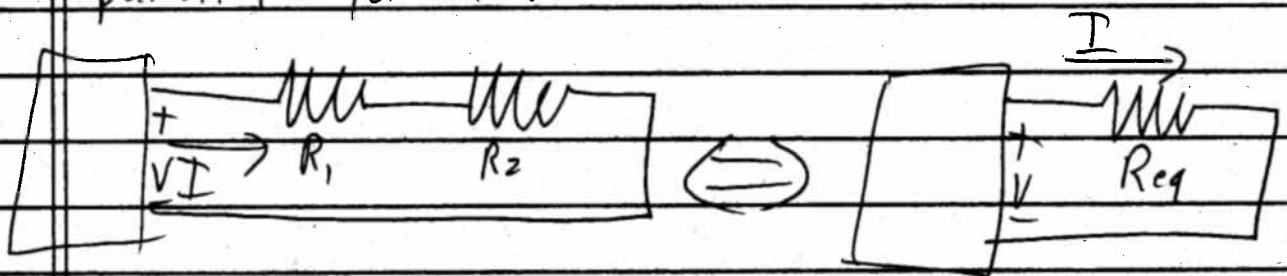I have already alluded to series + parallel equivalence:



R_{eq} is "equivalent" to $R_1 + R_2$ if, for the same voltage V across them the same current I flows thru them.