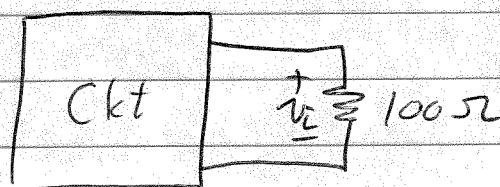


2014 - HW4 Solutions

①

1. 3-43

Linear ckt w/2 sources drives a 100Ω load R . Source 1 delivers $1W$ to load when Source 2 is off. Source 2 delivers $4W$ to load when Source 1 is off. Find power delivered to load when both sources are on.



$$\text{Src 1 on : } P_{L_1} = 1W = \frac{v_{L_1}^2}{100\Omega}$$

$$100 = v_{L_1}^2$$

$$\underline{v_{L_1} = 10V}$$

$$\text{Src 2 on : } P_{L_2} = 4W = \frac{v_{L_2}^2}{100\Omega}$$

$$400 = v_{L_2}^2$$

$$\underline{v_{L_2} = 20V}$$

$$\text{Both sources on} \rightarrow v_L = v_{L_1} + v_{L_2} = 10V + 20V$$

$$v_L = 30V$$

$$P_L = \frac{v_L^2}{100\Omega} = \frac{900}{100} = 9W$$

(2)

2. 3-44 Linear ckt driven by $v_s = 10V + i_s = 10mA$.

$$v_s \text{ on} + i_s \text{ off} \rightarrow v_{o1} = 2V$$

$$\text{Both on} \rightarrow v_o = 1V$$

Find v_o' when $v_s = 20V$ and $i_s = -20mA$

Solution: Find K 's in

$$v_o = K_1 v_s + K_2 i_s$$

$$v_o = v_{o1} + v_{o2}, \quad v_{o1} = 2V,$$

$$v_{o2} = v_o - v_{o1} = 1V - 2V = \underline{\underline{-1V}}$$


$$\text{So } K_1 = \frac{v_{o1}}{v_s} = \frac{2V}{10V} = 0.2$$

$$K_2 = \frac{v_{o2}}{i_s} = \frac{-1V}{10mA} = -0.1k = -100(\Omega)$$

$$\begin{aligned} \text{So } v_o' &= K_1(20V) + K_2(-20mA) \\ &= (0.2)(20V) + (-100\Omega)(-20mA) \\ &= 4V + 2V = \boxed{6V = v_o'} \end{aligned}$$

(3)

3. 3-46

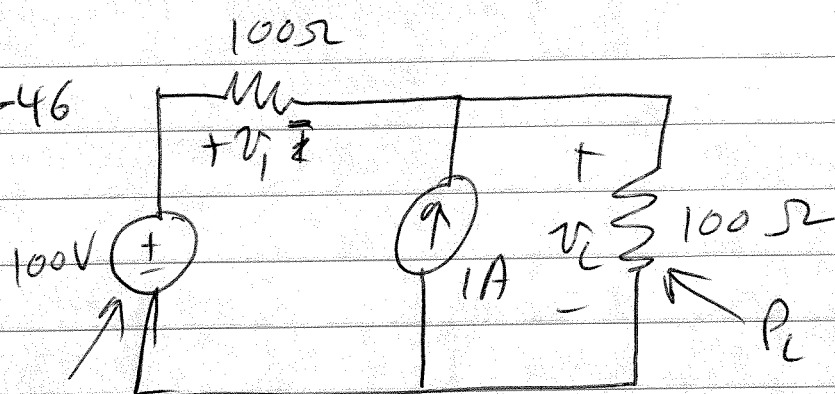 P_{S1}

Current src off, V_{src} delivers 25W to load R . How much power does it deliver to the load when both sources are on? Explain.

Solution: With V_{src} off and I_{src} on, current divides through the resistors equally, so $v_L' = 100\Omega(1/2A) = 50V$, and $-50V$ across the other, ~~resistor~~. $v_1' = -50V$


With V_{src} on and I_{src} off, the voltage divides across both resistors, $v_1'' = 50V$, $v_L'' = 50V$.

With both sources on, $v_L = v_L' + v_L'' = 50V + 50V = 100V$
and $v_1 = v_1' + v_1'' = -50V + 50V = 0V$

Turning on both sources simply drives all the current from the I_{src} through the load, and no current goes thru the V_{src} , so it delivers no power to the load.

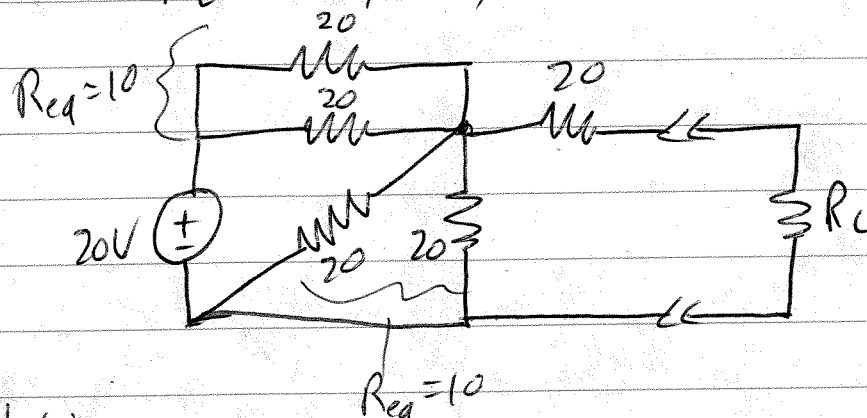
(4)

- 4 3-51 Find Ther. equiv. seen by R_L , find v_L when $R_L = 5\Omega, 10\Omega$, and 20Ω .




Solution

Turn V src off for "lookback" method:

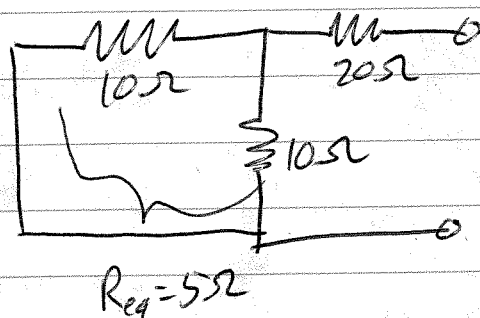

$$R_s = 20\Omega + 5\Omega = 25\Omega$$

Turn source on to get V_{oc} :

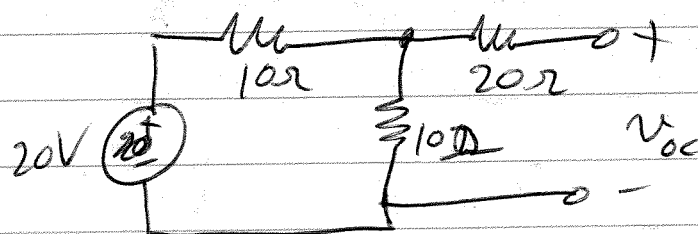


$$v_{oc} = \frac{10}{10+10} 20V = 10V$$

R_L	v_L
5Ω	$\frac{5}{30}(10V) = \frac{5}{3}V$
10Ω	$\frac{10}{35}(10V) = \frac{20}{7}V$
20Ω	$\frac{20}{45}(10V) = \frac{40}{9}V$

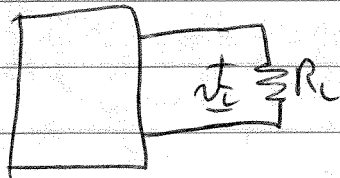(5)

5 3-53 - Linear ckt, ^{not} V_o measured for different R_L 's, determine V_{oc} + R_s .



R_L	i_L	v_L
$10k\Omega$	$91\mu A \rightarrow$	$910mV$
$1k\Omega$	$5mA \leftarrow$	$5V$
		should be $124mV$

Solution: Use Voltages + Voltage Division.

$$910mV = \frac{10k\Omega}{10k\Omega + R_s} V_s \text{ and } 5V = \frac{1k\Omega}{1k\Omega + R_s} V_s$$

Solve for V_s + R_s :

$$(5V)(1k\Omega) + 5V(R_s) = 1k\Omega V_s$$

$$5V + 5V\left(\frac{R_s}{1k}\right) = V_s$$

$$.91V = \frac{10k}{10k + R_s} \left[5V + 5V\left(\frac{R_s}{1k}\right) \right]$$

$$9.1k + .91R_s = 50k + 50k\left(\frac{R_s}{1k}\right)$$

$$= 50k + 50R_s$$

With correction, $.91V = \frac{10k\Omega}{10k\Omega + R_s} \left[0.124V + 0.124V\left(\frac{R_s}{1k\Omega}\right) \right]$

~~$9.1kV$~~

$$9.1k\Omega V + 0.91V R_s = 1.24k\Omega V + 1.24V R_s$$





$$7.86k\Omega V = 0.33V R_s$$

$$R_s = \frac{7.86k\Omega}{0.33} = 23.58k\Omega$$

$$V_s = 0.124V + 0.124V\left(\frac{23.58k\Omega}{1k\Omega}\right) = 3.05V$$

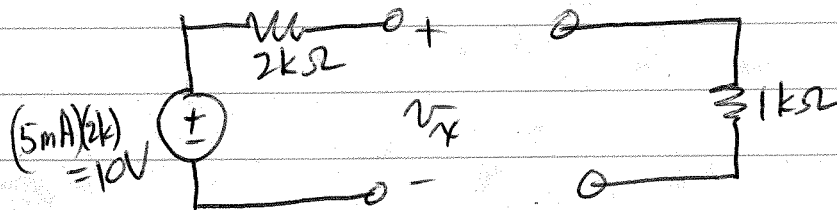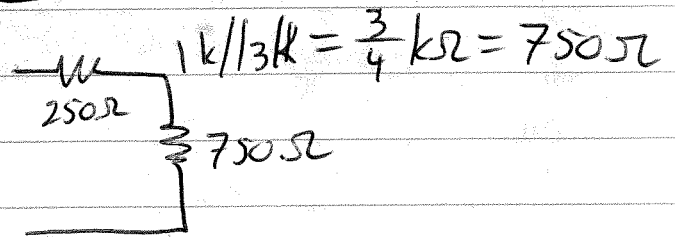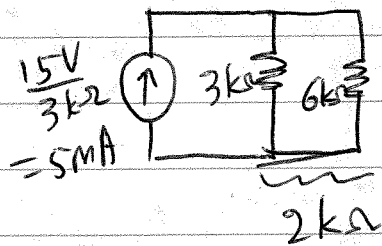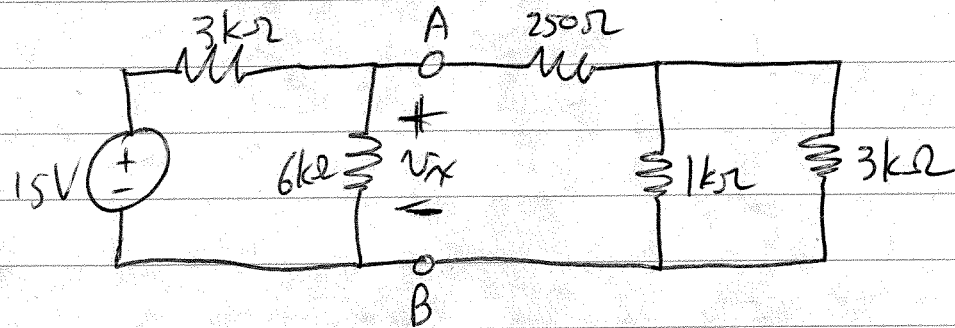(6)

6 3-56 Use Thevenin Eq.'s to right and left of terminals A+B to find v_x :




$$v_x = \frac{1k\Omega}{1k\Omega + 2k\Omega} (10V) = \frac{1}{3} (10V) = \underline{\underline{3.33V}}$$

(7)

7) Blue LED across a 2 terminal Théven source, $V_{oc} = 4V$, $R_T = 20\Omega$. IV characteristic plotted in text. Use graphical method to determine voltage across + current thru LED.

Solution: Find $I_{sc} = \frac{V_{oc}}{R_T} = \frac{4V}{20\Omega} = 0.2A$

From text:

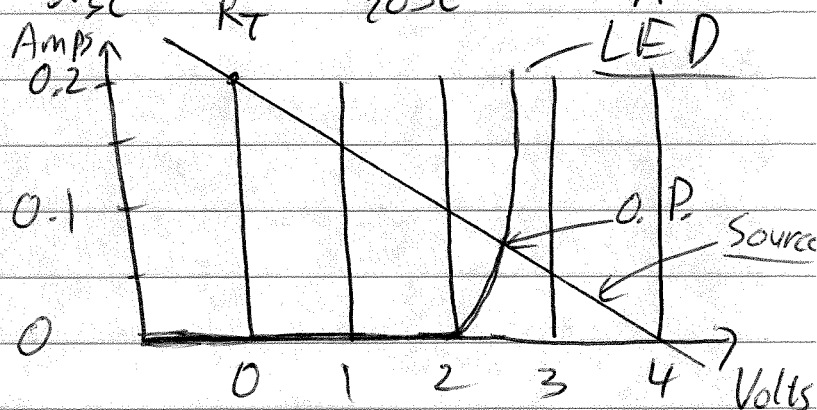


So $V_L = 2.5V$
 $I_L = 0.075A$

(8)

- 8.) 3-73. $5k\Omega$ R across a 2 terminal device, a current of 15mA is delivered. When a second $5k\Omega$ R is connected in parallel with first, a total of 20mA is delivered. Find max power available from src.

Solution

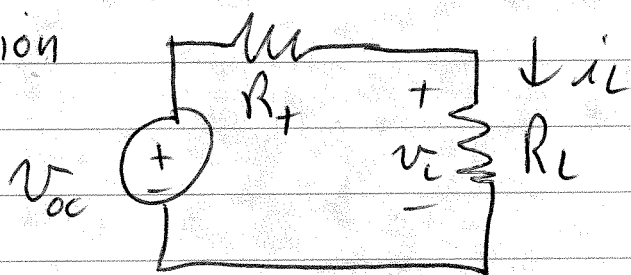

$$R_L = 5k\Omega, i_L = 15\text{mA} \Rightarrow \underline{v_L = 75\text{V}}$$

$$R_L = 2.5k\Omega (5k\Omega // 5k\Omega), i_L = 20\text{mA} \Rightarrow \underline{v_L = 50\text{V}}$$

Use Voltage Division:

$$75\text{V} = \frac{5k\Omega}{R_s + 5k\Omega} v_{oc} + 50\text{V} = \frac{2.5k\Omega}{R_s + 2.5k\Omega} v_{oc}$$

$$75\text{V} R_s + 375k\Omega V = 5k\Omega v_{oc}$$

$$\underline{\underline{\frac{75\text{V} R_s + 375k\Omega V}{5k\Omega} = v_{oc}}}$$

$$\frac{75\text{V} R_s}{5k\Omega} + 75\text{V} = v_{oc} \rightarrow 50\text{V} = \frac{2.5k\Omega}{R_s + 2.5k\Omega} \left(\frac{75\text{V} R_s}{5k\Omega} + 75 \right)$$

$$50\text{V} R_s + 125k\Omega V = \frac{187.5k\Omega V}{5k\Omega} R_s + 187.5k\Omega$$


$$(50\text{V} - 37.5\text{V}) R_s = (187.5 - 125)k\Omega V$$

$$12.5\text{V} R_s = 62.5k\Omega V$$

⑨

$$R_s = \frac{62.5}{12.5} \text{ k}\Omega = \underline{5 \text{ k}\Omega}$$
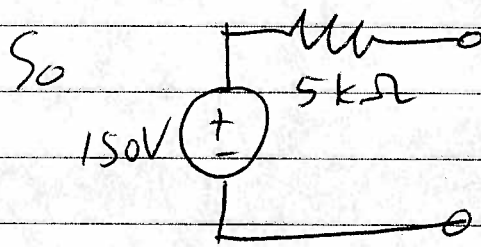
$$V_{oc} = 75V + \frac{75V}{5 \text{ k}\Omega} (5 \text{ k}\Omega) = 75V + 75V = \underline{150V}$$




is the Thev. Equivalent

Max power available:

$$P_{L \max} = \frac{\left(\frac{150V}{2}\right)^2}{5 \text{ k}\Omega} = \frac{(75V)^2}{5 \text{ k}\Omega} = \underline{\underline{\underline{1.125 W}}}$$

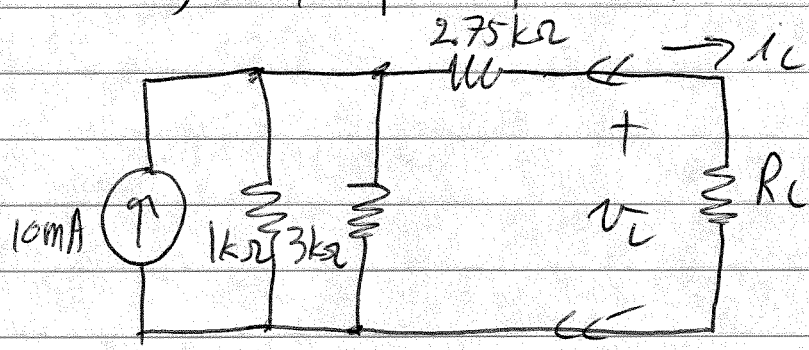q 3-75. For ckt below, find values of R_L that result in


- Max voltage. What is it?
- Max current. What is it?
- Max power. What is it?



$$R_1 = 1k\Omega // 3k\Omega$$

$$= \frac{3k\Omega^2}{4k\Omega}$$

$$R_1 = \frac{3}{4} k\Omega$$

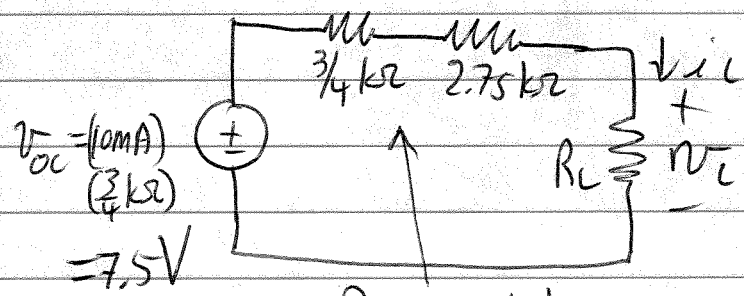

$$R_T = 3.5k\Omega$$

a) $V_{max} = 7.5V$ for $R_L = \infty$

b) $I_{max} = \frac{7.5V}{3.5k\Omega} = 2.14mA$ for $R_L = 0$

c) $P_{max} = \frac{(3.75V)^2}{3.5k\Omega} = 4.02mW$ for $R_L = 3.5k\Omega$

10 3-77 - Practical Src delivers 50 mA to a 300 Ω load and 12V to a 120 Ω load. Find max power available from source. (11)

$$R_L = 300 \Omega, \quad V_L = (300 \Omega)(50 \text{ mA}) = \underline{\underline{15 \text{ V}}}$$

$$R_L = 120 \Omega, \quad \underline{\underline{V_L = 12 \text{ V}}}$$

$$\text{Voltage Div. ① } 15 \text{ V} = \frac{300 \Omega}{R_s + 300 \Omega} V_{oc}$$

$$\text{② } 12 \text{ V} = \frac{120 \Omega}{R_s + 120 \Omega} V_{oc}$$

$$\text{Take ratio: } \frac{15 \text{ V}}{12 \text{ V}} = \frac{5}{4} = \frac{\frac{300}{R_s + 300} V_{oc}}{\frac{120}{R_s + 120} V_{oc}}$$

$$\frac{5}{4} = \frac{R_s + 120}{120} \cdot \frac{300}{R_s + 300} = \frac{R_s + 120}{R_s + 300} \left(\frac{5}{2} \right)$$

$$\left(\frac{2}{5} \right) \left(\frac{5}{4} \right) = \frac{1}{2} = \frac{R_s + 120}{R_s + 300}$$

$$R_s + 300 = 2R_s + 240$$

$$300 - 240 = (2 - 1)R_s = R_s$$

$$\underline{\underline{60 \Omega = R_s}}$$

$$\begin{aligned} \text{Substitute: } 15 \text{ V} &= \frac{300 \Omega}{60 \Omega + 300 \Omega} V_{oc} \\ &= \frac{300}{360} V_{oc} = \frac{5}{6} V_{oc} \\ \frac{90 \text{ V}}{5} &= 18 \text{ V} = \underline{\underline{V_{oc}}} \end{aligned}$$

$$P_{\max} = \frac{\left(\frac{V_{oc}}{2} \right)^2}{R_s} = \frac{(9 \text{ V})^2}{60 \Omega} = \frac{81}{60} \text{ W} = \frac{27}{20} \text{ W} = \underline{\underline{1.35 \text{ W}}}$$