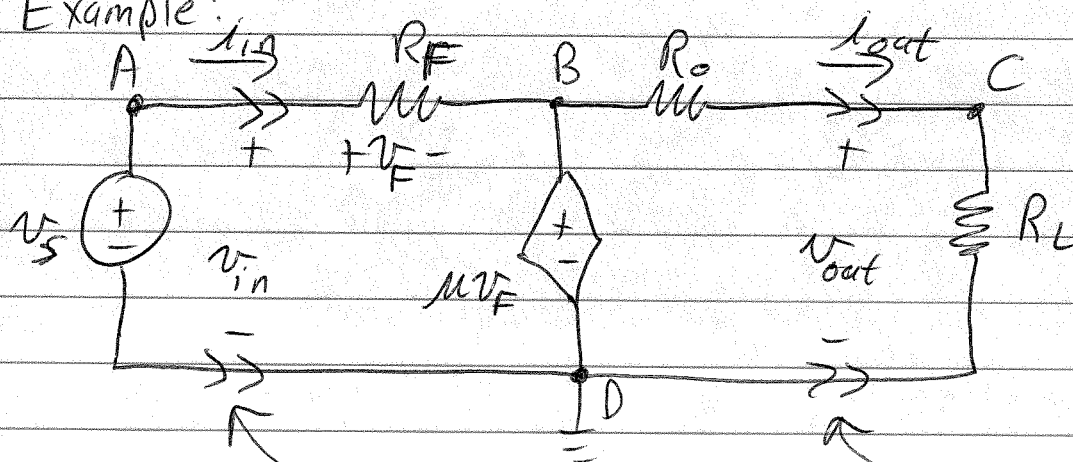


## Thevenin + Norton Equiv. Ckts w/ Dependent Sources

We have to make sure the dependent sources are active, so ~~the best way is to~~ we must either find  $V_{oc} + I_{sc}$ , or analyze the complete ckt to find  $v_{in} + i_{in}$ , then take

$$R_s = \frac{V_{oc}}{I_{sc}} \quad \text{or} \quad R_s = \frac{v_{in}}{i_{in}}$$

Example:



Find the input resistance and the  
Thevenin Equivalent Output Ckt for this  
ckt.

## Nodal Analysis

~~Input~~  $v_A = v_s, v_B = \mu v_F = \mu(v_A - v_B)$

$$v_F = (v_A - v_B) \xrightarrow{\text{arrow}}$$

$$(\mu+1)v_B = \mu v_A = \mu v_s$$

$$(C) \quad \frac{v_c - v_B}{R_o} + \frac{v_c}{R_L} = 0$$

$$v_B = \frac{\mu}{\mu+1} v_s$$

$$-\frac{1}{R_o} v_B + \left(\frac{1}{R_o} + \frac{1}{R_L}\right) v_c = 0$$

$$-\frac{1}{R_o} v_B + \left(\frac{R_o + R_L}{R_o R_L}\right) v_c = 0$$

$$v_c = \left(\frac{R_o R_L}{R_o + R_L}\right) \left(\frac{1}{R_o}\right) \left(\frac{\mu}{\mu+1}\right) v_s = v_{out}$$

Input Resistance

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{v_s}{\frac{v_A - v_B}{R_F}} = \frac{R_F v_s}{(v_A - v_B)}$$

$$R_{in} = \frac{R_F v_s}{v_s - \frac{\mu}{\mu+1} v_s} = \frac{R_F}{\left(\frac{\mu+1-\mu}{\mu+1}\right)} = \boxed{(\mu+1)R_F = R_{in}}$$

Output Thev. Equiv.

$$V_{oc} = \lim_{R_L \rightarrow \infty} V_{out}$$

$$= \lim_{R_L \rightarrow \infty} \frac{R_o R_o \mu}{R_o (1 + \underbrace{\frac{R_o}{R_L}}_0) R_o (\mu + 1)} V_s$$

$$V_{oc} = \frac{\mu}{\mu + 1} V_s$$

$$R_s = \frac{V_{oc}}{I_{sc}}$$

$$I_{out} = \frac{V_B - V_E}{R_o}$$

$$V_{out} = \left( \frac{R_L}{R_o + R_L} \right) \frac{\mu}{\mu + 1} V_s$$

$$= \frac{\mu}{\mu + 1} V_s - \frac{R_L}{R_o + R_L} \frac{\mu}{\mu + 1} V_s$$

$$I_{out} = \frac{\mu}{\mu + 1} \left[ 1 - \frac{R_L}{R_o + R_L} \right] V_s$$

$$= \frac{\mu}{\mu + 1} \left[ \frac{R_o}{R_o + R_L} \right] V_s$$

$$= \left( \frac{\mu}{\mu + 1} \right) \left( \frac{1}{R_o + R_L} \right) V_s$$

$$R_s = \frac{\left( \frac{R_L}{R_o + R_L} \right) \left( \frac{\mu}{\mu + 1} \right) V_s}{\left( \frac{\mu}{\mu + 1} \right) \left( \frac{1}{R_o + R_L} \right) V_s}$$

$$I_{sc} = \lim_{R_L \rightarrow 0} I_{out} = \frac{\mu}{\mu + 1} \frac{1}{R_o} V_s$$

$$R_s = R_o$$

$$R_s = \frac{V_{oc}}{I_{sc}} = \frac{\frac{\mu}{\mu + 1} V_s}{\left( \frac{\mu}{\mu + 1} \right) \left( \frac{1}{R_o} \right) V_s} = R_o$$

So the Thev. Equiv is

