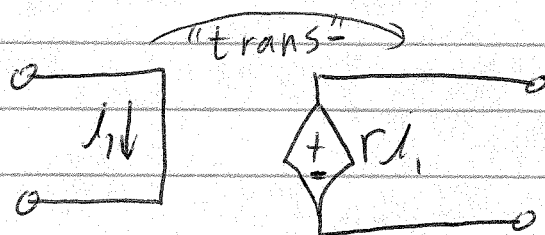


We will move on to Chapter 4 and talk about Active Ckts, which can take power from other places and inject it into a ckt, providing amplification or more power out than was put in.


Simplest Models: Dependent Sources
4 Types of Dependent Sources



~~CCVS~~ CCVS

$r = \text{trans resistance}$

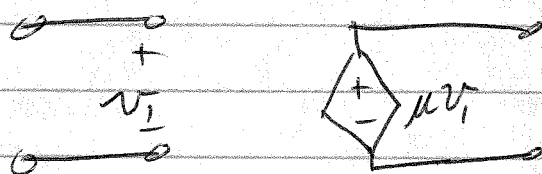This device is a trans-resistor or transistor




VCVS

$\mu = \text{Voltage Gain}$




CCCS

$\beta = \text{Current Gain}$

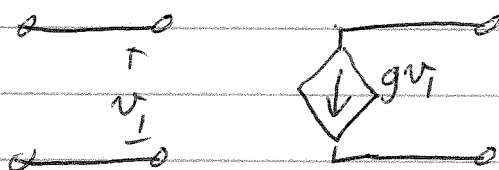

VCCS


$g = \text{trans conductance}$

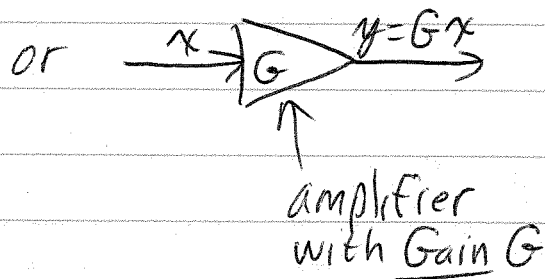

We will use diamonds for dependent sources,
not universal.

We analyse ckts ~~as~~ w/ Dependent Src. just
as we do with other elements, just remember
that if you use superposition you always
leave Dependent Sources turned ON, or active.

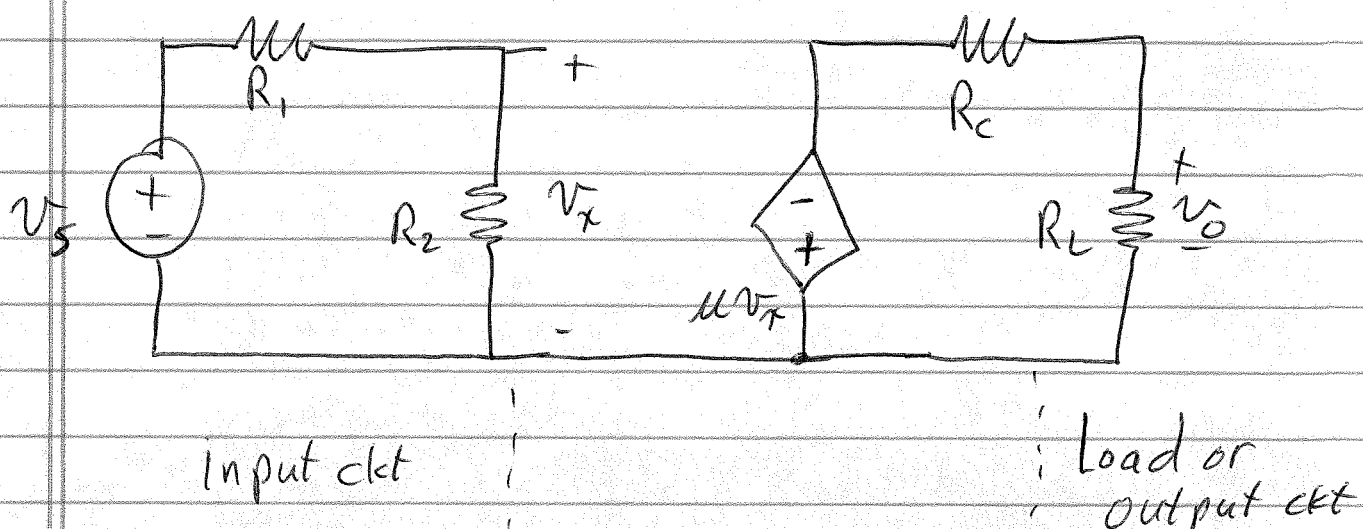Let's do a variation on an example
in the text:



Good thing about Dep. Src, they can separate a ckt into 2 parts that pass a value but do not otherwise interact.

Voltage Division: $v_o = \frac{R_L}{R_c + R_L} (-\mu v_x)$

$$v_o = -\mu \frac{R_L}{R_c + R_L} v_x$$

Find v_x :

Voltage Division:

$$v_x = \frac{R_2}{R_1 + R_2} v_s \longrightarrow v_o = -\mu \left(\frac{R_L}{R_c + R_L} \right) \left(\frac{R_2}{R_1 + R_2} \right) v_s$$

Inverting, gain G

$$v_o = G v_s$$

↑
gain

Let all R 's be $1\text{ k}\Omega$ and $\mu = 100,000 = 10^5$ as in

text:
$$v_o = -\mu \left(\frac{1}{2}\right) \left(\frac{1}{2}\right) v_s$$

$$= -10^5 \left(\frac{1}{4}\right) v_s = -25,000 v_s$$

"Input Power"

If $v_s = 100\text{ }\mu\text{V}$, $P_2 = \frac{(50\text{ }\mu\text{V})^2}{1\text{ k}\Omega} = \frac{25 \times 10^{-10}}{1 \times 10^3} \text{ W}$

$= 25 \times 10^{-7} \text{ W} = \underline{2.5\text{ }\mu\text{W}}$

$$v_o = -25,000(10^{-4}) = -2.5\text{ V}$$

output power

$$P_L = \frac{(-2.5\text{ V})^2}{1\text{ k}\Omega} = \frac{6.25}{1} \text{ mW} = 6.25 \text{ mW}$$

~~Power has increased~~ Output power is

$$\frac{6.25 \times 10^{-3} \text{ W}}{2.5 \times 10^{-6} \text{ W}} = 2500 \text{ times}$$

larger than the input power.


This power comes from the dependent src.

They are connected to batteries, the power grid, solar cells, ^{an arc reactor,} or something that provides power.

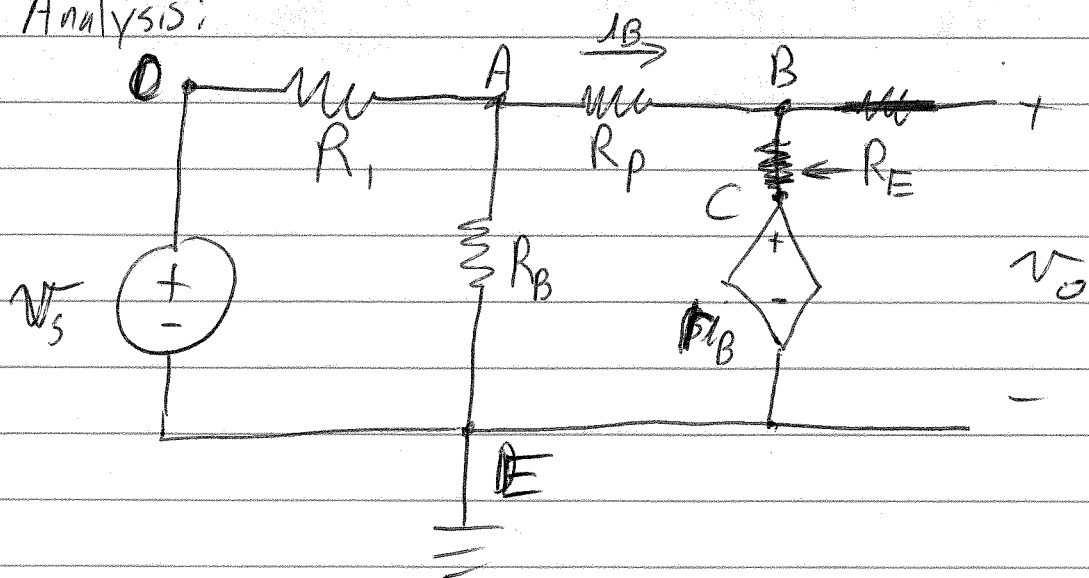(134)

We insert Dependent Sources into Nodal Analysis or Mesh Analysis ~~just as we did~~ simply by substituting the Dependent Output instead of a constant as we do for Independent Sources. We may also have to write the Control Parameter in terms of our variables (Node Voltages or Mesh Currents.)

For example, find V_o in this ckt using Node-Voltage Analysis:



1) Desired Output - $v_o = v_B$

2) Control Parameter - $i_B = \frac{v_A - v_B}{R_P}$

Fixed Nodes? $v_D = v_S$

$$v_C = r i_B = \frac{r}{R_P} (v_A - v_B)$$

$$(A) \quad \frac{v_A - v_D}{R_1} + \frac{v_A}{R_B} + \frac{v_A - v_B}{R_P} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_B} + \frac{1}{R_P} \right) v_A - \frac{1}{R_P} v_B = \frac{v_S}{R_1}$$

$$\frac{R_1 R_P + R_B R_P + R_1 R_B}{R_1 R_B R_P} v_A - \frac{1}{R_P} v_B = \frac{v_S}{R_1} \rightarrow (R_1 R_P + R_B R_P + R_1 R_B) v_A - R_1 R_B v_B = R_B R_P v_S$$

$$(B) \quad \frac{v_B - v_A}{R_P} + \frac{v_B - v_C}{R_E} = 0$$

$$-\frac{1}{R_P} v_A + \left(\frac{1}{R_P} + \frac{1}{R_E} \right) v_B - \frac{1}{R_E} \frac{r}{R_P} (v_A - v_B) = 0$$

$$\left(-\frac{1}{R_P} - \frac{r}{R_E R_P} \right) v_A + \left(\frac{1}{R_P} + \frac{1}{R_E} + \frac{r}{R_E R_P} \right) v_B = 0$$

$$- \left(\frac{R_E + r}{R_E R_P} \right) v_A + \left(\frac{R_E + R_P + r}{R_E R_P} \right) v_B = 0$$

$$\times R_E R_P: \quad - (R_E + r) v_A + (R_E + R_P + r) v_B = 0$$

$$\text{Need } v_B, \text{ so write } v_A = \frac{R_E + R_P + r}{(R_E + r)} v_B$$

$$\text{Sub into (A)} \quad \frac{(R_1 R_P + R_B R_P + R_1 R_B)(R_E + R_P + r)}{R_E + r} v_B - \cancel{\frac{1}{R_P} R_1 R_B} v_B = R_B R_P v_S$$

$$\cancel{v_B} = \frac{(R_1 R_p + R_B R_p + R_1 R_B)(R_E + R_p + r) - R_1 R_B (R_E + r)}{R_E + r} v_B = R_B R_p v_S$$

$$\text{Or } v_B = \frac{(R_E + r)(R_B R_p)}{(R_1 R_p + R_B R_p + R_1 R_B)(R_E + R_p + r) - R_1 R_B (R_E + r)} v_S$$

$$v_B = \frac{r \left(\frac{R_E}{r} + 1 \right) (R_B R_p)}{r \left[(R_1 R_p + R_B R_p + R_1 R_B) \left(\frac{R_E}{r} + \frac{R_p}{r} + 1 \right) - R_1 R_B \left(\frac{R_E}{r} + 1 \right) \right]} v_S$$

Very complicated

Take limit $r \rightarrow \infty$:


$$v_B = \frac{R_B R_p}{R_1 R_p + R_B R_p} v_S$$

$$v_B = \frac{R_B}{R_1 + R_B} v_S$$



less than 1

Another:

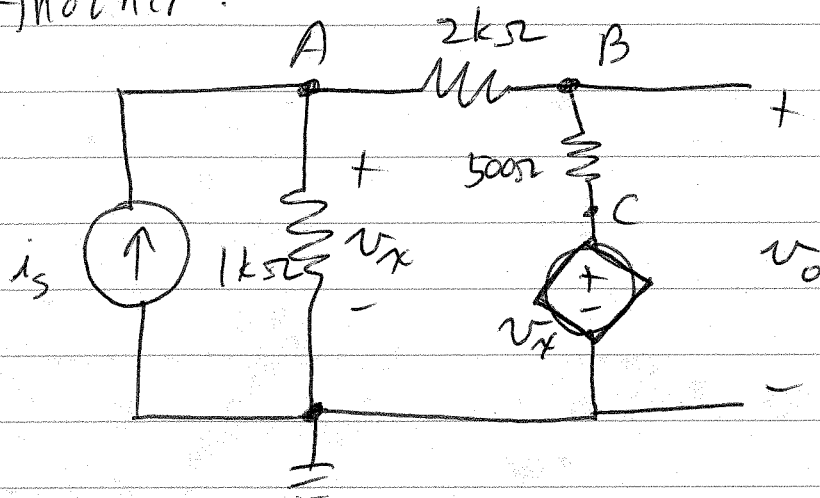

$$v_o = v_B$$

$$v_c = v_x$$

$$v_x = \frac{v_A}{4}$$

$$(A) \quad -i_s + \frac{v_A}{1k\Omega} + \frac{v_A - v_B}{2k\Omega} = 0$$

$$(2+1)v_A - v_B = 2k\Omega i_s$$

$$\underline{3v_A - v_B = 2k\Omega i_s}$$

$$(B) \quad \frac{v_B - v_A}{2k\Omega} + \frac{v_B - v_c}{500\Omega} = 0$$

$$-\frac{1}{2k\Omega}v_A + \left(\frac{1}{2k\Omega} + \frac{1}{500\Omega}\right)v_B - \frac{1}{500\Omega}(v_A) = 0$$

$$-\left(\frac{1}{2k\Omega} + \frac{1}{500\Omega}\right)v_A + \left(\frac{1}{2k\Omega} + \frac{1}{500\Omega}\right)v_B = 0$$

$$v_A = v_B$$


$$(A) \rightarrow 3v_B - v_B = 2k\Omega i_s$$

$$2v_B = 2k\Omega i_s$$

$$\underline{v_B = v_o = 1k\Omega i_s = 1000\Omega i_s}$$

In Mesh-Current Analysis we do similar things:

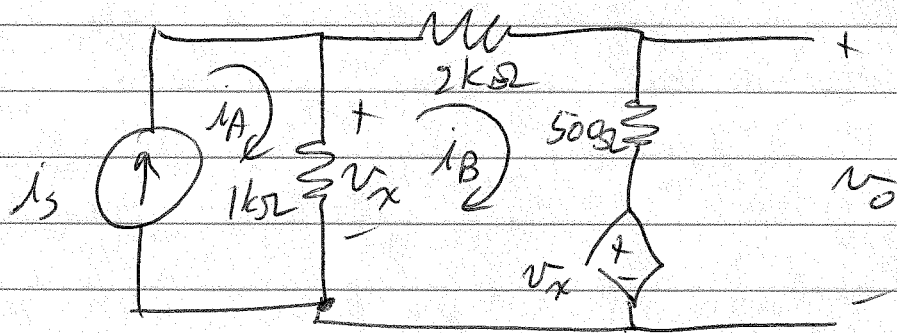Analyze the same ckt using Mesh Currents:



$$1) \text{ D.O. } v_o \neq v_x$$

$$v_o - v_x - 500\Omega i_B = 0$$

$$\underline{v_o = v_x + 500\Omega i_B}$$

$$2) v_x = 1k\Omega (i_A - i_B)$$

(A) Current source on outer edge:

$$\underline{i_A = i_s}$$

$$(B) \quad 2k\Omega i_B + 500\Omega i_B + v_x + 1k\Omega(i_B - i_A) = 0$$

$$\begin{array}{c} \swarrow \quad \downarrow \quad \searrow \\ 1k\Omega i_A \quad 2500\Omega i_B + 1k\Omega(i_A - i_B) + 1k\Omega(i_B - i_A) = 0 \end{array}$$

$$2500\Omega i_B + 2k\Omega(i_A - i_B) = 0$$

$$2500\Omega i_B = 0$$

$$2k\Omega i_A \quad i_B = 0$$

$$\text{So } v_o = v_x + 500\Omega i_B = v_x$$

$$v_o = \underline{\underline{1k\Omega i_A = 1000\Omega i_s}} \quad \text{as before.}$$