

Linearity

Linear - has inputs that produce outputs.

Output is Proportional to Input

$$\text{Out} = \cancel{G} \text{Input} \quad (\text{Homogeneity})$$

$$f(x) \cancel{f(x)} = Gx \quad \text{or Proportionality}$$

~~$$\text{Out}(\text{Sum of Inputs}) = K_1 I_1 + K_2 I_2 + K_3 I_3 + \dots$$~~

$$f(Kx) = K f(x)$$


Also Output (Sum of Inputs) = Sum of Outputs
due to each Input

$$f(x_1 + x_2) = f(x_1) + f(x_2)$$

(Additivity
or
Superposition)

Proportionality only applies to currents
and voltages, NOT TO POWER which is
non-linear.

Examples in text:

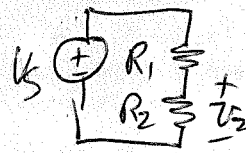


$$v_2 = \frac{R_2}{R_1 + R_2} (v_s) \quad (10\% \text{ in text})$$

$$G = \frac{R_2}{R_1 + R_2} (= K)$$


There are many ways of using these concepts in Circuit Analysis, one is the Unit Output Method, in which you ask "What input must be applied to get 1 (V or A or mV or mA, etc) for the output?"

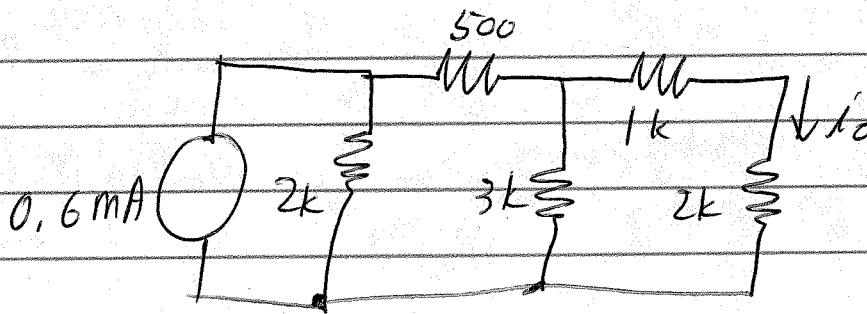
Exercise 3-24:

Use Unit Output Method to find i_o in this:




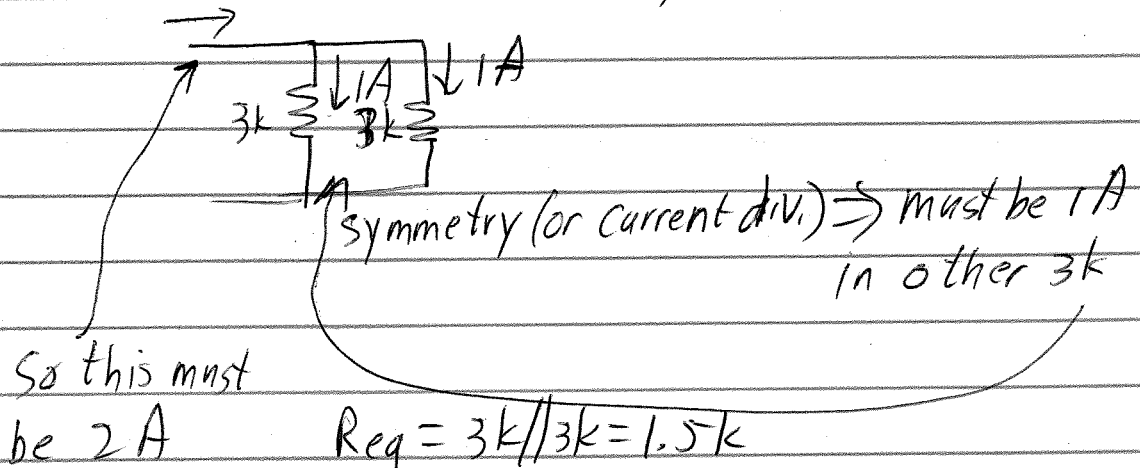If 1 A flows down in 2k, it also flows thru 1k,




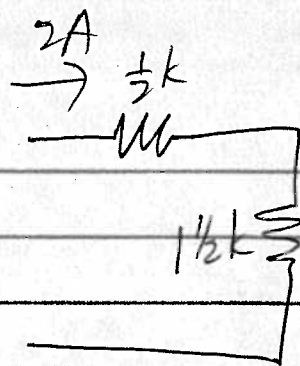

10%

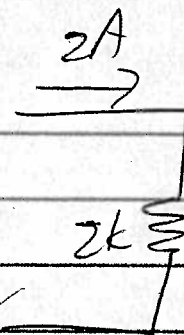


=

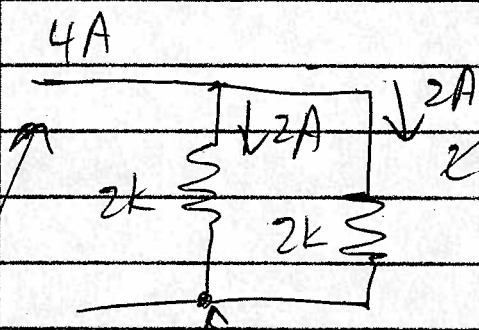

Again, symmetry \Rightarrow 2A in other $2k$
or a sum of 4A here

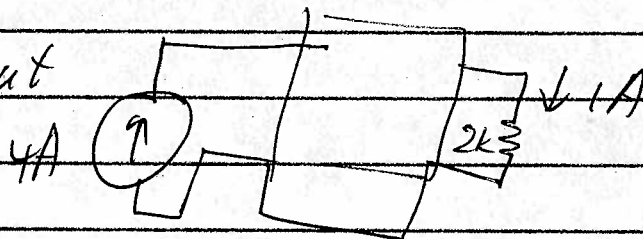So, to get 1A at output we would
need 4A at input



$$\text{So } 1A = K(4A)$$

$$K = \frac{1A \text{ (output)}}{4A \text{ (input)}} = \frac{1}{4}$$

$$\text{So } i_o(0.6mA) = \frac{1}{4}(0.6mA) = 0.15mA$$


input

This is usually useful in highly symmetric and relatively simple ckt's.

You can also use a "Unit Input Method," not in text, that goes "If a unit input is applied, what will the output be?" then

$$K = \frac{\text{output}}{1}$$

Apply to same problem:

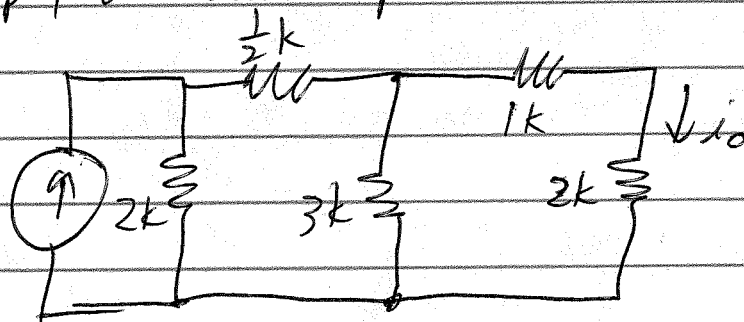


Go to far side + reduce:

$$1k + 2k = 3k$$




$$3k // 3k = 1.5k$$

$$1.5k + 0.5k = 2k$$

Now ask:

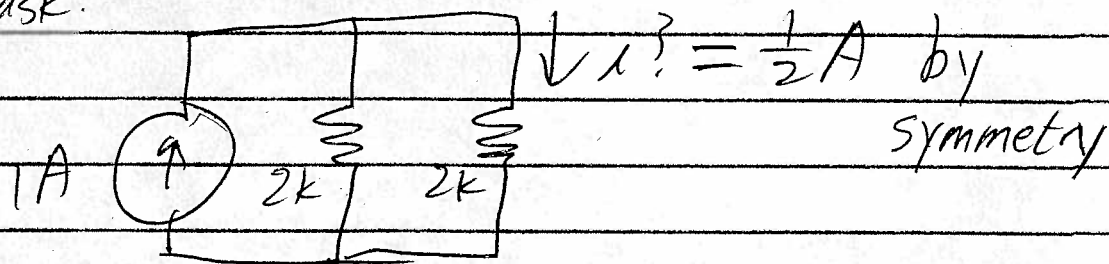

Back out

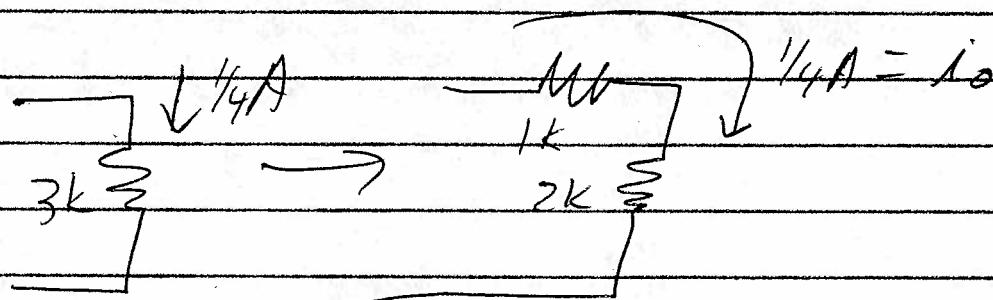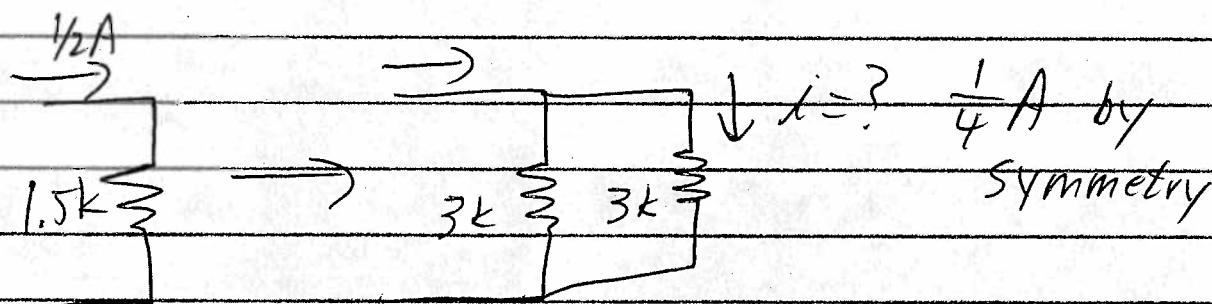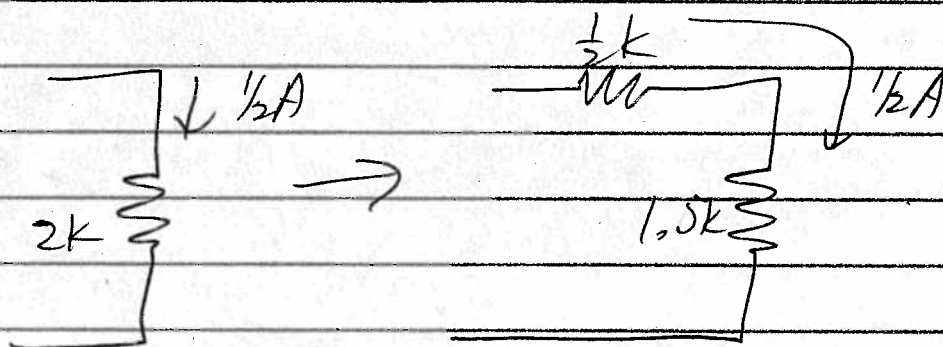

So 1A in produces $\frac{1}{4}A$ out, $K = \frac{\frac{1}{4}A}{1A} = \frac{1}{4}$

So a 0.6mA input produces $i_o = \frac{1}{4}(0.6mA) = 0.15mA$

Additivity (Superposition)

$$y(x_1, x_2, x_3, \dots) = K_1 x_1 + K_2 x_2 + \dots$$

Output due to many inputs = Sum of outputs due to each source with all other sources turned off.