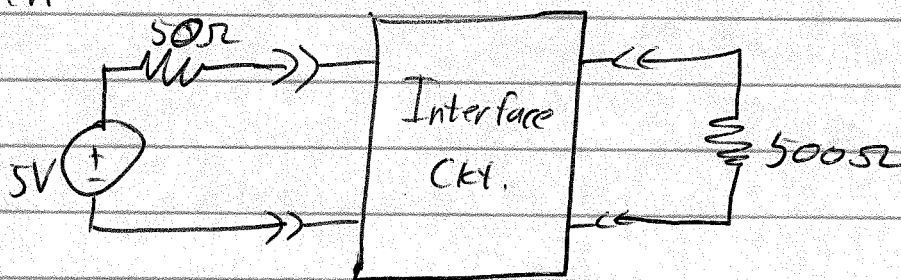


Make sure you read Section 4-5 on

Op Amp Circuit Design.

Taking one example, Ex 4-22:

Given



Design an interface ckt so that 200mW of power is delivered to the 500Ω load.

1<sup>st</sup> - Do we need an interface other than a wire? - What maximum power could

we get from 5V + 50Ω source?  $P_{\max} = \frac{1}{4} \frac{V_{oc}^2}{R_T}$

$$= \frac{1}{4} \frac{(5V)^2}{50\Omega} = \frac{1}{8} W$$

$$= 0.125 W = \underline{\underline{125 \text{ mW}}}$$

And this ~~is~~ would be into a 50Ω load, less into a 500Ω load, so we need gain.

2) Easiest to design for voltage gain, so let's think: To deliver 200mW power into  $500\Omega$  load, what must  $v_L$  be?


$$200 \text{ mW} = \frac{v_L^2}{500\Omega}$$

$$v_L^2 = (500\Omega)(0.2 \text{ W}) = 100 \text{ V}^2$$

$$\underline{v_L = \pm 10 \text{ V}}$$

To get  $\pm 10 \text{ V}$  out from a  $5 \text{ V}$  input we need a gain of  $K = \frac{v_{\text{out}}}{v_{\text{in}}} = \frac{\pm 10 \text{ V}}{5 \text{ V}} = \pm 2$ .

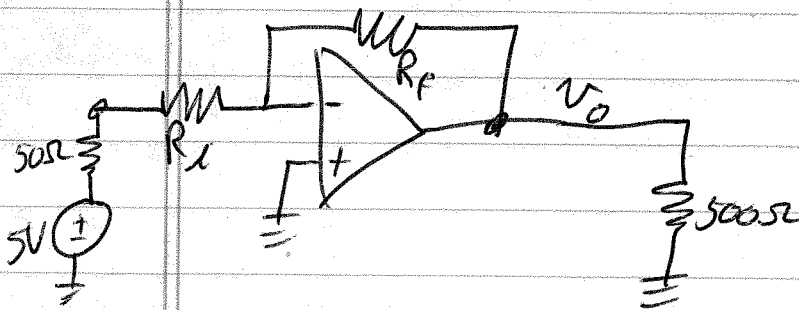Can get this either inverting or non-inverting:



$$v_o = - \frac{R_F}{R_i + 50\Omega} 5 \text{ V}$$

Such that  $\frac{R_F}{R_i + 50\Omega} = 2$   
Choose  $R_i$  large compared to  $50\Omega$ , say


$50 \text{ k}\Omega$ , ignore  $50\Omega$ , and pick  $R_F = 100 \text{ k}\Omega$ , so

$$\underline{v_o = - \frac{100 \text{ k}\Omega}{50 \text{ k}\Omega} 5 \text{ V} = -10 \text{ V}}$$

Could use any other combination of

$$R_f = 2R_i + R_i \gg 50\Omega$$

Non-inverting

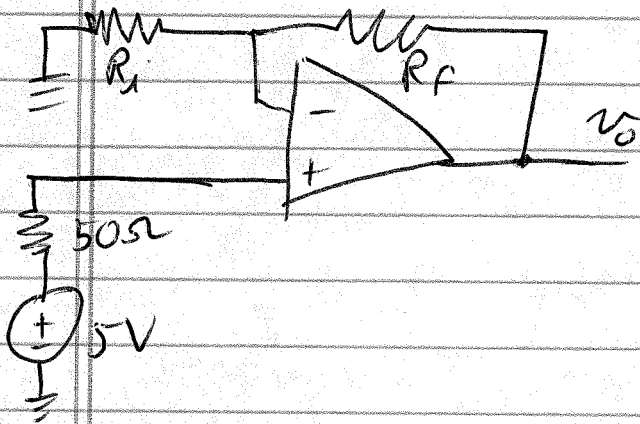

$$G = \left(1 + \frac{R_f}{R_i}\right) = 2$$

$$\text{or } \frac{R_f}{R_i} = 1$$

$$\text{or } R_f = R_i$$

No restrictions, although to keep currents reasonable we should use  $k\Omega$  range values.

Pick  $R_f = R_i = 10k\Omega$  and get

$$v_o = \left(1 + \frac{10k}{10k}\right) 5V = 2(5V) = \underline{\underline{10V}}$$

Pick from the 2?


- 1.) Noninverting draws no current from source, and uses same  $R$  values for  $R_f + R_i$  (no possibility of mixing them up)
- 2.) Inverting draws current from source (small.) + has different values for  $R_f + R_i$ .

Be sure to read the sections on  
 OP AMP Ckt. Design - (4-5)  
 Design + Evaluation Examples 4-22 + 4-23

and 4-6, OpAmp Circuit Applications


An example there is for "Instrumentation,"  
 a common use of Op Amps, taking a signal  
 from a sensor of some sort and changing  
 it to meet the needs of an input device  
 like an Analog to Digital Converter, or A/D  
 Converter, or ADC.

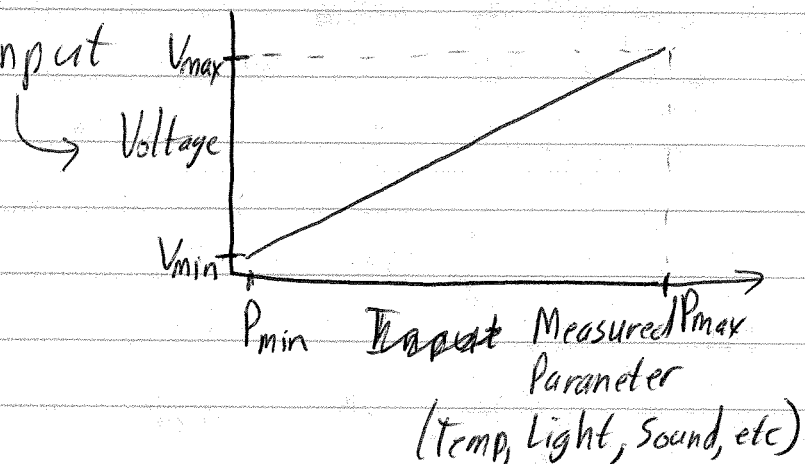The text shows examples of how to take  
 a linear input



180

and convert it to the desired range:

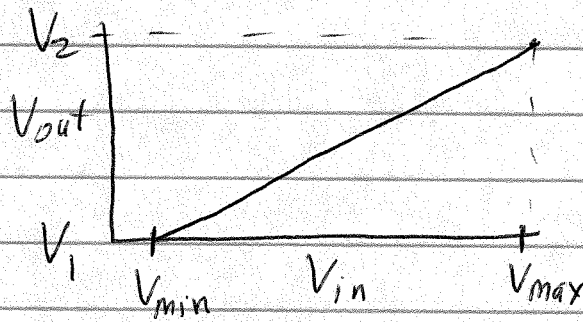


$$V_{out} = m V_{in} + b$$


$$m = \frac{V_2 - V_1}{V_{max} - V_{min}}$$

$$b = V_2 - m V_{max}$$

You can construct this using:

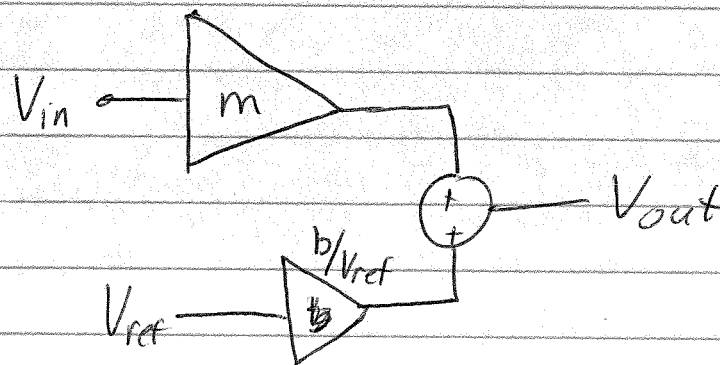

Example from text: Light meter

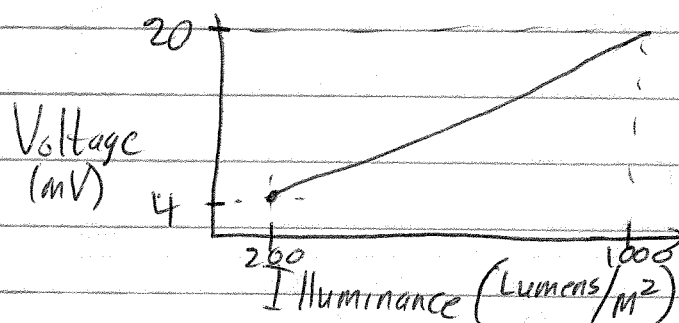

We want to scale this to fit an ADC that accepts 0-5V input.

Using our formulas:

$$m = \frac{5V - 0V}{20mV - 4mV} = \frac{5V}{16mV} = 312.5$$

$$b = 5V - (312.5)(20mV) = -1.25V$$

So our desired output will be

$$V_{out} = 312.5 V_{in} - 1.25V$$

312.5 is a little big to do in 1 step.

Factor it, choose an easy thing like

$$25: \quad \frac{312.5}{25} = 12.5 \text{ (exactly } \frac{1}{2} \text{ of 25, good)}$$

In the text, they chose to set the slope


with two inverting stages,  $312.5 = (-25)(-12.5)$

Let me do it as two noninverting stages

$$312.5 = (25)(12.5)$$


I will then subtract the intercept by scaling a standard voltage I can get in my circuit, say ~~1.25V~~ a regulated 5V, or scale by  $\frac{1.25V}{5V} = 0.25 = \frac{1}{4}$

Use a non inverting op amp to get the

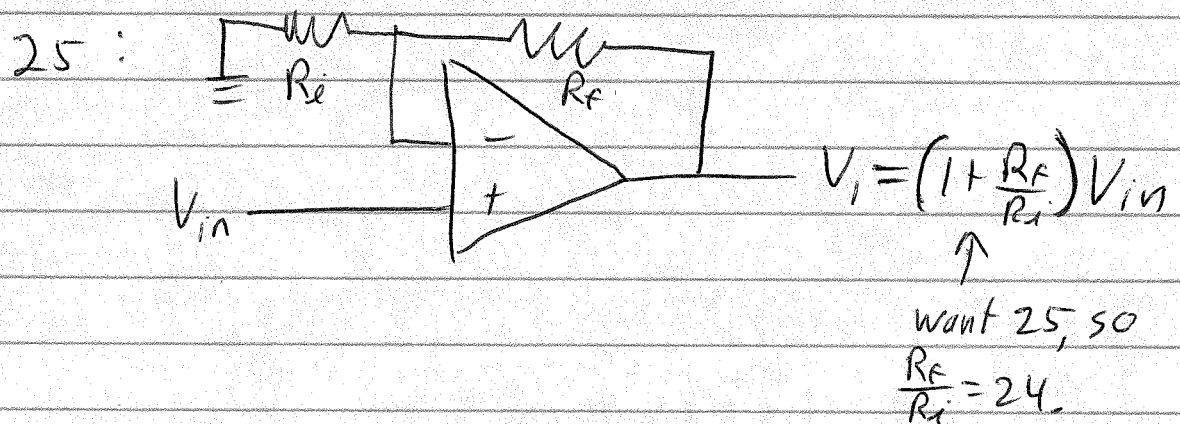

Pick  $R_i = 10k\Omega$ , so  
 $R_f = 240k\Omega$

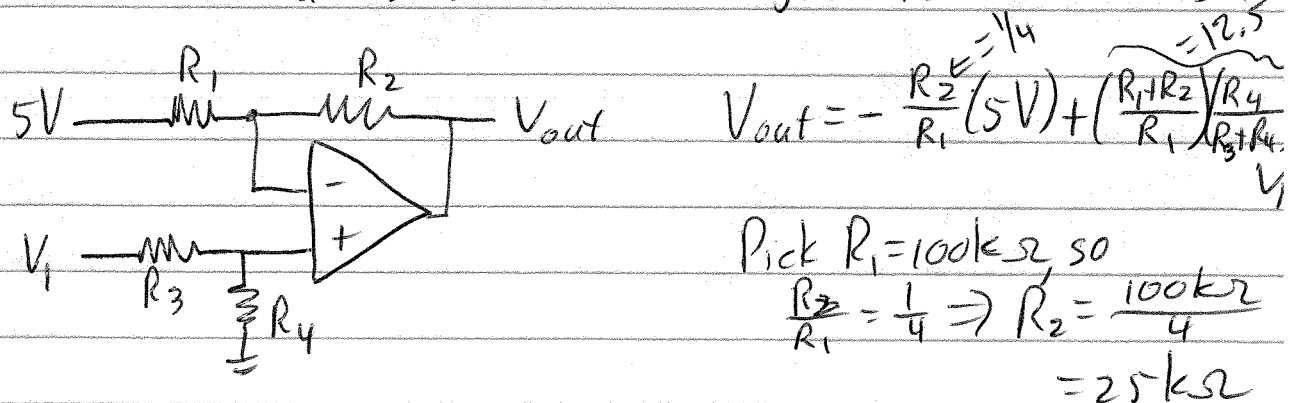Then use a subtractor to get  $12.5 + -0.25$ :





183

$$\text{So } \frac{R_1 + R_2}{R_1} = \frac{100\text{k}\Omega + 25\text{k}\Omega}{100\text{k}\Omega} = \frac{125\text{k}\Omega}{100\text{k}\Omega} = 1.25$$

$$\text{and we want } (1.25) \left( \frac{R_4}{R_3 + R_4} \right) = 12.5$$

$$\text{or } \frac{R_4}{R_3 + R_4} = 10$$

Pick  $R_3 = 100\text{k}\Omega$  (as a trial)

$$R_4 = 10(100\text{k}\Omega + R_4)$$

$$-9R_4 = 1000\text{k}\Omega$$

$$R_4 = -111.1\text{k}\Omega$$

↖ ! ! !

cannot do this ! ! !

$$\text{Look back: } V_{\text{out}} = - \frac{R_2}{R_1} (5V) + \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right)$$

↖ if this =  $\frac{1}{4}$ , then this =  $1\frac{1}{4}$ ,


requiring the  $\left( \frac{R_4}{R_3 + R_4} \right)$  to be

$> 1$ , but that is

impossible! !



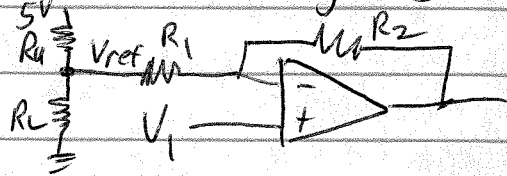So, we find out that this <sup>proposed solution</sup> ~~method~~ will not work, because of limitations on gains we can achieve.



Let's go ~~the~~ another way: Pick  ~~$\frac{R_4}{R_3 + R_4}$~~  to be

$R_4 = \infty$  (leave it out entirely) then  $R_3$

can be 0 and  $\frac{R_4}{R_3 + R_4} = 1. (\frac{\infty}{\infty})$

Now pick  $\frac{R_1 + R_2}{R_1} = 12.5$ , using  $R_2 = 100k\Omega$

$$R_1 + 100k\Omega = 12.5 R_1$$


$$100k\Omega = 11.5 R_1$$

$$R_1 = \frac{100k\Omega}{11.5} = 8.7k\Omega \text{ (This will be } R_1 + R_u // R_L \text{)}$$

Now  $\frac{R_2}{R_1} = \frac{100k\Omega}{8.7k\Omega} = 11.5$ , so to get

$$(11.5)(V_{ref}) = 1.25V \text{ we need } V_{ref} = \frac{1.25V}{11.5} = 0.1087V$$

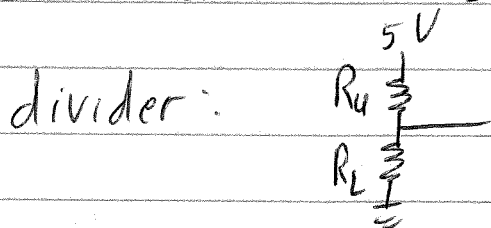I can achieve this from 5V using a voltage



divider:

$$0.1087V = \frac{R_L}{R_u + R_L} 5V$$

(185)

Pick  $R_L = 1\text{ k}\Omega$ , and get:

$$\left( \frac{1\text{ k}\Omega}{R_u + 1\text{ k}\Omega} \right) 5\text{ V} = 0.1087\text{ V}$$

$$\frac{1\text{ k}\Omega}{R_u + 1\text{ k}\Omega} = \frac{0.1087}{5} = 0.02174$$


$$1\text{ k}\Omega = 0.02174 R_u + 1\text{ k}\Omega(0.02174)$$

$$1\text{ k}\Omega - 21.74\Omega = 0.02174 R_u$$

$$\frac{978.26\Omega}{0.02174} = R_u = 45\text{ k}\Omega$$

$$\text{So } R_1 = 8.7\text{ k}\Omega - (1\text{ k}\Omega / 45\text{ k}\Omega) = 7.7\text{ k}\Omega$$

So this ckt should work:

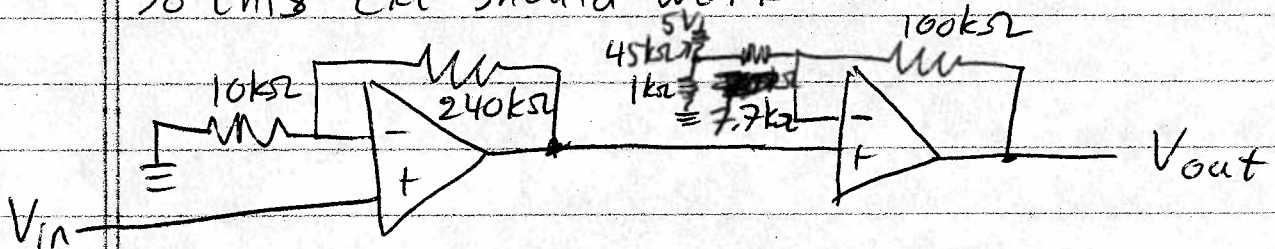

The text example came up with:

