

Superposition -

1) "Turn off" all ~~source~~ independent ideal sources:

$V_{src} \rightarrow$ short ckt ($V_s = 0$)

$I_{src} \rightarrow$ open ckt ($I_s = 0$)


2) Turn 1 src "on" and find output due to that src alone, Turn src "off"
Repeat for all N sources. (O_1, O_2, \dots, O_N)

3) Output with all sources on is (algebraic)


sum of ~~all~~ individual outputs:

$$O_T = \sum_{i=1}^N O_i$$

Text example:

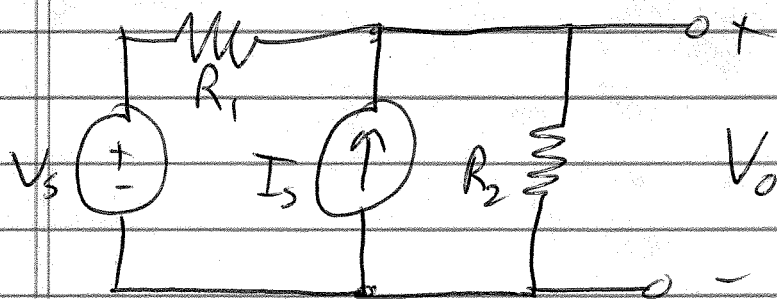

Could do src transformation:

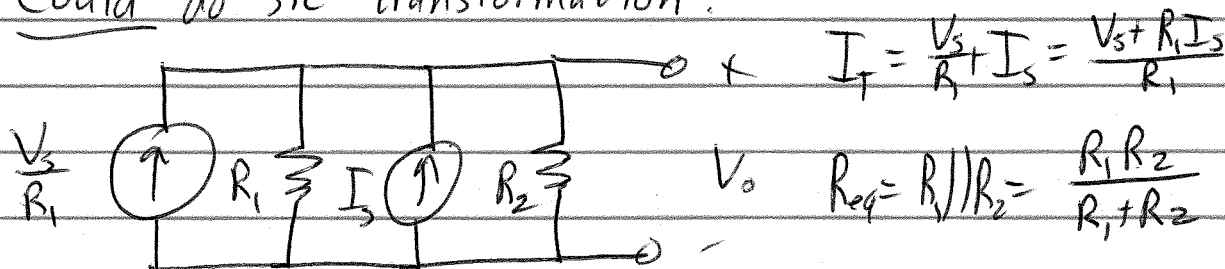


$$V_o = I_T R_{eq}$$

$$= \frac{V_s + R_1 I_s}{R_1} \cdot \frac{R_1 R_2}{(R_1 + R_2)} \quad \cancel{+ \frac{R_1 R_2}{R_1 + R_2} I_s}$$

$$\underline{V_o = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} I_s}$$

Or, we could use superposition!

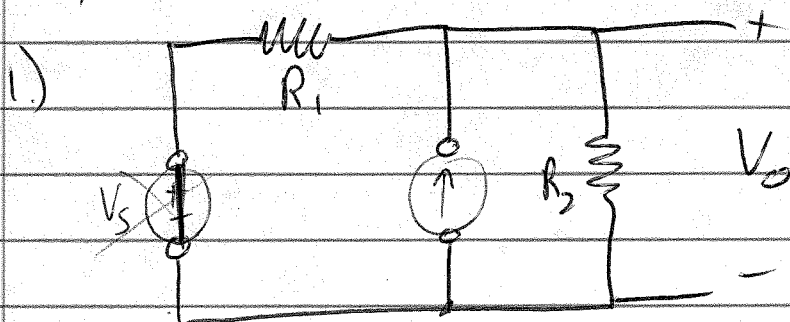

2) a) Turn on V_s , leave $I_s = 0$:
(draw)

Voltage Division: $V_{o1} = \frac{R_2}{R_1 + R_2} V_s$


b) V_s off, I_s on: I_s into parallel R 's:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}, \quad V_{o2} = \frac{R_1 R_2}{R_1 + R_2} I_s$$

3) Total:

$$\underline{V_o = V_{o1} + V_{o2} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} I_s}$$

Expand Example in Text:

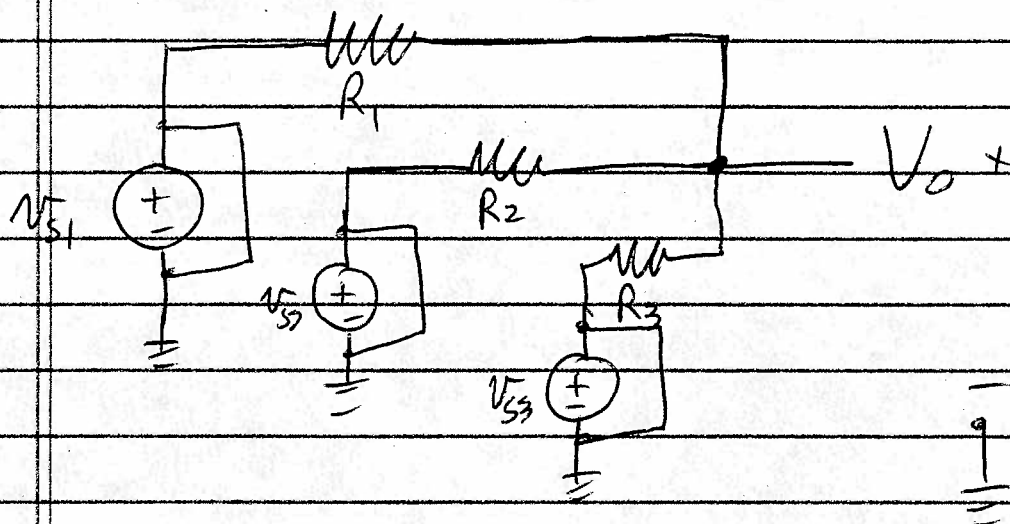

Superposition:

1) All off: ...

$$\begin{aligned}
 2.) \text{ a.) } v_{s1} \text{ on: } V_{o1} &= \frac{R_2 // R_3}{R_1 + R_2 // R_3} v_{s1} \\
 &= \frac{\frac{R_2 R_3}{R_2 + R_3}}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} v_{s1} \\
 &= \frac{\frac{R_2 R_3}{R_2 + R_3}}{\frac{R_1(R_2 + R_3) + R_2 R_3}{R_2 + R_3}} v_{s1}
 \end{aligned}$$

$$\begin{aligned}
 V_{o1} &= \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} v_{s1} \\
 \text{turn } v_{s1} \text{ off:}
 \end{aligned}$$

$$\text{b.) } v_{s2} \text{ on: } V_{o2} = \frac{R_1 // R_3}{R_2 + R_1 // R_3} v_{s2}$$

$$= \frac{R_1 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} v_{s2}$$

turn v_{s2} off

(111)

c) turn v_{s3} on: $V_{03} = \frac{R_1 // R_2}{R_3 + R_1 // R_2} v_{s3}$

$$V_{03} = \frac{R_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} v_{s3}$$

3) Turn all on:

$$V_o = V_{01} + V_{02} + V_{03}$$

$$= \frac{R_2 R_3 v_{s1} + R_1 R_3 v_{s2} + R_1 R_2 v_{s3}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

If all R's are equal: $R_1 = R_2 = R_3 = R$, then

$$V_o = \frac{R^2 v_{s1} + R^2 v_{s2} + R^2 v_{s3}}{R^2 + R^2 + R^2} = \frac{R^2 (v_{s1} + v_{s2} + v_{s3})}{3R^2}$$

$$V_o = \frac{1}{3} (v_{s1} + v_{s2} + v_{s3}) \quad (\text{Average})$$

or $= \frac{1}{3} v_{s1} + \frac{1}{3} v_{s2} + \frac{1}{3} v_{s3} \quad (\text{Weighted Sum})$

If R's not equal:

$$V_o = \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} v_{s1} + \frac{R_1 R_3}{R^2} v_{s2} + \frac{R_1 R_2}{R^2} v_{s3}$$

$$V_o = \frac{1}{\frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 R_3}} v_{s1} + \dots$$

$$V_o = \frac{1}{1 + \frac{R_1}{R_3} + \frac{R_1}{R_2}} v_{s1} + \dots$$