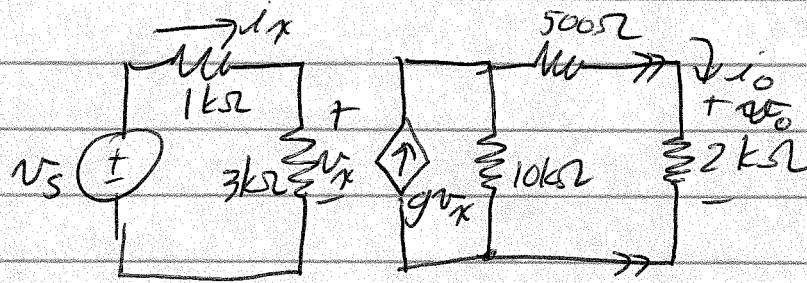


# HW 5 - Solutions

①

4-3 Find voltage gain and current gain ( $i_o/i_x$ ) for  $g = 2 \times 10^{-3} \text{ S}$ . For  $v_s = 5 \text{ V}$  find the power supplied by the input source and the power delivered to the load.



$$v_x = \frac{3 \text{ k}\Omega}{3 \text{ k}\Omega + 1 \text{ k}\Omega} v_s = \frac{3}{4} v_s$$

$$i_x = \frac{v_s}{4 \text{ k}\Omega} = .25 \times 10^{-3} v_s$$

Current division

$$i_o = \frac{10 \text{ k}\Omega}{2 \text{ k}\Omega + 500 \Omega + 10 \text{ k}\Omega} g v_x$$

$$= \frac{10 \text{ k}\Omega}{12.5 \text{ k}\Omega} g v_x$$

$$= \frac{1}{1.25} g v_x = \frac{4}{5} g v_x = 0.8 g v_x$$

$$i_o = (0.8)(2 \times 10^{-3}) v_x =$$

$$i_o = 1.6 \times 10^{-3} v_x = 1.6 \times 10^{-3} \left( \frac{3}{4} v_s \right) = 1.2 \times 10^{-3} v_s$$

$$v_o = 2 \text{ k}\Omega i_o = 3.2 v_x = 3.2 \left( \frac{3}{4} v_s \right) = 2.4 v_s$$

$$\text{Voltage Gain} = \frac{v_o}{v_s} = \frac{2.4 v_s}{v_s} = 2.4$$

$$\text{Current Gain} = \frac{i_o}{i_x} = \frac{1.2 \times 10^{-3} v_s}{.25 \times 10^{-3} v_s} = 4.8$$


(2)

$$v_o = 2.4 v_s = 2.4(5V) = 12V$$

$$P_L = \frac{v_o^2}{R_L} = \frac{(12V)^2}{2k\Omega} = \frac{144}{2k} W = \underline{72mW}$$

$$P_S = -i_x(5V) = -(0.25 \times 10^{-3})(5V)(5V) \\ = -625 \times 10^{-5} W = \underline{-6.25mW}$$

4-9 Find an expression for  $v_o/v_s$ :

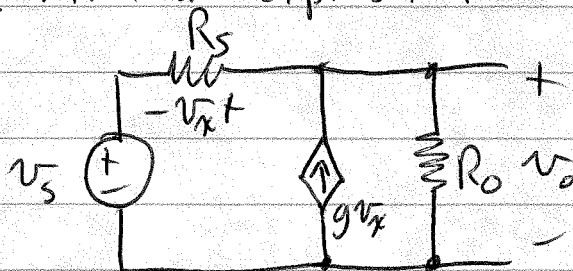

Nodal Analysis:  $\frac{v_o - v_s}{R_s} - g v_x + \frac{v_o}{R_o} = 0$

$$\left(\frac{1}{R_s} + \frac{1}{R_o}\right)v_o - \frac{1}{R_s}v_s - g(v_o - v_s) = 0$$


$$\left(\frac{1}{R_s} + \frac{1}{R_o} - g\right)v_o - \left(\frac{1}{R_s} - g\right)v_s = 0$$

$$\left(\frac{R_o + R_s - g R_o R_s}{R_o R_s}\right)v_o = \left(\frac{1 - g R_s}{R_s}\right)v_s$$

$$v_o = \left(\frac{R_o}{R_o + R_s - g R_o R_s}\right)(1 - g R_s)v_s$$

$$\boxed{\frac{v_o}{v_s} = \frac{R_o(1 - g R_s)}{(R_o + R_s - g R_o R_s)}}$$

(3)

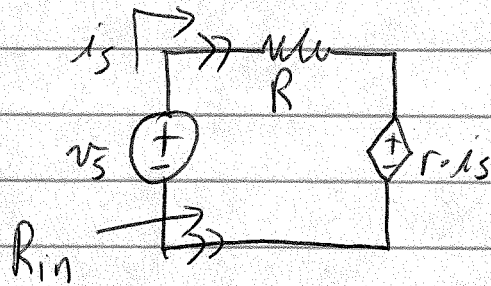4-15 Find  $R_{in}$ 

$$R_{in} = \frac{v_s}{i_s}$$

$$i_s = \frac{v_s - r \cdot i_s}{R} = \frac{1}{R} v_s - \frac{r}{R} i_s$$

$$\left(1 + \frac{r}{R}\right) i_s = \frac{1}{R} v_s$$


$$\frac{R+r}{R} i_s = \frac{1}{R} v_s$$

$$i_s = \frac{1}{R+r} v_s$$

$$R_{in} = \frac{v_s}{\frac{1}{R+r} v_s} = \underline{R+r}$$


(4)

4-23 Find the voltage gain of each:

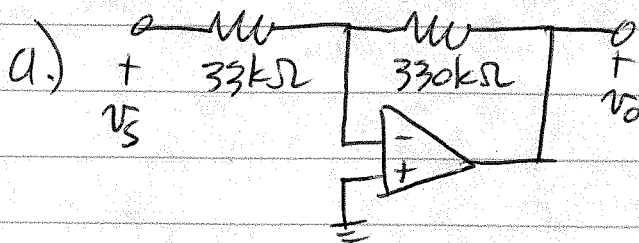

Inverting:
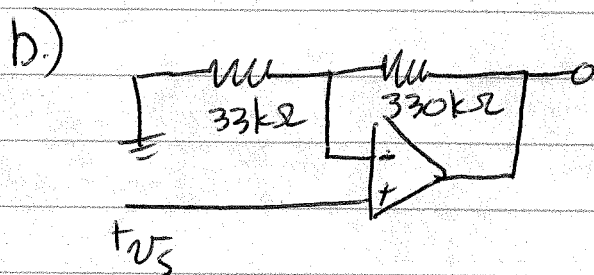
$$G = -\frac{330k\Omega}{33k\Omega} = -10$$




Noninverting

$$G = 1 + \frac{330k}{33k} = 11$$

4-25 Two Opamp ckts claim to have  $|G| = 100$ .


a.) Show that the claims are true.

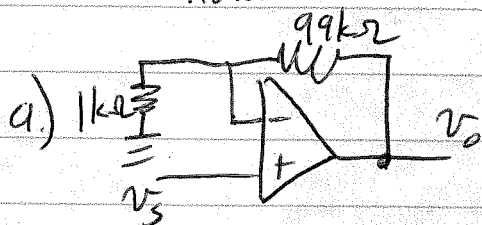b.) A practical src ~~at~~ with  $1k\Omega$  resistance is connected to input of each. Does the claim still hold?



Non inverting:
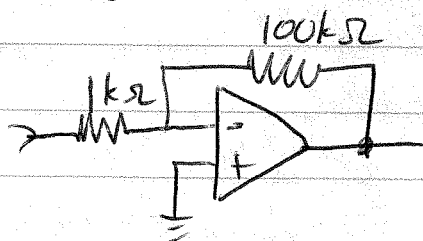
$$\text{Gain} = \left(1 + \frac{99k}{1k}\right) = 100 \checkmark$$




Inverting:

$$\text{Gain} = -\frac{100k}{1k} = -100 \checkmark$$

b.) Connecting to Non-Inverting, still holds.  $\checkmark$   
 Connecting to Inverting we must include internal  $R$  in Gain:  $G = -\frac{100k}{2k} = -50$

(5)

4-31 For ckt below,

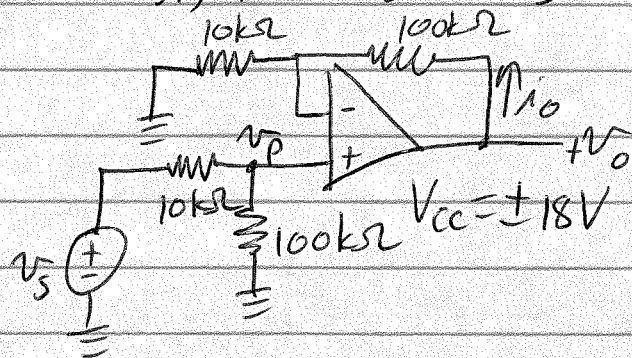a.) Find  $v_o$  in terms of  $v_s$ b.) Find  $i_o$  for  $v_s = 0.5V$ . Repeat for  $v_s = 2V$ .

a.) Non Inverting:  $v_o = \left(1 + \frac{100k}{10k}\right) v_p = 11 v_p$

Voltage Division:  $v_p = \frac{100k}{100k + 10k} v_s = \frac{10}{11} v_s$

So  $v_o = 11 \left(\frac{10}{11}\right) v_s = 10 v_s$

b.)  $i_o = \frac{v_o - v_p}{100k\Omega} = \frac{10 v_s - \frac{10}{11} v_s}{100k\Omega} = \frac{\frac{110 - 10}{11} v_s}{100k\Omega}$

$i_o = \frac{100}{11} v_s / 100k\Omega = \frac{1}{11} v_s \text{ (mA)}$

For  $v_s = \frac{1}{2}V$ ,  $i_o = \frac{1}{11} \left(\frac{1}{2}\right) \text{ mA} = \frac{1}{22} \text{ mA} = 0.045 \text{ mA}$   
 $v_o = 10 \left(\frac{1}{2}\right) = 5V$

For  $v_s = 2V$ ,  $i_o = \frac{1}{11} (2) \text{ mA} = \frac{2}{11} \text{ mA}$   
 $v_o = 10(2V) = 20V$  which exceeds  $V_{cc}$ ,

so  $v_o = 18V$  and  $i_o = \frac{(18 - \frac{10}{11}(2))V}{100k\Omega}$

$i_o = \frac{198 - 20}{11} = \frac{178}{11}$   
 $= 0.161 \text{ mA}$