

Let's combine Parallel RLC and RLC Step

Response into some examples.


First, we have to allow for there to be a
Forced Response (same type as the driving source)
in addition to the Natural Response:

$$y(t) = \text{Natural Response} + \text{Forced Response}$$

$\begin{array}{cc} \text{decays to zero} & \text{remains at} \\ \text{as } t \rightarrow \infty & t \rightarrow \infty \end{array}$

We have to evaluate constants ($A+B, C+D, E+F$) with
~~For example~~
the Forced Response included.

For example:

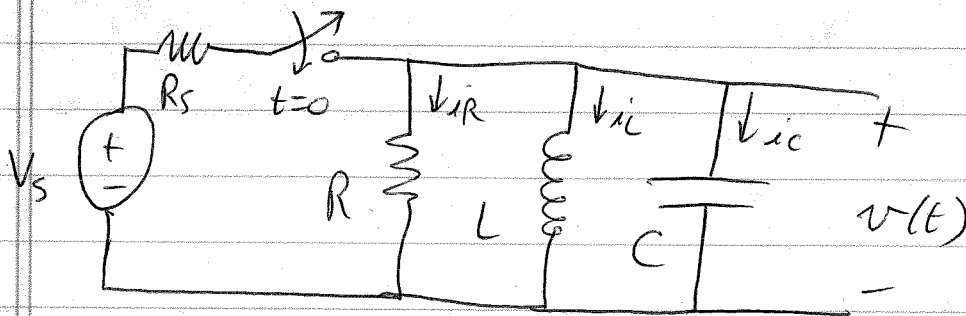


Find $v(t)$

$t=0^-$: Switch open, L a short, Can open clkt.

$$\left. \begin{array}{l} v(0^-) = 0 \\ i_L(0^-) = 0 \end{array} \right\} \text{source-free}$$

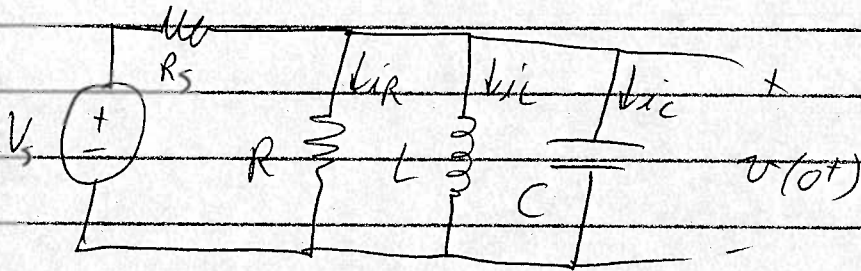$t=0^+$: Switch closed, but no charges have moved yet.



$$v(0^+) = 0 \quad (\text{b.c. } v_C \text{ must be continuous})$$

Look at V_{th} and $i_R = \frac{v(0^+)}{R}$. $i_L(0^+) = \frac{1}{L} \int_{-\infty}^{0^+} v(t) dt + i_L(0^-)$ $i_C = C \frac{dv}{dt}(0^+)$

$$\text{KCL: } \frac{v(t) - V_s}{R_s} + \frac{v(t)}{R} + i_L + C \frac{dv}{dt} = 0 \quad (\text{General})$$


$$t=0^+: \frac{v(0^+) - V_s}{R_s} + \frac{v(0^+)}{R} + i_L(0^+) + C \frac{dv}{dt}(0^+) = 0$$

$$C \frac{dv}{dt}(0^+) = \frac{V_s}{R_s}$$

$$\frac{dv}{dt}(0^+) = \frac{1}{R_s C} V_s$$

R_{eq} : Turn off V_s (short) ask what R_{eq} is seen by LC ? $R_{eq} = R_s // R$

$t=\infty$:

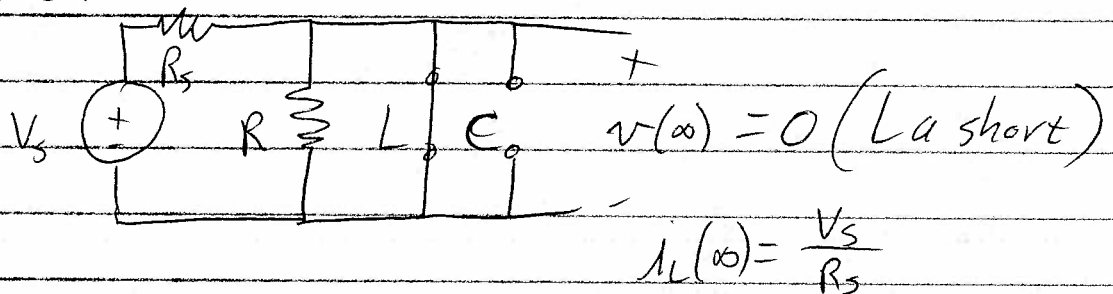

Now we need to know values:

Let's use $V_s = 5V$, $R_1 = 2k\Omega$, $R_2 = 2k\Omega$,

$L = 1H$, $C = \frac{1}{4}\mu F$ (as before.)

So, as before, $\omega_0 = \frac{1}{\sqrt{LC}} = 2,000 s^{-1}$

a.) Pick $R = 2k\Omega + R_s = 2k\Omega$, so $R_{eq} = 2k\Omega / 2k\Omega = 1k\Omega$

Now $\alpha_{par} = \frac{1}{2R_{eq}C} = \frac{1}{2(1k\Omega)(\frac{1}{4}\mu F)} = 2,000 s^{-1}$

So ckt. is Critically Damped.

$$v(t) = (C + Dt)e^{-\alpha t} + v(\infty)$$

but $v(\infty) = 0$, so

$$v(t) = (C + Dt)e^{-\alpha t}$$

$v(0^+) = 0 = C$, so

$$v(t) = Dt e^{-\alpha t}$$

$$\frac{dv}{dt} = D[e^{-\alpha t} - \alpha t e^{-\alpha t}]$$

$$= D e^{-\alpha t} [1 - \alpha t]$$

$$\frac{dv}{dt}(0) = D(1)[1] = D$$


(244)

$$D = \frac{1}{R_s C} V_s = \frac{1}{(2k)(\frac{1}{4}\mu)} (5V)$$

$$D = \frac{1}{\frac{1}{2}m} 5V = (2000)(5V) = 10,000 V/s$$

So
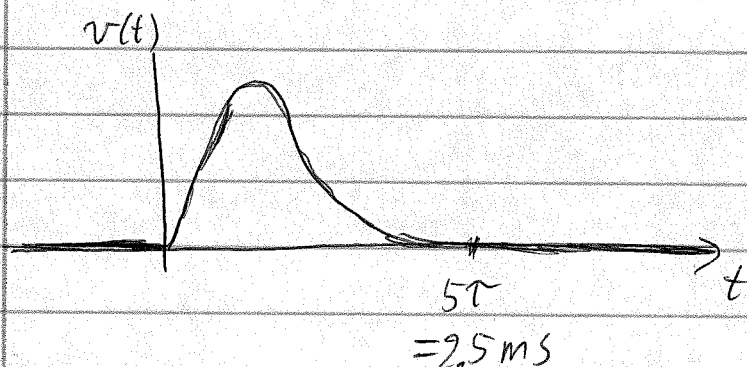
$$v(t) = (10,000 \frac{V}{s}) t e^{-2,000t} \quad \left(\tau = \frac{1}{2000} s = 500 \mu s \right)$$



Let's now pick $R = 10k\Omega$ & $R_s = 10k\Omega$, so

$R_{eq} = 5k\Omega$, AND let's ask for $i_L(t)$.

$$t=0^-: v(0^-) = 0 = v(0^+)$$

$$i_L(0^-) = 0 = i_L(0^+)$$

$$t=0^+: i_L(0^+) = 0 \text{ still}$$

$$IV: v_L = L \frac{di_L}{dt} \Rightarrow L \frac{di_L}{dt}(0^+) = v(0^+) = 0$$

$$\underline{\underline{\frac{di_L}{dt}(0^+) = 0}}$$

~~transient $i_L(t)$~~


$$R_{eq} = 5k\Omega, \text{ so } \alpha = \frac{1}{2R_{eq}C} = \frac{1}{2(5k)(\frac{1}{4}\mu)} = \frac{2}{5} k$$

$$= 400 s^{-1}$$

So underdamped: $\omega_d = \sqrt{(2000)^2 - (400)^2} = 1960$

$$i_L(t) = e^{-\alpha t} [E \cos \omega_d t + F \sin \omega_d t] + i_L(\infty)$$
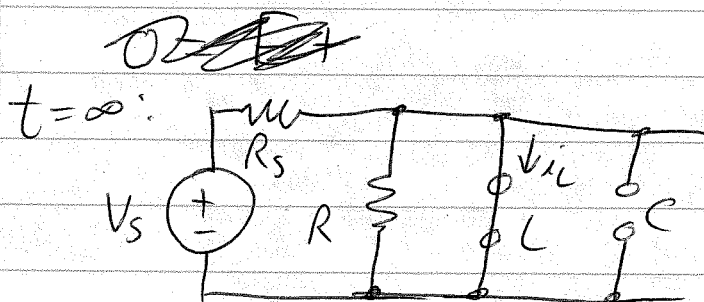
$$i_L(0^+) = (1) [E(1) + F(0)] + i_L(\infty)$$



All current through L : $i_L(\infty) = \frac{V_s}{R_s}$

Substitute

$$i_L(0^+) = (1) [E(1) + F(0)] + \frac{V_s}{R_s} = 0$$

$$E = -\frac{V_s}{R_s} = -\frac{5V}{5k} = -1 \times 10^{-3}$$

$$\frac{di}{dt} = -\alpha e^{-\alpha t} [E \cos \omega_d t + F \sin \omega_d t] + \omega_d e^{-\alpha t} [-E \sin \omega_d t + F \cos \omega_d t] + 0$$

$$\frac{di}{dt}(0^+) = -\alpha [E] + \omega_d [F]$$

For ours: $\frac{di}{dt}(0^+) = 0 = -400 \left(-\frac{V_s}{R_s} \right) + (1960)(F)$


$$1960 F = -400 \left(\frac{5V}{5k} \right)$$

$$= -0.4$$

$$F = -\frac{0.4}{1960} = -204 \times 10^{-6}$$

$$i_L(t) = e^{-400t} \left[-1 \times 10^3 \cos(1960t) - 204 \times 10^{-6} \sin(1960t) \right] + 1 \times 10^{-3}$$

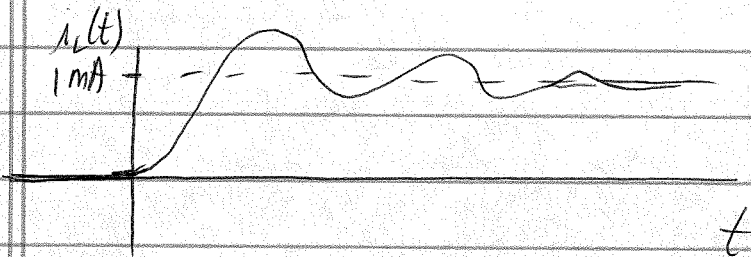
$$= e^{-400t} \left[-1 \text{ mA} \cos(1960t) - 0.204 \text{ mA} \sin(1960t) \right] + 1 \text{ mA}$$



$$\tau = \frac{1}{400} = 2.5 \times 10^{-3} = 2.5 \text{ ms}$$


$$T = \frac{2\pi}{\omega_d} = \frac{2\pi}{1960} = 3.2 \text{ ms} = \underline{\underline{1.28\tau}}$$

So should be:

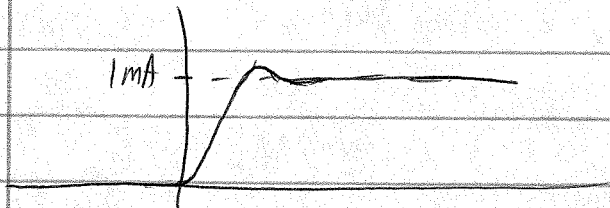


(247)

Note a couple of things

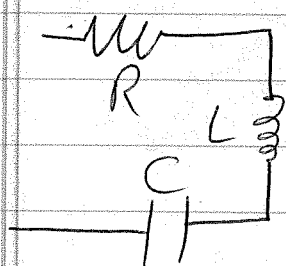

Series
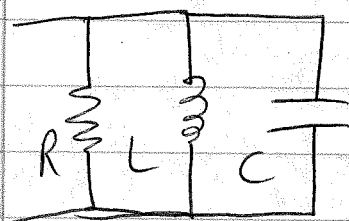
$$\alpha = \frac{R}{2L} \quad \uparrow R \quad \uparrow \alpha$$



Parallel

$$\alpha = \frac{1}{2RC} \quad \uparrow R \quad \downarrow \alpha$$

In under damped ckt, energy moves back and forth between $L + C$, with some being dissipated in R on each move.

In series, i must move thru R , so increasing R "burns up" more energy, so $\alpha \uparrow$. R active when L has energy.

In parallel, i can go straight from L to C , some goes thru R because of voltage, most when v is largest, when C stores the energy.

We wrote $\omega_0 = \frac{1}{\sqrt{LC}}$

and $\alpha = \frac{R_{eq}}{2L}$ or $\frac{1}{2RC}$

Text uses $\zeta \omega_0 = \alpha$ where ζ is the damping ratio

$$\zeta = \frac{\alpha}{\omega_0} = \frac{\sqrt{LC} R_{eq}}{2L} = \frac{1}{2} \sqrt{\frac{C}{L}} R_{eq} \text{ (series)}$$

Using this ~~ζ~~ notation: $\frac{\sqrt{LC}}{2RC} = \frac{1}{2} \sqrt{\frac{L}{C}} \frac{1}{R_{eq}} \text{ (parallel)}$

$\zeta > 1 \Rightarrow$ overdamped

$\zeta = 1 \Rightarrow$ critically damped

$\zeta < 1 \Rightarrow$ under damped

$$\text{and } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\zeta \omega_0 \pm \sqrt{(\zeta \omega_0)^2 - \omega_0^2}$$

$$= \omega_0 [-\zeta \pm \sqrt{\zeta^2 - 1}]$$

I will stick to $\alpha + \omega_0$ and not use ζ .