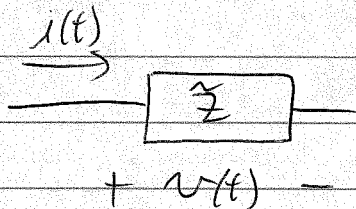


Now, let's ask about the power dissipated in an impedance. We must do the power calculation in the Time domain, because it is not linear:



$$p(t) = v(t) i(t)$$

Given $v(t) = V_0 \cos(\omega t)$

$$\tilde{Z} = Z_0 \angle \theta$$

Phasor Domain

$$\hat{V} = V_0 \angle 0^\circ$$

$$\tilde{Z} = Z_0 \angle \theta$$

$$\hat{I} = \frac{\hat{V}}{\tilde{Z}} = \frac{V_0 \angle 0^\circ}{Z_0 \angle \theta} = \frac{V_0}{Z_0} \angle -\theta$$

$$i(t) = \frac{V_0}{Z_0} \cos(\omega t - \theta)$$

$$p(t) = V_0 \cos(\omega t) \left(\frac{V_0}{Z_0} \cos(\omega t - \theta) \right)$$

$$= \frac{V_0^2}{Z_0} \cos(\omega t) \cos(\omega t - \theta)$$

$$= \frac{V_0^2}{Z_0} \cos(\omega t) [\cos(\omega t) \cos(\theta) + \sin(\omega t) \sin(\theta)]$$

$$= \frac{V_0^2}{Z_0} [\cos^2(\omega t) \cos(\theta) + \cos(\omega t) \sin(\omega t) \sin(\theta)]$$

Recall:

$$\begin{aligned}\cos(2\omega t) &= \cos(\omega t + \omega t) \\ &= \cos(\omega t)\cos(\omega t) - \sin(\omega t)\sin(\omega t) \\ &= \cos^2(\omega t) - \sin^2(\omega t) \\ &= \cos^2(\omega t) - [1 - \cos^2(\omega t)] = 2\cos^2(\omega t) - 1\end{aligned}$$

~~$$\text{or } \cos^2(\omega t) = \frac{1}{2}(\cos(2\omega t) + \sin^2(\omega t))$$~~

$$\text{or } \cos^2(\omega t) = \frac{1}{2}(\cos(2\omega t) + 1)$$

$$\begin{aligned}\text{And } \sin(2\omega t) &= \sin(\omega t + \omega t) \\ &= \sin(\omega t)\cos(\omega t) + \cos(\omega t)\sin(\omega t) \\ &= 2\sin(\omega t)\cos(\omega t)\end{aligned}$$

$$\text{So } p(t) = \frac{V_0^2}{Z_0} \left[\frac{1}{2}(\cos(2\omega t) + 1)\cos(\theta) + \frac{1}{2}\sin(2\omega t)\sin(\theta) \right]$$

$$= \frac{V_0^2}{Z_0} \left[\frac{1}{2}\cos\theta + \frac{1}{2}(\cos(2\omega t)\cos(\theta) + \sin(2\omega t)\sin(\theta)) \right]$$

$$= \frac{V_0^2}{Z_0} \left[\frac{1}{2}\cos(\theta) + \frac{1}{2}\cos(2\omega t - \theta) \right]$$


$$\underline{p(t) = \frac{1}{2} \frac{V_0^2}{Z_0} [\cos(\theta) + \cos(2\omega t - \theta)]}$$

First, assume $\theta = 0$, that is, \tilde{Z} is a resistor: $Z_0 = R$

$$p_R(t) = \frac{1}{2} \frac{V_0^2}{R} [1 + \cos(2\omega t)]$$

$$p(t) = \frac{1}{2} \frac{V_0^2}{Z_0} [\cos(\theta) + \cos(2\omega t - \theta)]$$

If we have a capacitor only,

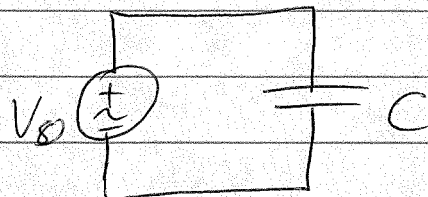


then $Z_c = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$, $\theta = -90^\circ$ and $\cos(\theta) = 0$.

$$p_c(t) = \frac{1}{2} \frac{V_0^2}{Z_0} [\cos(2\omega t + 90^\circ)]$$

$$p_c(t) = \frac{1}{2} \omega C V_0^2 [\cos(2\omega t + 90^\circ)]$$

If an inductor:

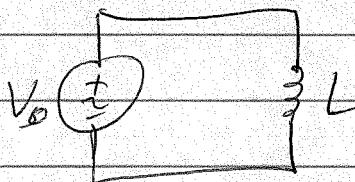

$$Z_L = j\omega L = \omega L \angle 90^\circ$$

$$\cos(90^\circ) = 0$$

$$p_L(t) = \frac{1}{2} \frac{V_0^2}{\omega L} [\cos(2\omega t - 90^\circ)]$$

The instantaneous power is interesting, but what matters more is the Time Average Power,

$$P = \frac{1}{T} \int_0^T p(t) dt = \text{Average Power, where } T = \frac{1}{f} = 1 \text{ period of } \cos(\omega t)$$

~~$$P_R = \frac{1}{T} \int_0^T \frac{1}{2} V_R I_R \cos(2\omega t) dt = 0$$~~

Look at P for each component:

$$\begin{aligned} P_R &= \frac{1}{T} \int_0^T \frac{1}{2} V_R I_R (1 + \cos(2\omega t)) dt \\ &= \frac{1}{T} \left(\frac{1}{2} V_R I_R \right) \left[\int_0^T dt + \int_0^T \cos(2\omega t) dt \right] \end{aligned}$$

$$P_R = \frac{1}{T} \left(\frac{1}{2} V_R I_R \right) [T + 0]$$

$$= \frac{1}{2} V_R I_R = \frac{1}{2} \frac{V_0^2}{R} = \frac{1}{2} R I_R^2$$

Note: ~~IF~~ Do not forget the $\frac{1}{2}$!!

Note: IF I distribute the 2 into $V_R + I_R$,

and call them V_{eff} or $V_{\text{RMS}} = \frac{V_R}{\sqrt{2}}$
and I_{eff} or $I_{\text{RMS}} = \frac{I_R}{\sqrt{2}}$

then $P_R = V_{\text{RMS}} I_{\text{RMS}} = \frac{V_{\text{RMS}}^2}{R} = I_{\text{RMS}}^2 R$ just like DC.

RMS is a way to get a positive number:
(Root Mean Square)

$$A \cos(\omega t)$$

$$\text{Avg} = 0$$

$$A^2 \cos^2(\omega t)$$

$$\text{Avg} = \frac{1}{2} A^2$$

$$\sqrt{A^2 \cos^2(\omega t)}$$

$$\text{Root MS} = \frac{1}{\sqrt{2}} A$$

Others:
$$P_c = \frac{1}{T} \int_0^T \frac{1}{2} \omega C V_c^2 \cos(2\omega t - 90^\circ) dt$$

$$= \frac{1}{T} \frac{1}{2} \frac{2\pi}{T} C V_c^2 \int_0^T \underbrace{\cos(2\omega t - 90^\circ)}_0 dt$$

$P_c = 0$ \square

And.
$$P_L = \frac{1}{T} \frac{1}{2\omega L} V_L^2 \int_0^T \underbrace{\cos(2\omega t + 90^\circ)}_0 dt$$

$P_L = 0$ \square

Inductors and Capacitors store some energy during $\frac{1}{2}$ the cycle, then return it to the circuit during the other half of the cycle, but do not dissipate any energy.

For a general impedance \tilde{Z} , let $\frac{V_0}{\tilde{Z}_0} = I_0$, then $\tilde{Z}_0 \angle \theta$

$$p(t) = \frac{1}{2} V_0 I_0 [\cos(\theta) + \cos(2\omega t - \theta)]$$

$$\text{and } P = \frac{1}{2} V_0 I_0 \left[\frac{1}{T} \int_0^T \cos(\theta) dt + \frac{1}{T} \int_0^T \cos(2\omega t - \theta) dt \right]$$

$$= \frac{1}{2} V_0 I_0 [\cos(\theta) + 0]$$

$$= \frac{1}{2} V_0 I_0 \cos(\theta) = V_{RMS} I_{RMS} \cos \theta$$