

We need to move on to Ch. 3 to get some tools for analyzing larger circuits systematically, ~~then~~ and for designing ckts. to meet specific needs.

There are 6 important sections, some longer, some shorter, so let's get started:


The first general technique is called, in this text, Node-Voltage Analysis, which I will sometimes call Nodal Analysis.

This is a very general method, it can be applied to all circuits, and is the basis for all the computer <sup>circuit analysis</sup> programs I know of.

## Node Voltage Analysis:

1) Uses the ~~idea~~ "altitude" idea and ~~finds~~ the Voltage of every node of a circuit with respect to one node, called the reference, or ground.

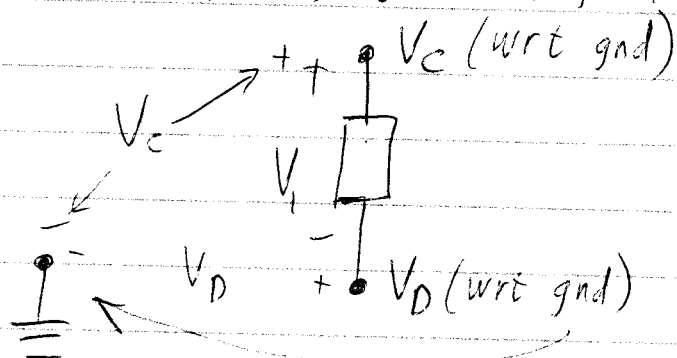2) The voltage drop across any element is then the Voltage of the node at the + end, minus the Voltage of the node at the - end.




$$V_1 = V_C - V_D$$

3) Write KCL at every node except the reference node.

4) Express each  $I$  in the KCL expressions in terms of the node voltages.

5) Collect terms and solve for the node voltages.

## Example

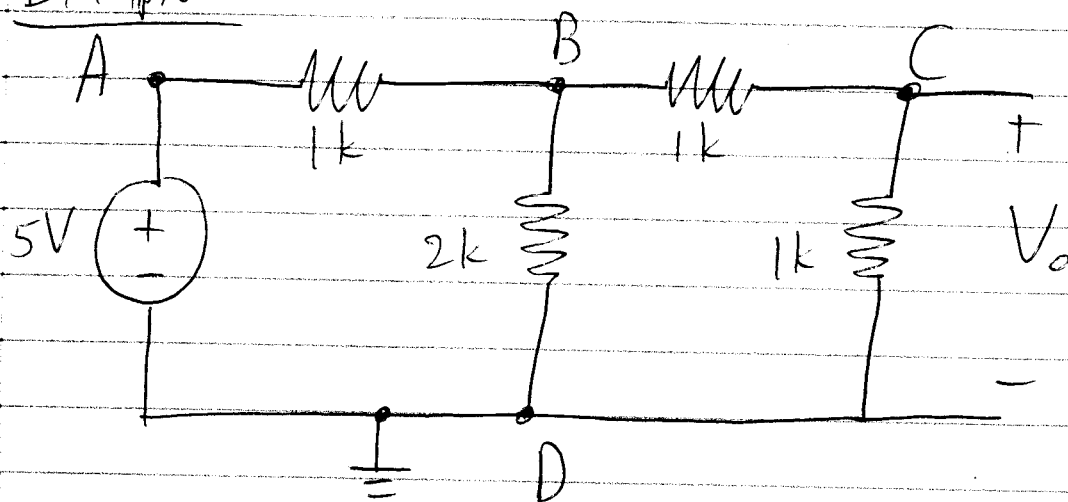

Label nodes - 4

Select Reference - D

Write desired output in terms of node  $V$ 's:  $V_o = V_c - V_D$   
 Remaining: 3 nodes

$$\underline{\underline{V_o = V_c}}$$

Voltage sources connected to Reference?

Yes -  $5V \Rightarrow \underline{\underline{V_A = 5V}}$  one is done.

Remaining: 2 nodes (B + C)

$$B: \frac{V_B - V_A}{1k} + \frac{V_B - 0}{2k} + \frac{V_B - V_C}{1k} = 0$$

$$\times 2k: 2(V_B - V_A) + V_B + 2(V_B - V_C) = 0$$

$$2V_B - 2V_A + V_B + 2V_B - 2V_C = 0$$

$\nwarrow$   
 known

$$\underline{\underline{5V_B - 2V_C = 2V_A = 2(5V) = 10V}}$$

$$C: \frac{V_c - V_B}{1k} + \frac{V_c - 0}{1k} = 0$$

$$\times 1k: V_c - V_B + V_c = 0$$

$$\begin{aligned} 2V_c - V_B &= 0 \\ \underline{2V_c} &= \underline{V_B} \end{aligned}$$

usual form. Now to solve for  $V_B + V_c$

$$\begin{aligned} \text{Back Substitute: } 5V_B - 2V_c &= 10V \\ 5V_B - V_B &= 10V \\ 4V_B &= 10V \end{aligned}$$

$$V_B = \frac{10}{4}V = 2.5V$$

$$V_c = \frac{1}{2}V_B = \frac{2.5V}{2} = \underline{\underline{1.25V}}$$

Another way to solve:

$$\begin{aligned} 2 \text{ Eqn's} \quad 5V_B - 2V_c &= 10V \\ -1V_B + 2V_c &= 0 \end{aligned}$$

$$\text{Write as matrix: } \begin{pmatrix} 5 & -2 \\ -1 & 2 \end{pmatrix} \begin{pmatrix} V_B \\ V_c \end{pmatrix} = \begin{pmatrix} 10V \\ 0 \end{pmatrix}$$

Add row 1 + row 2:  $\begin{pmatrix} 5-1 & 2-2 \end{pmatrix} \begin{pmatrix} V_B \\ V_C \end{pmatrix} = 10V$

$$\begin{pmatrix} 4 & 0 \end{pmatrix} \begin{pmatrix} V_B \\ V_C \end{pmatrix} = 10V$$

$$4V_B = 10V$$

$$V_B = 2.5V$$

$$2V_C = V_B$$

$$V_C = \frac{1}{2} V_B = \frac{2.5V}{2} = 1.25V$$