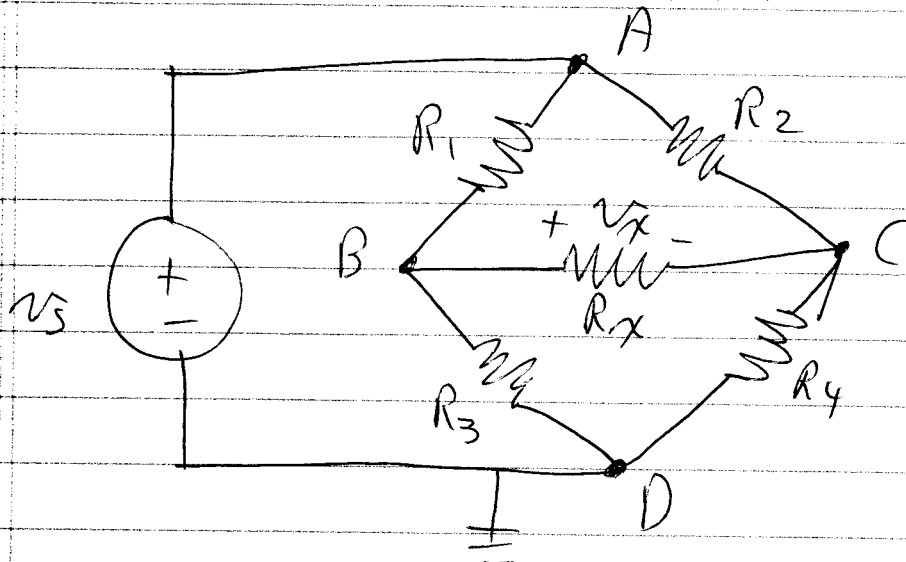


(84)

Let's look at another:

Prob 3-10
in text

D = reference

 $v_A = v_S$ (supernode w/reference)Only need $v_B + v_C$:

$$\frac{v_B - v_S}{R_1} + \frac{v_B - v_C}{R_x} + \frac{v_B}{R_3} = 0$$

$$(B) \quad \left(\frac{1}{R_3} + \frac{1}{R_1} + \frac{1}{R_x}\right)v_B - \frac{1}{R_x}v_C = \frac{1}{R_1}v_S$$

$$\frac{v_C - v_S}{R_2} + \frac{v_C - v_B}{R_x} + \frac{v_C}{R_4} = 0$$

$$(C) \quad -\frac{1}{R_x}v_B + \left(\frac{1}{R_2} + \frac{1}{R_x} + \frac{1}{R_4}\right)v_C = \frac{1}{R_2}v_S$$

Under what conditions will $v_x = 0$?Write in terms of nodes: $v_x = v_B - v_C$

$$v_x = 0 = v_B - v_C \Rightarrow v_B = v_C$$

If $v_B = v_C$ then we have:

$$\left(\frac{1}{R_3} + \frac{1}{R_1} + \cancel{\frac{1}{R_x}}\right)v_B - \cancel{\frac{1}{R_x}}v_B = \frac{1}{R_1}v_S$$

$$\underline{\left(\frac{1}{R_3} + \frac{1}{R_1}\right)v_B = \frac{1}{R_1}v_S = \left(\frac{R_1 + R_3}{R_1 R_3}\right)v_B}$$

and $-\cancel{\frac{1}{R_x}}v_B + \left(\frac{1}{R_2} + \cancel{\frac{1}{R_x}} + \frac{1}{R_4}\right)v_B = \frac{1}{R_2}v_S$

$$\left(\frac{1}{R_2} + \frac{1}{R_4}\right)v_B = \frac{1}{R_2}v_S = \left(\frac{R_4 + R_2}{R_2 R_4}\right)v_B$$

Re-write these as:

$$v_S = R_1 \left(\frac{R_1 + R_3}{R_1 R_3}\right)v_B = \frac{R_1 + R_3}{R_3}v_B$$

and $v_S = R_2 \left(\frac{R_2 + R_4}{R_2 R_4}\right)v_B = \frac{R_2 + R_4}{R_4}v_B$

Equate these: $\frac{R_1 + R_3}{R_3}v_B = \frac{R_2 + R_4}{R_4}v_B$


$$\frac{R_1 + R_3}{R_3} = \frac{R_2 + R_4}{R_4}$$

$$\frac{R_1}{R_3} + 1 = \frac{R_2}{R_4} + 1$$

$$\underline{\underline{\frac{R_1}{R_3} = \frac{R_2}{R_4}}}$$

This is often called a Wheatstone Bridge, and has taken on mystical stature. People immediately tense up when they hear ~~the~~ the name, but it really is very simple:

Another representation:

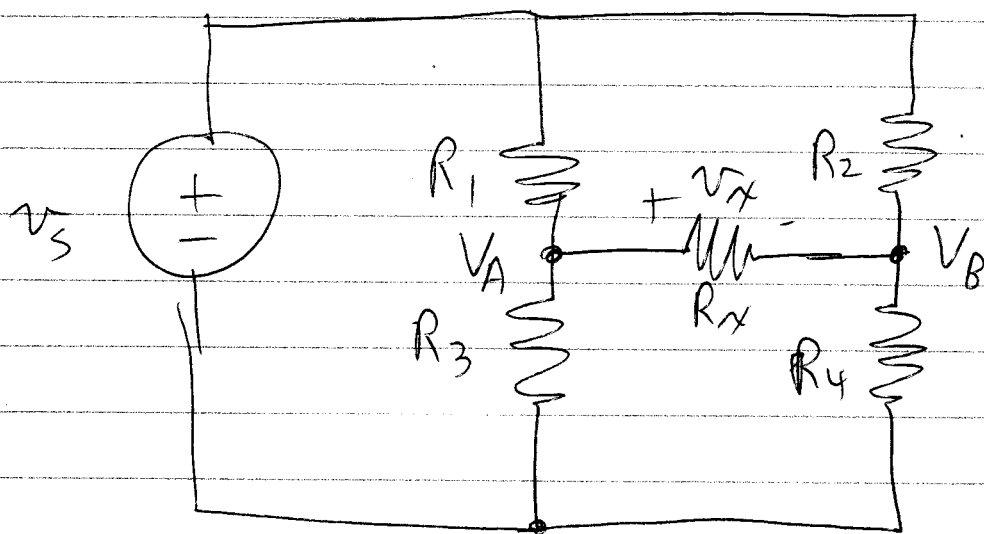

Do you agree this is the same?
If we remove R_x (erase) then we just have 2 voltage dividers, I can write

$$V_A = \frac{R_3}{R_1 + R_3} v_s \quad \text{and} \quad V_B = \frac{R_4}{R_2 + R_4} v_s$$

If these are to be equal, then

$$V_A = \left(\frac{R_3}{R_1 + R_3} \right) V_S$$

$$\frac{R_3}{R_1 + R_3} V_S = \frac{R_4}{R_2 + R_4} V_S$$

Take reciprocal: $\frac{R_1 + R_3}{R_3} = \frac{R_2 + R_4}{R_4}$

$$\frac{R_1}{R_3} + 1 = \frac{R_2}{R_4} + 1$$

as before.

We can do this because, when $V_X = 0$,
no current flows through R_X .