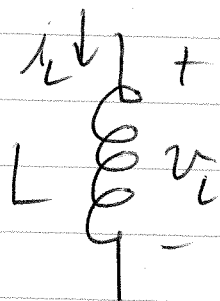


Inductors - the other energy storing element



IV:

$$v_L = L \frac{di}{dt}$$

L = inductance

Units: 1 Henry (H) = $\frac{1 \text{ V} \cdot \text{s}}{1 \text{ A}}$

Invert: $v_L = L \frac{di}{dt}$
 $\int_0^t v_L(x) dx = \int_{i(0)}^{i(t)} L di$

$$= L [i_L(t) - i_L(0)]$$

$$L i_L(t) = L i_L(0) + \int_0^t v_L(x) dx$$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(x) dx$$

\uparrow Final Condition \uparrow Initial Condition ($t=0$) $\underbrace{\hspace{2cm}}$ change from $t=0$ to $t=t$

or $i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(t') dt'$

or $i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(t) dt$

Again, mathematicians cringe, but we know.

Power + Energy

$$p_L(t) = i_L(t) v_L(t)$$

$$= i_L(t) L \frac{di_L}{dt}$$

$$= L i_L(t) \frac{di_L}{dt}$$

$$p_L(t) = \frac{di_L}{dt} \left(\frac{1}{2} L i_L^2(t) \right)$$

So $w_L(t) = \frac{1}{2} L i_L^2(t)$ is the energy stored
 \uparrow
 always positive (in the magnetic field)


and $p_L(t)$ is the rate at which energy is stored(t)
 or returned(-) to the system.

- Summary
1. $v_L = 0$ if i_L is a constant. L is a short ckt to DC.
 2. ~~Current~~ i_L is continuous, or cannot change instantaneously, $i_L(0^-) = i_L(0^+)$.
 3. Stores energy.

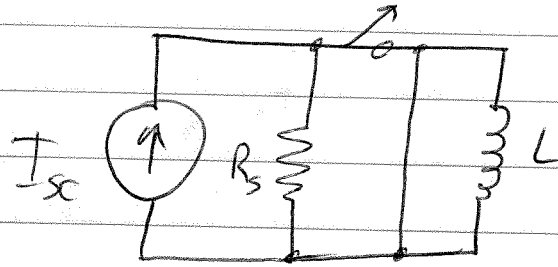Examples + Exercises (6-6 thru 6-8) in text.


Read + Do examples & Exercises 6-13 & 6-14 & 6-15.

L 's cannot store energy for as long as C 's can because they require a current to flow:



No matter how good you try to make it, there will be some resistance and it will dissipate the energy.

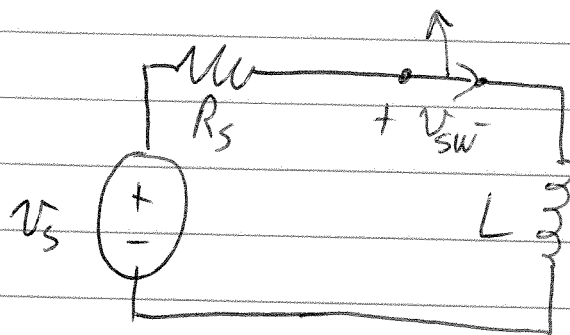L 's can generate big voltages when you try to turn them off:



An electric motor is an inductor
say in a fan.

Try turning this off suddenly and you can get big voltages across the switch, so big that sparks jump.