
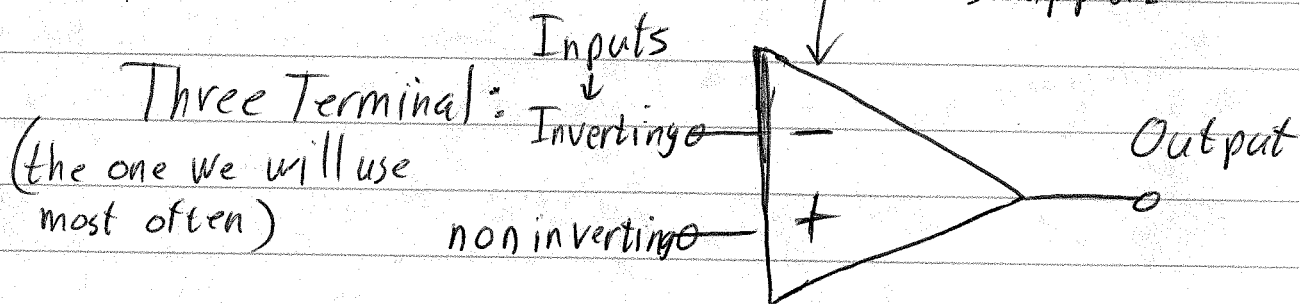


We're going to now introduce a device that you will not see in PHY 122, which contains a Dependent Source. It is the Operational Amplifier, or Op Amp. A pretty good history is in the book, page 177, so I will not repeat it here.

Symbols:

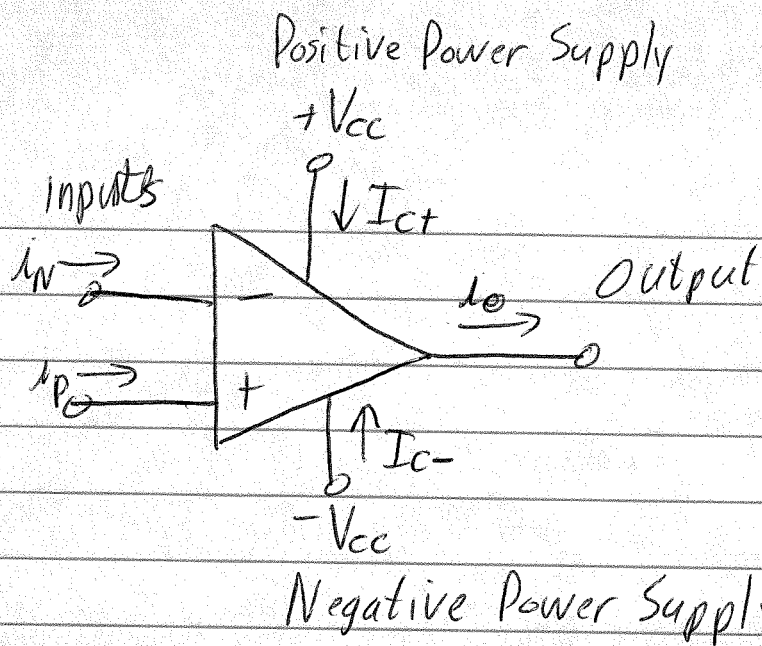

This contains a Dependent Source, so can insert energy into the circuit that contains it, so must be getting that energy from somewhere. It is implicit in the 3 Terminal model, and made explicit in the 5 Terminal model:




If we name currents in or out of all wires (draw and name) then we can apply KCL:

$$i_o = I_{C+} + I_{C-} - i_{p0} + i_{in} \quad (\text{correct KCL})$$

The 3 Terminal model does not include  $I_{C+}$  or  $I_{C-}$ ,  
~~since~~ giving us  $i_o = i_{p0} + i_{in}$  which implies  
 that the output current comes from the inputs,  
 which is incorrect. ~~We will never~~

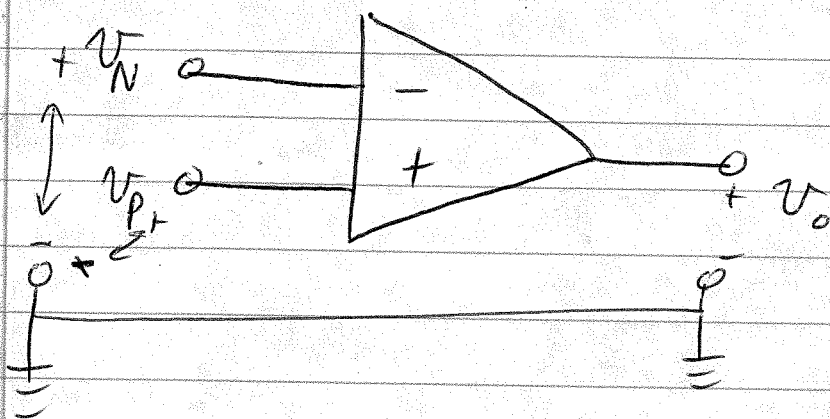The output voltage of an op amp is  
 proportional to the difference between the  
 two input voltages:




$$v_o = A(v_p - v_N) \quad \text{I will also often use } (v_p = v_+) \text{ and } (v_N = v_-)$$

or

$$v_o = A(v_+ - v_-)$$

$A$  (called the Open-Loop Voltage Gain) is very large, typically  $> 10^5$ .

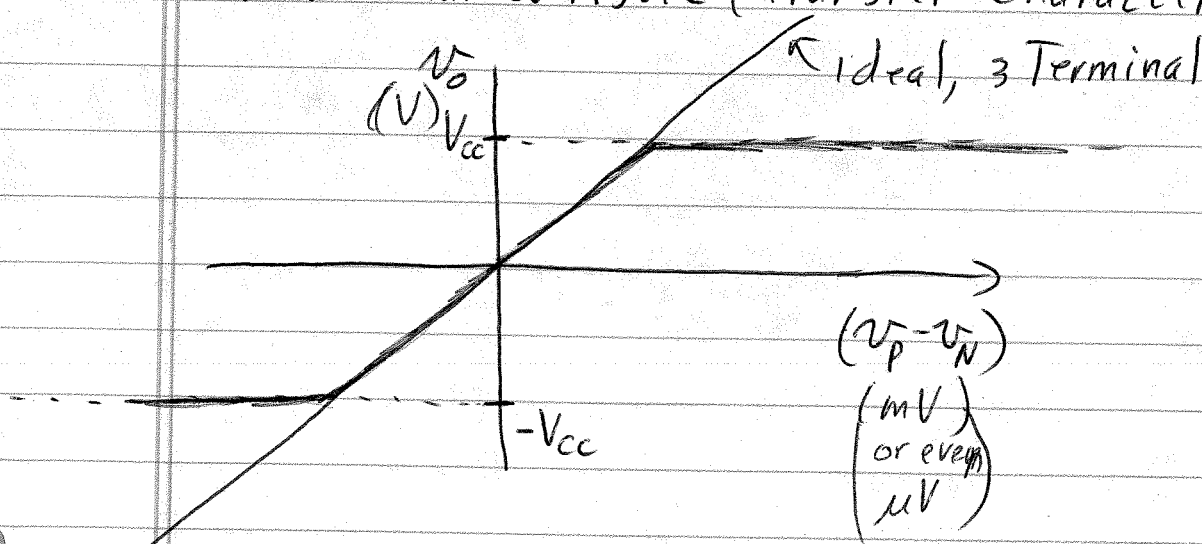V-V characteristic (Transfer Characteristics)




In reality, the output cannot exceed the Power Supply voltage (or maybe a little less)

so there are places where the outputs  
flattens out. (draw)

3 modes: + and - Saturation Modes  
and Linear Mode in between.

Usually we use Op-Amps for the Linear Mode,  
but sometimes we actually want it to  
be in saturation, more on that later.

Ideal Op Amp Model, in linear range:

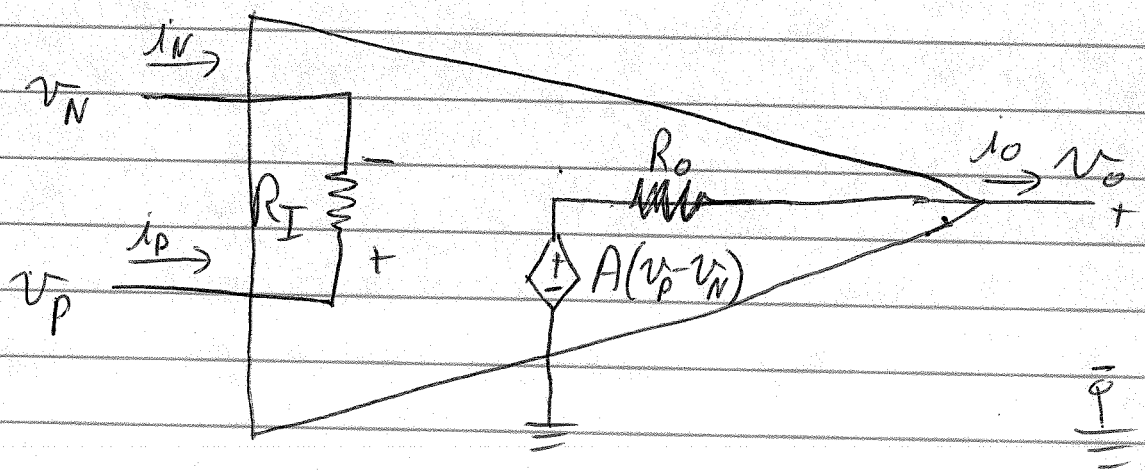

Parameters:

~~R<sub>f</sub>~~

Range

$R_I$

$$10^6 \leq R_I \leq 10^{12} \Omega$$

$R_o$

$$1-10 \leq R_o \leq 100 \Omega$$

$A$

$$10^5 \leq A \leq 10^8$$

To operate in Linear Mode, the output is limited to  $+V_{cc}$  and  $-V_{cc}$ , so

$$\cancel{+V_{cc}} \leq A(v_p - v_n) \leq \cancel{-V_{cc}}$$

$$-V_{cc} \leq A(v_p - v_n) \leq V_{cc}$$

$$\text{or } -\frac{V_{cc}}{A} \leq (v_p - v_n) \leq \frac{V_{cc}}{A}$$

Since  $A$  is very large we take the  $\lim_{A \rightarrow \infty}$

$$-0 \leq (v_p - v_n) \leq 0$$

This means  $v_p - v_n = 0$

$$\text{or } \underline{v_p = v_n}$$

(The Ideal Op Amp will work to make  $v_p = v_n$ )

Also, since  $R_I$  is very large, we take the  $\lim_{R_I \rightarrow \infty}$ , which makes the inputs ~~an~~ open ckts:

$$\underline{i_p = 0}, \quad \underline{i_n = 0}$$

Golden Rules for an Ideal Op Amp with resistive negative feedback (More on that later)

$$1) i_p = i_n = 0$$

$$2) v_p = v_n$$