

Thevenin + Norton Equivalents



Same as before, using Phasors:

$$\tilde{V}_{oc} = \tilde{Z}_T \tilde{I}_{sc} = \tilde{V}_T$$

$$\tilde{I}_{sc} = \frac{\tilde{V}_{oc}}{\tilde{Z}_T} = \tilde{I}_N$$

$$\tilde{Z}_T = \frac{\tilde{V}_{oc}}{\tilde{I}_{sc}}$$

Same example:

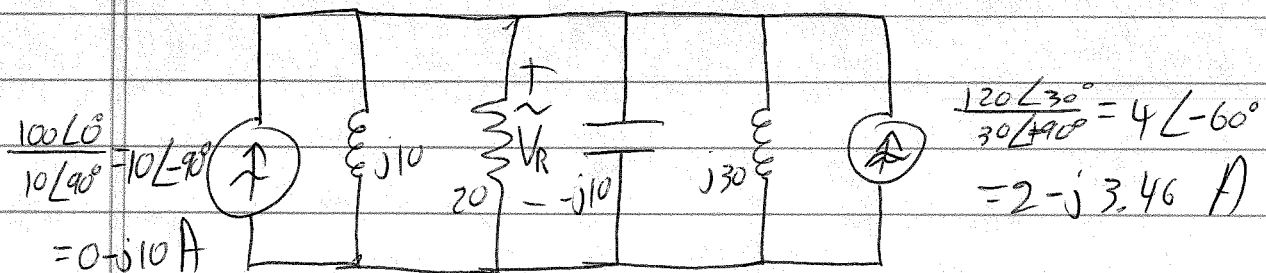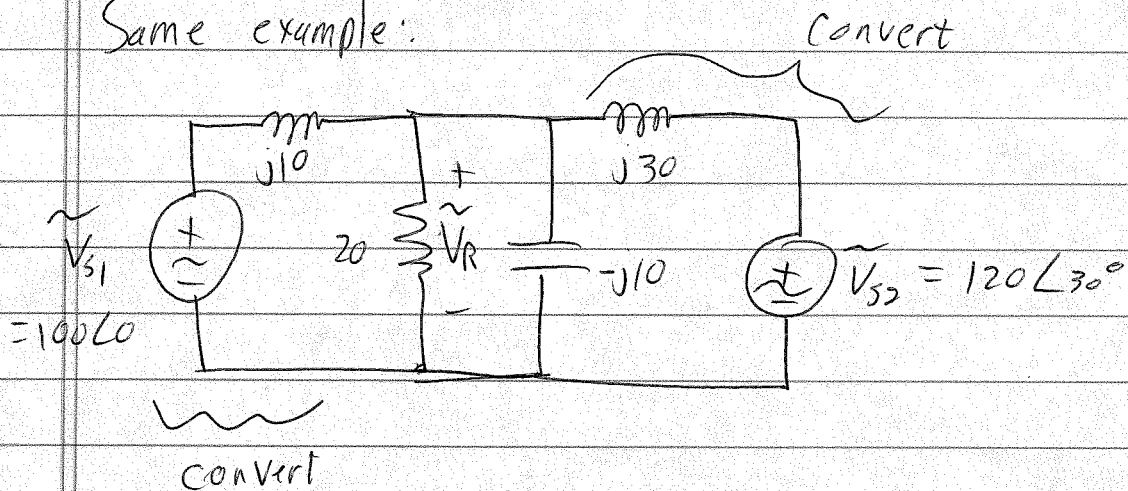

Need voltage across whole thing:

$$\tilde{V}_R = \tilde{Z}_{eq} \tilde{I}_T$$

$$\tilde{I}_T = 0 - j10 A + 2 - j3.46 A = 2 - j13.46 A = 13.6 \angle -81.55^\circ$$

$$\tilde{Z}_{eq} = \frac{1}{\frac{1}{j10} + \frac{1}{20} + \frac{1}{-j10} + \frac{1}{j30}} = \frac{1}{\frac{1}{20} + \frac{1}{j60}} = \frac{1}{\frac{j3 + 2}{j60}} = \frac{j60}{2 + j3} = \frac{60 \angle 90^\circ}{3.606 \angle 56.31^\circ}$$

$$\tilde{Z}_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{j30}} = \frac{1}{\frac{j3 + 2}{j60}} = \frac{j60}{2 + j3} = \frac{60 \angle 90^\circ}{3.606 \angle 56.31^\circ}$$

$$= 16.64 \angle 33.69^\circ$$

$$\text{So } \tilde{V}_R = \tilde{Z}_{eq} \tilde{I}_T = (16.64 \angle 33.69^\circ)(13.61 \angle -81.55^\circ)$$

$$\underline{\tilde{V}_R = 226 \angle -47.86^\circ} \quad \text{as before}$$