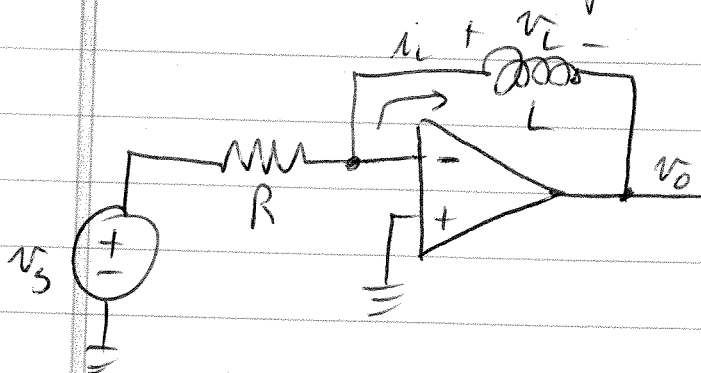


"Duality" - Interchange i + v in all statements
and change L + C , and ~~ever~~ R for $\frac{1}{R}$, and
 everything remains correct.

List on	KVL	→	KCL
pg 292	→ Loop	→	Node
	R		Conductance
	V src		I src
	Ther.		Norton
	S.C.		O.C.
	Series		Parallel
	C		L

$$i_C = C \frac{dv_C}{dt} \longleftrightarrow v_L = L \frac{di_L}{dt}$$

C 's + L 's with Op-Amps



$$v_P = v_N = 0$$

$$\frac{v_N - v_s}{R} + i_L = 0$$

$$-\frac{1}{R} v_s + i_L(0) + \frac{1}{L} \int_0^t v_L(x) dx = 0$$

$$\text{Take } \frac{d}{dt}: -\frac{1}{R} \frac{dv_s}{dt} + 0 + \frac{1}{L} v_L(t) = 0$$


But $v_L = v_N - v_O = 0 - v_O(t) = -v_O(t)$

so $-\frac{1}{R} \frac{dv_S}{dt} + \frac{1}{L} (-v_O) = 0$

$$v_O = -\frac{L}{R} \frac{dv_S}{dt}$$

Inverting differentiator using L.

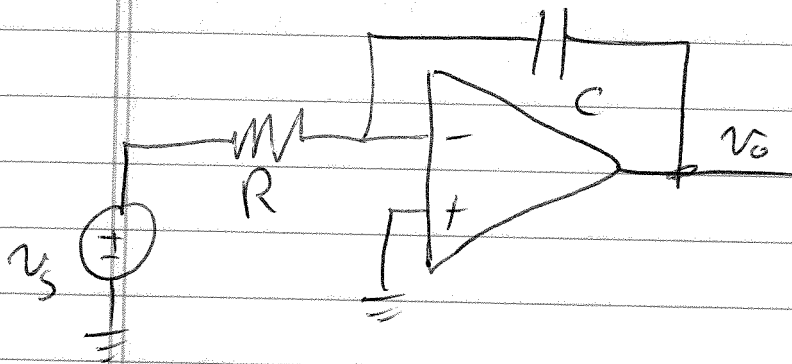
Examples in text are using C's instead of L's:



Inverting Integrator:

$$v_O = v_O(0) - \frac{1}{RC} \int_0^t v_S(x) dx$$

and

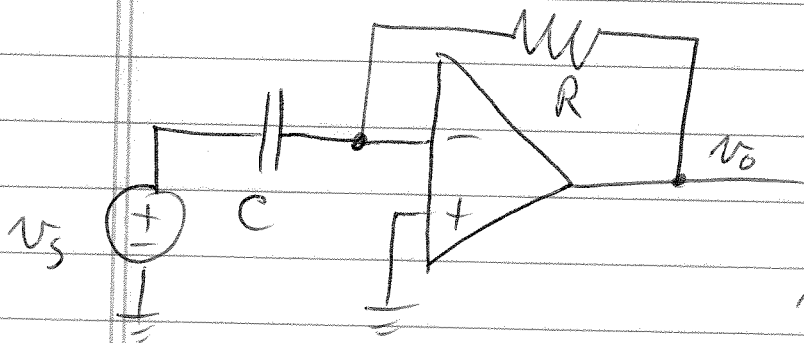

Inverting Differentiator:

$$v_O = -RC \frac{dv_S(t)}{dt}$$



Usually we use C's rather than L's because

C's are 1) cheaper, 2) lighter, 3) smaller, 4) more "contained" than L's.

Read + Do examples + Exercises 6-9 + 6-10.



L + C combinations: (I'm not going to do the derivations, you can read them.)

C's

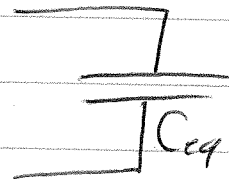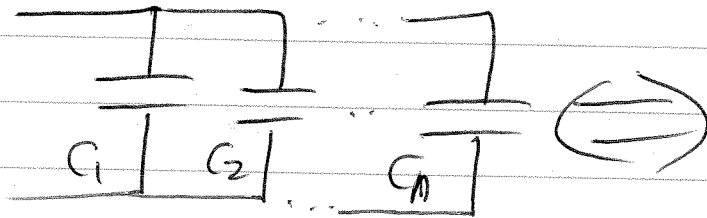

$$C_{eq} = \sum_{i=1}^n C_i$$



Capacitors in parallel add

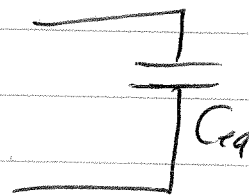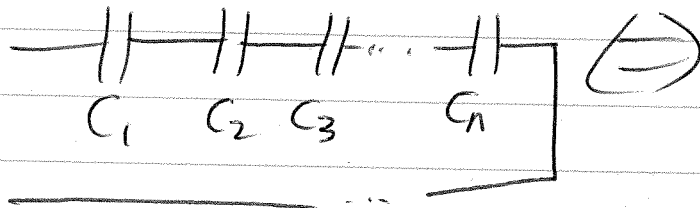



$$C_{eq} = \frac{1}{\sum_{i=1}^n \frac{1}{C_i}}$$

C's in series combine as $\frac{1}{\sum \frac{1}{C}}$

L's

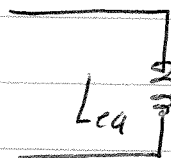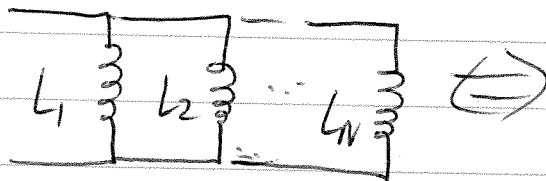
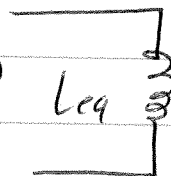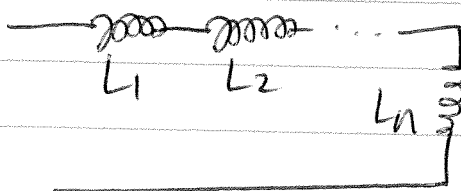
$$L_{eq} = \frac{1}{\sum_{i=1}^n \frac{1}{L_i}}$$



$$L_{eq} = \sum_{i=1}^n L_i$$