

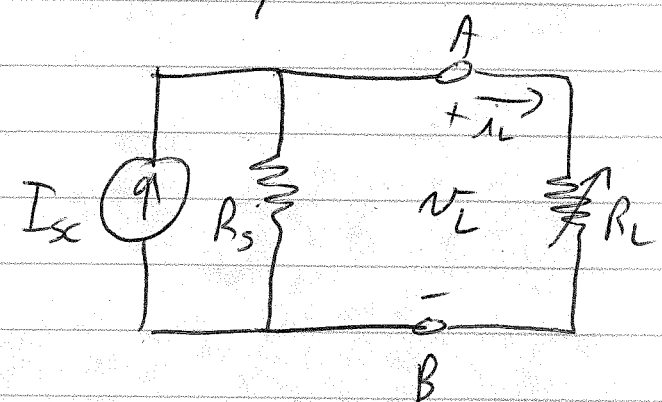


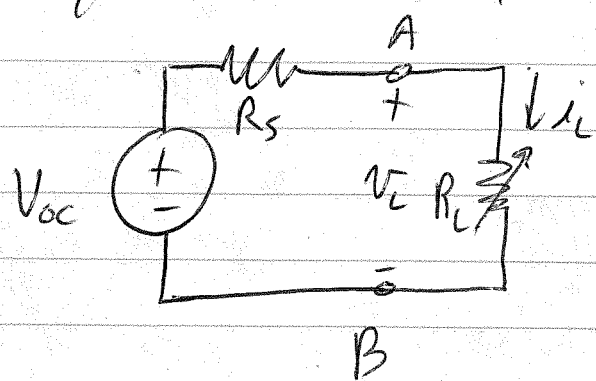Another way to use Thevenin + Norton
Equivalents: Load Line Analysis



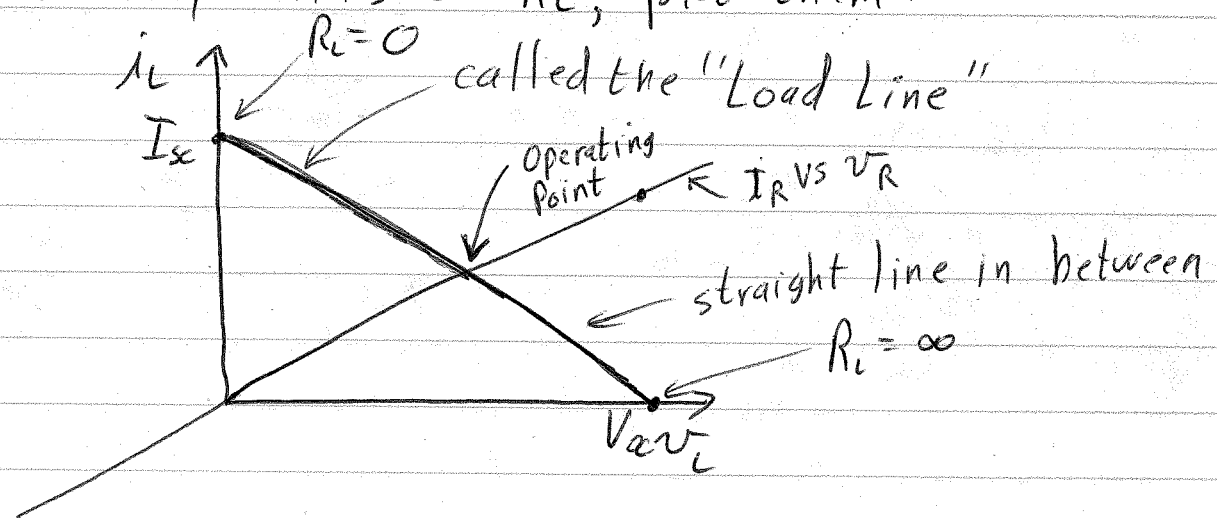Put on an external ^{Variable} resistor and measure $V_L + i_L$ for many values of R_L , plot them:



What if I put a fixed resistor R_i in place of the load, what would $V_L + i_L$ be?

On same plot, put I_R vs V_R : $V_R = R_i I_R$
or $I_R = \frac{1}{R_i} V_R$ (slope = $\frac{1}{R_i}$)



Maximum power is dissipated in R_L when these two lines ~~are perpendicular, or when~~

~~$R_L = R_S$~~ . Point of closest approach to the ~~origin~~ intersect at $(\frac{V_{oc}}{2}, \frac{I_{sc}}{2})$ or a slope of

$$\frac{\frac{1}{2}I_{sc} - 0}{\frac{1}{2}V_{oc} - 0} = \frac{I_{sc}}{V_{oc}} = \frac{1}{R_S}$$

This is even more useful when the load is non-linear, ~~$I_L \neq KV_L$~~ but is instead a different function. like an exponential. A good

example is a diode:

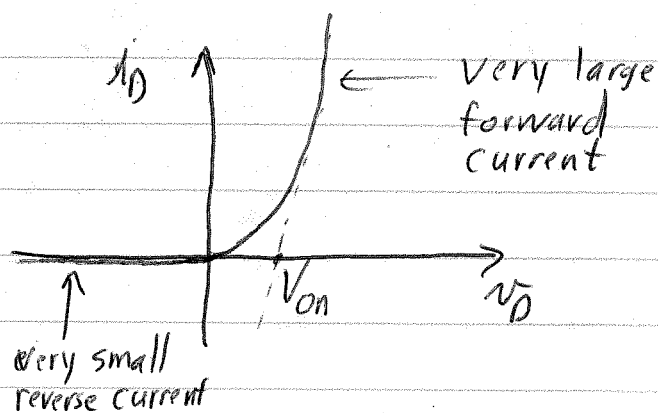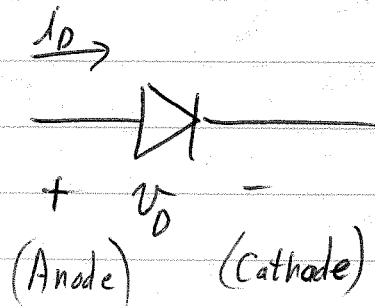


Limited by forward current
and Reverse Voltage

Reverse Biased : Forward Biased


You can write various formulas to describe this curve, but all are nonlinear.

If you put this in a simple ckt:

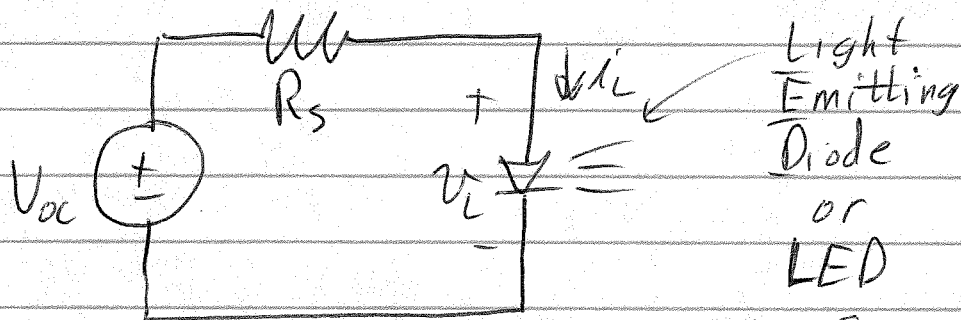

Max Current: 40 mA
Optimum Current: 20 mA

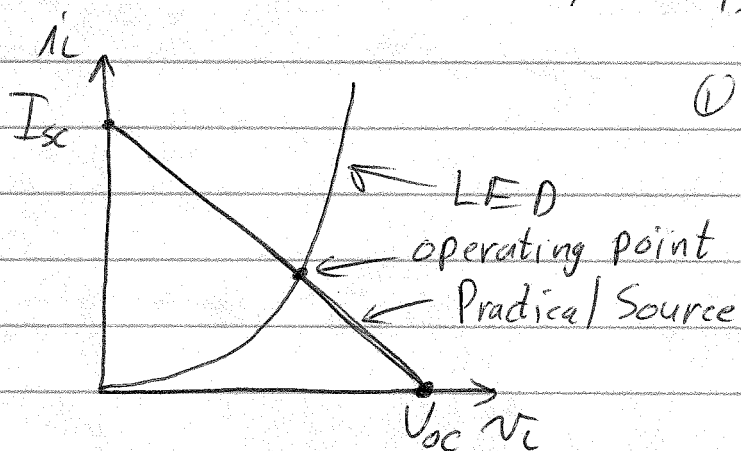Cannot solve this analytically, can do it graphically,



① Remove LED, plot I_L vs R_L

More probably:

