

3. Build the circuit shown in figure 4. Use $1\mu\text{F}$ capacitor.
- Set $V_{\text{IN}} = 10V_{\text{pp}}$ square wave at 1kHz with no DC component. Use oscilloscope q to plot V_{OUT} vs. time and V_{IN} vs. time on the same axis.
 - Repeat (a) with $V_{\text{IN}} = 0.8V_{\text{pp}}$ 10
 - Repeat (a) for circuit in figure 5. Show your graph in the report. 11

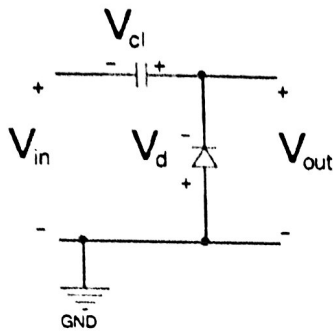


Figure 4.

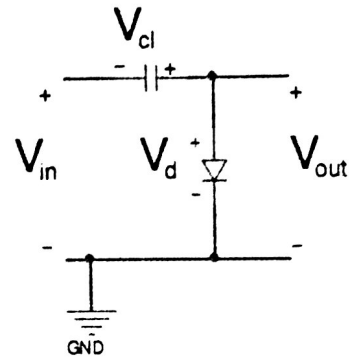


Figure 5.

4. Build the circuit shown in figure 6. Set V_{IN} to a square wave at 2kHz alternating between -5V and 5V . Sketch V_1 , V_2 , V_3 , V_4 and V_{OUT} . Measure the ripple. Comment on the observed and computed results.

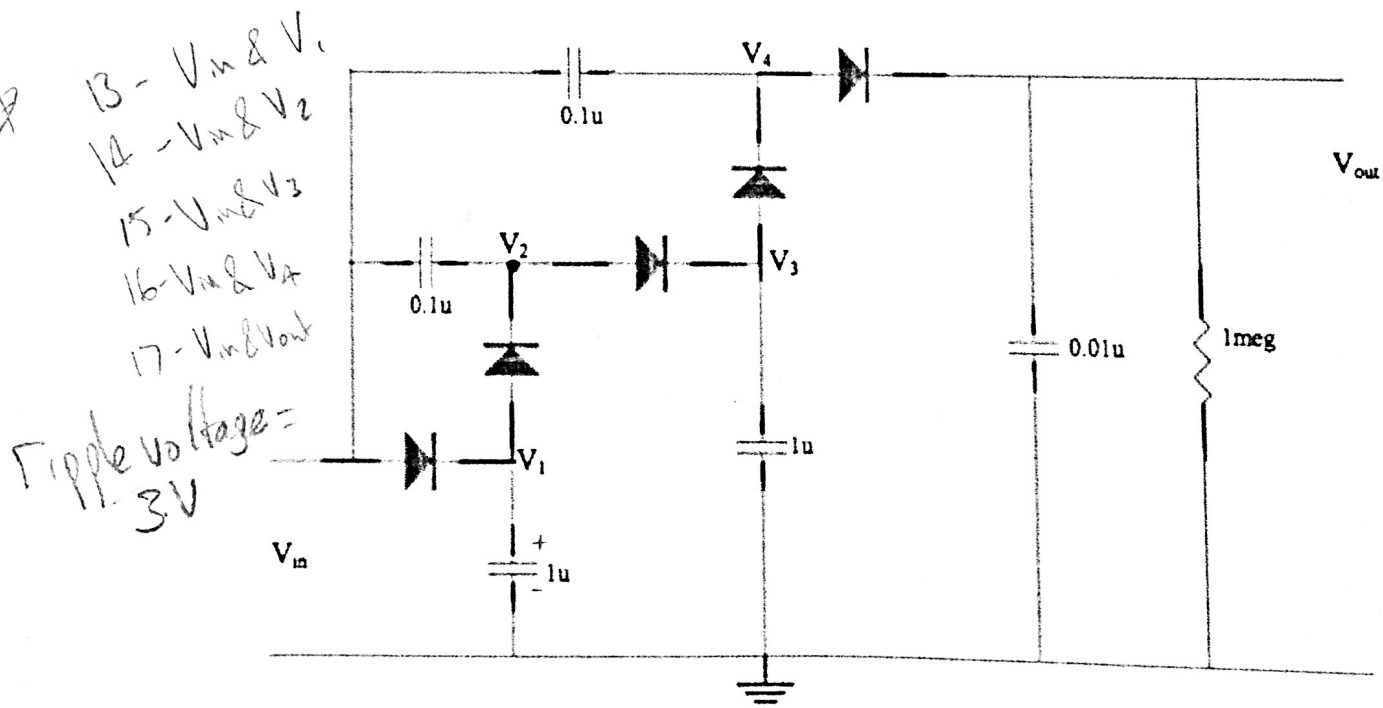


Figure 6

REPORT

Please follow the instructions given in the experiment section and work out a report of your own. Each team should submit a separate report.