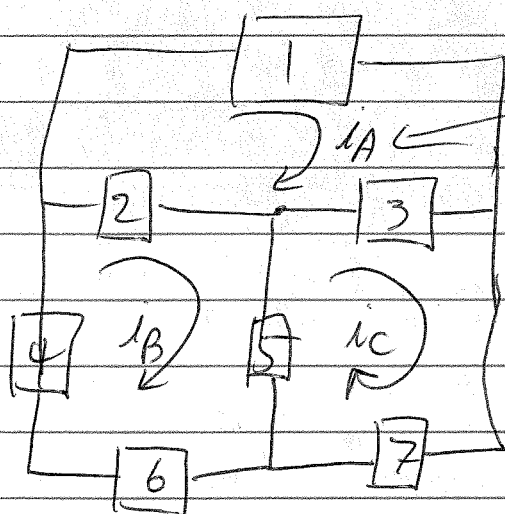


## Mesh-Current Analysis

In a direct analogy to Node-Voltage Analysis, we can propose that Currents can be used to analyze circuits instead of voltages. Any planar circuit can be drawn as meshes, loops of the ckt that do not contain other elements. Only 2-terminal elements can be allowed, and it can be visualized as this:




"Mesh Currents,"  
fictional, only  
2 currents <sup>can</sup> flow  
thru a single element

We now use KVL around each mesh, and Ohm's Law, to write a set of  $M$  equations

in  $M$  unknowns. Sometimes we can simplify these before we start. Let's take a look.

Start with the example in the text:

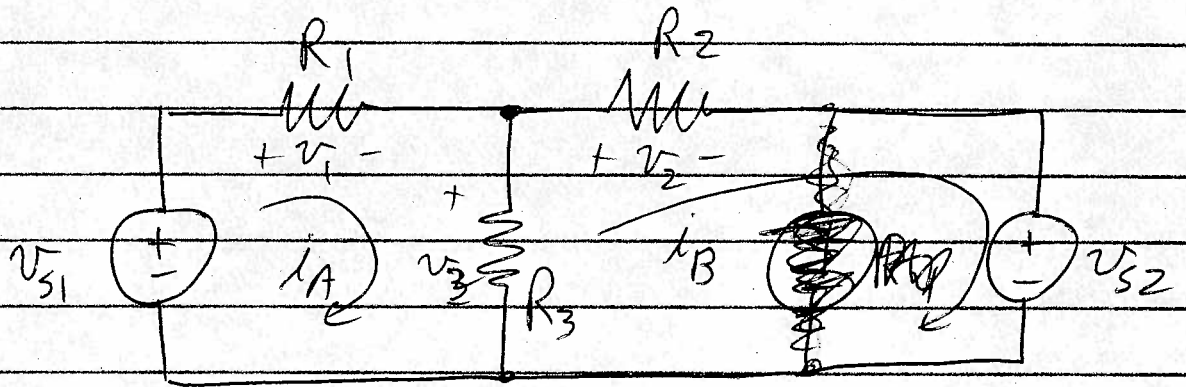

- 1) We propose 2 currents,  $i_A$  and  $i_B$  flowing clockwise in each mesh.
- 2) There are no current sources, so both  $i_A$  &  $i_B$  are unknown.
- 3) Write KVL (+ Apply Ohm's Law) around each ~~loop~~ Mesh. Book starts at bottom left, I tend to start at top left:

$$(A) \quad +R_1 i_A + R_3(i_A - i_B) - v_{S1} = 0$$

collect terms:  $(R_1 + R_3) i_A - R_3 i_B = v_{S1}$

$$(B) \quad R_2 i_B + v_{S2} + R_3(i_B - i_A) = 0$$

$$-R_3 i_A + (R_2 + R_3) i_B = -v_{S2}$$

Matrix:

$$\begin{pmatrix} (R_1 + R_3) & -R_3 \\ -R_3 & (R_2 + R_3) \end{pmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} v_{S1} \\ -v_{S2} \end{pmatrix}$$

$$\Delta = (R_1 + R_3)(R_2 + R_3) - (-R_3)(-R_3)$$

$$= (R_1 R_2 + R_1 R_3 + R_2 R_3 + R_3^2) - R_3^2$$

$$\Delta_A = \begin{vmatrix} v_{S1} & -R_3 \\ -v_{S2} & (R_2 + R_3) \end{vmatrix} = v_{S1}(R_2 + R_3) - (-v_{S2})(-R_3)$$

$$= v_{S1}(R_2 + R_3) - R_3 v_{S2}$$

$$\Delta_B = \begin{vmatrix} (R_1 + R_3) & v_{S1} \\ -R_3 & -v_{S2} \end{vmatrix} = -(R_1 + R_3)v_{S2} - (-R_3)(v_{S1})$$

$$= R_3 v_{S1} - (R_1 + R_2)v_{S2}$$


$$i_A = \frac{\Delta_A}{\Delta} = \frac{v_{S1}(R_2 + R_3) - R_3 v_{S2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

(91)


Read the section in the text, as well.

~~When~~ Recall that Voltage Sources require special handling in Node<sup>-Voltage</sup> Analysis. Well now Current Src's require some thought in Mesh-Current Analysis.

First, Practical Current Sources:

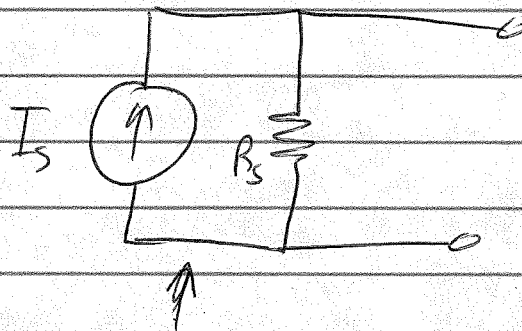

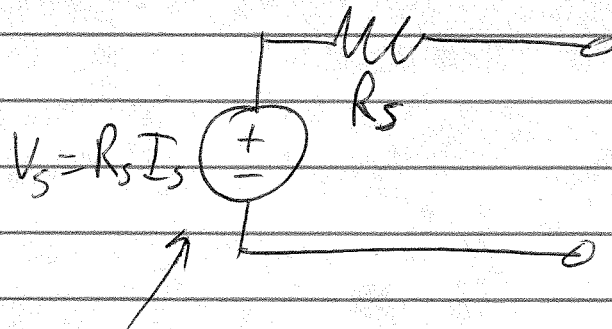contains a mesh, so increases our Mesh Count by 1. Convert, if possible, to




Voltage sources are easily handled in M-C Analysis.

(92)

If you cannot convert a Current Source, then there are 2 possible cases:

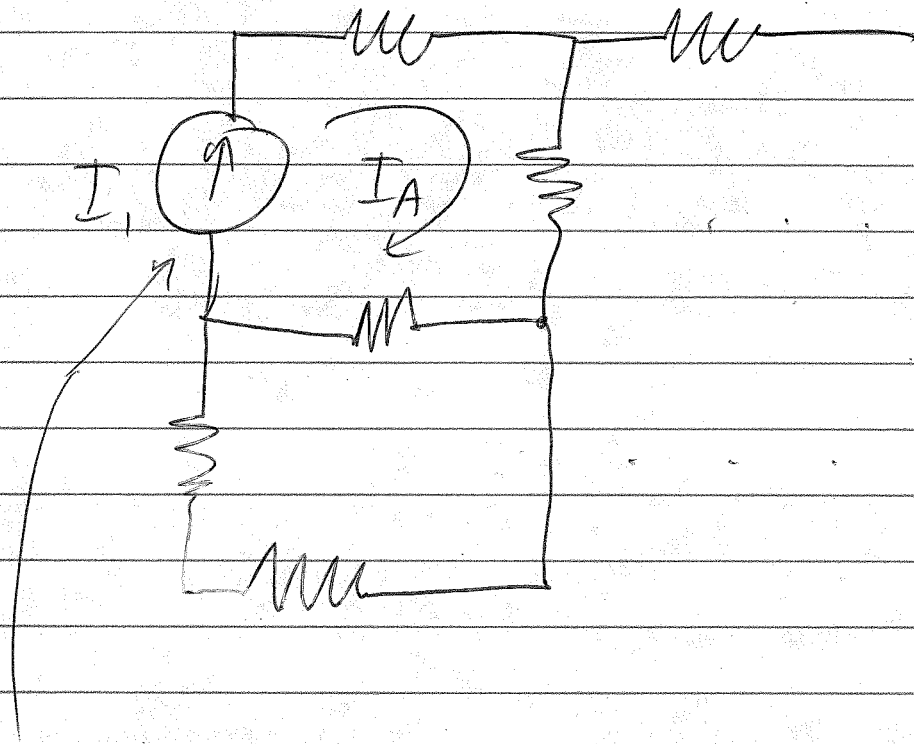
1.)  $I_{\text{source}}$  is on "outside" of a mesh:



Only 1 Mesh Current goes through  $I_{\text{src}}$ ,

$I_A = I_1$ , so reduces Mesh Count by 1.

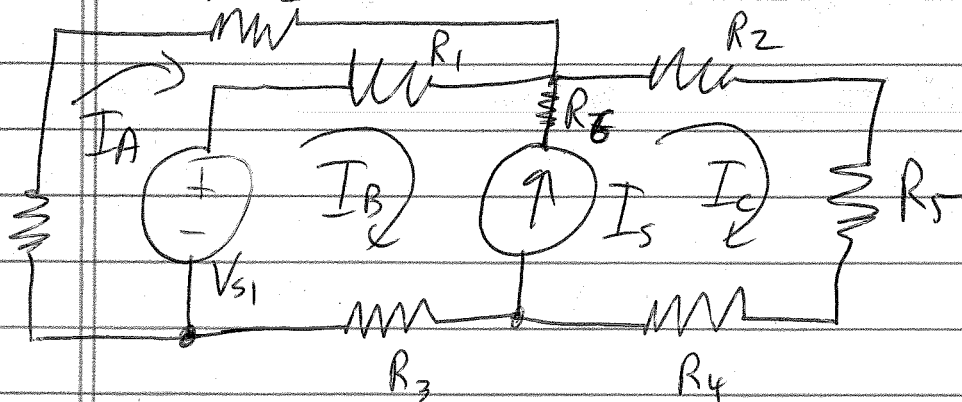2.)  $I_{\text{source}}$  is common to 2 Meshes:



(93)

Now, we write that the Source Current is Equal to the Sum of the Mesh Currents:

$$I_s = I_c - I_B$$

↑  
M.C. in same  
direction as  
 $I_s$

←  
M.C. in opposite  
direction as  $I_s$ .

And now we ~~write~~ combine B+C into a

"Super Mesh":  $R_1(I_B - I_A) + R_2 I_c + R_5 I_c + R_4 I_c$


$$+ R_3 I_B - \cancel{I_s} = 0$$

Note —  $R_7$  does not appear and ~~is~~ does not affect the mesh currents.




Text Example 3-9:

Find  $i_o$ :

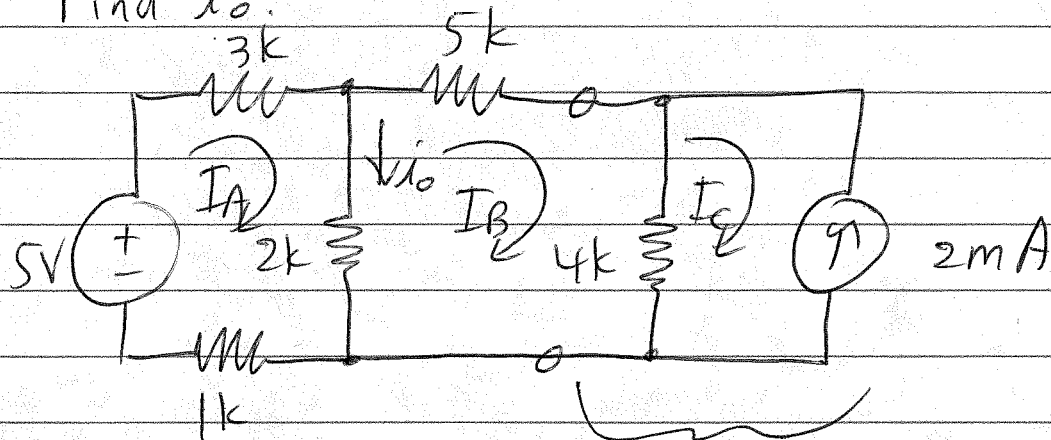

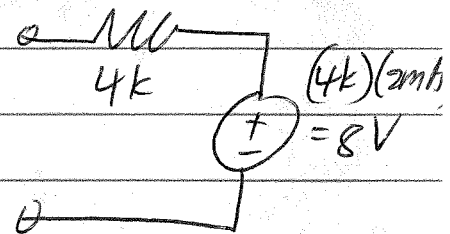in text they ~~convert~~ convert to V-src:



We will assume we did not see that possibility and continue.

Propose  $I_A, I_B, I_C$  (draw).

Express Desired Output in terms of  $I$ 's:

$$i_o = I_A - I_B$$

Find  $I$  src's: There is 1, 2mA, on outside:

$$I_C = -2mA$$

Write KVL:

$$3kI_A + 2k(I_A - I_B) + 1kI_A - 5V = 0$$

$$(3k + 2k + 1k)I_A - 2kI_B = 5V$$

$$\underline{6kI_A - 2kI_B = 5V}$$

$$5kI_B + 4k(I_B - I_C) + 2k(I_B - I_A) = 0$$

$$-2kI_A + (5k + 4k + 2k)I_B + 4k(-2mA) = 0$$

$$\underline{-2kI_A + 11kI_B = -8V}$$

$$\Delta = \begin{vmatrix} 6k & -2k \\ -2k & 11k \end{vmatrix} = (6k)(11k) - (-2k)(-2k)$$

$$= 66M - 4M = 62k^2$$

$$\Delta_A = \begin{vmatrix} 5V & -2k \\ -8V & 11k \end{vmatrix} = (11k)(5V) - (-8V)(-2k)$$

$$= 55kV - 16kV = 39kV$$

$$I_A = \frac{39kV}{62k^2} = \frac{39}{62} \frac{V}{k\Omega} = \underline{0.629mA}$$

$$\Delta_B = \begin{vmatrix} 6k & 5V \\ -2k & -8V \end{vmatrix} = (6k)(-8V) - (-2k)(5V)$$

$$= -48kV + 10kV = -38kV$$

$$I_B = \frac{-38kV}{62(k\Omega)^2} = \underline{-0.613mA}$$



Q06

$$\text{So } i_o = I_A - I_B = 0.629 \text{ mA} - (-0.613 \text{ mA}) \\ = 1.242 \text{ mA}$$