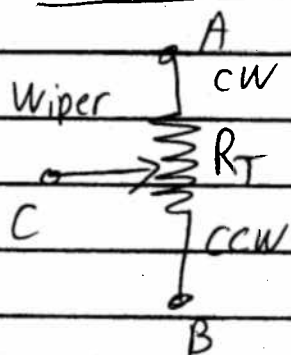


Good summary ~~in~~ in Table 2-37
of text.

Application of Voltage Division:

We began using a device in lab yesterday:

Potentiometer (Pot) or Variable Resistor.



Think of this as a knob
you turn to change the
setting, like a volume
control.


The wiper makes contact in the middle
portions of the resistor, dividing it
into 2 parts:

$$R_{AB} = R_T \quad R_{AC} + R_{CB} = R_T$$

So, when turned fully CCW, $R_{AC} = R_T$
 $R_{CB} = 0$

and when fully CW: $R_{AC} = 0$
 $R_{CB} = R_T$


It helps to think like this:

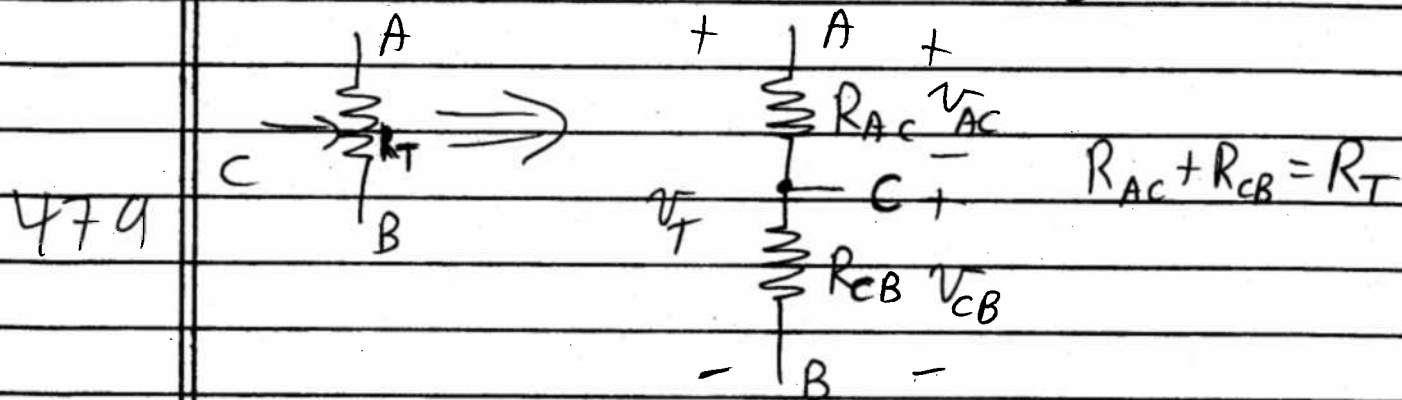

Resume


Example of Ckt Reduction - Ex 2-27 (pg 56)

Find v_o in:

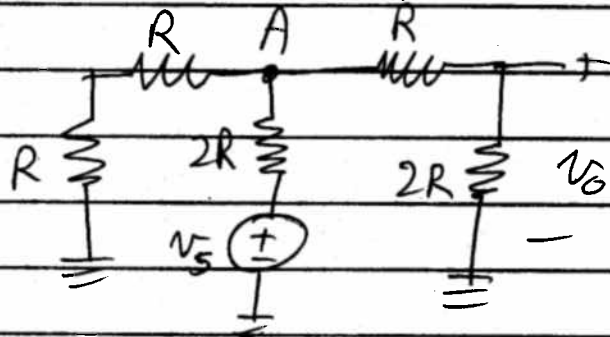


Text solves like this:

Rearrange w/ A at top & v_5 on left:


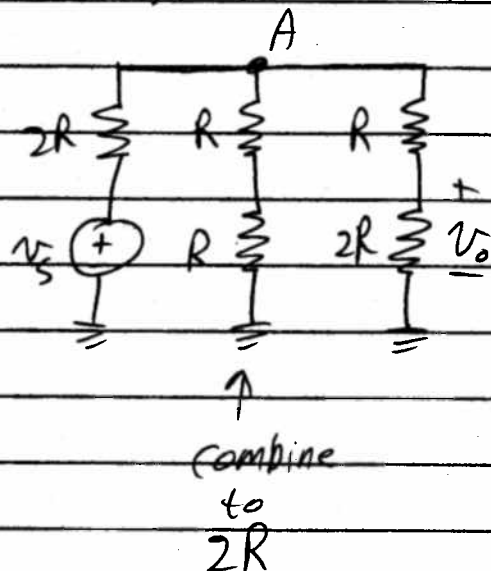


Go to "Far Side" from V_o : see Pract V_s src // $2R$


Convert Pract V_s to Pract I_s :

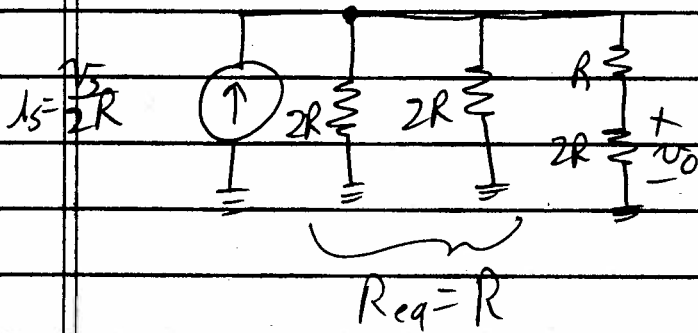

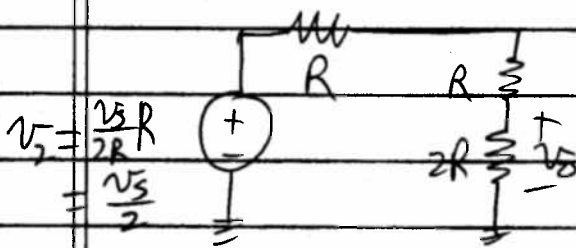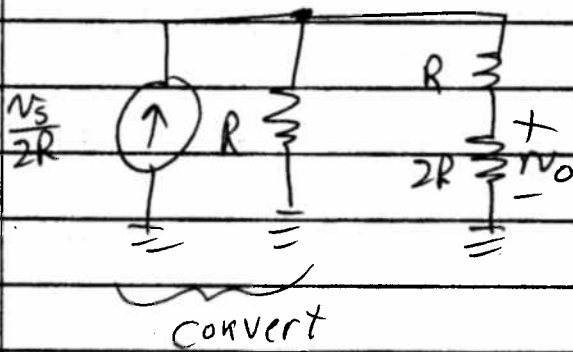← always keep the thing you are looking for!
Do not combine into a $3R$.



Text stopped here,
I would go on:

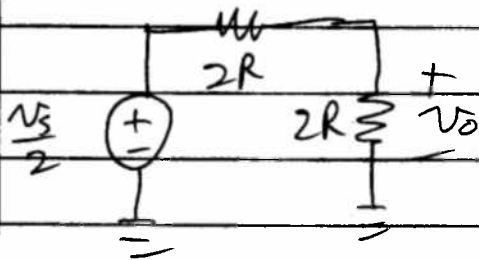

Now it is pretty obvious:

$$V_o = \frac{1}{2} \left(\frac{V_s}{2} \right) = \frac{V_s}{4}$$