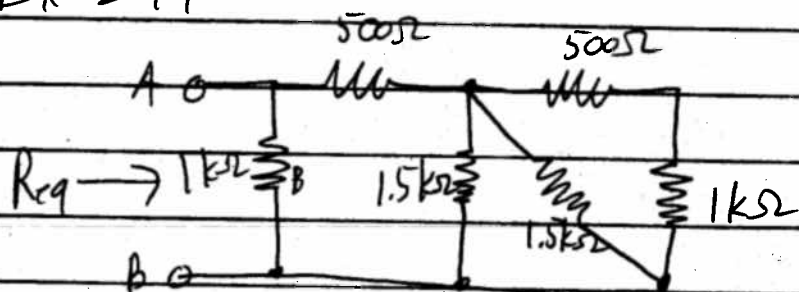


Things that look complicated can often be reduced to a single equivalent resistor:

Ex 2-14



Go to the "Far Side" and work your way

back: $500\Omega + 1k\Omega = 1.5k\Omega$

$$1.5k // 1.5k = 0.75k$$


$$.75k // 1.5k = \frac{(\frac{3}{4})(\frac{3}{2})}{\frac{3}{4} + \frac{3}{2}} k = \frac{\frac{9}{8}}{\frac{9}{4}} k = \frac{1}{2} k\Omega$$

$$\frac{1}{2}k + \frac{1}{2}k = 1k\Omega$$

$$\underline{1k\Omega // 1k\Omega = 500\Omega}$$

It is useful to think about how you would measure the resistance of an unknown device;


DUT = Device Under Test

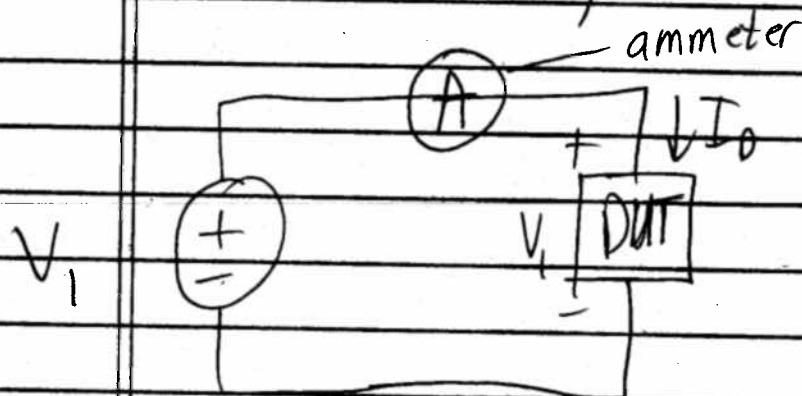

① Apply a known voltage across the DUT, V_1 .

② Measure the current thru the device I_D .

$$R_{eq} = \frac{V_1}{I_D}$$

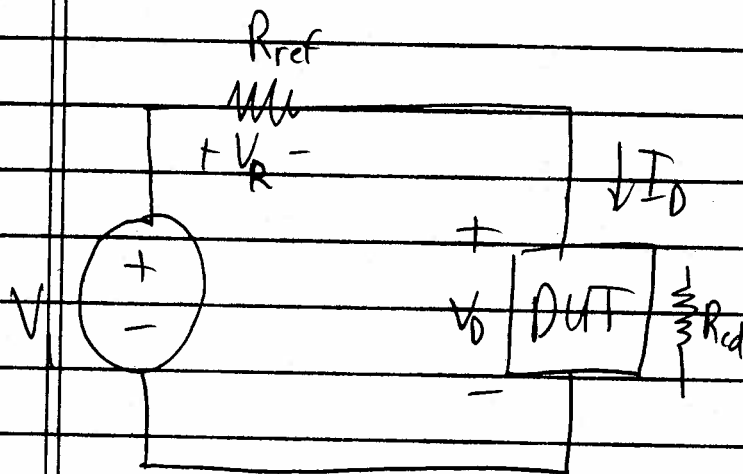

~~Use Voltage division~~

① Apply known voltage across DUT and R_{ref} .

② Measure V_R across R_{ref} .


③ Calculate R_{eq} from Voltage Division

$$V_R = \frac{R_{ref}}{R_{ref} + R_{eq}} V_1$$

$$R_{ref} + R_{eq} = R_{ref} \left(\frac{V_1}{V_R} \right)$$

$$R_{eq} = R_{ref} \left(\frac{V_L}{V_R} \right) - R_{ref}$$
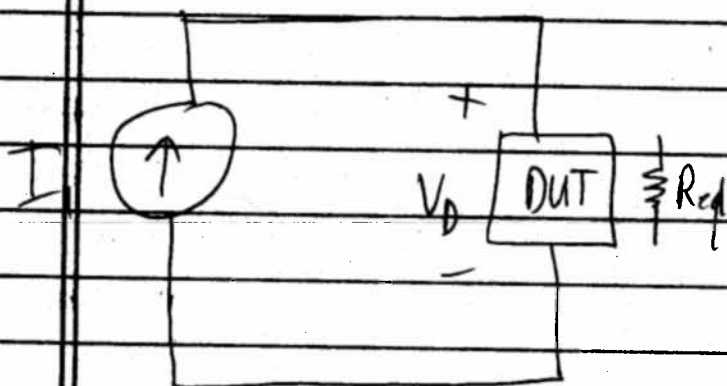
$$R_{eq} = R_{ref} \left[\frac{V_L}{V_R} - 1 \right]$$




① send known current through DUT


② Measure voltage across DUT

$$③ R_{eq} = \frac{V_D}{I}$$

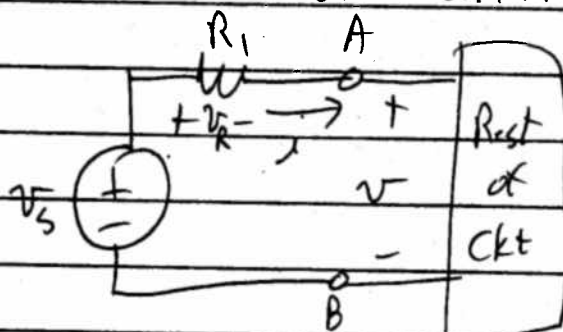I have already alluded to Practical Sources, to avoid the difficulties of ideal Sources:



A

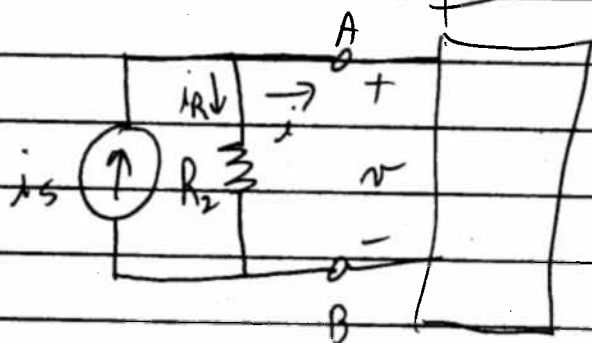

B

What if the "Rest of Ckt" is the same in these two cases, then ~~we want v and i to be the same~~ under what values of v_s , i_s , and $R_1 + R_2$ will v and i be the same?

A: KVL: $v_R + v - v_s = 0$

Ohm's $v_s = v_R + v$ ~~$v_s = v_R + v$~~
 $v_R = iR_1$

B: KCL: $-i_s + i_R + i = 0$

Ohm's $i_s = i_R + i$
 $i_R = \frac{v}{R_2}$

A \rightarrow $v_s = iR_1 + v$
 $\frac{v_s - v}{R_1} = i$



$i = \frac{v_s - v}{R_1} \rightarrow$

$i = -\frac{1}{R_1}v + \frac{v_s}{R_1}$

B \rightarrow ~~i_s~~ $i_s = \frac{v}{R_2} + i$

$i = i_s = \frac{v}{R_2}$

$= -\frac{1}{R_2}v + i_s \rightarrow$

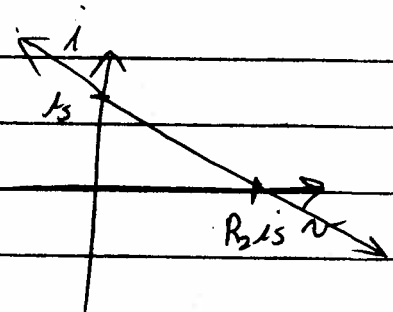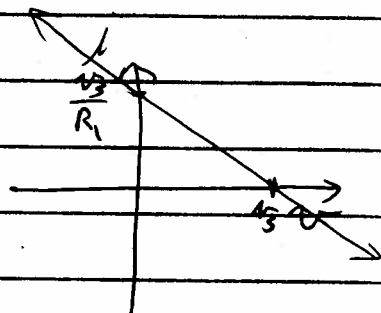

We want these to be the same, so the intercepts must be equal, or

$$y \text{ intercepts: } \frac{v_s}{R_1} = i_s$$



$$x \text{ intercepts: } v_s = R_2 i_s \rightarrow i_s = \frac{v_s}{R_2}$$

$$\frac{v_s}{R_1} = \frac{v_s}{R_2} \Rightarrow R_1 = R_2 = R$$

$$\text{So } \underline{i_s = \frac{v_s}{R}}$$


and $v_s = R_2 i_s$ like Ohm's Law.

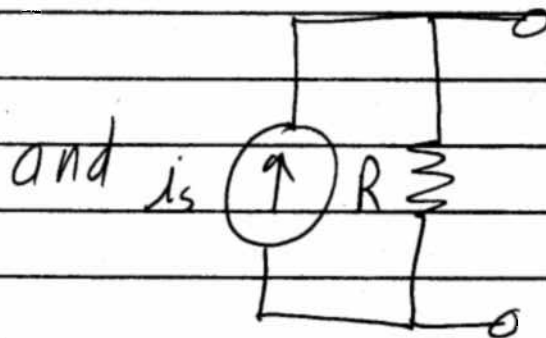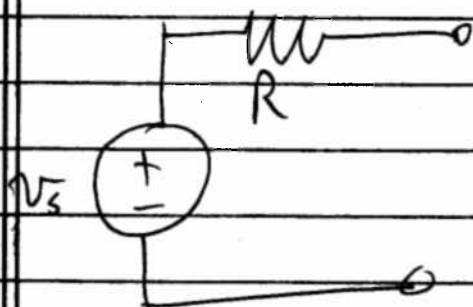So, from the point of view of the "Rest of the Ckt", these two are identical:




where $v_s = R i_s$

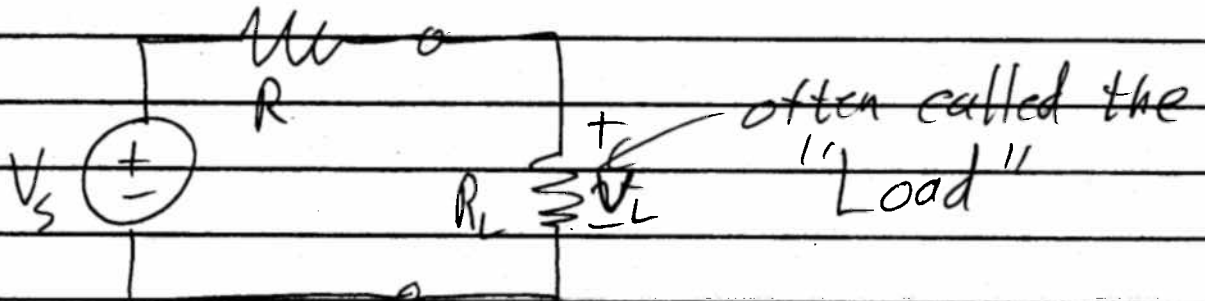Now we can see why the lights dim when the refrigerator turns on:



Voltage Division:
$$V_L = \frac{R_L}{R + R_L} V_s$$

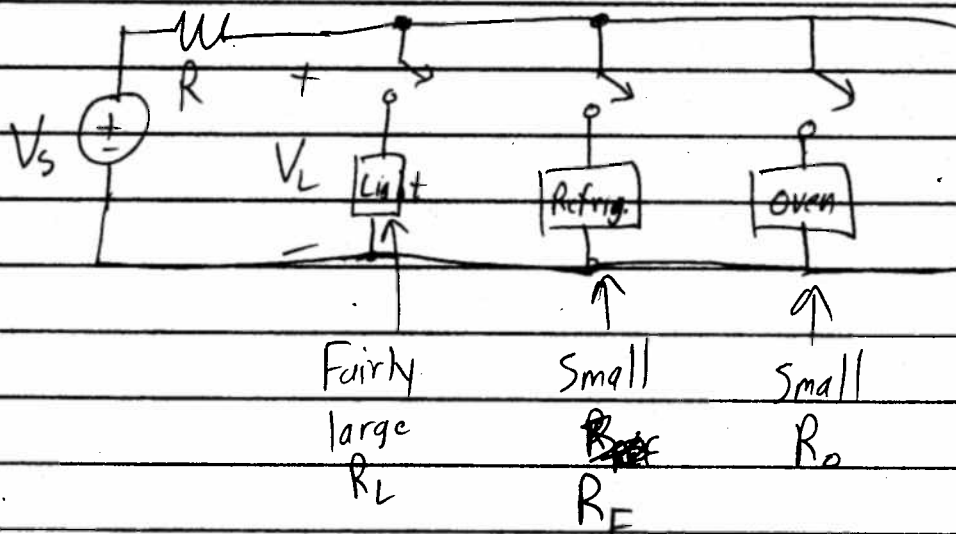~~When~~ Devices in your house are in parallel:



Add a small R_F in parallel with a large R_L gives a small R_L ,

$$V_L = \frac{R_L}{R + R_L} V_S \rightarrow \text{decrease } R_L \text{ and you decrease } V_L \Rightarrow \text{dimming of Light.}$$

We haven't said it yet, but here it is:

Ideal Voltage Srcs in series add:

$$\text{---} \oplus \text{---} \oplus \text{---} \Rightarrow \text{---} \oplus \text{---} \quad v_{eq} = v_1 + v_2$$

1. Voltage Srcs are never put in parallel. (No need) (or impossible)

$$v_1 \oplus v_2 = ???$$

Ideal Current Srcs in parallel add:

$$\text{---} \ominus \text{---} \ominus \text{---} \Rightarrow \text{---} \ominus \text{---} \quad i_{eq} = i_1 + i_2$$

1. Current Srcs are never put in series. (No need) (or impossible)

$$i_1 \ominus i_2 = ???$$