

Problem 2–32. Figure P2–32 shows a subcircuit connected to the rest of the circuit at four points.

- (a). Use element and connection constraints to find v_x and i_x .

Label the 5-k Ω resistor as R_1 with the current flowing from left to right. Label the 2-k Ω resistor as R_2 with the positive sign at the bottom. Using Ohm's law, we can compute $i_1 = v_1/R_1 = 20/5000 = 4$ mA. The KCL equation at the center node is $4 \text{ mA} + i_1 - i_2 - i_x = 0$. Substituting in the known values, we can solve for i_x as $i_x = 4 + i_1 - i_2 = 4 + 4 - 6 = 2$ mA. Using Ohm's law $v_x = R_x i_x = (8000)(0.002) = 16$ V.

- (b). Show that the sum of the currents into the rest of the circuit is zero.

The sum of the currents entering the rest of the circuit is $-i_1 + i_2 - 4 + i_x = -4 + 6 - 4 + 2 = 0$ mA.

- (c). Find the voltage v_A with respect to the ground in the circuit.

From the ground to v_A there are three voltages. First, there is an increase across the voltage source of 12 V. Next, there is an increase across R_x of 16 V. Finally, there is a decrease across R_2 of $v_2 = R_2 i_2 = (2000)(0.006) = 12$ V. Therefore, $v_A = 12 + 16 - 12 = 16$ V.

Problem 2–35. Find the equivalent resistance R_{EQ} in Figure P2–35.

The $10\text{-}\Omega$ resistor and the $30\text{-}\Omega$ resistor are in parallel. That combination is in series with the $7.5\text{-}\Omega$ resistor. We can calculate the equivalent resistance as follows:

$$R_{\text{EQ}} = 7.5 + (30 \parallel 10) = 7.5 + \frac{1}{\frac{1}{30} + \frac{1}{10}} = 7.5 + \frac{(30)(10)}{30 + 10} = 7.5 + 7.5 = 15 \Omega$$

Problem 2–36. Find the equivalent resistance R_{EQ} in Figure P2–36.

Combine the $33\text{-k}\Omega$ and $47\text{-k}\Omega$ resistors in series to get an equivalent resistance of $33 + 47 = 80 \text{ k}\Omega$. The $80\text{-k}\Omega$ resistance is in parallel with the $100\text{-k}\Omega$ resistor, which yields an equivalent resistance of $100 \parallel 80 = 44.4 \text{ k}\Omega$. That resistance is in series with the $68\text{-k}\Omega$ resistor, which yields $R_{\text{EQ}} = 68 + 44.4 = 112.4 \text{ k}\Omega$.

Problem 2–37. Find the equivalent resistance R_{EQ} in Figure P2–37.

Working from the right to the left, combine the $10\text{-k}\Omega$ resistor in parallel with the $15\text{-k}\Omega$ resistor to get an equivalent resistance of $6 \text{ k}\Omega$. That resistance is in series with the $33\text{-k}\Omega$ resistor, which yields an equivalent resistance of $39 \text{ k}\Omega$. Finally, combine the $39\text{-k}\Omega$ resistance in parallel with the $56\text{-k}\Omega$ resistor to get $R_{\text{EQ}} = 22.99 \text{ k}\Omega$.

Problem 2–42. In Figure P2–42 find the equivalent resistance between terminals A-B, A-C, A-D, B-C, B-D, and C-D.

For A-B, ignore the $20\text{-}\Omega$ resistor and the $10\text{-}\Omega$ resistor connected to terminal D. We then have

$$R_{AB} = [100 \parallel (60 + 40)] + 30 = [100 \parallel 100] + 30 = 50 + 30 = 80 \Omega$$

For A-C, ignore the $30\text{-}\Omega$ resistor and the $10\text{-}\Omega$ resistor connected to terminal D. We then have

$$R_{AC} = [60 \parallel (100 + 40)] + 20 = [60 \parallel 140] + 20 = 42 + 20 = 62 \Omega$$

For A-D, ignore the $30\text{-}\Omega$ resistor and the $20\text{-}\Omega$ resistor. We then have

$$R_{AD} = [60 \parallel (100 + 40)] + 10 = [60 \parallel 140] + 10 = 42 + 10 = 52 \Omega$$

For B-C, ignore the A terminal and the $10\text{-}\Omega$ resistor. We then have

$$R_{BC} = 30 + [40 \parallel (100 + 60)] + 20 = 30 + [40 \parallel 160] + 20 = 30 + 32 + 20 = 82 \Omega$$

For B-D, ignore the A terminal and the $20\text{-}\Omega$ resistor. We then have


$$R_{BD} = 30 + [40 \parallel (100 + 60)] + 10 = 30 + [40 \parallel 160] + 10 = 30 + 32 + 10 = 72 \Omega$$

For C-D, ignore the A terminal and the $30\text{-}\Omega$ resistor. In the center of the circuit, the wire shorts out the 60 , 100 , and $40\text{-}\Omega$ resistors, so we then have

$$R_{CD} = 20 + 0 + 10 = 30 \Omega$$

Problem 2–50. Two 10-k Ω potentiometers (a variable resistor whose value between the two ends is 10 k Ω and between one end and the wiper—the third terminal—can range from 0 Ω to 10 k Ω) are connected as shown in Figure P2–50. What is the range of R_{EQ} ?


At the limits of their settings, the two potentiometers are either in series or parallel. These represent the maximum and minimum equivalent resistances that the combination can take. When the potentiometers are arranged in parallel, the equivalent resistance is $R_{EQ} = 10 \parallel 10 = 5$ k Ω . When the potentiometers are arranged in series, the equivalent resistance is $R_{EQ} = 10 + 10 = 20$ k Ω . The equivalent resistance ranges between 5 and 20 k Ω .

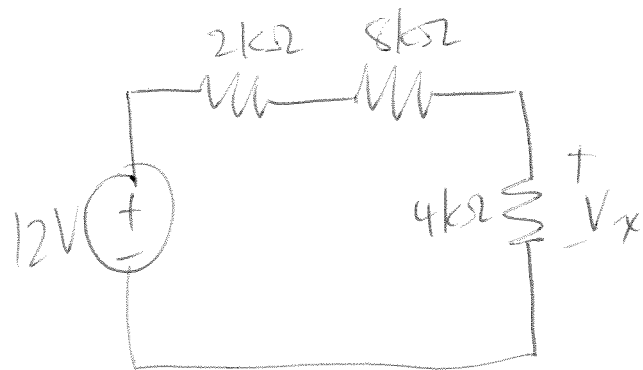

Problem 2-54. Use voltage division in Figure P2-54 to find v_x .

Apply the equation for voltage division to get

$$v_x = \left(\frac{4}{2 + 8 + 4} \right) (12) = 3.4286 \text{ V}$$

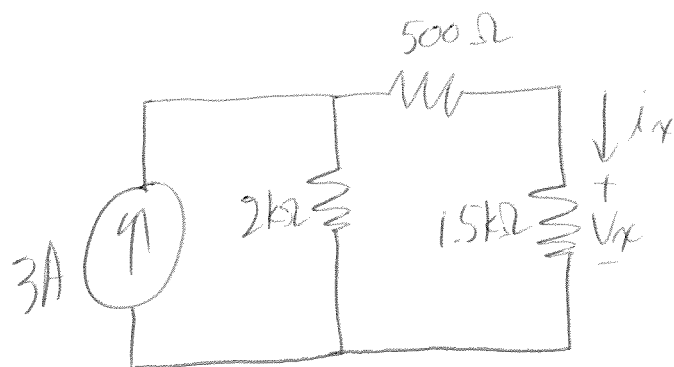


Problem 2-56. Use current division in Figure P2-56 to find i_x and v_x .

Combine the $500\text{-}\Omega$ and the $1.5\text{-k}\Omega$ resistors in series to get an equivalent resistance of $2\text{ k}\Omega$. Now apply current division as follows:

$$i_x = \left(\frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{2}} \right) (3) = \left(\frac{1}{2} \right) (3) = 1.5\text{ A}$$

$$v_x = (1500)(1.5) = 2250\text{ V} = 2.25\text{ kV}$$

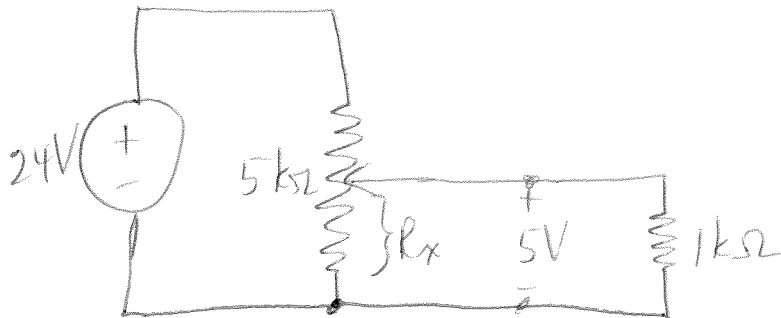

Problem 2-60. (A) The $1\text{-k}\Omega$ load in Figure P2-60 needs 5 V across it to operate correctly. Where should the wiper on the potentiometer be set (R_X) to obtain the desired output voltage?

Figure P2-60 shows an equivalent circuit with the potentiometer split into its two equivalent components. To solve the problem, find an equivalent resistance for the parallel combination of resistors and then apply

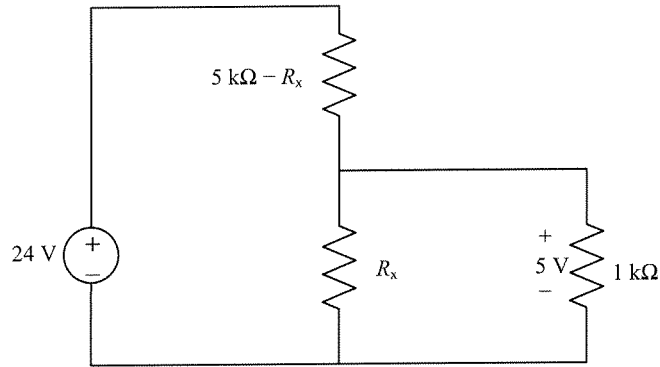


Figure P2-60

voltage division to find an expression for R_x . Solve for R_x and select the positive result.

$$R_{\text{EQ}} = R_x \parallel 1000 = \frac{1000R_x}{1000 + R_x}$$

$$5 \text{ V} = \frac{R_{\text{EQ}}}{5000 - R_x + R_{\text{EQ}}} (24 \text{ V})$$

$$5 = \left[\frac{\frac{1000R_x}{1000 + R_x}}{5000 - R_x + \frac{1000R_x}{1000 + R_x}} \right] (24) = \frac{24000R_x}{(5000 - R_x)(1000 + R_x) + 1000R_x}$$


$$1 = \frac{4800R_x}{5 \times 10^6 + 4000R_x - R_x^2 + 1000R_x}$$

$$-R_x^2 + 5000R_x + 5 \times 10^6 = 4800R_x$$

$$R_x^2 - 200R_x - 5 \times 10^6 = 0$$

$$R_x = -2138 \text{ or } 2338 \Omega$$

$$R_x = 2.338 \text{ k}\Omega$$

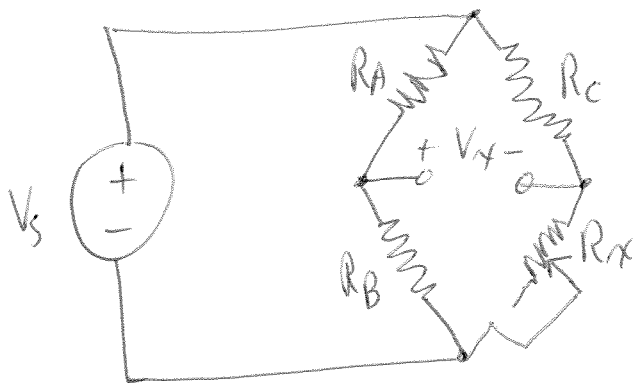

Problem 2–63. (A) Figure P2–63 shows a voltage bridge circuit, that is, two voltage dividers in parallel with a source v_S . One resistor R_X is variable. The goal is often to “balance” the bridge by making $v_x = 0$ V. Derive an expression for R_X in terms of the other resistors when the bridge is balanced.

Let the node between resistors R_A and R_B have a voltage v_1 and let the node between resistors R_C and R_X have a voltage v_2 . The goal is to make v_1 equal v_2 so that v_x is zero. Use voltage division to derive expressions for v_1 and v_2 , set those expressions equal, and solve for R_X .

$$v_1 = \frac{R_B}{R_A + R_B}(v_S)$$

$$v_2 = \frac{R_X}{R_C + R_X}(v_S)$$

$$\frac{R_B v_S}{R_A + R_B} = \frac{R_X v_S}{R_C + R_X}$$

$$R_B(R_C + R_X) = R_X(R_A + R_B)$$

$$R_B R_C + R_B R_X = R_A R_X + R_B R_X$$

$$R_X = \frac{R_B R_C}{R_A}$$