
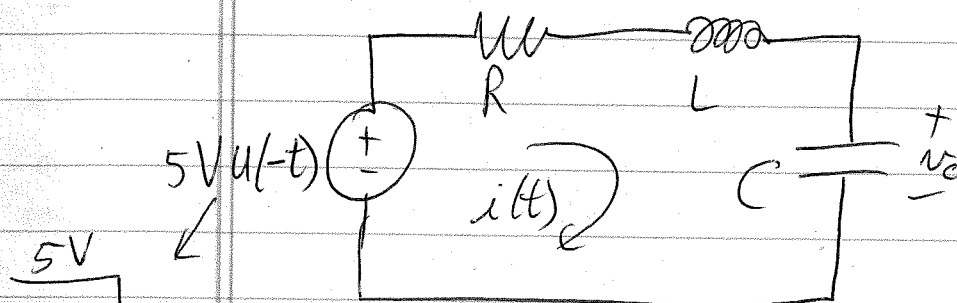


Example

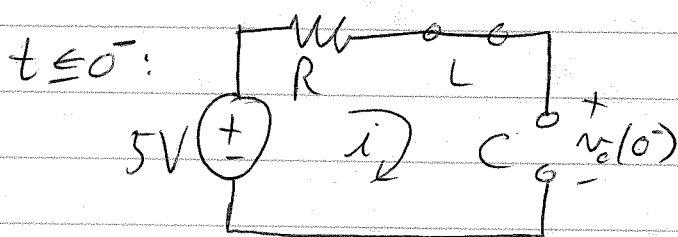


Find $i(t)$ for $t > 0$.




$$\underline{i(0^-) = i_L(0^-) = 0} \quad (C \text{ is an open ckt.})$$

$$\underline{v_c(0^-) = 5V}$$

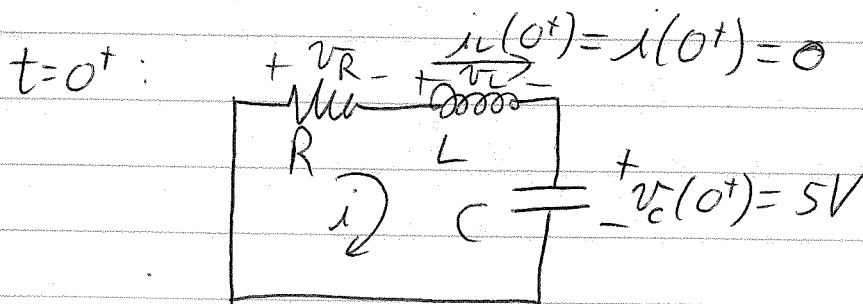

$$\begin{aligned} v_R + v_L + v_C &= 0 \\ R i + L \frac{di}{dt} + v_C &= 0 \\ \frac{di}{dt} &= -\frac{1}{L} (v_C + R i) \\ \frac{di}{dt}(0^+) &= -\frac{1}{L} (v_C(0^+) + 0) \\ &= -\frac{1}{L} (5V) \\ &= -\frac{5V}{L} \end{aligned}$$

$t = \infty$:

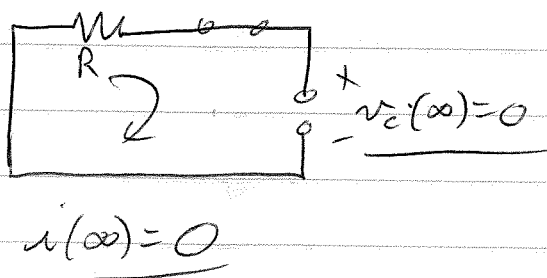

Try different
values of R

Leave these fixed

(234)

Values: $R = 8.5 \text{ k}\Omega$, $L = 1 \text{ H}$, $C = 0.25 \mu\text{F} = \frac{1}{4} \mu\text{F}$

$$\alpha = \frac{R}{2L} = \frac{8.5 \text{ k}\Omega}{2(1 \text{ H})} = 4250 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1 \text{ H})(\frac{1}{4} \mu\text{F})}} = \frac{1}{\frac{1}{2} \text{ ms}} = 2,000 \text{ s}^{-1}$$

$\alpha > \omega_0$, so this is overdamped

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -4250 \pm \sqrt{(4250)^2 - (2000)^2} \\ = -4250 \pm 3750$$

$$s_1 = -4250 + 3750 = -500$$

$$s_2 = -4250 - 3750 = -8,000$$

$$i(t) = Ae^{-500t} + Be^{-8000t}$$

$$i(0) = 0 = A + B, \Rightarrow B = -A, \text{ so}$$

$$i(t) = A[e^{-500t} - e^{-8000t}]$$

$$\frac{di}{dt} = A[-500e^{-500t} + 8000e^{-8000t}]$$

$$\frac{di}{dt}(0^+) = A[-500 + 8000] = 7500A$$

~~KVL @ t=0^+ : $Ri(0^+) + L\frac{di}{dt}(0^+) + v_C(0^+) = 0$ from $t=0^+$:~~

~~$Ri(0^+) + L\frac{di}{dt}(0^+) + v_C(0^+) = 0$~~

~~$0 + L\frac{di}{dt}(0^+) + 5V = 0$~~


$$\frac{di}{dt}(0^+) = -\frac{5V}{L} = -5 \text{ A/s}$$

$$\text{So } -5 \frac{\text{A}}{\text{s}} = 7500 \text{ s}^{-1} \text{A}$$

$$-\frac{5}{7500} = A$$

$$-\frac{2}{3} \text{mA} = A$$
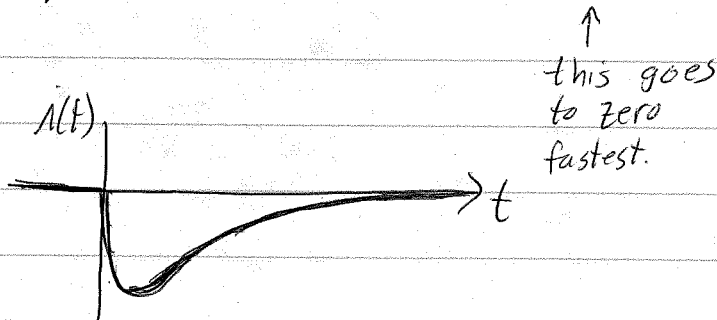
$$i(t) = -\frac{2}{3} \text{mA} [e^{-500t} - e^{-8000t}]$$



Now let $R = 4 \text{ k}\Omega$, L & C remain.

$$\alpha = \frac{R}{2L} = \frac{4 \text{ k}\Omega}{2(1 \text{ H})} = 2,000 \text{ s}^{-1}$$

$$\omega_0 = 2,000 \text{ s}^{-1} \text{ (as before)}$$

$\alpha = \omega_0 \Rightarrow$ critically damped.

$$i(t) = (C + Dt)e^{-\alpha t}$$


$$i(0^+) = C = 0, \text{ so}$$

$$i(t) = Dte^{-\alpha t}$$

$$\frac{di}{dt} = D[e^{-\alpha t} - \alpha te^{-\alpha t}]$$

$$\frac{di}{dt}(0^+) = D[1 - 0] = D = -\frac{5}{L} = -5 \text{ A/s.}$$

so $i(t) = -5 t e^{-2000t}$

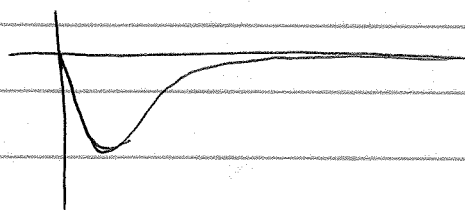

looks like over-damped,
just gets to 0 faster,

Let $R = 1 \text{ k}\Omega$:

$$\alpha = \frac{R}{2L} = \frac{1000}{2(1)} = 500 \text{ s}^{-1}$$

$$\omega_0 = 2000 \text{ s}^{-1}$$

~~under~~ $\alpha < \omega_0 \Rightarrow$ underdamped

$$\begin{aligned} \omega_d &= \sqrt{\omega_0^2 - \alpha^2} \\ &= \sqrt{(2000)^2 - (500)^2} \\ &= 1936 \text{ s}^{-1} \end{aligned}$$

$$i(t) = e^{-\alpha t} [E \cos(\omega_d t) + F \sin(\omega_d t)]$$

$$i(0^+) = E = 0$$

$$F = \frac{\frac{di}{dt}(0^+) + \alpha i(0^+)}{\omega_d} = \frac{-5 \text{ A/s} + \cancel{\alpha(0)}}{1936 \text{ s}^{-1}}$$


$$F = -2.58 \text{ mA}$$

So

$$i(t) = e^{-500t} [-2.58 \text{ mA} \sin(1936t)]$$

$$= -2.58 \text{ mA} e^{-500t} \sin(1936t)$$

237

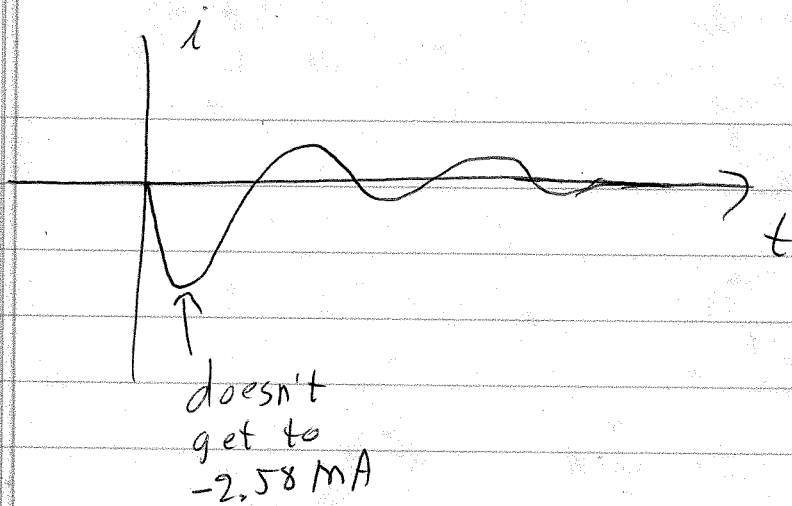

238

From these we can get other ~~the~~ parameters,
like $v_R(t) = Ri(t) \Rightarrow$ same shape, just a scale factor.


$$v_L(t) = L \frac{di(t)}{dt}$$

$$v_C(t) = \frac{1}{C} \int i(x) dx + v_C(0)$$

or use KVL

$$v_C(t) = -v_L(t) - v_R(t)$$

Case A:

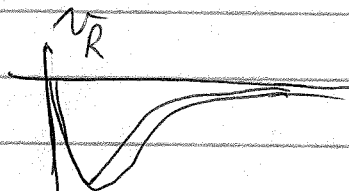


$$\begin{aligned} v_R(t) &= Ri(t) \\ &= R\left(-\frac{2}{3}\text{mA}\right)\left[e^{-500t} - e^{-8000t}\right] = -5.667\text{V}\left[e^{-500t} - e^{-8000t}\right] \end{aligned}$$

$$v_L(t) = L\left(-\frac{2}{3}\text{mA}\right)\left[-500e^{-500t} + 8000e^{-8000t}\right]$$


$$= -\frac{2}{3}\text{mV}\left[-500e^{-500t} + 8000e^{-8000t}\right]$$
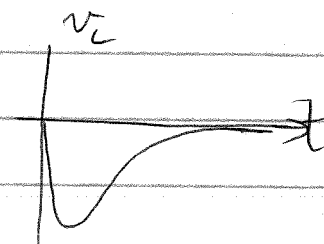
$$= +0.333\text{V}e^{-500t} - 5.333\text{V}e^{-8000t}$$




$$v_C(t) = -0.333\text{V}e^{-500t} + 5.333\text{V}e^{-8000t} + 5.667\text{V}e^{-500t} - 5.667\text{V}e^{-8000t}$$
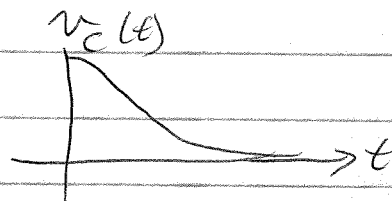
$$\begin{aligned} &\text{make shape} \\ &= 5.333\text{V}e^{-500t} - 0.333\text{V}e^{-8000t} \end{aligned}$$



What about $L+C$ in parallel?

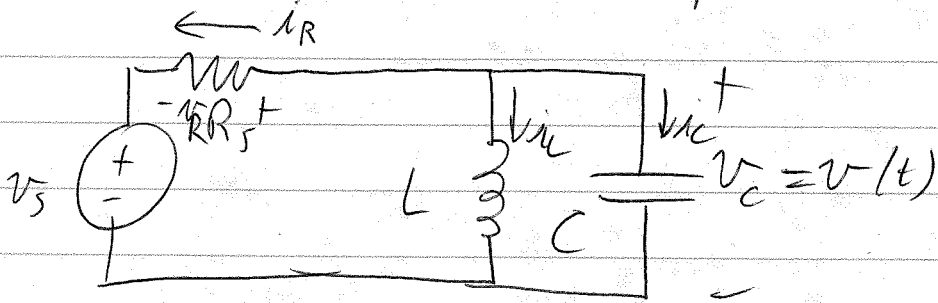

KCL: $i_R + i_L + i_C = 0$

$$\frac{v - v_s}{R} + \frac{1}{L} \int_0^t v(x) dx + i_L(0) + C \frac{dv}{dt} = 0$$

~~We get zero input~~

Take $\frac{d}{dt}$: $C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v(t) = \frac{1}{R} \frac{dv_s}{dt}$

Characteristic eqn: $Cs^2 + \frac{1}{R}s + \frac{1}{L} = 0$

or $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$

$$s_{1,2} = \frac{-\frac{1}{RC} \pm \sqrt{(\frac{1}{RC})^2 - 4(1)(\frac{1}{LC})}}{2(1)}$$

$$= -\frac{1}{2RC} \pm \sqrt{(\frac{1}{2RC})^2 - (\frac{1}{LC})}$$

Now let $\alpha_{\text{par}} = \frac{1}{2RC}$ + $\omega_0 = \frac{1}{\sqrt{LC}}$ (as before)

$$s_{1,2} = -\alpha_{\text{par}} \pm \sqrt{\alpha_{\text{par}}^2 - \omega_0^2}$$

So, parallel LC gives same results except

$$\alpha_{\text{par}} = \frac{1}{2RC} = \frac{1}{2\tau_c}$$

(240)

For series we had

$$\alpha_{\text{ser}} = \frac{R}{2L} = \frac{1}{2(L/R)} = \frac{1}{2\tau_L}$$

I remember these as follows:


Series LC has a common Current. Current is the state variable for an Inductor,

$$\text{so } \alpha_{\text{ser}} = \frac{1}{2\tau_L}$$

Parallel LC has a common Voltage. Voltage is the state variable for a Capacitor,

$$\text{so } \alpha_{\text{par}} = \frac{1}{2\tau_C}$$

Example:

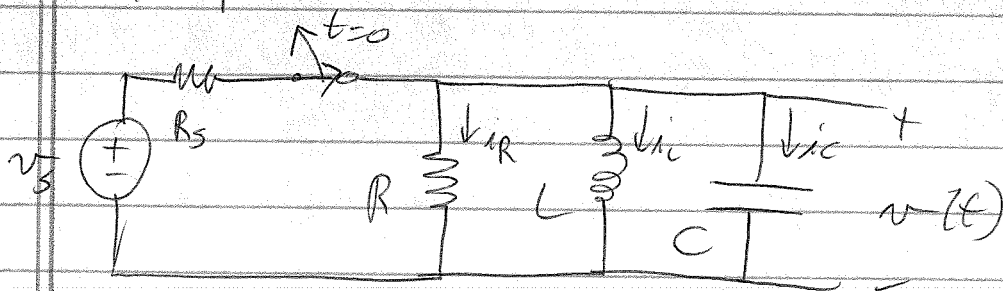

Find $v(t)$.