

Introduction to Audio and Music Engineering

Lecture 16

Topics:

- Tone and frequency spectra
- Filtering and frequency content of signals
- RC Low-pass and high-pass filters
- RLC Band pass filters
- Filter banks and Graphic Equalizers

Tone?

- The quality or character of sound
- The characteristic quality or timbre of a particular instrument or voice.
- The character or quality of a musical sound or voice as distinct from its pitch and intensity.


Frequency → pitch

Sound pressure level → intensity (loudness)

Attack, Spectrum, Spectral evolution → tone (timbre)

Tone is related to the spectrum of a waveform.

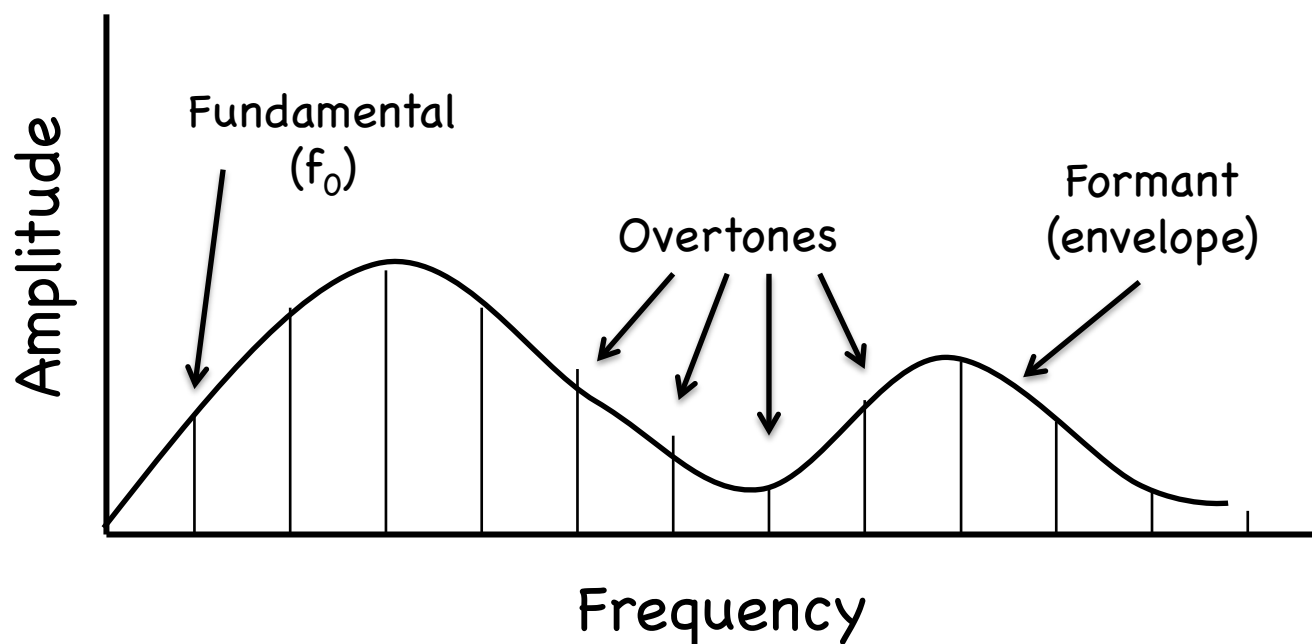The spectrum is a display of the frequency content of a waveform.




If the overtones are at integer multiples of the fundamental they are called harmonics, e.g., $2f_0 \rightarrow 2^{\text{nd}}$ harmonic, etc.

Most musical sounds have harmonic (or nearly so) overtones.


Back to circuits ...

Applying a filter to alter tone ...


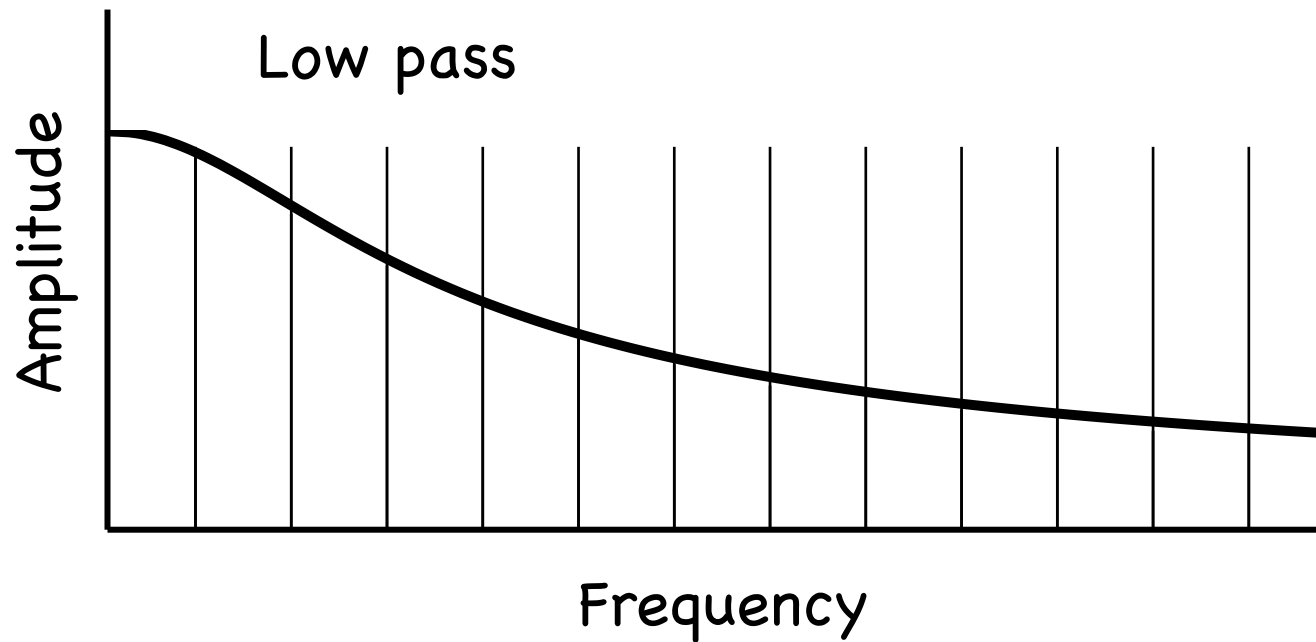


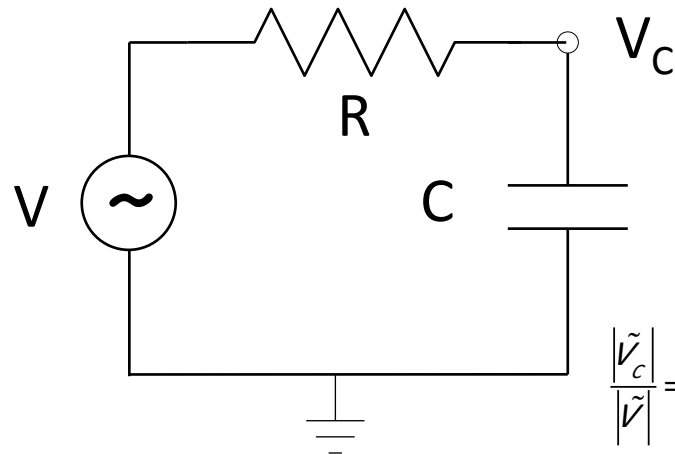Examples ...


1st order RC low-pass and high-pass filters



$$\frac{|\tilde{V}_C|}{|\tilde{V}|} = \left[\frac{1}{1 + \omega^2 R^2 C^2} \right]^{1/2}$$

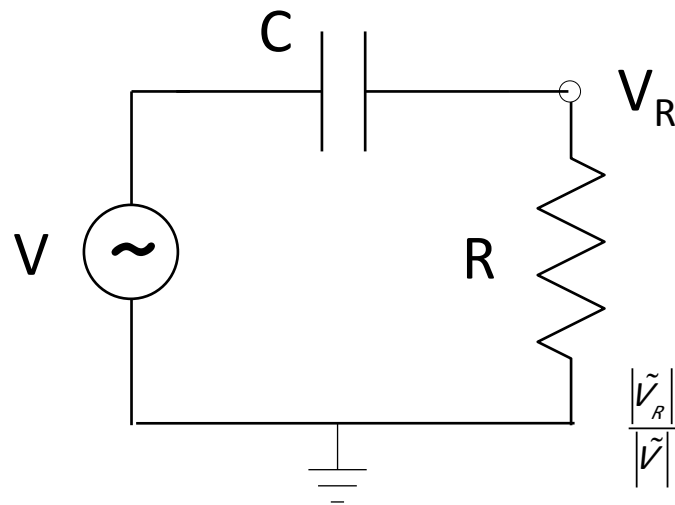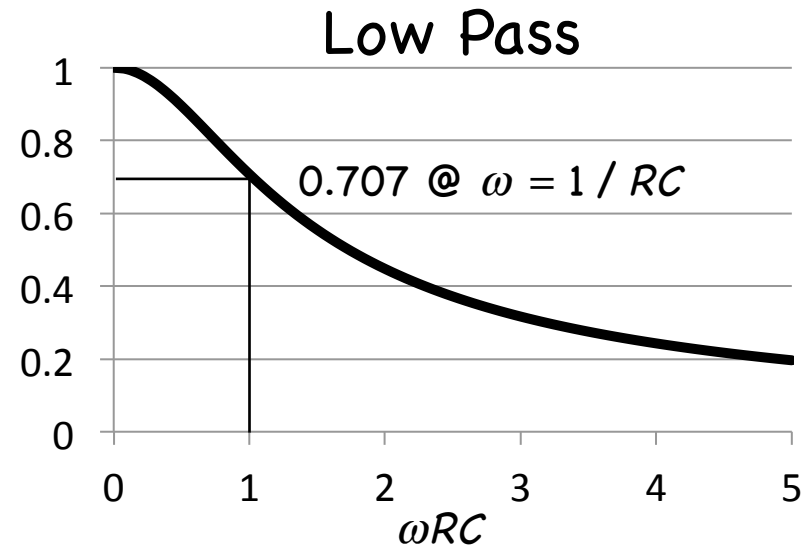


$$\frac{|\tilde{V}_R|}{|\tilde{V}|} = \left[\frac{\omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2} \right]^{1/2}$$

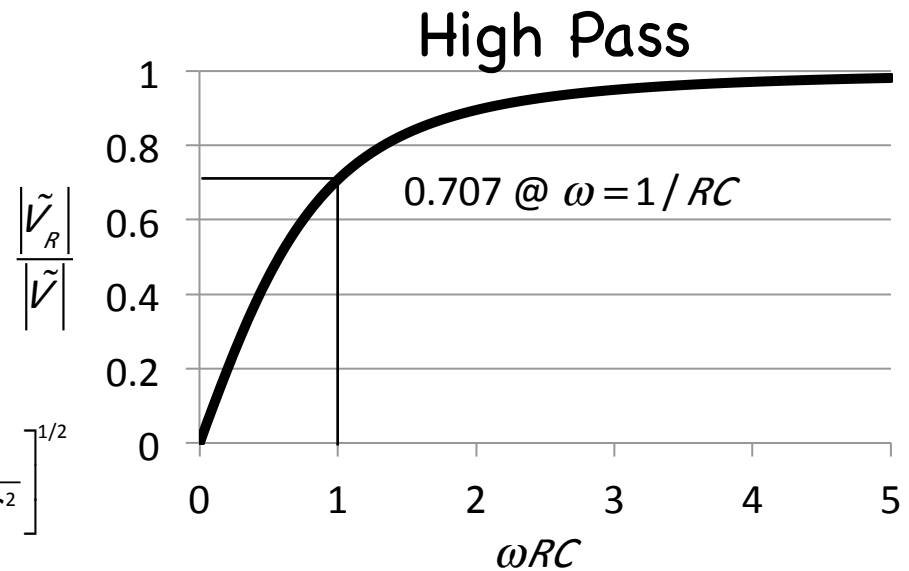


Matlab Simulation

Begin with harmonic overtone series.

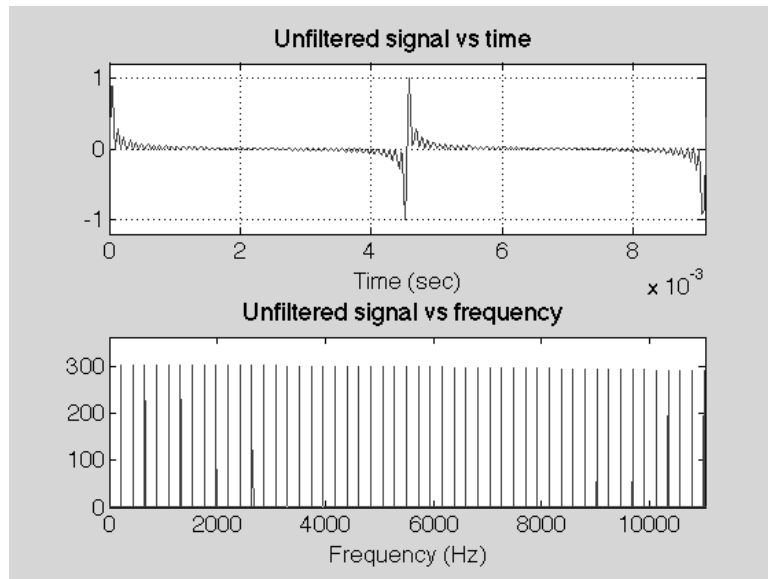
Equal amplitude sine waves
at integer multiples of f_0




High Pass

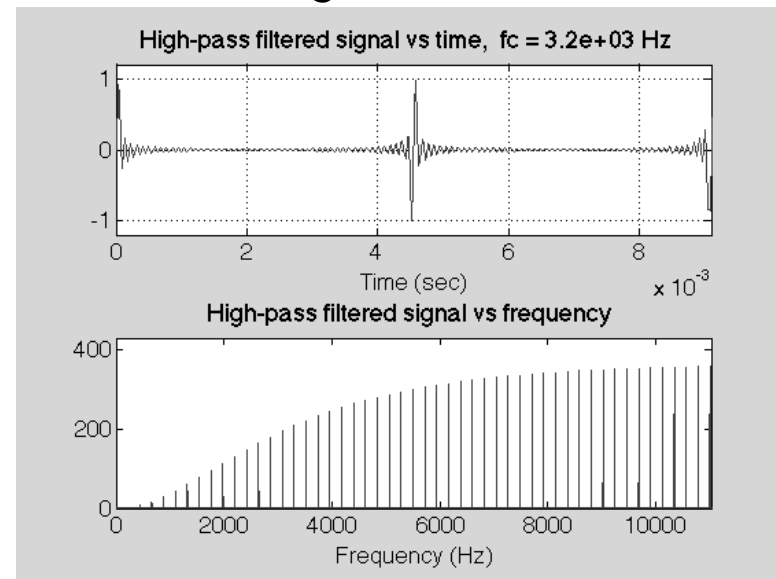

Low Pass

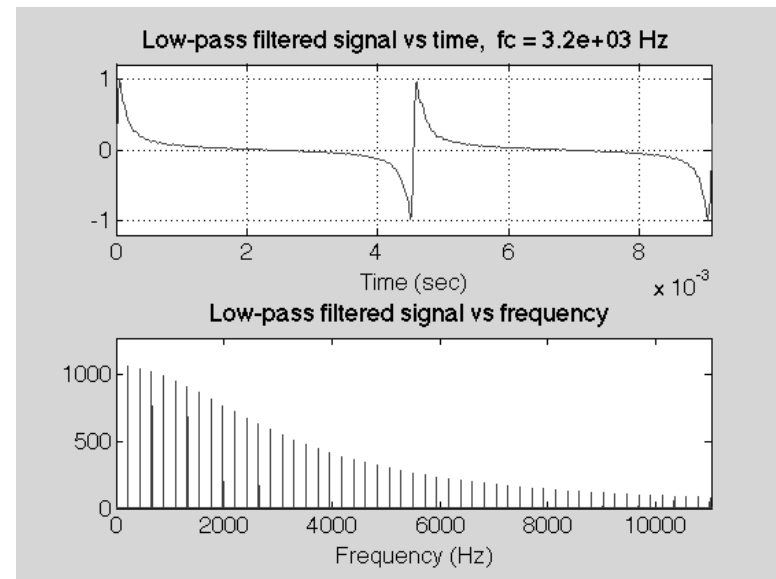

Band Pass Filters

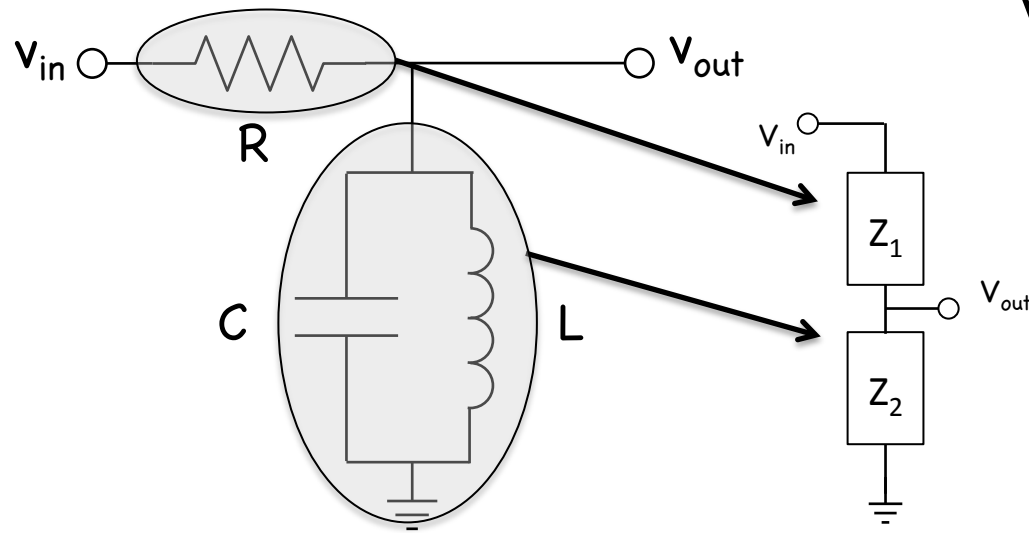


Voltage divider: R & L//C

$$V_{out} = V_{in} \frac{Z_2}{Z_1 + Z_2}$$

$$L//C = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - \omega^2 LC}$$
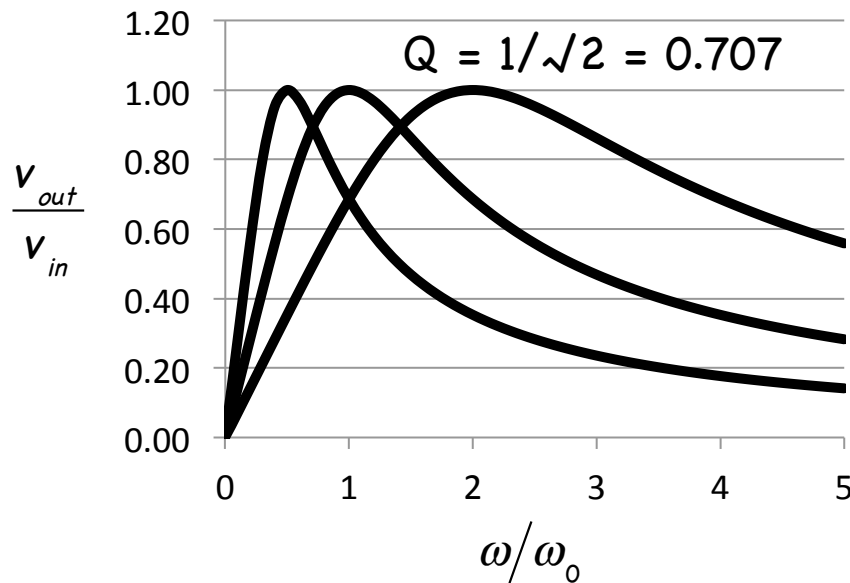
$$V_{out} = V_{in} \frac{\frac{j\omega L}{1 - \omega^2 LC}}{R + \frac{j\omega L}{1 - \omega^2 LC}}$$



$$V_{out} = V_{in} \frac{\frac{\omega}{\omega_0} Q}{\left[\left(1 - \frac{\omega^2}{\omega_0^2} \right)^2 + \frac{\omega^2}{\omega_0^2} Q^2 \right]^{1/2}}$$


$$\omega_0 = \frac{1}{(LC)^{1/2}}$$

$$Q = \frac{\omega_0 L}{R}$$


Graphic Equalizer

Bank of bandpass filters ...

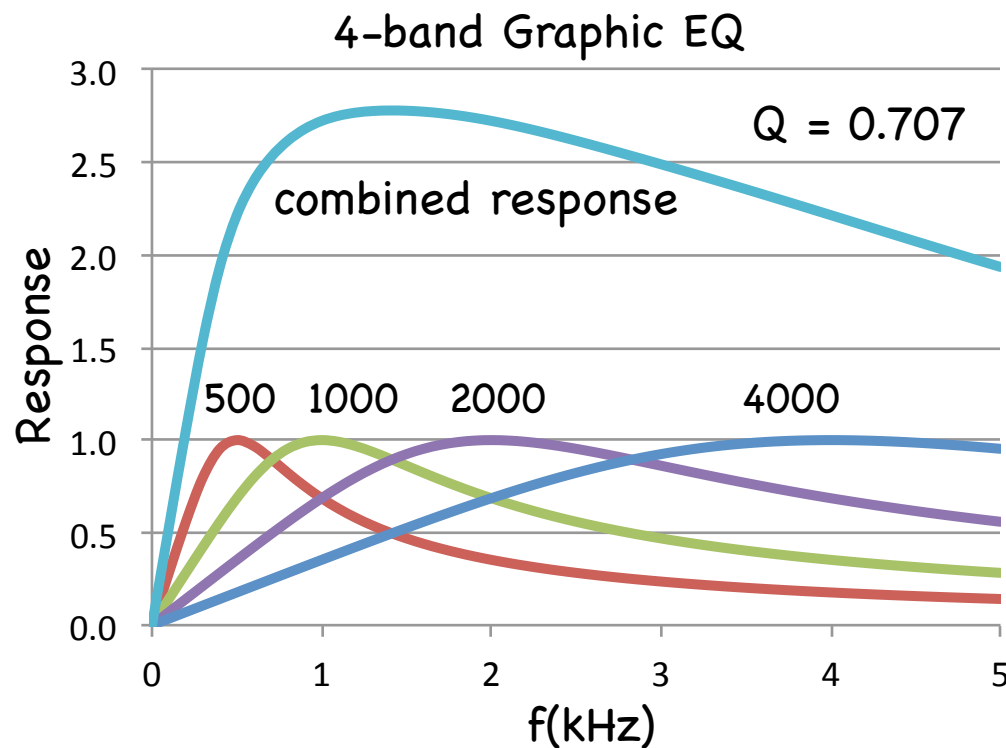$Q = 1/\sqrt{2} = 0.707 \rightarrow$ Butterworth Bandpass (2nd order)



Fletcher Munson - hearing response

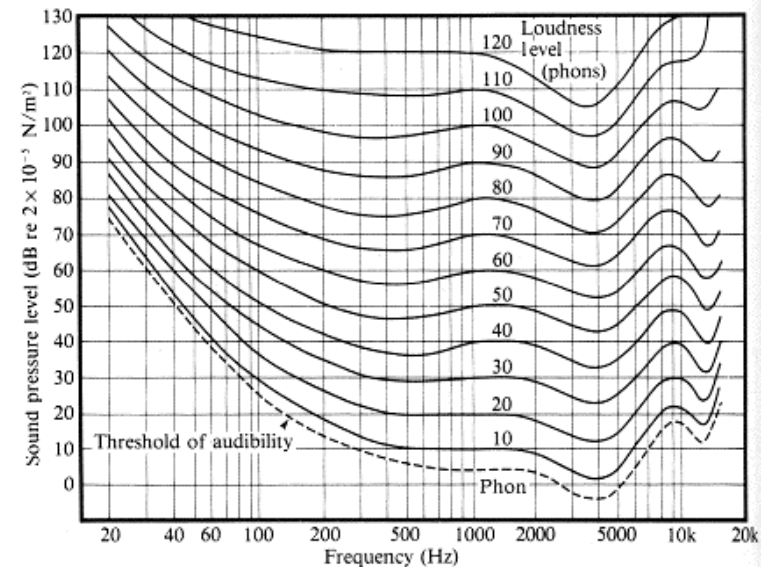

It's OK if the filter response decreases a bit (≈ -3 dB) at high frequencies because human hearing sensitivity increases ($\approx +20$ dB).



Octave filters (Constant "Q")

Center frequencies increase by octaves (x2):



$$f_{n+1} = 2f_n$$

Fractional bandwidth is fixed:



$$\Delta f_n / f_n = Q^{-1}$$

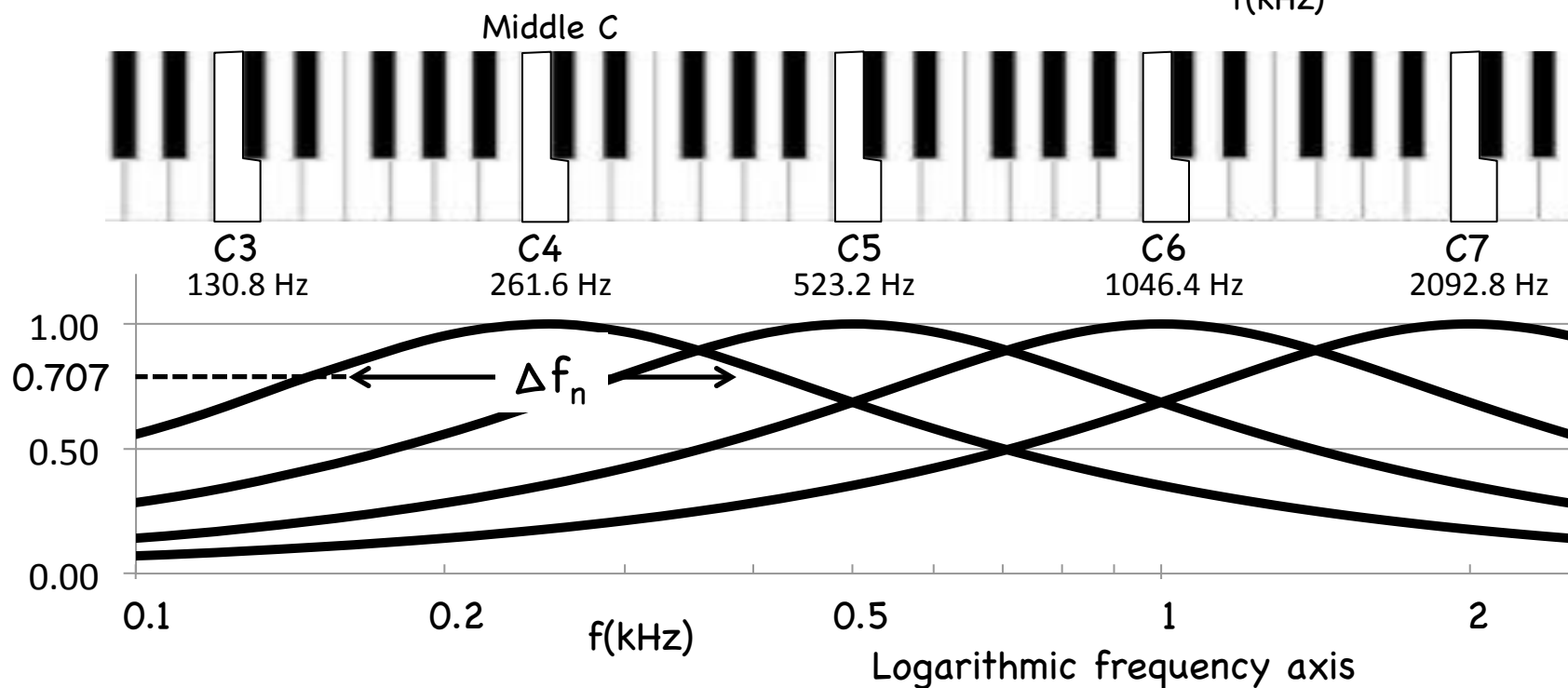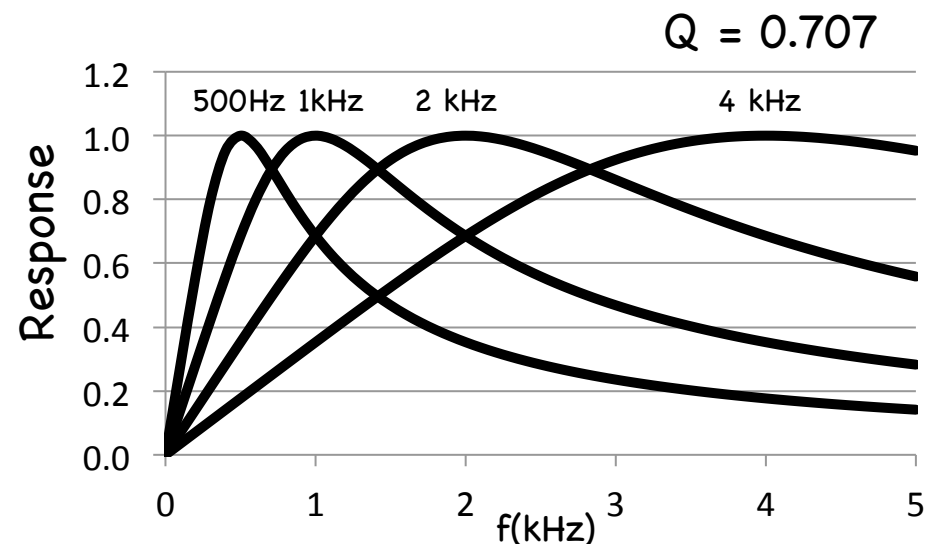

Filter Performance ...

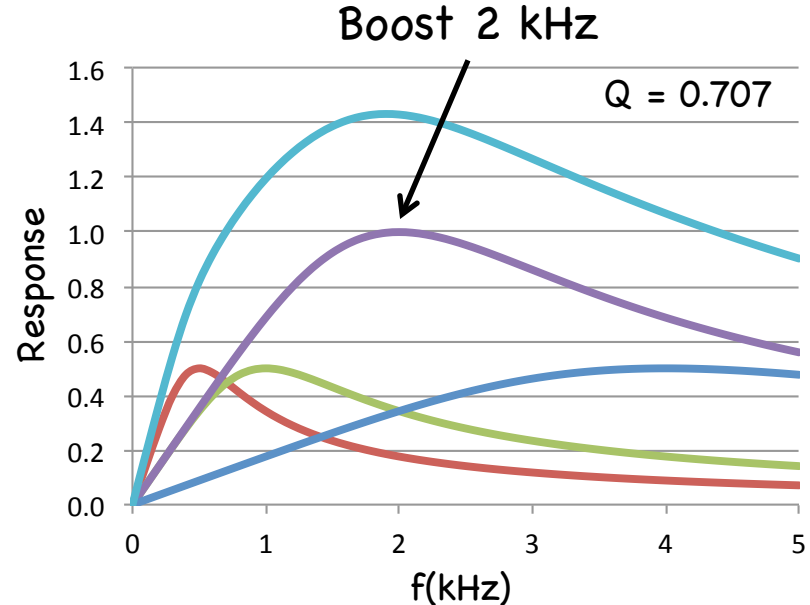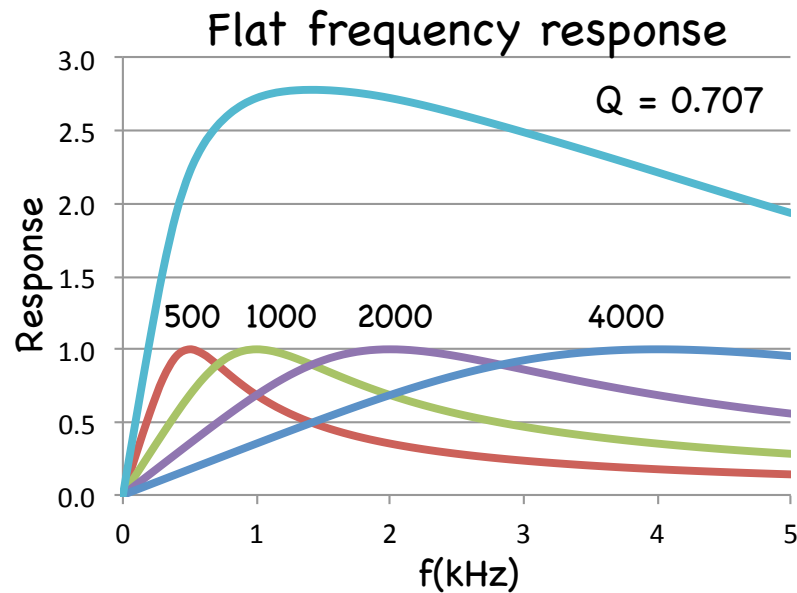

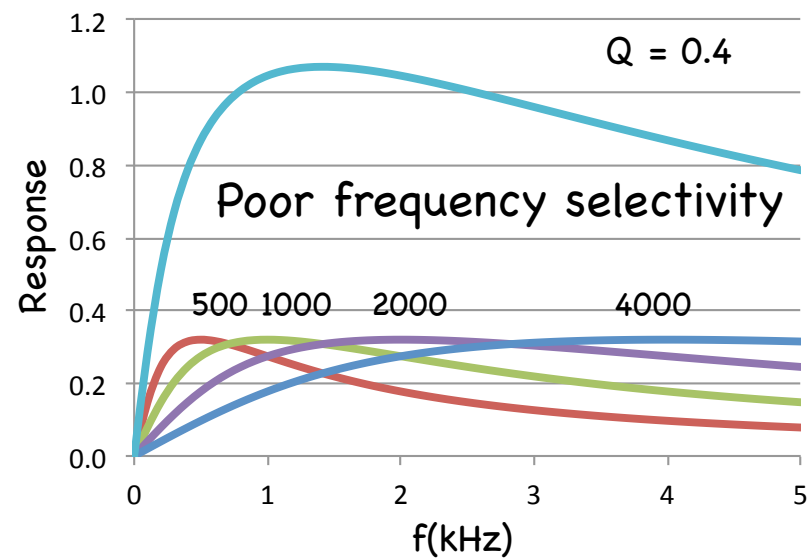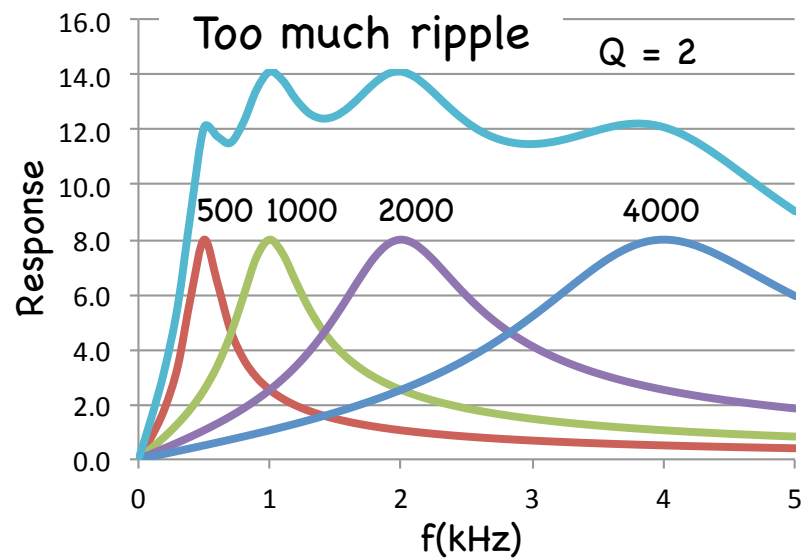Tradeoff between ripple and frequency selectivity ...



10-Band Graphic EQ Demonstration using Matlab/Simulink

$f_c = [31.5, 63, 125, 250, 500, 1000, 2000, 4000, 8000, 16000]$ Hz

