

This is variously called the

Zero-Input Response (text)  
 Natural Response  
 Source-Free Response


We wrote all this down using the

State Variables  $v_c + i_c$ , now I will

tell you that the form (exponential decay)

applies to every response in the ckt.

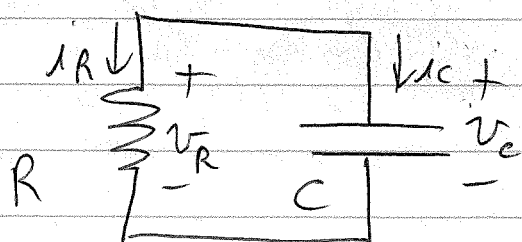For example, if I asked about the current through the resistor in the RC ckt:



$$v_c(0^-) = V_0$$

$$v_c = \begin{cases} V_0 & t < 0 \\ V_0 e^{-t/RC} & t \geq 0 \end{cases}$$

$$i_R = -i_C \quad \text{but} \quad i_C = C \frac{dv_c}{dt}$$

$$\text{so} \quad \frac{dv_c}{dt} = -\frac{1}{RC} V_0 e^{-t/RC}$$

$$\text{and} \quad i_R = -\left(-\frac{1}{RC}\right) V_0 e^{-t/RC} = \frac{C}{RC} V_0 e^{-t/RC} = \frac{1}{R} V_0 e^{-t/RC}$$

OR we could say:

This is a Zero-Input Response, so

$i_R(t) = I_0 e^{-t/RC}$  will be the form.


$$I_0 = i_R(0^+) = \frac{v_R(0^+)}{R} = \frac{v_C(0^+)}{R} \quad (R \text{ and } C \text{ in parallel})$$


but  $v_C(0^+) = v_C(0^-) = V_0$ , so

$$I_0 = \frac{V_0}{R} \text{ and } \underline{\underline{i(t) = \frac{V_0}{R} e^{-t/RC}}}$$

Do lots of examples and exercises.

The next step is to ask "What if the source is on for  $t > 0$ , say as a constant?"

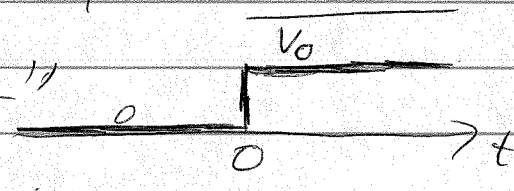IE: a "step ~~resp~~ input" 

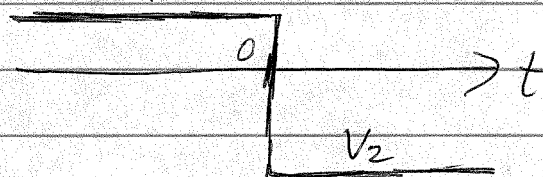or even 

In this case we must include the "forcing function" for  $t > 0$ , and the <sup>total</sup> response is the sum

$$v_T(t) = v_F(t) + v_N(t)$$



We know this is  $v_N(t) = K e^{-t/\tau}$  but we cannot evaluate  $K$  yet.

The forced response  $v_F$  is a solution to  $\frac{dv_F}{dt} + \frac{1}{\tau} v_F = \frac{1}{\tau} V_0$  (or  $\frac{1}{\tau} V_2$ ) etc

We are looking for a particular solution to this equation, and indeed taking  $v_F = V_0$  is a solution, since  $0 + \frac{1}{\tau} V_0 = \frac{1}{\tau} V_0$  is true.


So  $v_T(t) = V_0 + Ke^{-t/\tau}$  is the total solution.

Evaluate  $K$  now:


$$v_T(0^+) = V_0 + Ke^{-0} = 0$$

$$K = -V_0$$
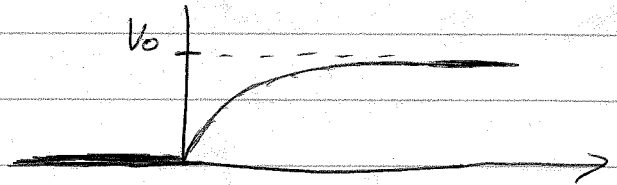
$$\text{So } v_T(t) = V_0 - V_0 e^{-t/\tau} = V_0(1 - e^{-t/\tau})$$




Example:

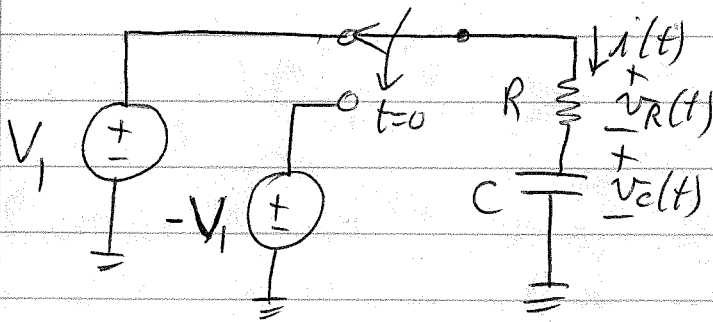

Find  $v_C(t)$ ,  $v_R(t)$ ,  
and  $i(t)$

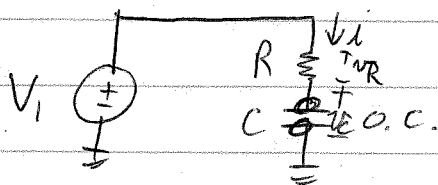$t=0^-$ : Find IC of state variable, others are interesting.




$$v_C(0^-) = V_1$$

$$v_R(0^-) = 0$$

$$i(0^-) = 0$$

2)  $t=0^+$ :

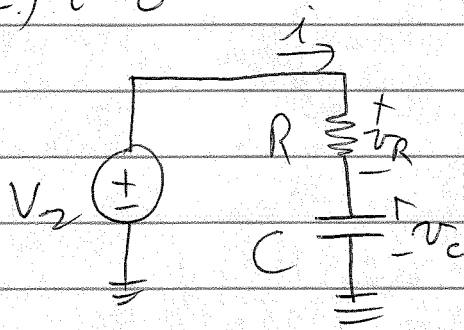

$\tau = RC$

$v_C(0^+) = v_C(0^-) = V_1$  (state var.)


KVL:  $v_R + v_C - V_2 = 0$   
 $v_R + v_C = V_2$

or  $v_R(0^+) + v_C(0^+) = V_2$

$v_R(0^+) = V_2 - v_C(0^+) = V_2 - V_1 = -2V_1$  (not continuous)

$i = \frac{v_R}{R} \Rightarrow i(0^+) = \frac{v_R(0^+)}{R} = \frac{V_2 - V_1}{R}$  (not continuous)  
 $= -\frac{2V_1}{R}$

3)  $t \rightarrow \infty$ :

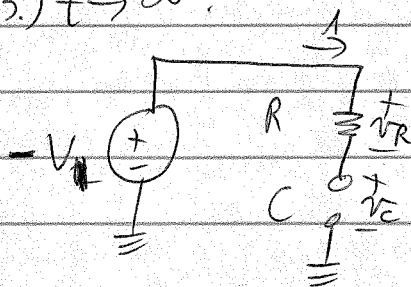

$v_C(\infty) = -V_1$  (not zero)

$v_R(\infty) = 0$

$i(\infty) = 0$

these are particular solutions for  $v_C, v_R, i$ .

~~So  $v_C(t) = V_2 + K e^{-t/\tau}$~~

So, for  $t > 0$ :

~~$v_C(t) = V_2 + K e^{-t/\tau}$~~

$v_C(t) = -V_1 + K e^{-t/\tau}$

$v_C(0^+) = V_1 = -V_1 + K$

$K = V_1 + V_1 = 2V_1$

so

$v_C(t) = -V_1 + (2V_1) e^{-t/\tau}$

$= v_C(\infty) + (v_C(0^+) - v_C(\infty)) e^{-t/\tau}$



AND  $v_R(t) = 0 + Ke^{-t/\tau}$   
 $v_R(0^+) = (-V_2 - V_1) = K$

so  $v_R(t) = (-2V_1)e^{-t/\tau} = -2V_1e^{-t/\tau}$

AND

$i(t) = \cancel{0} + Ke^{-t/\tau}$   
 $i(0^+) = \frac{V_2 - V_1}{R} = K$

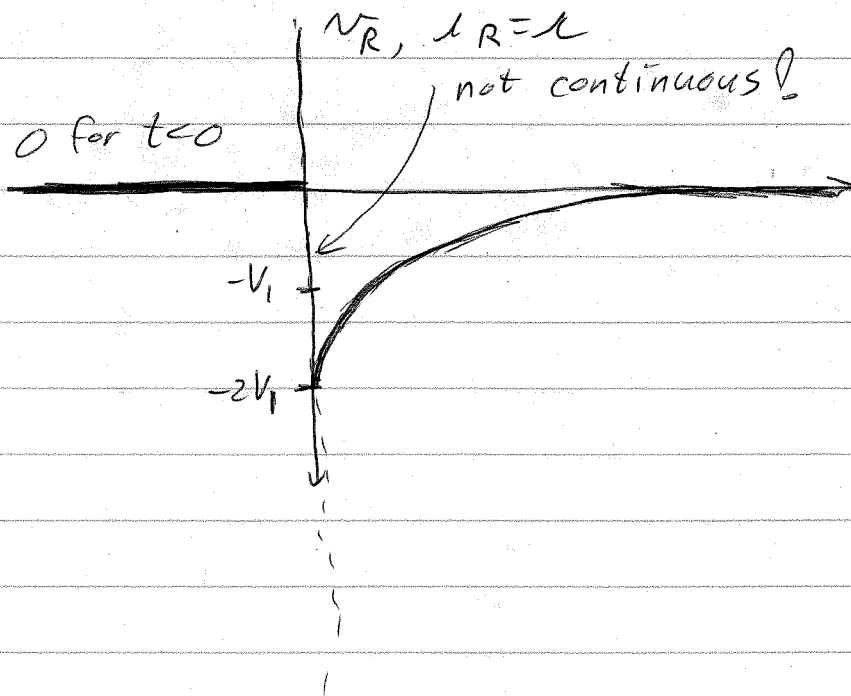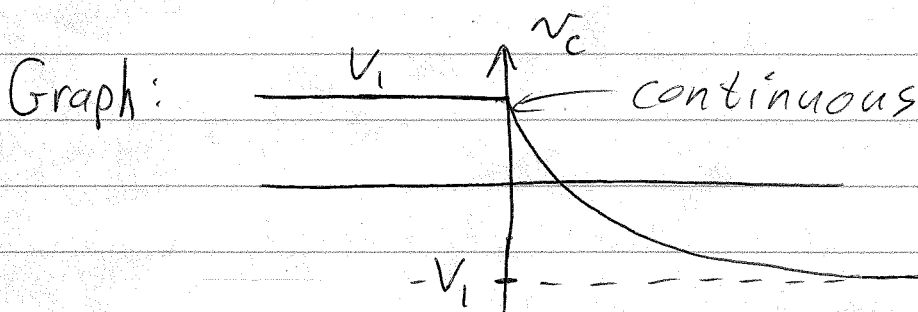so  $i(t) = \frac{V_2 - V_1}{R} e^{-t/\tau} = -\frac{2V_1}{R} e^{-t/\tau}$




So, in general, the Total Response of Anything in a 1<sup>st</sup> order ckt ~~is~~ to a step input is:

$$y(t) = \begin{cases} y(0^-) & t < 0 \\ y(\infty) + (y(0^+) - y(\infty))e^{-t/\tau} & t \geq 0 \end{cases}$$

First Order Step Response

(Zero Input is ~~area~~ a special case when  $y(\infty) = 0$ )

Example

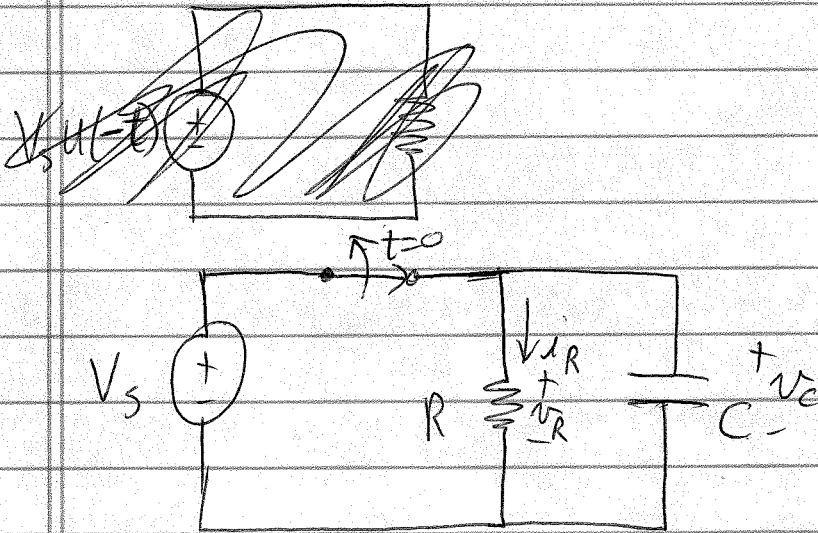

Find  $i_R(t)$ .

Solution: Note  $v_R = v_C$  +  $i_R = \frac{v_R}{R} = \frac{v_C}{R}$  (always)

$$t=0^+ : v_C(0^-) = V_s$$

$$v_R(0^-) = V_s$$

$$i_R(0^-) = \frac{V_s}{R}$$

$$t=0^+: v_c(0^+) = v_c(0^-) = V_s \quad (\text{Must be})$$

$$\text{so } v_R(0^+) = v_c(0^+) = V_s$$

$$\text{and } i_R(0^+) = \frac{V_s}{R}$$


} these are continuous because of circuit layout, not because they have to be.

$$t=\infty: i_R(\infty) = 0 \quad (\text{source-free})$$


$$\text{so } i_R(t) = \begin{cases} \frac{V_s}{R} & t < 0 \\ \frac{V_s}{R} e^{-t/\tau} & t \geq 0 \end{cases}$$



Example:

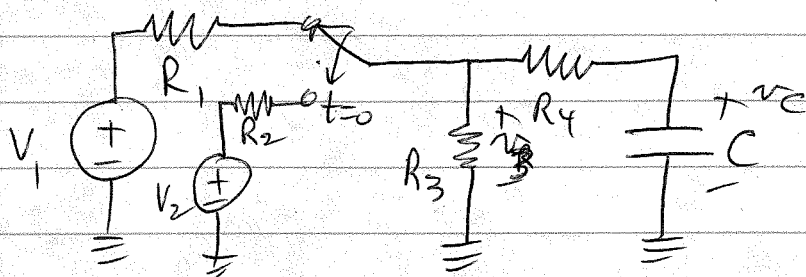Find  $v_3(t)$ . $t=0^-$ : Ignore  $V_2 + R_2$ ,  $C$  is an open ckt, ignore  $R_4$ .

$$\underline{v_C(0^-) = \frac{R_3}{R_1 + R_3} V_1 = v_3(0^-)}$$

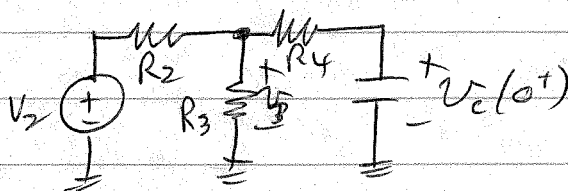 $t=0^+$ : Ignore  $V_1 + R_1$ :  $\underline{v_C(0^+) = v_C(0^-)}$ 

$$R_{eq} = \frac{R_2 R_3}{R_2 + R_3} + R_4$$

$$\text{KCL: } \frac{v_3 - V_2}{R_2} + \frac{v_3 - v_C}{R_4} + \frac{v_3}{R_3} = 0$$

$$\left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) v_3 = \frac{1}{R_2} V_2 + \frac{1}{R_4} v_C(0^+)$$

$$\frac{R_3 R_4 + R_2 R_4 + R_2 R_3}{R_2 R_3 R_4} v_3 =$$

$$v_3 = \frac{R_3 R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4} V_2 + \frac{R_2 R_3}{R_2 R_3 + R_2 R_4 + R_3 R_4} \left( \frac{R_3}{R_1 + R_3} \right) V_1$$

$$v_3(0^+) = \frac{1}{\frac{R_2}{R_4} + \frac{R_3}{R_4} + 1} V_2 + \left( 1 + \frac{R_3}{R_4} + \frac{R_2}{R_3} \right) \left( \frac{1}{1 + \frac{R_1}{R_3}} \right) V_1$$

$t \rightarrow \infty$ : Ignore  $V_1 + R_1$ ,  $C$  is an Open Ckt, ignore  $R_4$ .

$$v_3(\infty) = \frac{R_3}{R_2 + R_3} V_2 = \frac{1}{1 + \frac{R_2}{R_3}} V_2$$

$$\text{So, } v_3(t) = \begin{cases} \frac{R_3}{R_1 + R_3} V_1 = \frac{1}{1 + \frac{R_1}{R_3}} V_1 & t < 0 \end{cases}$$

~~$$\frac{1}{R_4 + R_2} V_2 + \left[ \frac{1}{1 + \frac{R_2 + R_3}{R_4}} V_2 + \left( \frac{1}{1 + \frac{R_2}{R_3} + \frac{R_3}{R_4}} \right) \left( \frac{1}{1 + \frac{R_1}{R_3}} \right) V_1 - \frac{1}{1 + \frac{R_2}{R_3}} V_2 \right]$$~~

$$\left[ \frac{1}{1 + \frac{R_2}{R_3}} V_2 + \left[ \frac{1}{1 + \frac{R_2 + R_3}{R_4}} V_2 + \left( \frac{1}{1 + \frac{R_2}{R_3} + \frac{R_3}{R_4}} \right) \left( \frac{1}{1 + \frac{R_1}{R_3}} \right) V_1 - \frac{1}{1 + \frac{R_2}{R_3}} V_2 \right] e^{-t/\tau}$$


where  $\tau = R_{eq} C = \left( R_4 + \frac{R_2 R_3}{R_2 + R_3} \right) C$

Let all the R's be equal, so

$$v_3(t) = \begin{cases} \frac{1}{2} V_1 & t < 0 \\ \frac{1}{2} V_2 + \left[ \frac{1}{3} V_2 + \left( \frac{1}{3} \right) \left( \frac{1}{2} \right) V_1 - \frac{1}{2} V_2 \right] e^{-t/\tau} & t \geq 0 \\ = \frac{1}{2} V_2 + \left[ \left( \frac{1}{3} - \frac{1}{2} \right) V_2 + \frac{1}{6} V_1 \right] e^{-t/\tau} \\ = \frac{1}{2} V_2 + \left[ -\frac{1}{6} V_2 + \frac{1}{6} V_1 \right] e^{-t/\tau} \end{cases}$$

Pick  $V_1 = 1V$ ,  $V_2 = -1V$ , so
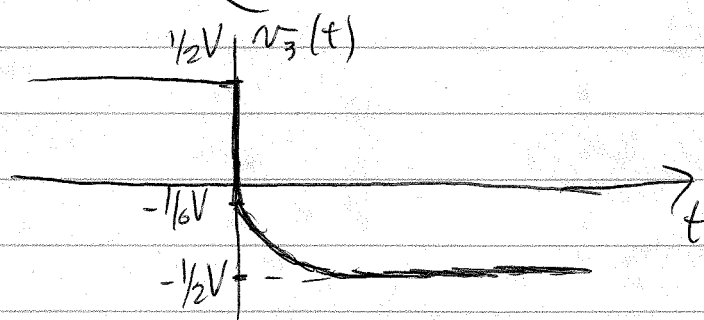
$$v_3(t) = \begin{cases} \frac{1}{2} V & t < 0 \\ -\frac{1}{2} V + \left[ \frac{1}{6} V + \frac{1}{6} V \right] e^{-t/\tau} & t \geq 0 \\ = -\frac{1}{2} V + \frac{1}{3} V e^{-t/\tau} \end{cases}$$



$$\tau = \left( R + \frac{R^2}{2R} \right) C = \underline{\underline{\frac{3}{2} RC}}$$