

$$V_1 + V_2 - V = 0$$

$$V = V_1 + V_2$$

$$V = R_1 I + R_2 I$$

$$V = (R_1 + R_2) I$$

$$V_R - V = 0$$


$$V_R = V$$

$$V = R_{eq} I$$

$$V = R_{eq} I$$

$$\text{or } R_{eq} = R_1 + R_2$$


True for  $N$  series resistors:

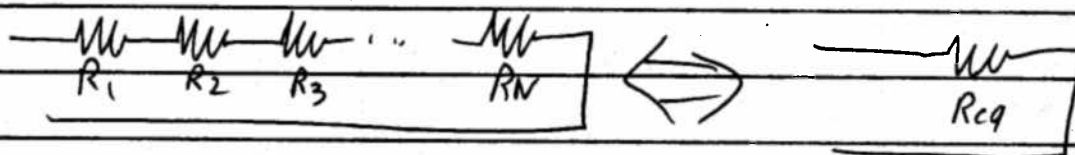

$$R_{eq} = \sum_{i=1}^N R_i$$

Parallel:


Use Conductance  $G = \frac{1}{R}$

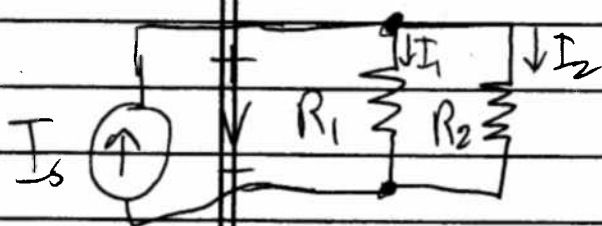

$$I_1 = G_1 V$$

$$I_2 = G_2 V$$

$$I_s = I_1 + I_2$$

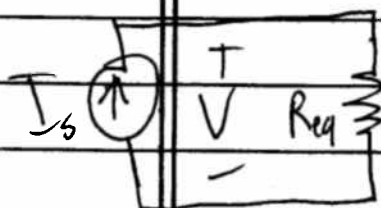


$$I_s = G_{eq} V$$

$$I = G_{eq}V = I_1 + I_2 = G_1V + G_2V \\ = (G_1 + G_2)V$$


$$\text{or } G_{eq} = G_1 + G_2 \text{ or } \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Same for N parallel :
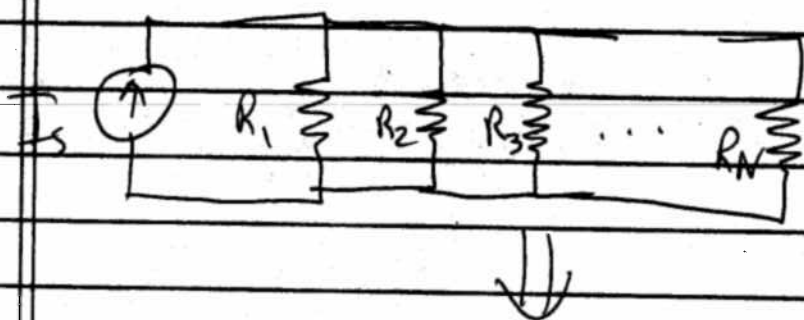
$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$


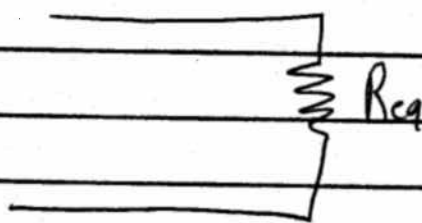
$$= \frac{1}{\frac{R_2 + R_1}{R_1 R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$



$$G_{eq} = \sum_{i=1}^N G_i$$

$$\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$

$$R_{eq} = \left( \sum_{i=1}^N \frac{1}{R_i} \right)^{-1}$$

Results: Series: ①  $R_{eq}$  is larger than any single resistor.

② If one  $R$  is much larger than all others, it dominates.

③  $R_1 = R_2 = R, R_{eq} = 2R$

Parallel: (1)  $R_{eq}$  is smaller than any single  $R$ .

(2) If one  $R$  is much smaller than all others, it dominates.

(3)  $R_1 = R_2 = R, R_{eq} = \frac{1}{2}R$