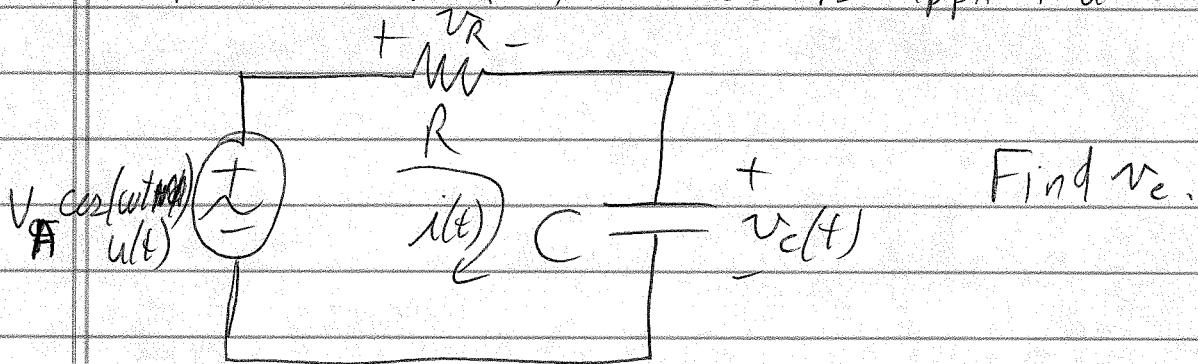


I will quickly touch on 1st order ckt responses to Sinusoidal Inputs, you should read the section 7.4 on this, and on the response to Exponential Inputs.

If a sinusoidal source is applied at $t=0$,



~~We can write $\cos(\omega t + \phi) = a \cos(\omega t) + b \sin(\omega t)$~~

We are given (or can figure out) that $v_c(0) = V_0$
 where ~~$\tan \phi = \frac{b}{a}$~~
 ~~$\phi = \tan^{-1}(\frac{b}{a})$~~

~~We need to find~~

Once again, $v_c(t) = \text{Natural Response} + \text{Forced Response}$

~~and the DE is $\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{1}{RC} V_F \cos(\omega t + \phi)$~~

Once again, $v_c(t) = \text{Natural Response} + \text{Forced Response}$
 $= K e^{-t/RC} + V_F \cos(\omega t + \phi)$

We can write: $V_F \cos(\omega t + \phi) = a \cos \omega t + b \sin \omega t$
 where $\tan \phi = \frac{b}{a}$ or $\phi = \tan^{-1}(\frac{b}{a})$
 $+ V_F = \sqrt{a^2 + b^2}$

So we

222

We will need to find $a+b$.

Put v_F into the DE:

$$RC \frac{d}{dt}(a \cos \omega t + b \sin \omega t) + (a \cos \omega t + b \sin \omega t) = V_A \cos \omega t$$

$$RC(-a \omega \sin \omega t + b \omega \cos \omega t) + (a \cos \omega t + b \sin \omega t) = V_A \cos \omega t$$

$$(b \omega RC + a) \cos \omega t + (-RC \omega a + b) \sin \omega t = V_A \cos \omega t$$

Can only be true if coeff's of $\cos \omega t$ and coeff's of $\sin \omega t$ are equal:

$$\omega RC b + a = V_A \quad \text{and} \quad -\omega RC a + b = 0$$

$$b = \omega RC a$$

$$\begin{aligned} (\omega RC)(\omega RC a) + a &= V_A \\ a(1 + (\omega RC)^2) &= V_A \end{aligned}$$

$$a = \frac{V_A}{1 + (\omega RC)^2} \rightarrow b = \frac{\omega RC}{1 + (\omega RC)^2} V_A$$

$$\text{So } v_c(t) = K e^{-t/RC} + \frac{1}{1 + (\omega RC)^2} V_A \cos \omega t + \frac{\omega RC}{1 + (\omega RC)^2} V_A \sin \omega t$$

$$\text{I.C.: } v_c(0) = K + \frac{1}{1 + (\omega RC)^2} V_A (1) + 0 = V_0$$

$$\text{or } K = V_0 - \frac{1}{1 + (\omega RC)^2} V_A$$

So:

$$v_c(t) = \left[V_0 - \frac{1}{1 + (\omega RC)^2} V_A \right] e^{-t/RC} + \frac{V_A}{1 + (\omega RC)^2} [\cos \omega t + \omega RC \sin \omega t]$$

$$v_c(t) = \underbrace{\left[V_0 - \frac{1}{1+(\omega RC)^2} V_A \right] e^{-t/RC}}_{\text{natural response}} + \underbrace{\frac{V_A}{1+(\omega RC)^2} \left[\cos(\omega t + \phi) \right]}_{\text{forced response}}$$

$$\text{where } \phi = \tan^{-1}\left(-\frac{\omega RC}{1}\right) = -\tan^{-1}(\omega RC)$$

natural
response

↑
decays to
zero

forced response.

↑
continues forever;

1.) SAME FREQUENCY as
input (ω)

2.) Different Amplitude + Phase

3.) Proportional to input

$$v_c(t) = \left[V_0 - \frac{1}{1+(\omega RC)^2} V_A \right] e^{-t/RC} + \frac{V_A}{\sqrt{1+(\omega RC)^2}} \cos(\omega t + \phi), \quad \phi = \tan^{-1}(-\omega RC)$$

"sinusoidal steady state"
 $t \gg 0$, all natural
responses have died out.

ALSO "AC response"

The step response we already spent time on is

the ~~the~~ "Zero Frequency Response": $\omega = 0$

$$\begin{aligned} v_c(t) &= [V_0 - 1 V_A] e^{-t/RC} + \frac{V_A}{1} (1) \\ &= V_A + [V_0 - V_A] e^{-t/RC} \quad \checkmark \end{aligned}$$