

From now on you can use these general results, which can be obtained in several ways:

Given a complex number

$$\hat{A} = a + jb = \sqrt{a^2 + b^2} \angle \tan^{-1}\left(\frac{b}{a}\right) \quad \text{complex conjugate}$$

$$\begin{aligned} \frac{1}{\hat{A}} &= \frac{1}{a + jb} = \frac{a - jb}{(a^2 + b^2)} = \frac{\hat{A}^*}{|\hat{A}|^2} = \frac{1}{\sqrt{a^2 + b^2} \angle \tan^{-1}\left(\frac{b}{a}\right)} = \frac{1 \angle 0^\circ}{\sqrt{a^2 + b^2} \angle \tan^{-1}\left(\frac{b}{a}\right)} \\ &\quad \downarrow \qquad \qquad \qquad \downarrow \\ &\quad \frac{\sqrt{a^2 + b^2} \angle \tan^{-1}\left(\frac{-b}{a}\right)}{(a^2 + b^2)} \qquad \qquad \qquad \frac{1}{\sqrt{a^2 + b^2}} \angle -\tan^{-1}\left(\frac{b}{a}\right) \\ &= \frac{1}{\sqrt{a^2 + b^2}} \angle -\tan^{-1}\left(\frac{b}{a}\right) \qquad \qquad \qquad = \frac{1}{\sqrt{a^2 + b^2}} \angle -\tan^{-1}\left(\frac{b}{a}\right) \end{aligned}$$

So, in the future, if you have

$$\begin{aligned} \frac{\hat{A}}{\hat{B}} &= \hat{A} \left(\frac{1}{\hat{B}} \right) = \hat{A} \left(\frac{\hat{B}^*}{|\hat{B}|^2} \right) \\ &= \frac{\hat{A} \hat{B}^*}{|\hat{B}|^2} \end{aligned}$$

$$\begin{aligned} \text{So, } \frac{3 + 4j}{4 + 3j} &= \frac{(3 + 4j)(4 - 3j)}{(4^2 + 3^2)} = \frac{(3)(4) + (4)(3) + j(16 - 9)}{25} \\ &= \frac{24 + j7}{25} = \frac{\sqrt{24^2 + 7^2} \angle \tan^{-1}\left(\frac{7}{24}\right)}{25} = \frac{1}{25} \angle \tan^{-1}\left(\frac{7}{24}\right) \\ &= \frac{1}{25} \angle 16.26^\circ \end{aligned}$$


Superposition in Phasor Domain

Superposition ^{always} holds in time domain. ~~at the~~

" holds in phasor domain at single frequency.

If sources have different frequencies, analyse at each frequency, convert to time domain, then add up.

Example 8-15

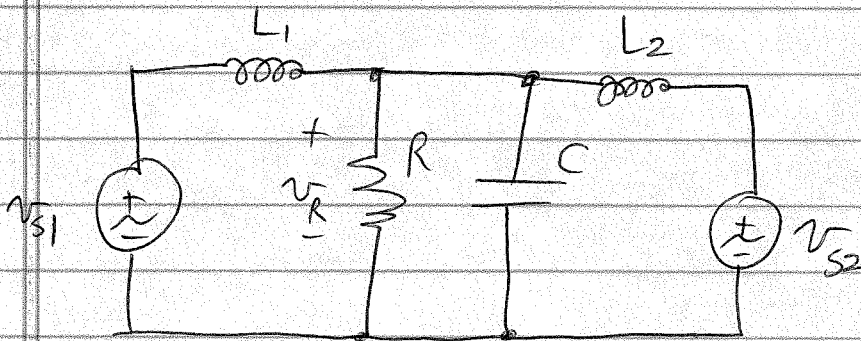

Find $v_R(t)$ for $R=20\Omega$, $L_1=2\text{mH}$, $L_2=6\text{mH}$, $C=20\mu\text{F}$,

$$v_{s1}=100\cos(5000t)\text{V} + v_{s2}=120\cos(5000t+30^\circ)\text{V}.$$


Text solution:

$$j\omega L_1 = j(5000)(2\text{mH}) = j10\ \Omega$$

$$j\omega L_2 = j(5000)(6\text{mH}) = j30\ \Omega$$

$$\frac{1}{j\omega C} = -j \frac{1}{(5000)(20\ \mu\text{F})} = -j \frac{1}{100\text{m}} = -j10\ \Omega$$

Turn off src 2:

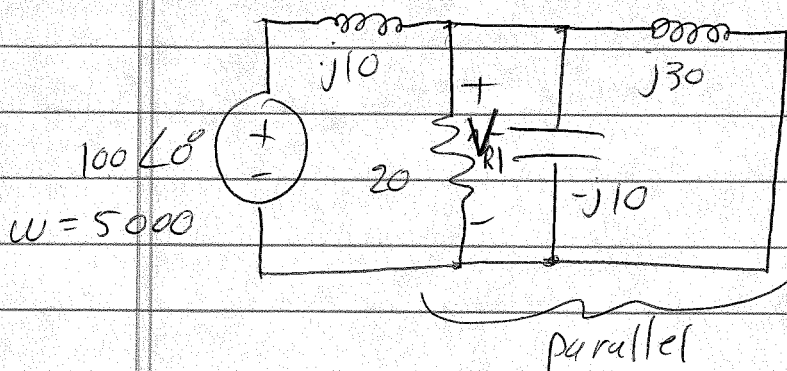

Common denom? $j60$

$$\tilde{Z}_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{-j10} + \frac{1}{j30}} = \frac{1}{\frac{1}{20} - \frac{j}{10} + \frac{j}{30}}$$

$$= \frac{1}{\frac{j3 - 6 + 2}{j60}} = \frac{j60}{-4 + j3} \cdot \frac{-4 - j3}{-4 - j3}$$

$$= \frac{180 - j240}{4^2 + 3^2} = \frac{180 - j240}{16 + 9} = \frac{180 - j240}{25} = 7.2 - j9.6$$

$$\tilde{Z}_{eq} = 12\angle -53.13^\circ$$

By Voltage Division: $\tilde{V}_{R1} = \frac{\tilde{Z}_{eq}}{j10 + \tilde{Z}_{eq}} 100\angle 0^\circ$


$$= \frac{7.2 - j9.6}{7.2 - j9.6 + j10} 100\angle 0^\circ$$

$$= \frac{12\angle -53.13^\circ}{7.211\angle 3.18^\circ} 100\angle 0^\circ = 166\angle -56.31^\circ$$

(279)

$$\tilde{V}_{R1} = 92.08 - j138 \text{ V}$$

Turn on $S_2 + S_1$ off

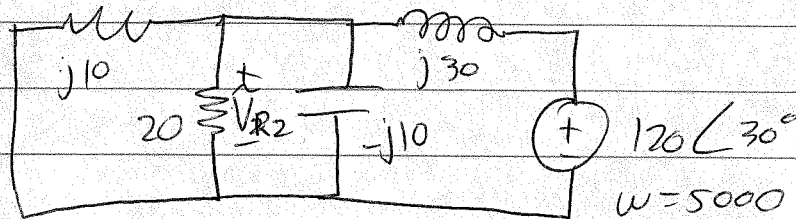

parallel

$$\tilde{Z}_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{j10} + \frac{1}{-j10}} = \frac{1}{\frac{1}{20} - j\frac{1}{10} + j\frac{1}{10}} = \underline{\underline{20\Omega - j0}}$$

$$\text{Voltage Division: } \tilde{V}_{R2} = \frac{20\Omega}{20\Omega + j30\Omega} \cdot \frac{20\angle 0^\circ}{36.06\angle 56.31^\circ} \cdot 120\angle 30^\circ$$

$$= (0.555\angle -56.31^\circ)(120\angle 30^\circ)$$

$$\tilde{V}_{R2} = 66.56\angle -26.31^\circ = 59.66 - j29.50$$


$$\tilde{V}_R = \tilde{V}_{R1} + \tilde{V}_{R2} = 92.08 - j138 + (59.66 - j29.50) \text{ V}$$

$$= 151.74 - j167.5 = 226\angle -47.8^\circ$$

Alternate:

Write Nodal Analysis Eqs in Phasor domain w/was

Variable:

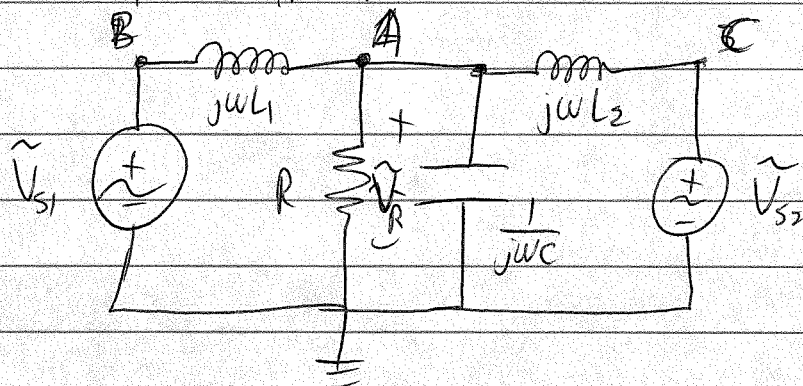

$$\frac{\tilde{V}_A - \tilde{V}_{s1}}{j\omega L_1} + \frac{\tilde{V}_A}{R} + \frac{\tilde{V}_A}{1/j\omega C} + \frac{\tilde{V}_A - \tilde{V}_{s2}}{j\omega L_2} = 0$$

$$\left(\frac{1}{j\omega L_1} + \frac{1}{R} + j\omega C + \frac{1}{j\omega L_2} \right) \tilde{V}_A = \frac{1}{j\omega L_1} \tilde{V}_{s1} + \frac{1}{j\omega L_2} \tilde{V}_{s2}$$

Common denom
 $j\omega L_1 L_2 R$

$$\left(\frac{RL_2 + j\omega L_1 L_2 + j\omega C(j\omega L_1 L_2 R) + L_1 R}{j\omega L_1 L_2 R} \right) \tilde{V}_A = \frac{1}{j\omega} \left(\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right)$$

~~$$R(L_1 + L_2) + j\omega L_1 L_2 C$$~~

$$\frac{R(L_1 + L_2) - \omega^2 L_1 L_2 RC + j\omega L_1 L_2}{j\omega L_1 L_2 R} \tilde{V}_A = \frac{1}{j\omega} \left(\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right)$$

~~$$\frac{1}{L_1 L_2 R} \left(R(L_1 + L_2) - \omega^2 L_1 L_2 RC + j\omega L_1 L_2 \right) \tilde{V}_A = \frac{1}{j\omega} \left(\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right)$$~~

$$\frac{1}{L_1 L_2 R} \left[R(L_1 + L_2) - \omega^2 L_1 L_2 RC + j\omega L_1 L_2 \right] \tilde{V}_A = \left(\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right)$$

$$\begin{aligned}\tilde{V}_A &= \frac{L_1 L_2 R}{[R(L_1 + L_2) - \omega^2 L_1 L_2 RC + j\omega L_1 L_2]} \left[\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right] \\ &= \frac{L_1 L_2 R}{\sqrt{[R(L_1 + L_2) - \omega^2 L_1 L_2 RC]^2 + (\omega L_1 L_2)^2}} \angle -\tan^{-1} \left(\frac{\omega L_1 L_2}{R(L_1 + L_2) - \omega^2 L_1 L_2 RC} \right) \left[\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right] \\ &= \tilde{K} \left[\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right]\end{aligned}$$

Check values:

$$\begin{aligned}\tilde{K} &= \frac{(2\text{mH})(6\text{mH})(20\Omega)}{\sqrt{[20(2\text{mH} + 6\text{mH}) - (5000)^2(2\text{mH})(6\text{mH})(20)(20\mu\text{F})]^2 + [(5000)(2\text{mH})(6\text{mH})]^2}} \\ &= \frac{240 \times 10^{-6}}{\sqrt{[160 \times 10^{-3} - 120 \times 10^{-3}]^2 + (60 \times 10^{-3})^2}} = \frac{240 \times 10^{-6}}{\sqrt{(40 \times 10^{-3})^2 + (60 \times 10^{-3})^2}} \\ &= \frac{240 \times 10^{-6}}{72.11 \times 10^{-3}} = 3.328 \times 10^{-3}\end{aligned}$$

$$\begin{aligned}\tilde{V}_A &= 3.328 \times 10^{-3} \angle -\tan^{-1} \left(\frac{60 \times 10^{-3}}{40 \times 10^{-3}} \right) \left[\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right] \\ &= 3.328 \times 10^{-3} \angle -56.31^\circ \left[\frac{1}{2\text{mH}} 100 \angle 0^\circ + \frac{1}{6\text{mH}} 120 \angle 30^\circ \right] \\ &\quad \left[50,000 \angle 0^\circ + 20,000 \angle 30^\circ \right] \\ &\quad \left[50,000 + j0 + 17,320 + j10,000 \right] \\ &\quad \left[67,320 + j10,000 \right] \\ &\quad \left[68,059 \angle 8.45^\circ \right]\end{aligned}$$

$$\tilde{V}_A = 226 \angle -47.9^\circ \checkmark$$

Look back at

$$\tilde{V}_A = \frac{L_1 L_2 R}{[R(L_1 + L_2) - \omega^2 L_1 L_2 RC + j\omega L_1 L_2]} \left[\frac{1}{L_1} \tilde{V}_{s1} + \frac{1}{L_2} \tilde{V}_{s2} \right]$$

If $V_{s1} + V_{s2}$ had been at different frequencies,

we could have evaluated this at each frequency

(With V_s at the other frequency set to zero), converted

each to the time domain, then added them up.