

# Introduction to Audio and Music Engineering

## Lecture 17

### Topics:


- Guitar pickups
- Guitar tone and volume controls
- Wah pedal – variable bandpass filter
- Amplifier project
- Tone control
- Gain control – distortion
- Speaker cabinet
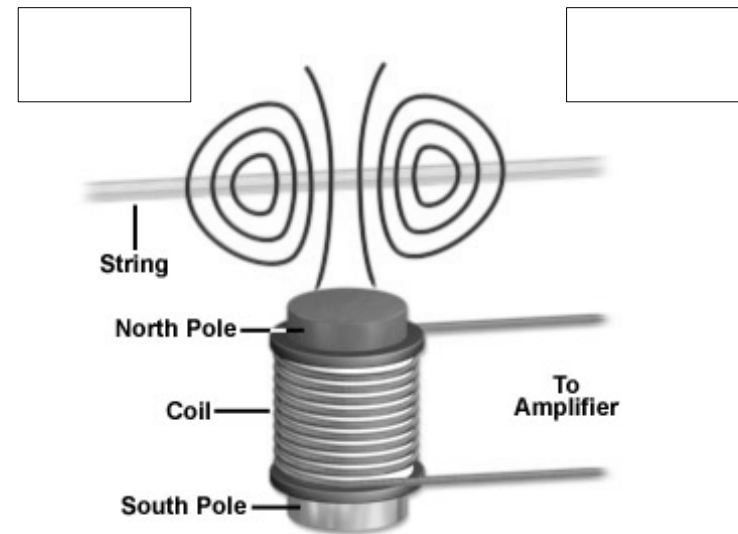
# Guitar Pickups



5,000 → 6,000 turns of 44 AWG wire



44 AWG  $\approx$  0.05 mm (2x dia of human hair)



<http://www.magnet.fsu.edu/education/tutorials/java/guitarpickup/>


$$V = -N \frac{d\Phi_B}{dt}$$

# Electrical model of a guitar pickup

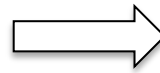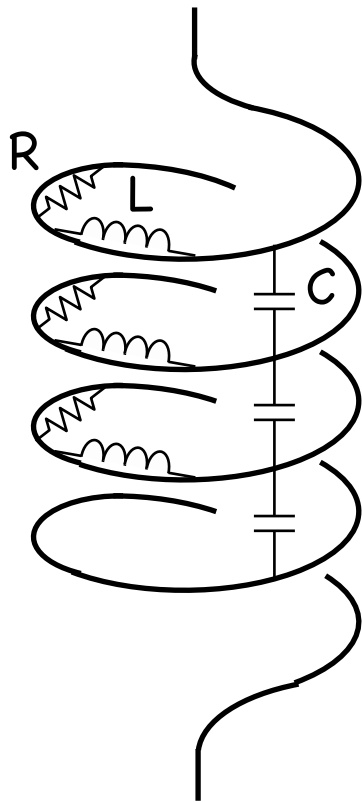


6000 turns  
 $L \approx 2$  Henry  
 $C \approx 120$  pF  
 $R \approx 5,000 \Omega$  (DC resistance)\*

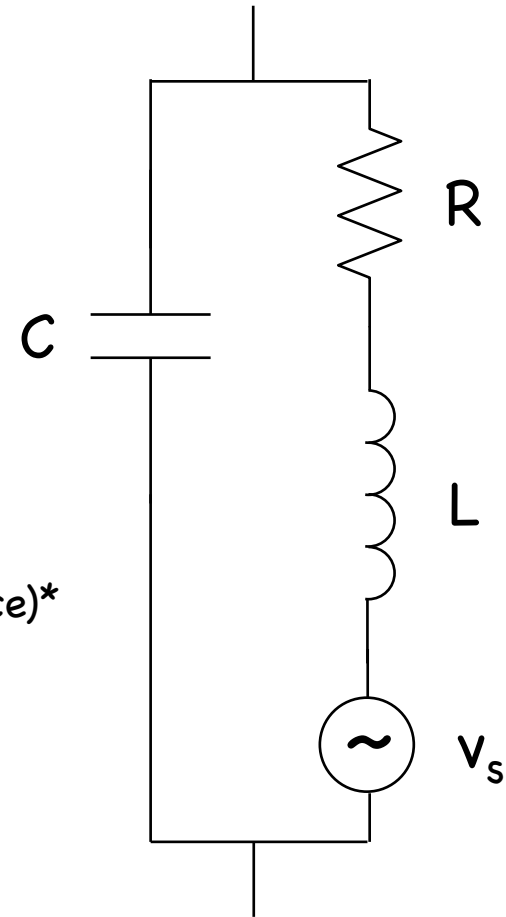$v_s$  = voltage signal  
induced in coil  
from string motion



\* Effective resistance at audio frequencies  $\approx 10\times$  DC resistance due to losses in the magnets
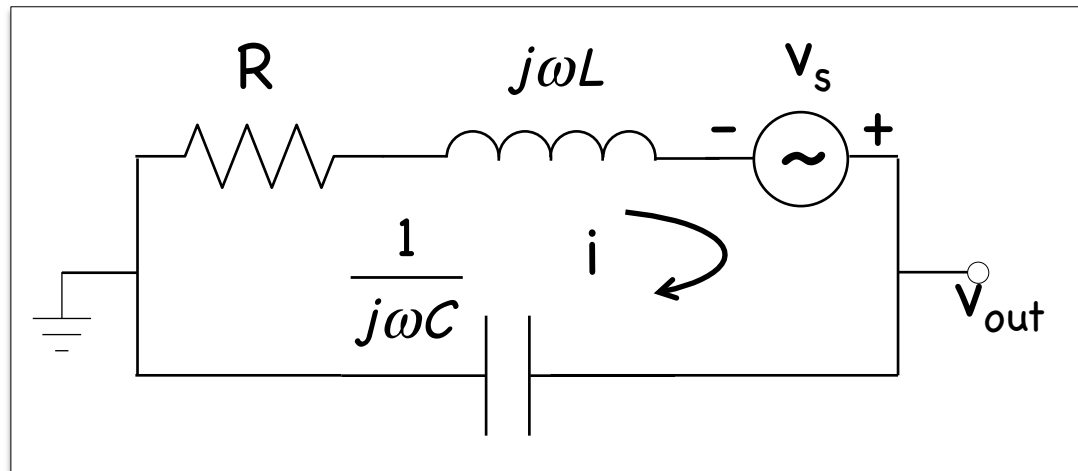
# Guitar pickup analysis: Find the output voltage, $v_{out}$



Resonant frequency

$$\omega_r^2 = \frac{1}{LC}$$

"Q" quality factor

$$Q = \frac{1}{\omega_r RC} = \frac{1}{2\pi} \frac{T}{RC}$$

T is the period of the resonance of the circuit

Apply KVL:

$$-iR - j\omega Li + v_s - \frac{1}{j\omega C} i = 0$$


$$i = \frac{v_s}{R + j\omega L + \frac{1}{j\omega C}}$$

$$v_{out} = i \frac{1}{j\omega C} = v_s \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$





$$v_{out} = v_s \frac{1}{1 - \omega^2/\omega_r^2 + j\omega/(\omega_r Q)}$$

$$|v_{out}| = v_s \frac{1}{\left[ (1 - \omega^2/\omega_r^2)^2 + \omega^2/(\omega_r^2 Q^2) \right]^{1/2}}$$

# Frequency response of pickups

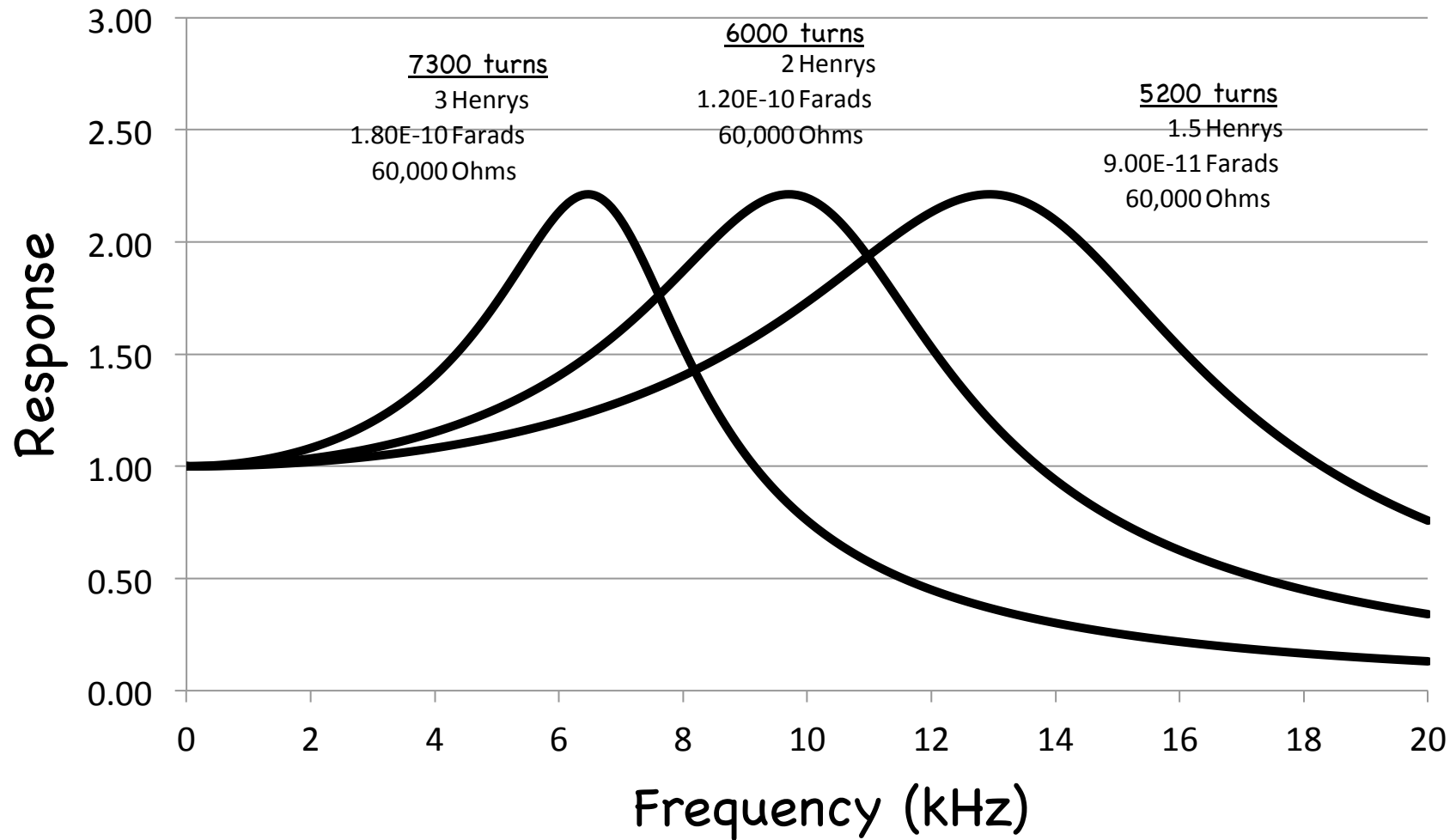


# Guitar tone & volume control circuit

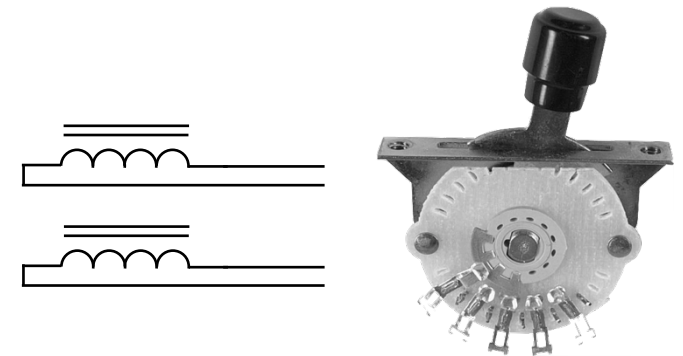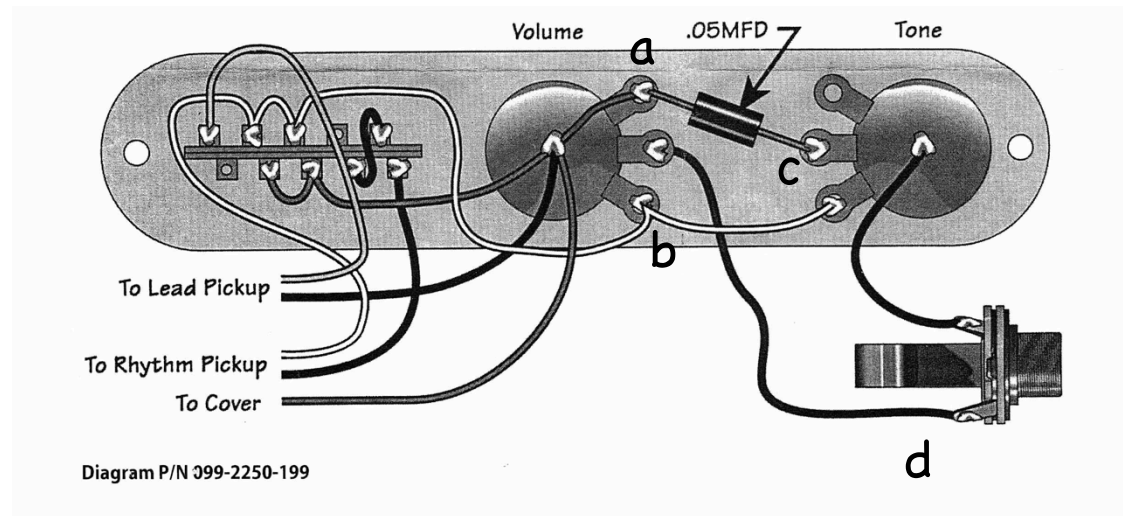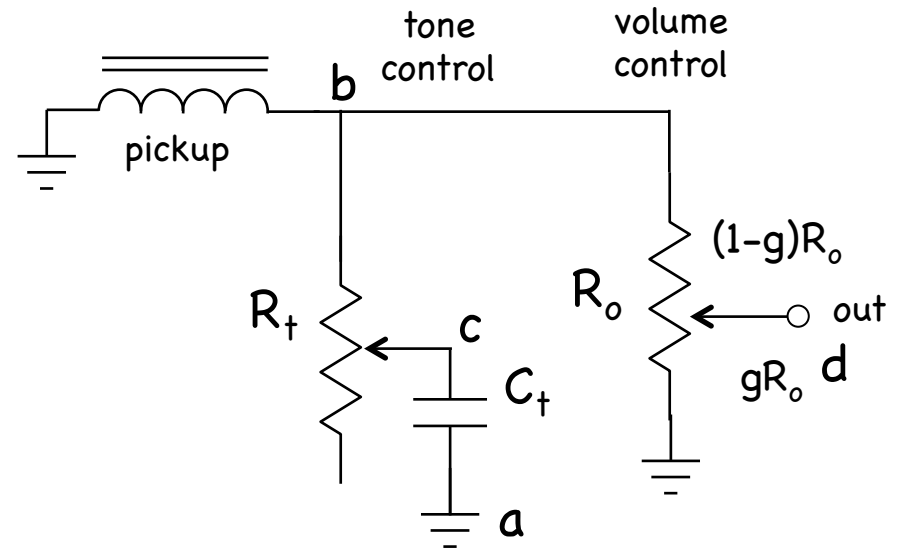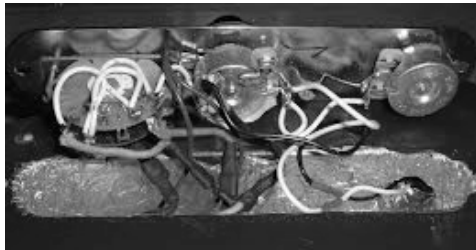


- 4-way Selector switch
- 1) Bridge (lead) pickup
  - 2) Neck (rhythm) pickup
  - 3) Parallel combination
  - 4) Series combination

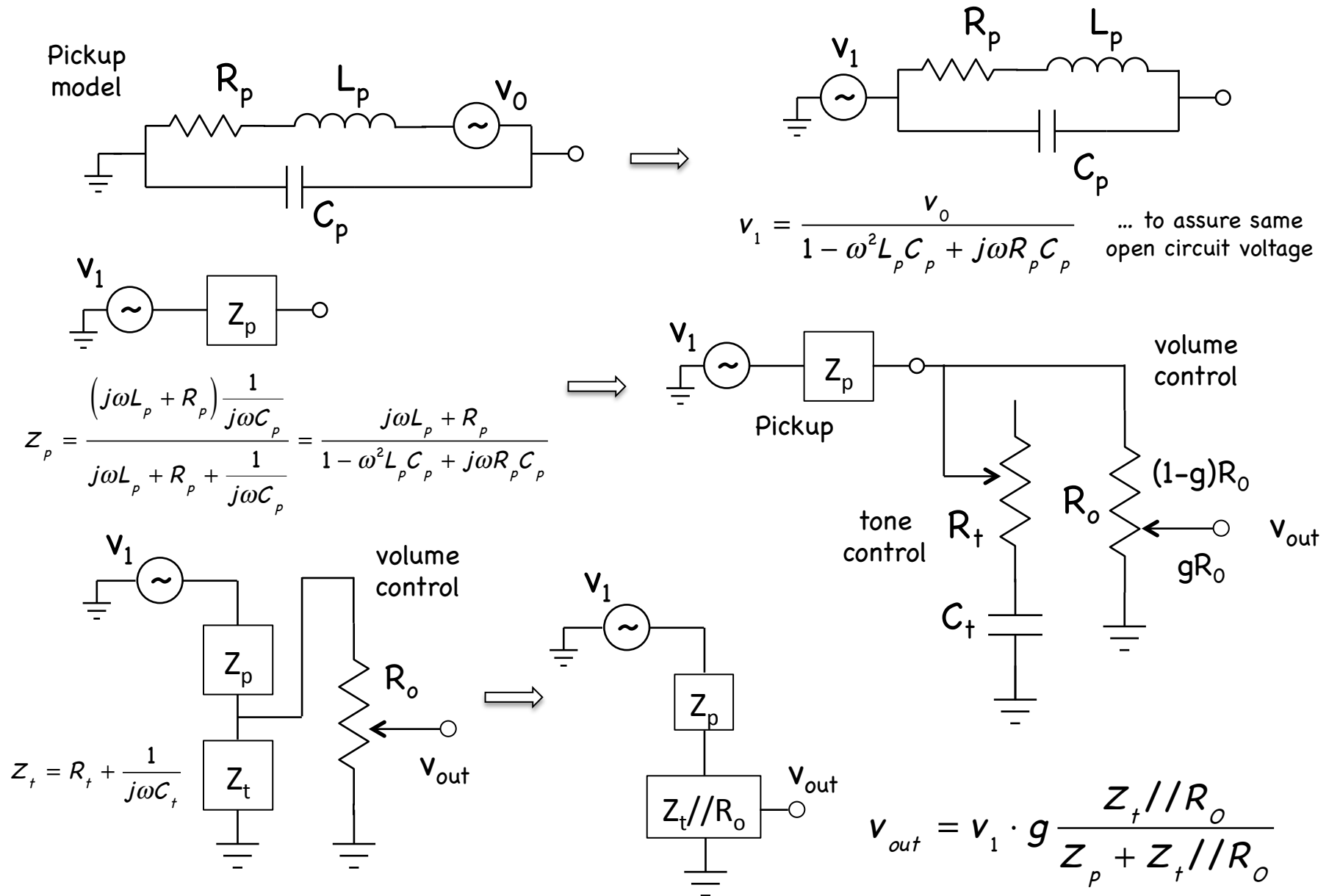
## Analysis of pickup and control circuit ...



# Tone control frequency response ...

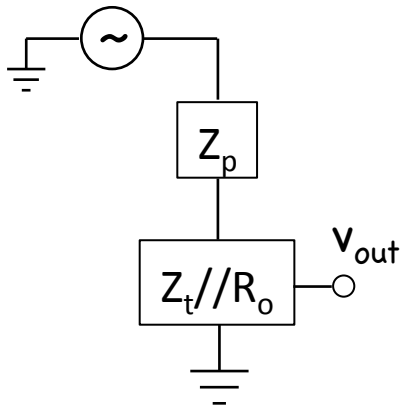
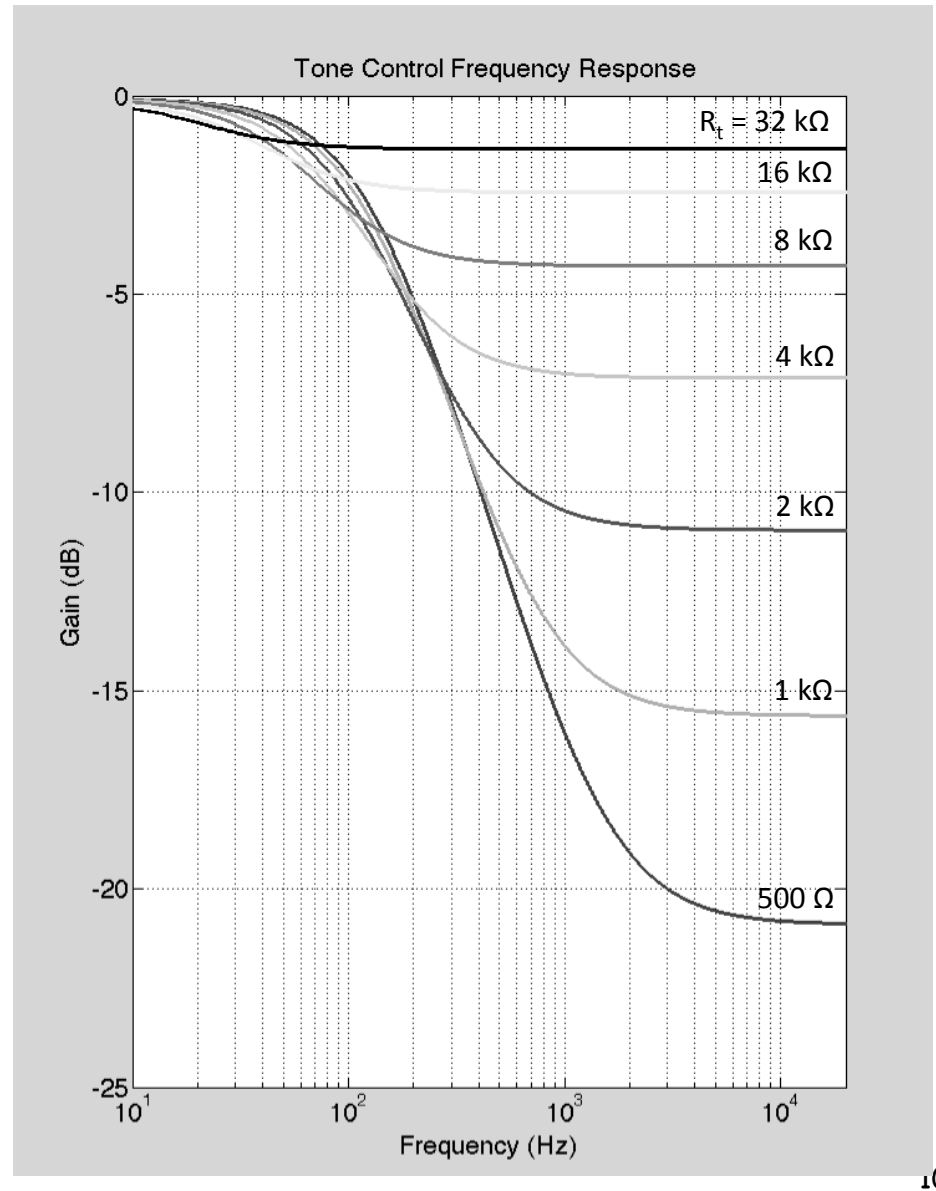
$$v_{out} = v_1 \cdot g \frac{Z_t // R_o}{Z_p + Z_t // R_o}$$








# Wah Pedal




<https://www.youtube.com/watch?v=kMqGuF8VoRo>

<http://www.youtube.com/watch?v=HyfKQhTRwkU>

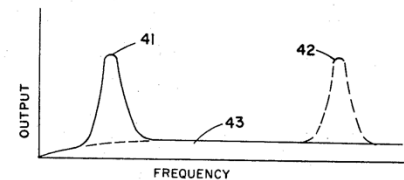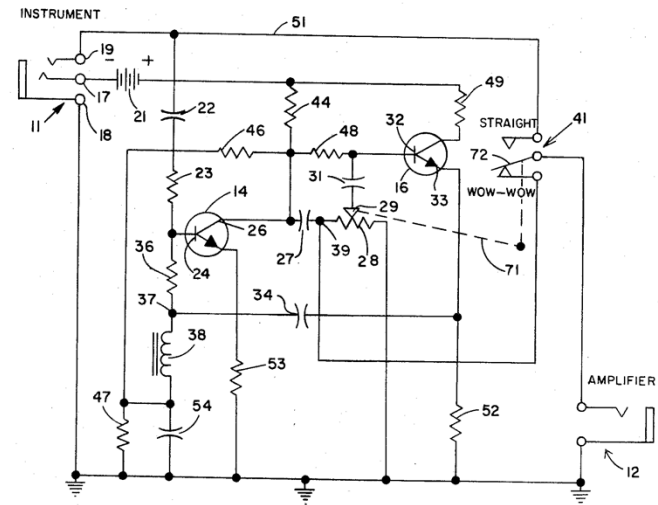
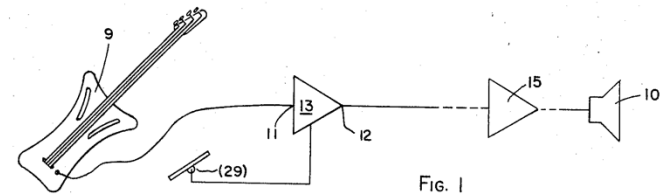
Sept. 22, 1970 **B. J. PLUNKETT ET AL** **3,530,224**  
 FOOT CONTROLLED CONTINUOUSLY VARIABLE PREFERENCE  
 Filed Feb. 24, 1967 **CIRCUIT FOR MUSICAL INSTRUMENTS** 2 Sheets-Sheet 1



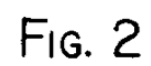INVENTORS  
 BRADLEY J. PLUNKETT  
 LESTER L. KUSHNER  
*Warren T. Jessup*  
 ATTY



# Wah Pedal – Variable Bandpass Filter

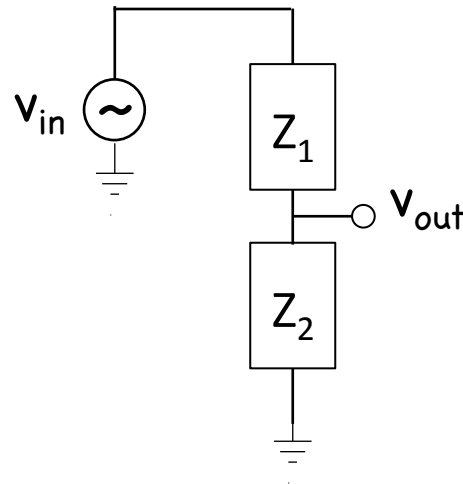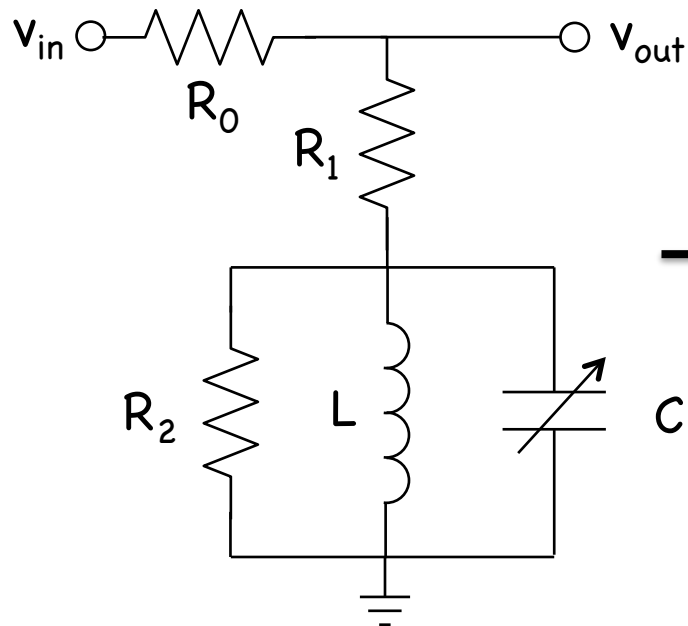

## Typical Values

$$R_0 = 68 \text{ k}\Omega$$


$$R_1 = 1.5 \text{ k}\Omega$$

$$R_2 = 33 \text{ k}\Omega$$


$$L = 0.5 \text{ H}$$

$$C = 0.01 \text{ }\mu\text{F} \rightarrow 1 \text{ }\mu\text{F}$$

“shelving” band-pass filter

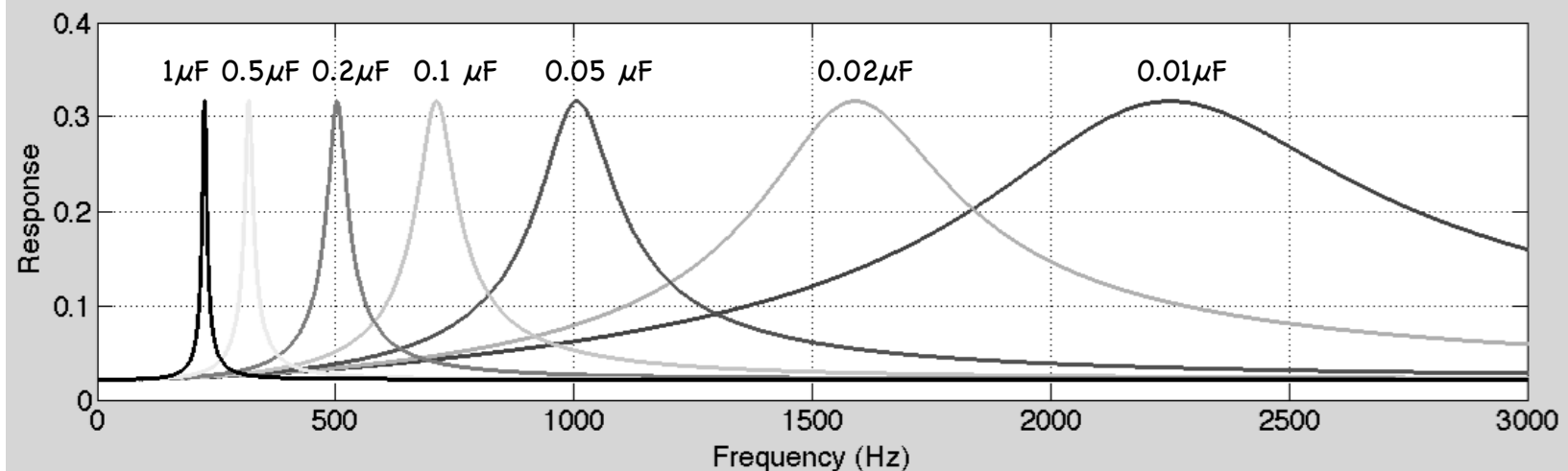

# Op Amp Wah Pedal

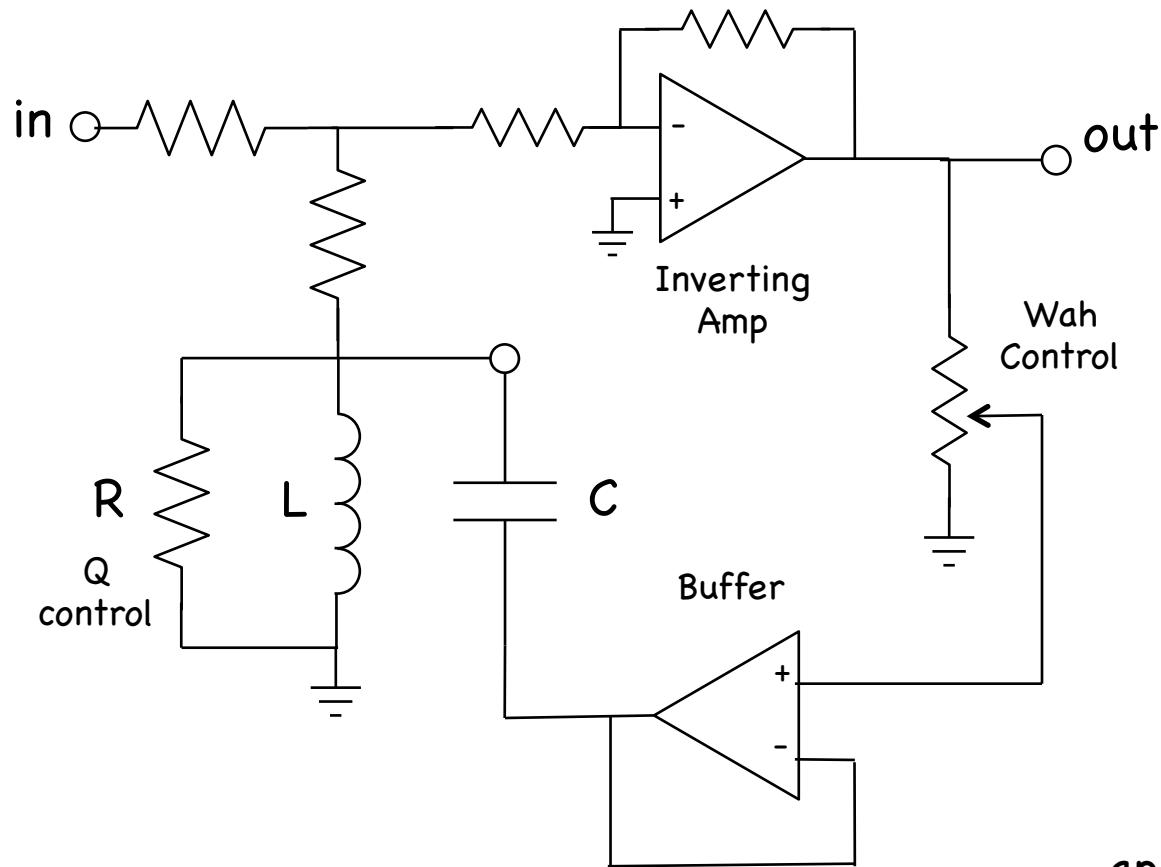

$$I = j\omega \boxed{C} \cdot \boxed{V}$$

Diagram illustrating the relationship between current  $I$ , voltage  $V$ , and capacitance  $C$ . The equation is  $I = j\omega \boxed{C} \cdot \boxed{V}$ . The diagram shows a capacitor  $C$  with current  $I$  flowing upwards and voltage  $V$  across it. A feedback arrow points from the bottom terminal to the equation.

Feedback changes the apparent size of  $C$ , thereby shifting the resonant frequency


# Full Schematic

Tone


Gain

Volume

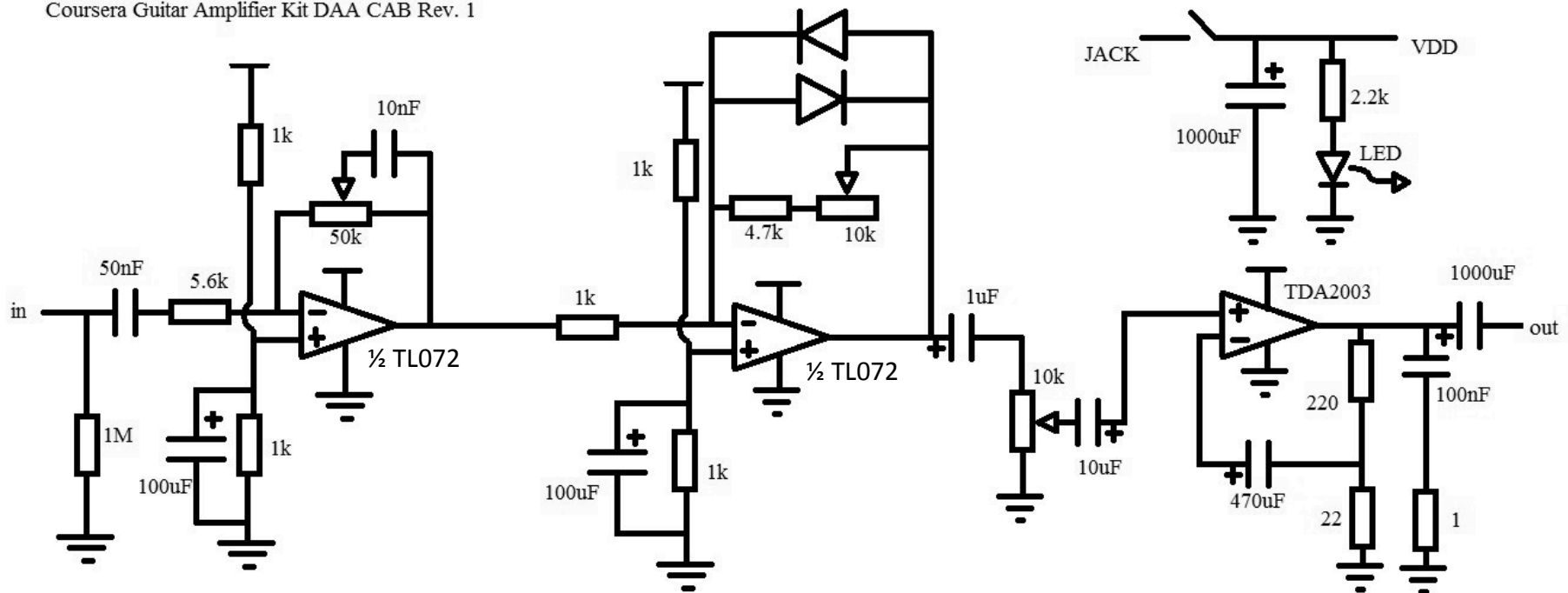
Copyright 2013  
University of Rochester  
Coursera Guitar Amplifier Kit DAA CAB Rev. 1




# Tone control circuit

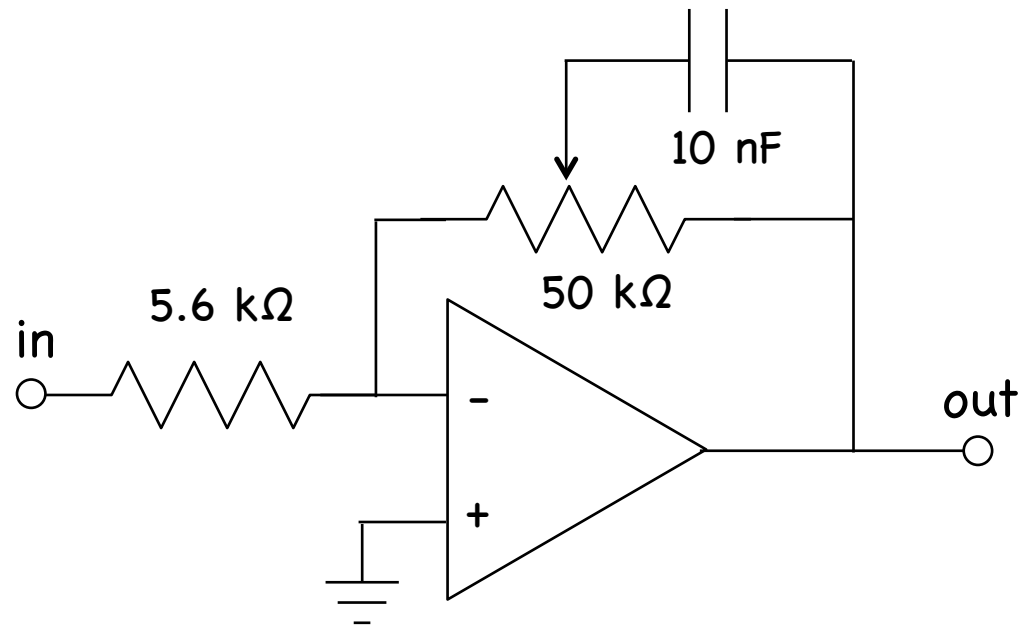

$$0 \leq g \leq 1$$

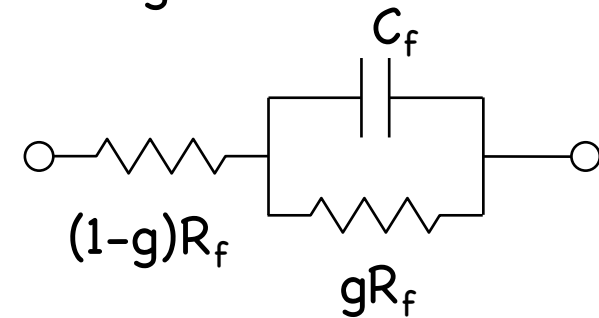

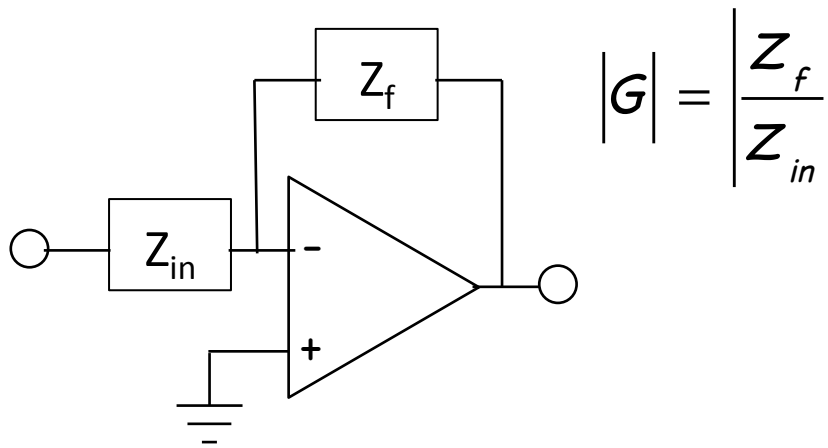
$$Z_f = (1 - g)R_f + \frac{\frac{1}{j\omega C_f} \cdot gR_f}{\frac{1}{j\omega C_f} + gR_f}$$




$$|G| = \frac{1}{R_{in}} \left| (1 - g)R_f + \frac{gR_f}{1 + jg\omega R_f C_f} \right|$$
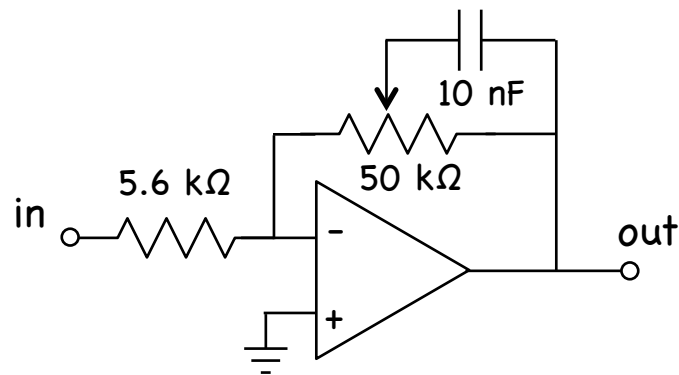
# Frequency response versus tone pot setting




$$|G| = \frac{1}{R_{in}} \left| (1 - g)R_f + \frac{gR_f}{1 + jg\omega R_f C_f} \right|$$

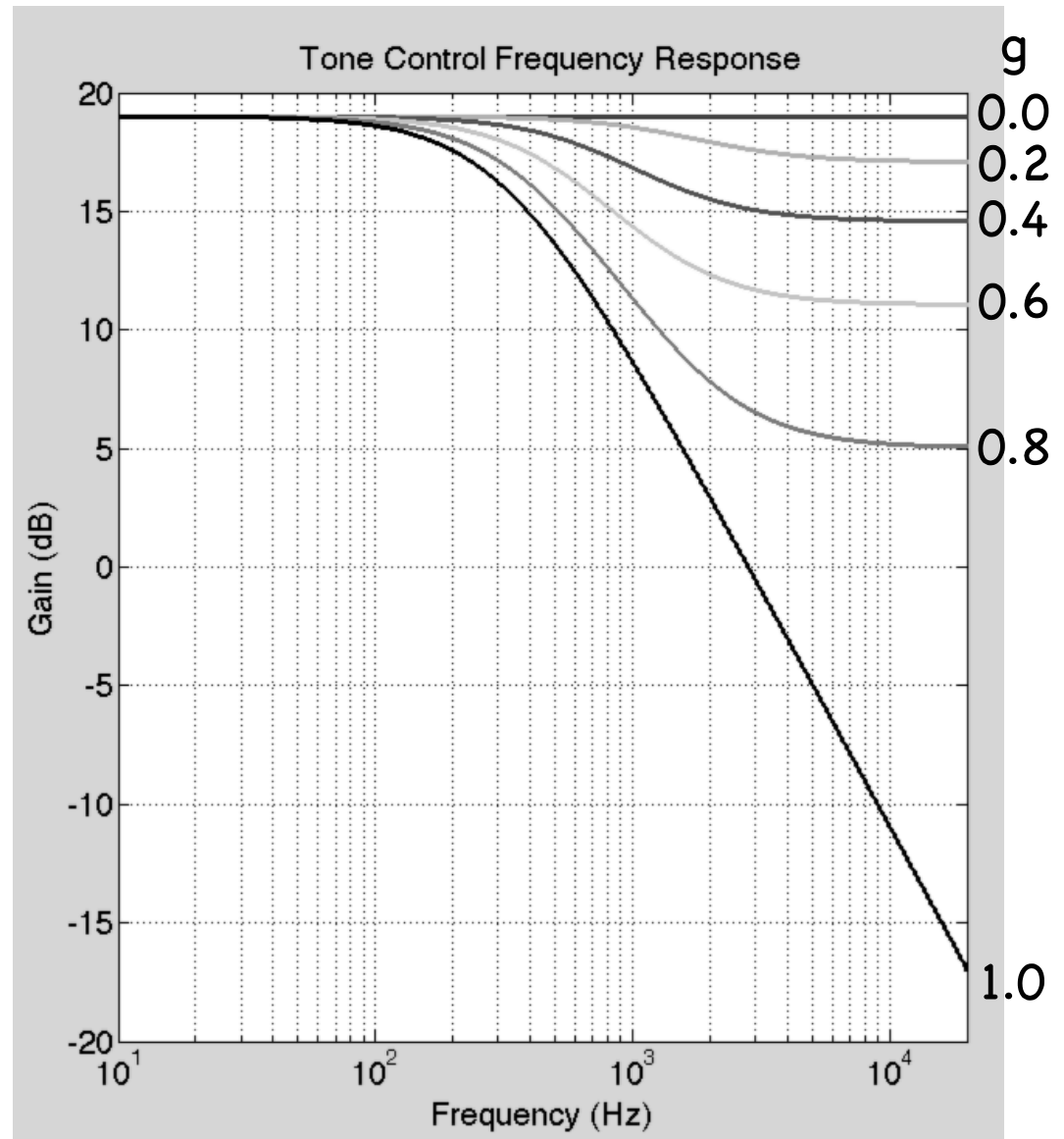



# Gain control - distortion

## Diode

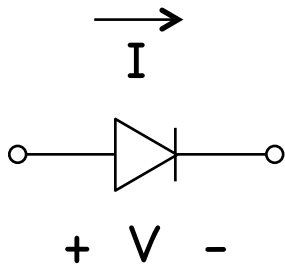

$$I = I_0 \left( e^{V/V_T} - 1 \right)$$

$$V_T \approx 0.026 \text{ V}$$

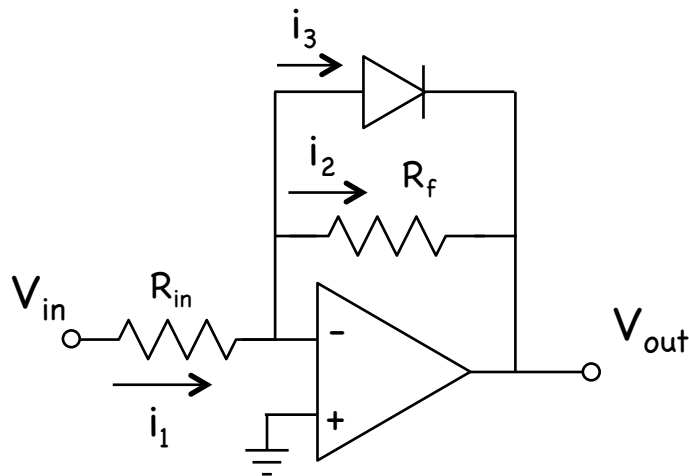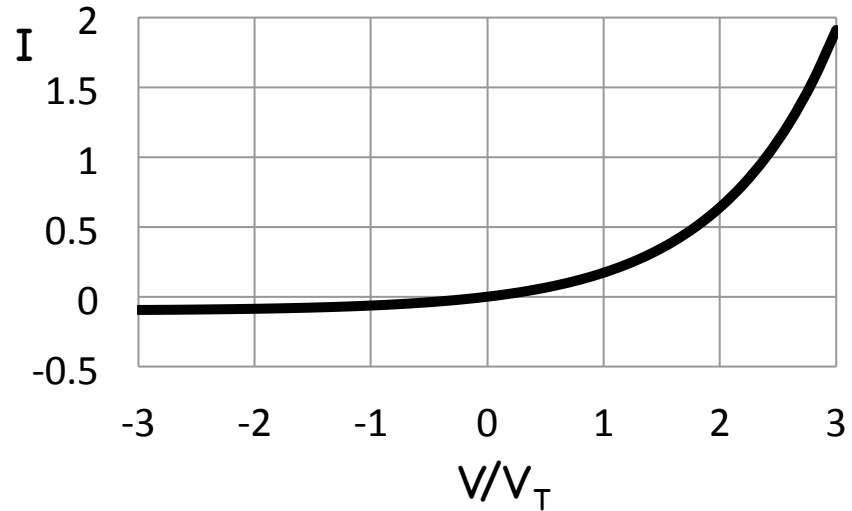

$$\text{KCL: } i_1 = i_2 + i_3$$

$$\frac{V_{in} - 0}{R_{in}} = \frac{0 - V_{out}}{R_f} + I_0 \left( e^{(0 - V_{out})/V_T} - 1 \right)$$

$$V_{in} = R_{in} \left[ I_0 \left( e^{\frac{-V_{out}}{V_T}} - 1 \right) - \frac{V_{out}}{R_f} \right]$$

Can't solve analytically for  $V_{out}$  but we can use a graphical technique




# Graphical solution for $V_{out}$ vs. $V_{in}$

$$V_{in} = R_{in} \left[ I_0 \left( e^{\frac{-V_{out}}{V_T}} - 1 \right) - \frac{V_{out}}{R_f} \right]$$


Find  $V_{in}$  as a function of  $V_{out}$  but then plot it as  $V_{out}$  vs.  $V_{in}$

But don't forget that this is an inverting amplifier configuration!

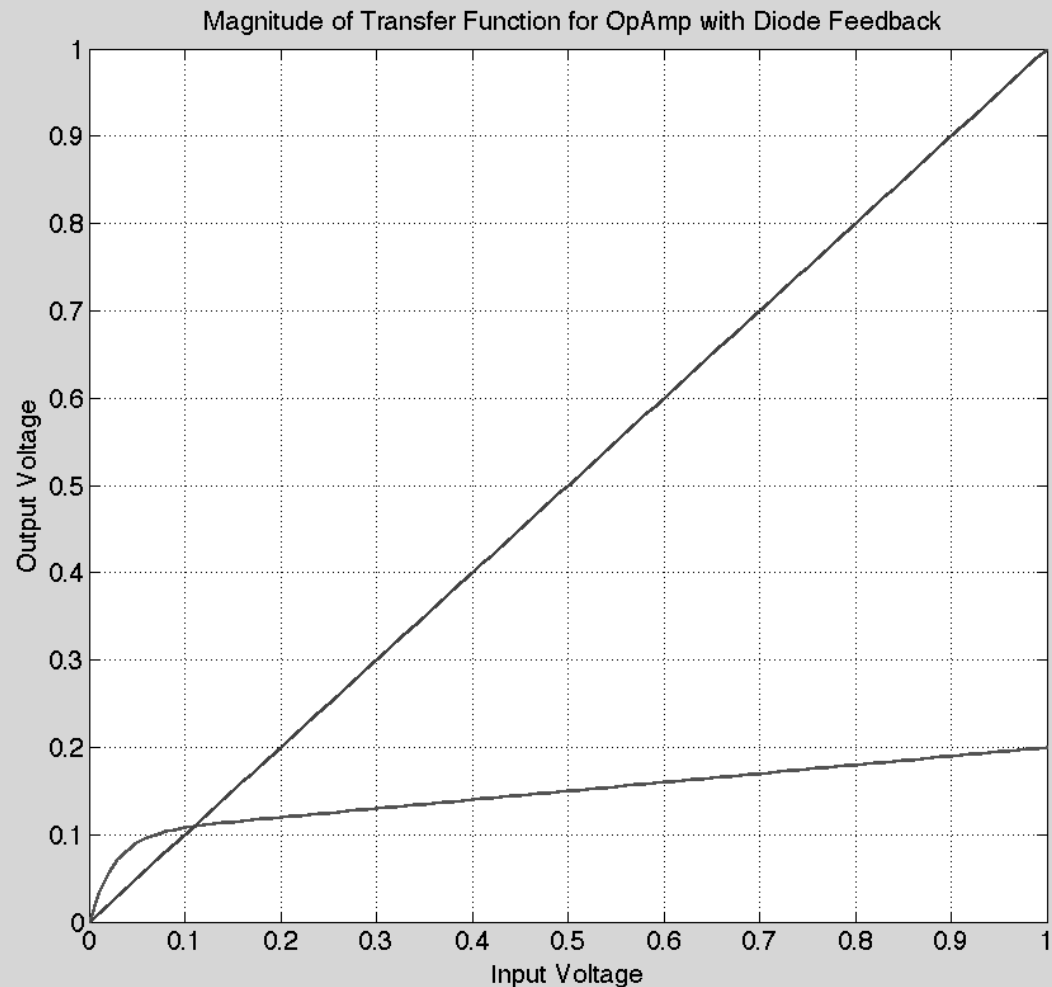That's why we plotted the magnitude of the transfer function.



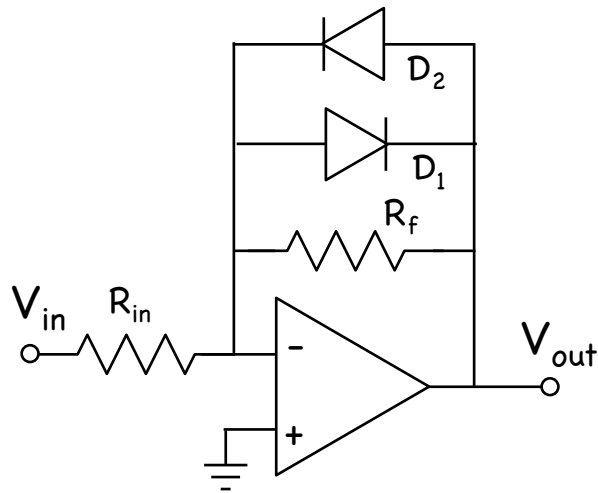
# Making the transfer function symmetrical



$D_1$  conducts for  $V_{in} > 0$ ,  
( $V_{out}$  will be negative)

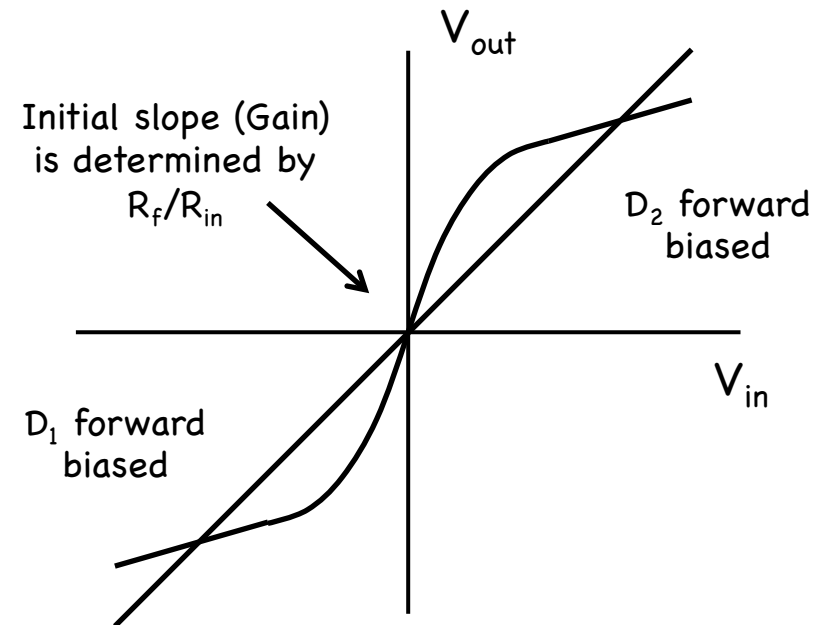$D_2$  conducts for  $V_{in} < 0$ ,  
( $V_{out}$  will be positive)



# Speaker Cabinet Design



- Guitar amplifiers normally have an open back so the cabinet has little acoustical effect
- Bass cabinet design – to obtain better bass response from the amplifier the cabinet should be properly sized.



# Thiele-Small parameters for project speaker

## SPEAKER SPECIFICATIONS

Model Number:	55-2970	
GENERAL SPECIFICATIONS		
Nominal Diameter:	6.5 inch	
Rated Lmpedance:	8 ohms	
Operating Bandwidth:	60-8k hz (-3dB)	
Power Handling Capacity:	50 Watts	
Sensitivity (1W/M):	88 dB(+3dB)	
Voice Coil Diameter:	1 inch	
THIELE-SMALL PARAMRTERS		
Resonance Frequency	Fs:	40 HZ
DC Resistance	Re:	7.2 ohm
Mechanical Q Factor	Qms:	3.66
Electrical Q Factor	Qes:	0.4796
Total Q Factor	Qts:	0.424
Equivalent Cas air load	Vas:	26.93 L
Surface Area of Cone	Sd:	0.0139 m2
Efficiency Bandwidth Product	EBP	83.4
Voice Coil Over Hang	X-max	3.5 mm
Voice Coil Inductance	Le	0.3875mH
PHYSICAL INFORMATION		
Basket:	Pressed steel chassis	
Magnet Type:	16.6 OZ	
Cone Material:	PP	
Surround:	Rubber	
Dust Cap:	PP	
Damper:	cloth	

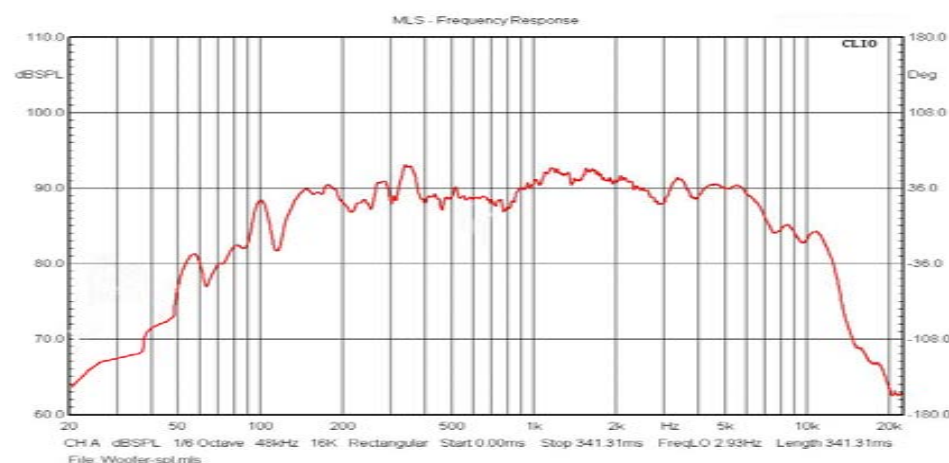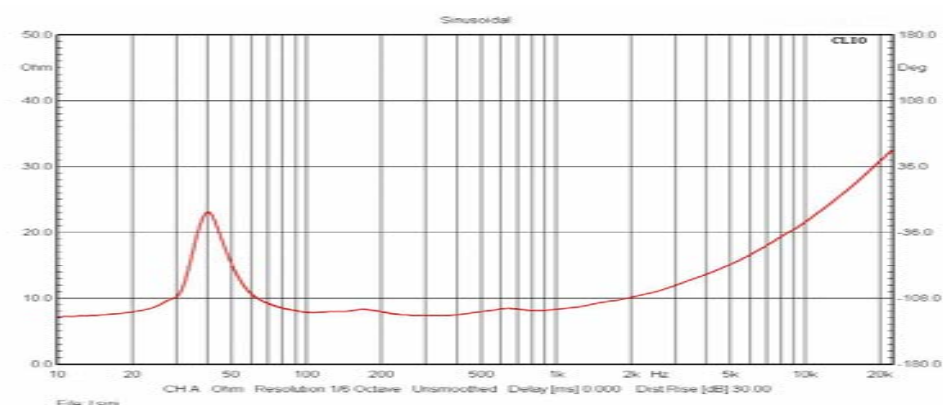

Date: 2010/6/28

## Following Rob's Week 5 Lecture 1 example ...

$$f_s = 40 \text{ Hz}$$

$$Q_{ts} = 0.424$$

$$V_{AS} = 26.93 \text{ liters}$$

$$\text{Choose } Q_{cb} = 1 \quad \text{so } Q_{cb}/Q_{ts} = 2.36$$

$$\frac{V_{as}}{V_{box}} = \left( \frac{Q_{cb}}{Q_{ts}} \right)^2 - 1 \quad \frac{V_{as}}{V_{box}} = (2.36)^2 - 1 = 4.57$$

$$V_{box} = \frac{V_{AS}}{4.57} = \frac{26.93}{4.57} = 5.89 \text{ liters} = 5890 \text{ cm}^3$$

Using the ratio, 0.618 : 1 : 1.618  
...we find approximately  
11 cm x 18 cm x 29 cm

