
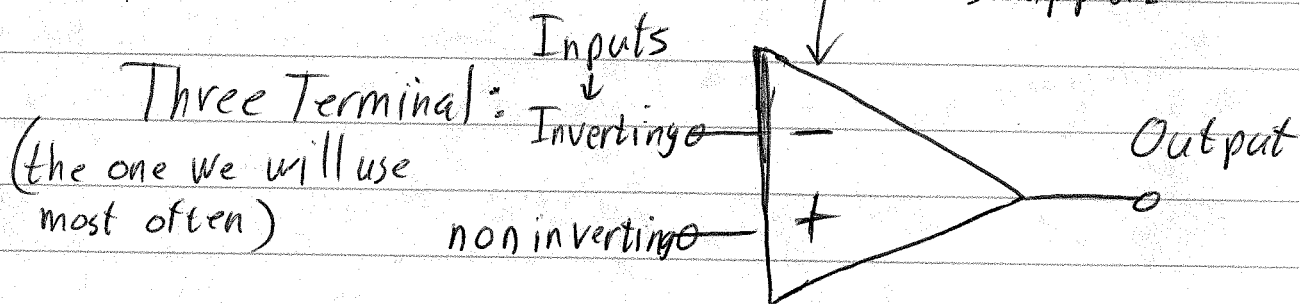


We're going to now introduce a device that you will not see in PHY 122, which contains a Dependent Source. It is the Operational Amplifier, or Op Amp. A pretty good history is in the book, page 177, so I will not repeat it here.

Symbols:

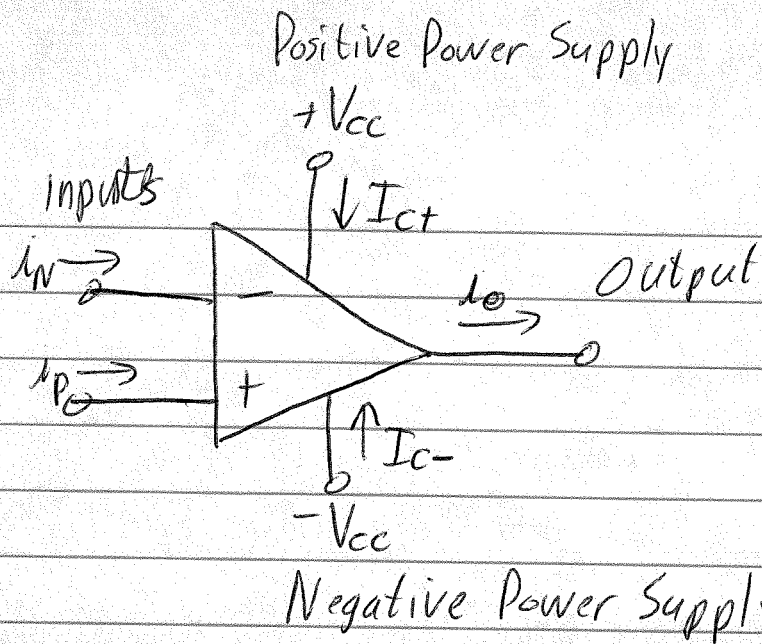

This contains a Dependent Source, so can insert energy into the circuit that contains it, so must be getting that energy from somewhere. It is implicit in the 3 Terminal model, and made explicit in the 5 Terminal model:




If we name currents in or out of all wires (draw and name) then we can apply KCL:

$$i_o = I_{C+} + I_{C-} - i_{p0} + i_{in} \quad (\text{correct KCL})$$

The 3 Terminal model does not include I_{C+} or I_{C-} ,
~~since~~ giving us $i_o = i_{p0} + i_{in}$ which implies
 that the output current comes from the inputs,
 which is incorrect. ~~We will never~~

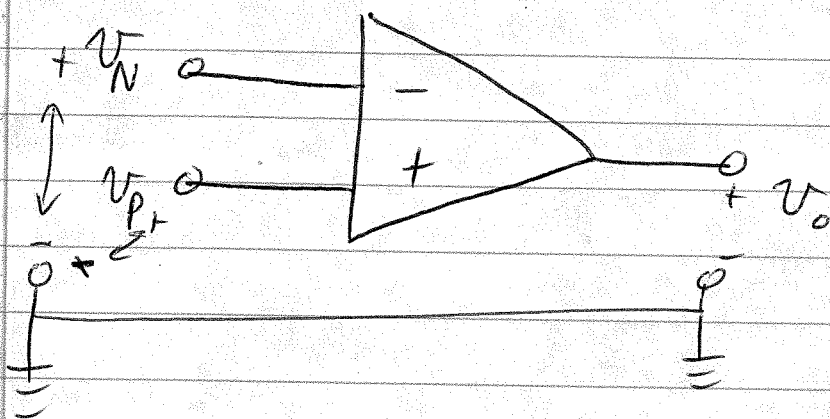The output voltage of an op amp is
 proportional to the difference between the
 two input voltages:




$$v_o = A(v_p - v_N) \quad \text{I will also often use } (v_p = v_+)$$

or and $(v_N = v_-)$

$$v_o = A(v_+ - v_-)$$

A (called the Open-Loop Voltage Gain) is very large, typically $> 10^5$.

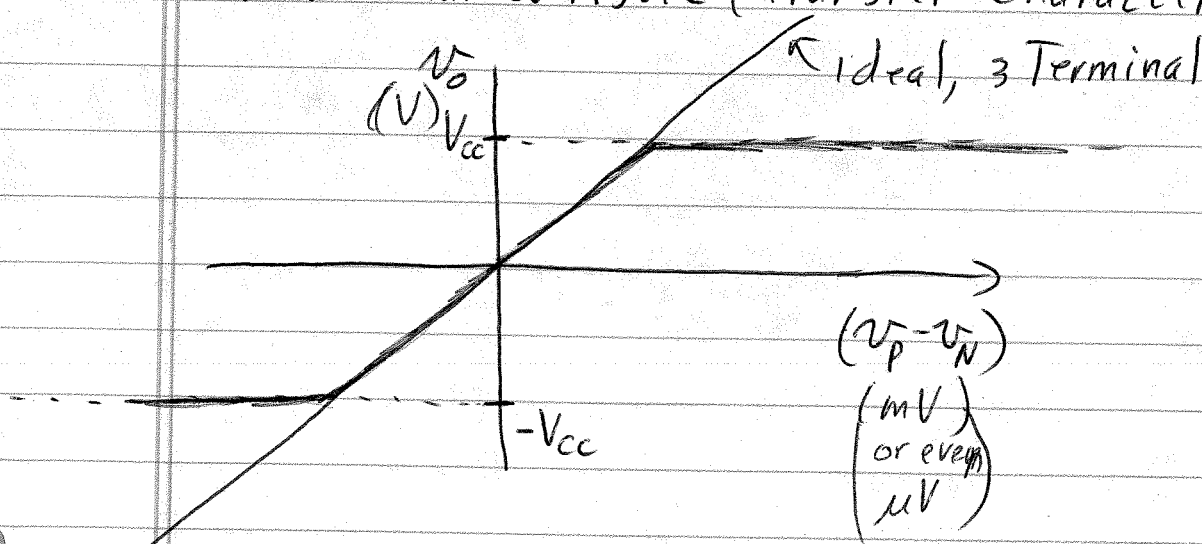V-V characteristic (Transfer Characteristics)




In reality, the output cannot exceed the Power Supply voltage (or maybe a little less)

so there are places where the outputs
flattens out. (draw)

3 modes: + and - Saturation Modes
and Linear Mode in between.

Usually we use Op-Amps for the Linear Mode,
but sometimes we actually want it to
be in saturation, more on that later.

Ideal Op Amp Model, in linear range:

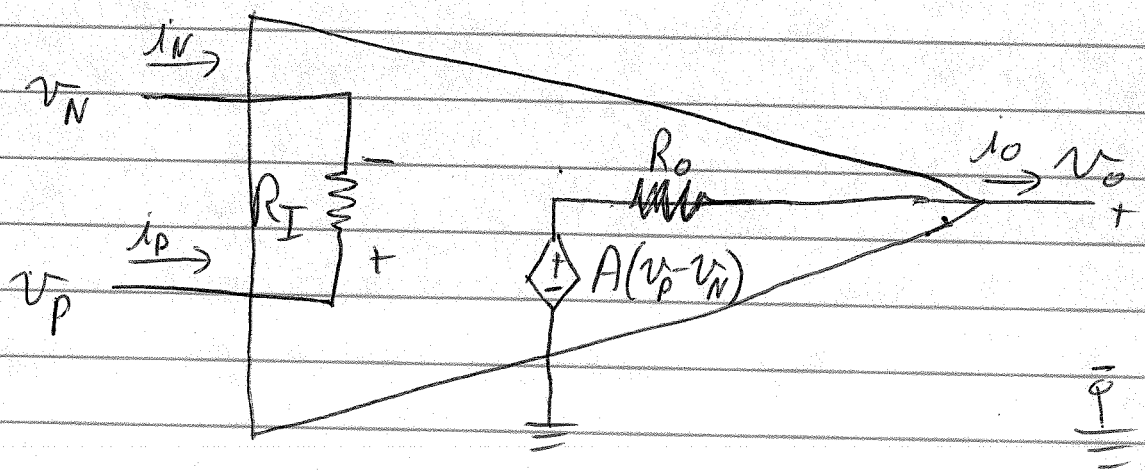

Parameters:

~~R_I~~

Range

R_I

$$10^6 \leq R_I \leq 10^{12} \Omega$$

R_o

$$1-10 \leq R_o \leq 100 \Omega$$

A

$$10^5 \leq A \leq 10^8$$

To operate in Linear Mode, the output is limited to $+V_{cc}$ and $-V_{cc}$, so

$$\cancel{+V_{cc}} \leq A(v_p - v_n) \leq \cancel{-V_{cc}}$$

$$-V_{cc} \leq A(v_p - v_n) \leq V_{cc}$$

$$\text{or } -\frac{V_{cc}}{A} \leq (v_p - v_n) \leq \frac{V_{cc}}{A}$$

Since A is very large we take the $\lim_{A \rightarrow \infty}$

$$-0 \leq (v_p - v_n) \leq 0$$

This means $v_p - v_n = 0$

$$\text{or } \underline{v_p = v_n}$$

(The Ideal Op Amp will work to make $v_p = v_n$)

Also, since R_I is very large, we take the $\lim_{R_I \rightarrow \infty}$, which makes the inputs ~~an~~ open ckts:

$$\underline{i_p = 0}, \quad \underline{i_n = 0}$$


Golden Rules for an Ideal Op Amp with resistive negative feedback (More on that later)

$$1) \quad i_p = i_n = 0$$

$$2) \quad v_p = v_n$$

Drawn differently
in text, this is the
more usual way.

Example

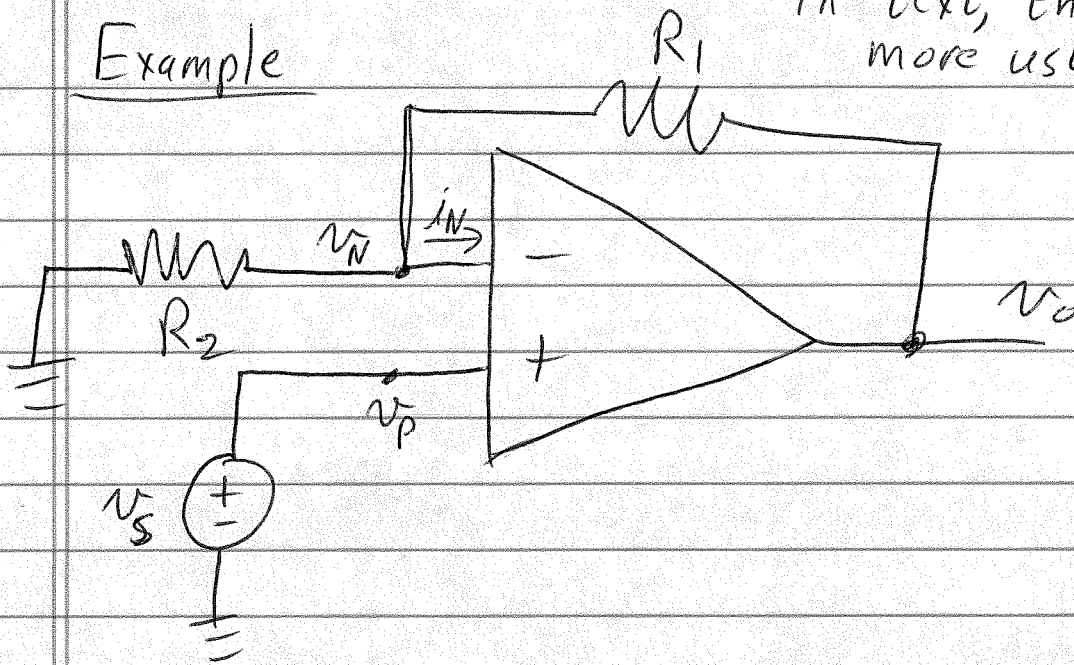

Analyzed differently in text, I'm going to
apply a pretty standard, general, approach.

- 1.) There is resistive ~~feed~~ negative feedback
(resistor from output to - input) so

Golden Rules apply.

- 2.) Apply KCL at inverting input.

$$\frac{v_N - 0}{R_2} + \frac{v_N - v_o}{R_1} + \cancel{i_N} = 0 \quad \text{but } i_N = 0 \text{ by G.R. 1}$$

$$\left(\frac{1}{R_2} + \frac{1}{R_1}\right)v_N - \frac{1}{R_1}v_o = 0$$

$$\frac{R_1 + R_2}{R_1 R_2} v_N - \frac{1}{R_1} v_o = 0$$

$$\frac{1}{R_1} v_o = \frac{R_1 + R_2}{R_1 R_2} \hat{v}_N$$

$$v_o = R_1 \frac{R_1 + R_2}{R_1 R_2} \hat{v}_N$$

$$v_o = \left(1 + \frac{R_1}{R_2}\right) \hat{v}_N$$

3.) Use $\hat{v}_N = \hat{v}_p$: Look at \hat{v}_p : $\hat{v}_p = \hat{v}_s$, so $\hat{v}_N = \hat{v}_s$, so

$$v_o = \left(1 + \frac{R_1}{R_2}\right) v_s$$

$$(\text{Output}) = G (\text{Input})$$

$$G = \left(1 + \frac{R_1}{R_2}\right)$$

feedback R or R_f

$$G = \left(1 + \frac{R_f}{R_i}\right)$$

input R or R_i

G is positive, so Non inverting

Can choose $\frac{R_f}{R_i}$ to be about


anything we want, usually

limit it to be < 1000

G is called the Closed Loop Gain, because

R_1 has "Closed the Loop" to provide feedback.

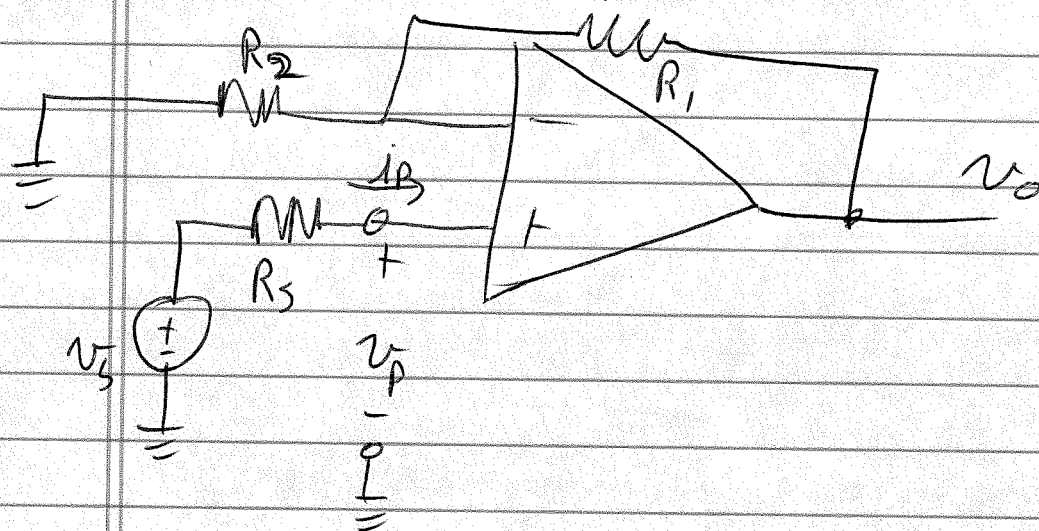What if we have a Practical Source providing the input instead of an Ideal Src?



$$\text{KVL: } R_s i_p + v_p - v_s = 0$$

but $i_p = 0$, so $R_s(0) = 0$, or

$$0 + v_p - v_s = 0$$


$$v_p = v_s \text{ as before}$$

~~GR1~~ Equivalent of $i_p = i_n = 0$ are the words,

GR2: No current flows in or out of the inputs of an Ideal Op Amp. (always true)

GR1 With resistive feed back, an Ideal Op Amp works to make $v_p = v_n$.

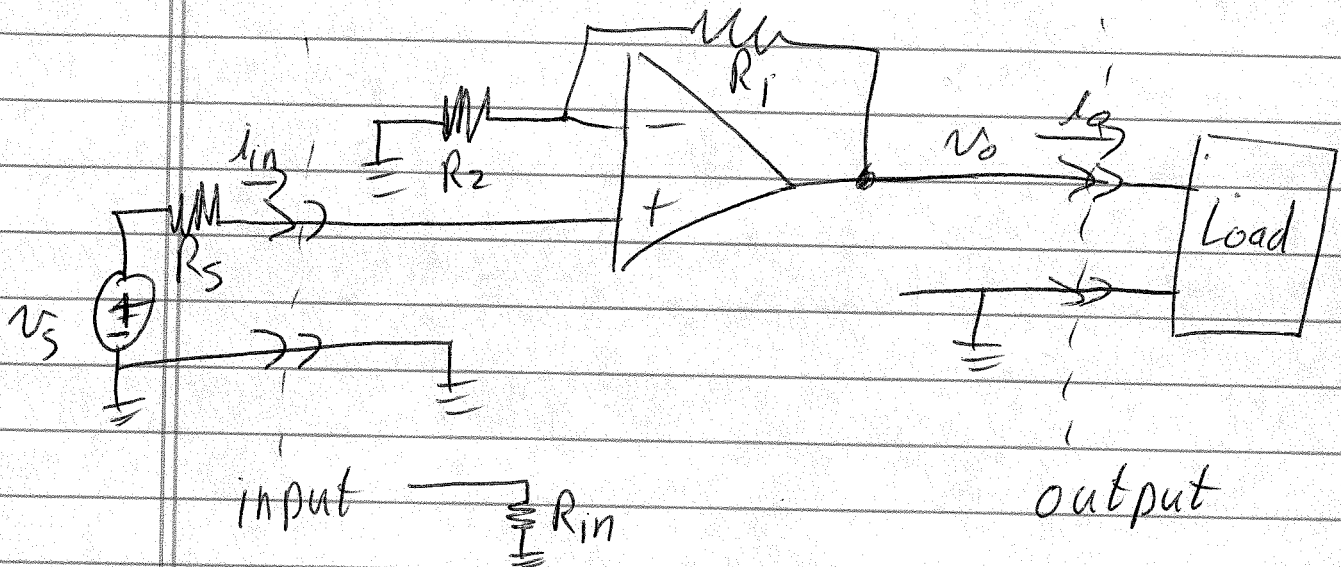What are the Thevenin Input + Output Equivalents?




For all inputs, $i_{in} = 0$,
so

$$R_{in} = \frac{v_s}{i_{in}}$$

$$R_{in} = \frac{v_s}{0} = \infty$$

We know v_{oc} already,
$$v_{oc} = \left(1 + \frac{R_f}{R_2}\right) v_s$$

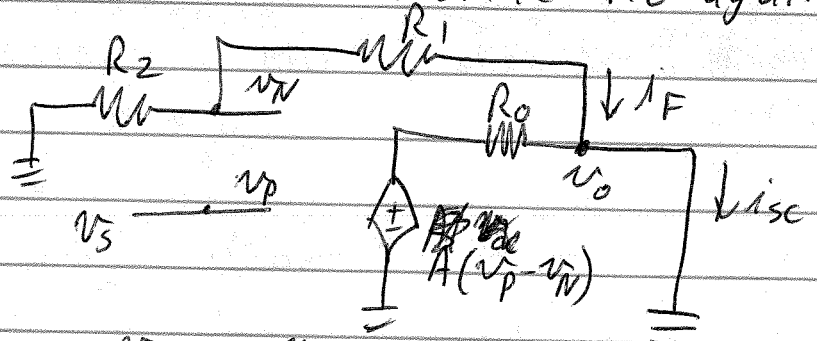To put a short ckt in we have to include R_o again:



Inv Input: $\frac{v_N}{R_2} + \frac{v_N - v_o}{R_f} = 0$ but $v_o = 0$, so $v_N = 0$

$$A(v_P - v_N) = A v_s$$

$$I_{sc} = \frac{A v_s}{R_o} = \frac{A}{R_o} v_s$$

$$\text{So } R_S = \frac{v_{oc}}{i_{sc}} = \frac{\left(1 + \frac{R_1}{R_2}\right) v_S}{\frac{A}{R_0} v_S} = \frac{R_0}{A} \left(1 + \frac{R_1}{R_2}\right) \leftarrow \text{call this } G$$

for the case $\left(1 + \frac{R_1}{R_2}\right) \ll A$ (say $0.1A$)

~~We can ignore~~

$$R_S = R_0 \frac{G}{A} \text{ in most cases } G \ll A, \\ \text{so } R_S \ll R_0 \\ \text{or } \underline{\underline{R_S \approx 0 \Omega}}$$

So the Thev. Eq. output is:

