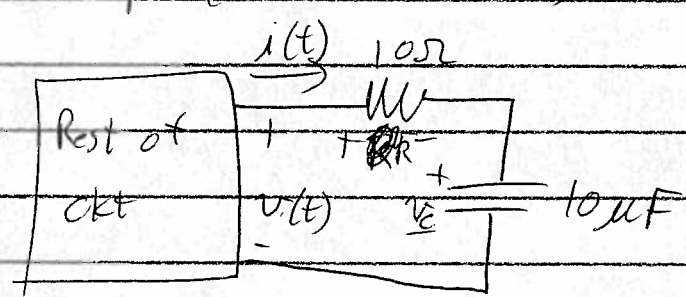


Everything we have done so far can be thought of as the limit as $\omega \rightarrow 0$ in what we are now going to do!

All of our analysis tools, Nodal Analysis, Mesh Analysis, Voltage + Current Division, Op Amps, ... can be done using Sinusoidal Steady State ~~and~~ and Phasor Notation.

Example: (8-5 of text)




Given that $i(t) = 4 \cos(5000t)$ A, find $v(t)$

Solution: This is the Time Domain ckt. Convert

to Phasor (or Frequency) Domain:
 $\hat{I} = 4 \angle 0^\circ$ A, $\omega = 5000$,
 $\hat{Z}_R = 10 \Omega + j0$


$$\tilde{Z}_C = \frac{1}{j\omega C} = \frac{1}{j(5000)(10\mu)} = -j \frac{1}{50 \text{ m}} = -j(0.02)(k)\Omega$$
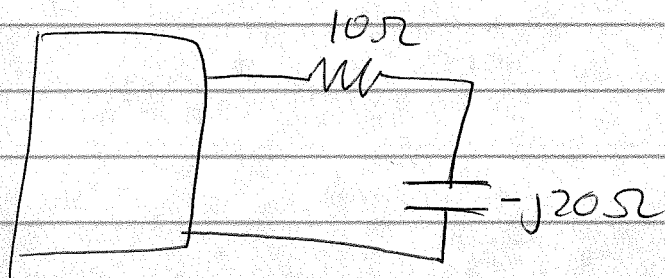
$$\underline{\underline{= -j20 \Omega}}$$



$$\tilde{Z}_{Eq} = (10\Omega) + (-j20\Omega) = (10 - j20)\Omega$$

$$= 22.36 \angle -63.43^\circ \Omega$$

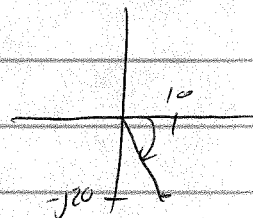

$$\tilde{V} = \tilde{Z}_{eq} \tilde{I} = (22.36 \angle -63.43^\circ \Omega) (4 \angle 0^\circ \text{A})$$

$$\tilde{V} = 89.44 \angle -63.43^\circ \text{V}$$

~~$$v(t) = 89.44 \cos(5000t - 63.43^\circ) \text{V}$$~~

$$v(t) = 89.44 \cos(5000t - 63.43^\circ) \text{V}$$

We can get \tilde{V}_C or \tilde{V}_R by voltage division

$$\begin{aligned}
 \tilde{V}_C &= \frac{\tilde{Z}_C}{\tilde{Z}_R + \tilde{Z}_C} \tilde{V} \\
 &= \frac{-j20}{10 - j20} (89.44 \angle -63.43^\circ \text{ V}) \\
 &= \frac{20 \angle -90^\circ}{22.36 \angle -63.43^\circ} (89.44 \angle -63.43^\circ \text{ V}) \\
 &= (0.894 \angle -26.57^\circ) (89.44 \angle -63.43^\circ \text{ V}) \\
 &= \underline{\underline{80 \angle -90^\circ \text{ V}}} = \underline{\underline{-j 80 \text{ V}}}
 \end{aligned}$$


$$\begin{aligned}
 \tilde{V}_R &= \frac{10 \angle 0^\circ}{22.36 \angle -63.43^\circ} (89.44 \angle -63.43^\circ \text{ V}) \\
 &= \frac{(10)(89.44)}{22.36} \angle (0^\circ - 63.43^\circ - (-63.43^\circ)) \\
 \tilde{V}_R &= \underline{\underline{40 \angle 0^\circ \text{ V}}} = \underline{\underline{40 + j0 \text{ V}}}
 \end{aligned}$$

This gets us into Section 8-3, so you should read and do all exercises and examples through that.

As I have already stated, or at least alluded to, we can combine impedances just like resistors:



Ex:

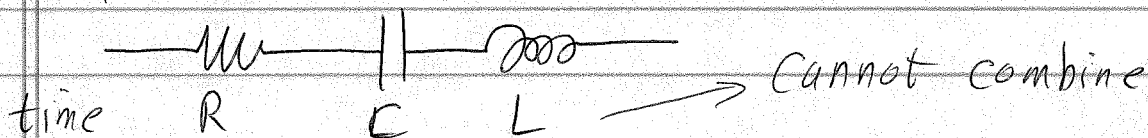

freq: $R \quad \frac{1}{j\omega C} \quad j\omega L \rightarrow \tilde{Z}_{eq} = R + \frac{1}{j\omega C} + j\omega L$

$$= R + j\left(-\frac{1}{\omega C} + \omega L\right)$$

$$= R + j\left(\frac{\omega^2 LC}{\omega C} - \frac{1}{\omega C}\right)$$

$$\tilde{Z}_{eq} = R + j\left(\frac{\omega^2 LC - 1}{\omega C}\right)$$

If we were told, $R = \overset{1k\Omega}{\cancel{100\Omega}}$, $C = 1\mu F$, $\cancel{100\Omega} L = 1mH$, $\omega = 1000$,

then $\tilde{Z}_{eq} = \overset{K}{\cancel{100}}\Omega + j\left(\frac{(10^3)^2(1\mu F \cdot 1mH) - 1}{(10^3)(10^{-6})}\right)\Omega$

$$= \overset{K}{\cancel{100}}\Omega + j\left(\frac{10^6(10^{-9}) - 1}{10^{-3}}\right)\Omega$$


$$= \overset{K}{\cancel{100}}\Omega + j\left(\frac{10^{-3} - 1}{10^{-3}}\right)\Omega$$

We'll, $10^{-3} - 1 = -0.999$, so

$$\tilde{Z}_{eq} = 1k\Omega + j\left(\frac{-0.999}{10^{-3}}\right)\Omega$$

$$= 1k\Omega - j999\Omega$$

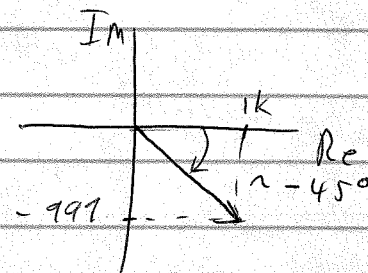\uparrow $\text{Im}(\tilde{Z}_{eq}) < 0$, so
Capacitive



We could also have gone back to

$$\tilde{Z}_{eq} = \tilde{Z}_R + \tilde{Z}_C + \tilde{Z}_L$$

$$= 1k\Omega + \left(-j \frac{1}{10^3 \times 10^{-9}}\right) + j(10^3 \times 10^{-3})\Omega$$

\nwarrow Impedance of capacitor

$$= 1k\Omega + (-j1k\Omega) + j(1)\Omega$$

\nwarrow impedance of inductor

$$= 1k\Omega - j(1000 - 1)\Omega = 1k\Omega - j999\Omega$$

$$|\tilde{Z}_C| > |\tilde{Z}_L| \Rightarrow \text{capacitive}$$


Try decreasing $|\tilde{Z}_C|$ by increasing C , + Increase \tilde{Z}_L by $\uparrow L$
Use $C = 1000 \mu F$ and $L = 100 mH$,

$$\tilde{Z}_{eq} = 1k\Omega + j\left(-\frac{1}{(10^3)(10^{-3})} + (10^3)(10^{-1})\right)\Omega$$

$$= 1k\Omega + j(-1 + 10^2)\Omega = 1k\Omega + j99\Omega$$

This is now inductive, since $\text{Im}(\tilde{Z}_{eq}) > 0$.
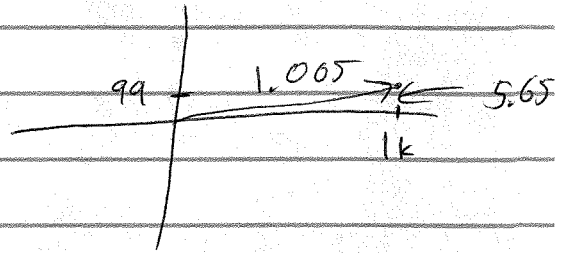
$$\tilde{Z}_{eq} = 1.005 \angle 5.65^\circ$$



Go back to the general expression:

$$\tilde{Z}_{eq} = R + j \left(\frac{\omega^2 LC - 1}{\omega C} \right) = R + j X_{eq}$$

The circuit is on resonance ^{at the frequency} where the reactance goes to zero, that is, when $\frac{\omega_o^2 LC - 1}{\omega_o C} = 0$

$$\text{or } \omega_o^2 LC - 1 = 0$$

$$\text{or } \omega_o^2 LC = 1$$

$$\omega_o^2 = \frac{1}{LC}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

Look familiar??

Series RLC:


$$\tilde{Z}_{eq} = R + j \left(\frac{\omega^2 LC - 1}{\omega C} \right)$$

$$= \sqrt{R^2 + \left(\frac{\omega^2 LC - 1}{\omega C} \right)^2} \angle \tan^{-1} \left(\frac{\omega^2 LC - 1}{\omega C R} \right)$$

$$= \sqrt{\frac{(\omega RC)^2 + (\omega^2 LC - 1)^2}{(\omega C)^2}} \angle \tan^{-1} \left(\frac{\omega^2 LC - 1}{\omega RC} \right)$$

Get used to certain combinations, like $\omega RC + \omega^2 LC$.
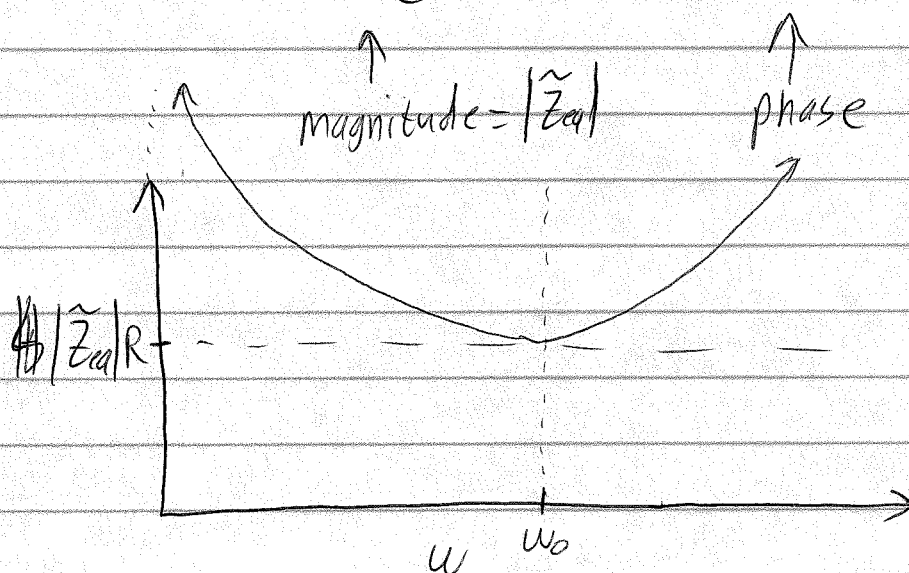
$$\tilde{Z}_{eq} = \frac{\sqrt{(\omega RC)^2 + (\omega^2 LC - 1)^2}}{\omega C} \angle \tan^{-1} \left(\frac{\omega^2 LC - 1}{\omega RC} \right)$$



$$\lim_{\omega \rightarrow 0} |\tilde{Z}_{eq}| = \frac{\sqrt{0 + (0-1)^2}}{0} = \infty$$

$$\lim_{\omega \rightarrow \infty} |\tilde{Z}_{eq}| = \frac{\sqrt{\infty^2 + (\infty^2)^2}}{\infty} = \frac{\infty^2}{\infty} = \infty$$

Can show that minimum occurs at $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\text{or } |\tilde{Z}_{eq}| = \frac{\sqrt{(\omega RC)^2}}{\omega C} = \frac{\omega RC}{\omega C} = R$$



What about phase?

$$\phi = \tan^{-1} \left(\frac{\omega^2 LC - 1}{\omega RC} \right)$$



$$\lim_{\omega \rightarrow 0} \phi = \tan^{-1} \left(\frac{0^2 - 1}{0} \right) = \tan^{-1}(\infty) = -90^\circ$$

$$\lim_{\omega \rightarrow \infty} \phi = \tan^{-1} \left(\frac{\infty^2 - 1}{\infty} \right) = \tan^{-1}(\infty) = 90^\circ$$
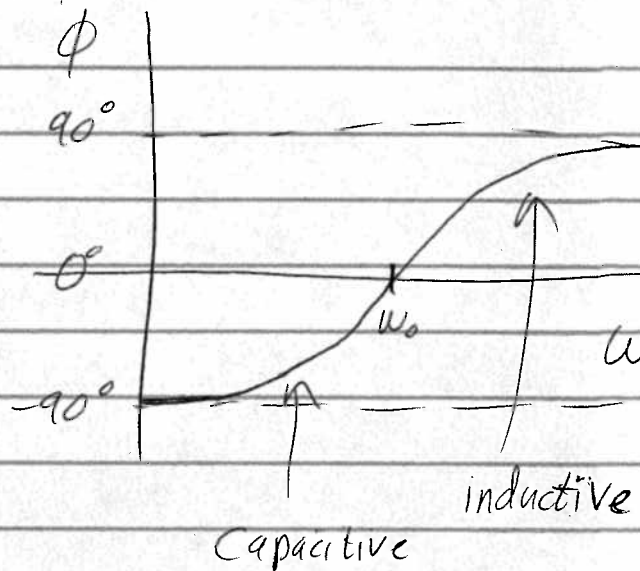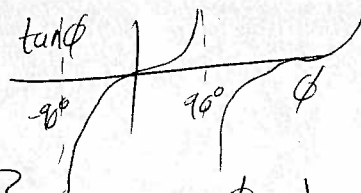
$$\omega = \omega_0 : \phi = \tan^{-1} \left(\frac{1 - 1}{\omega_0 RC} \right) = \tan^{-1}(0) = 0^\circ$$



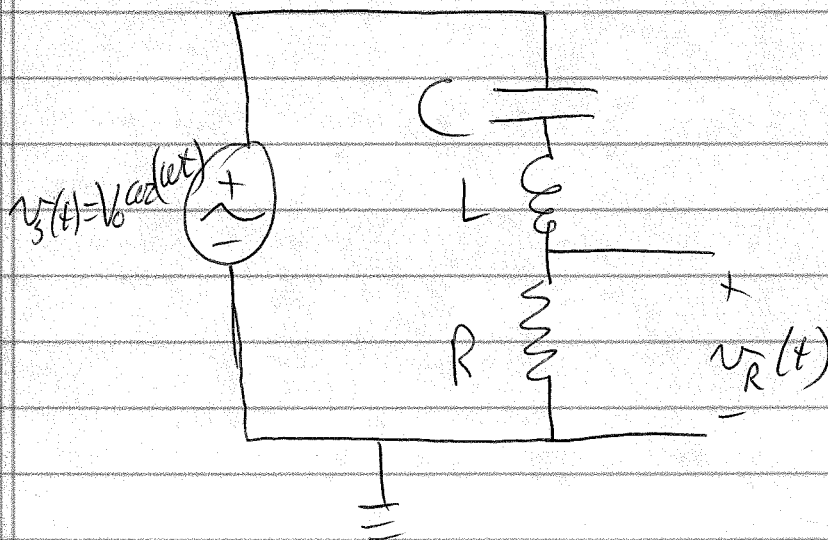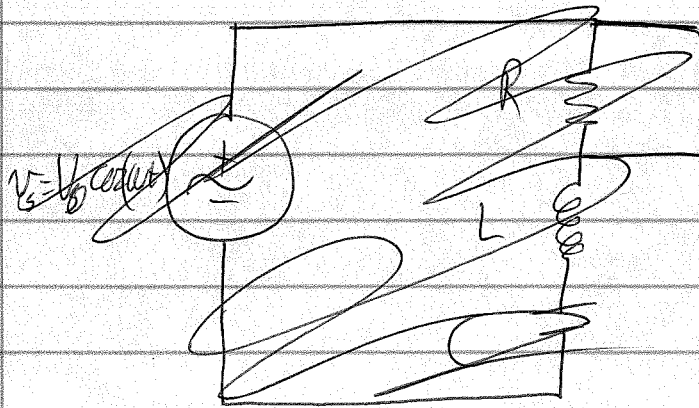
What if I asked you for the ~~current through~~
~~this~~ voltage across the resistor, $v_R(t)$, if a voltage
 source $v_s(t) = V_0 \cos(\omega t)$ was applied to it:



We could use \tilde{Z}_{eq} from before, find $\tilde{I} = \frac{\tilde{V}_s}{\tilde{Z}_{eq}}$,
 then multiply by $\tilde{Z}_R = R$ to get $\tilde{V}_R = V_R \angle \phi_R$, then

$$v_R(t) = V_R \cos(\omega t + \phi_R)$$

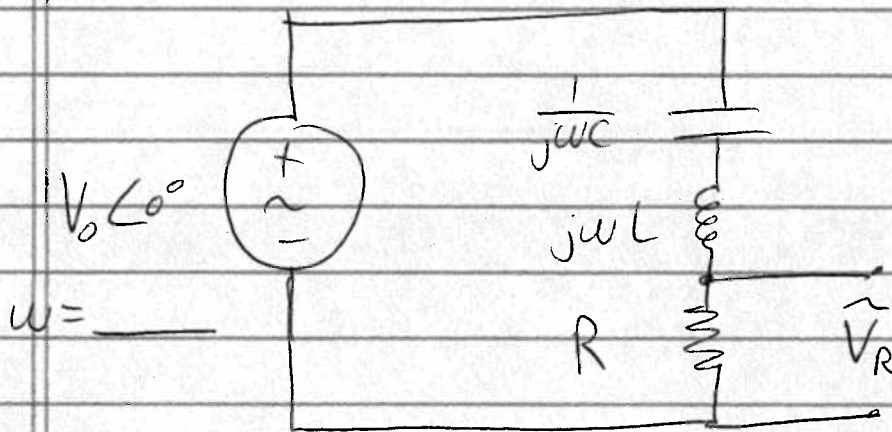Or, starting from scratch, we could convert to phasor (or frequency) domain:



Use Voltage Division:

$$\tilde{V}_R = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} V_0 \angle 0^\circ$$

$$= \frac{R}{\frac{j\omega RC + (-\omega^2 LC) + 1}{j\omega C}} V_0 \angle 0^\circ$$

$$= \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC} V_0 \angle 0^\circ$$

$$= j\omega RC \left(\frac{1}{(1 - \omega^2 LC) + j\omega RC} \right) V_0 \angle 0^\circ$$

Recall: $\frac{1}{a + jb} = \frac{a - jb}{a^2 + b^2}$ \uparrow

$$\tilde{V}_R = j\omega RC \left(\frac{(1-\omega^2 LC) - j\omega RC}{(1-\omega^2 LC)^2 + (\omega RC)^2} \right) V_o \angle 0^\circ$$

~~multiply~~ move the j inside $()$, pull denom. out:

$$\tilde{V}_R = \frac{\omega RC}{(1-\omega^2 LC)^2 + (\omega RC)^2} (j(1-\omega^2 LC) - (-1)\omega RC) V_o \angle 0^\circ$$

$$= \frac{\omega RC}{(1-\omega^2 LC)^2 + (\omega RC)^2} ((\omega RC) + j(1-\omega^2 LC)) V_o \angle 0^\circ$$




to multiply these
we need both in
polar form:

$$\tilde{V}_R = \frac{\omega RC}{(1-\omega^2 LC)^2 + (\omega RC)^2} \left[\sqrt{(\omega RC)^2 + (1-\omega^2 LC)^2} \angle \tan^{-1} \left(\frac{1-\omega^2 LC}{\omega RC} \right) \right] V_o \angle 0^\circ$$

$$\begin{array}{c} \uparrow \\ A \end{array} \quad \begin{array}{c} \uparrow \\ \sqrt{A} \end{array} \quad + \quad \frac{\sqrt{A}}{A} = \frac{1}{\sqrt{A}}$$
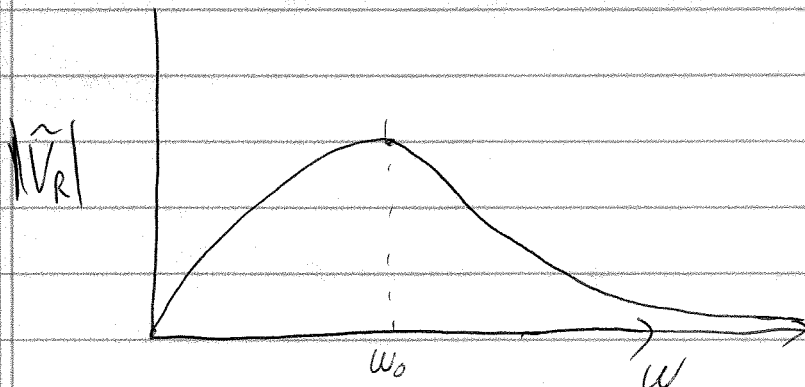
$$\tilde{V}_R = \left[\frac{\omega RC}{\sqrt{(1-\omega^2 LC)^2 + (\omega RC)^2}} \angle \tan^{-1} \left(\frac{1-\omega^2 LC}{\omega RC} \right) \right] V_o \angle 0^\circ$$



$$\omega \rightarrow 0: |\tilde{V}_R| = \frac{0}{\sqrt{0^2 + 1}} = 0$$

$$\omega \rightarrow \infty: |\tilde{V}_R| = \frac{\infty}{\sqrt{\infty^2 + \infty^2}} = \frac{\infty}{\infty^2 + \infty} = 0$$

Peak at $\omega = \omega_0$