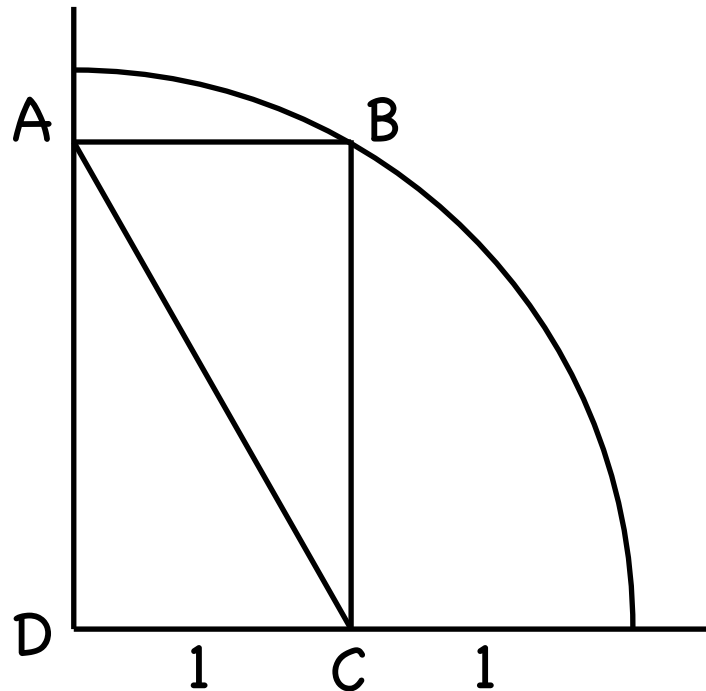


Puzzler


Guess the Diagonal

A rectangle is inscribed in the quadrant of a circle as shown. Given the distances indicated, can you accurately determine the length of the diagonal AC ?



Solution: 2

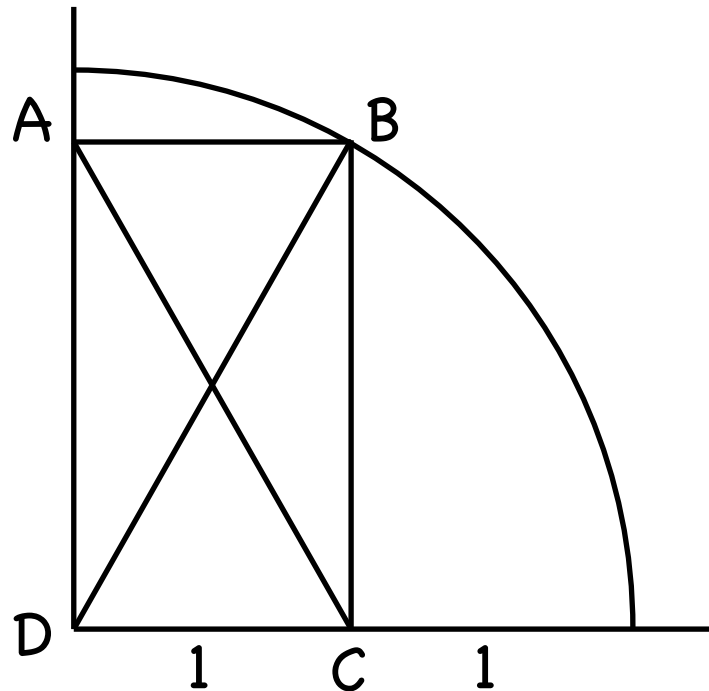Line AC is one diagonal of the rectangle. The other diagonal, BD, is also the radius of the circle, which is equal to 2. Since the two diagonals of the rectangle are equal, then $AC = BD = 2$ units!




Introduction to Audio and Music Engineering

Lecture 13

Topics:

- Using KVL and KCL
- Energy and Power
- Impedance matching
- Introduction to Operational Amplifiers


A larger current divider

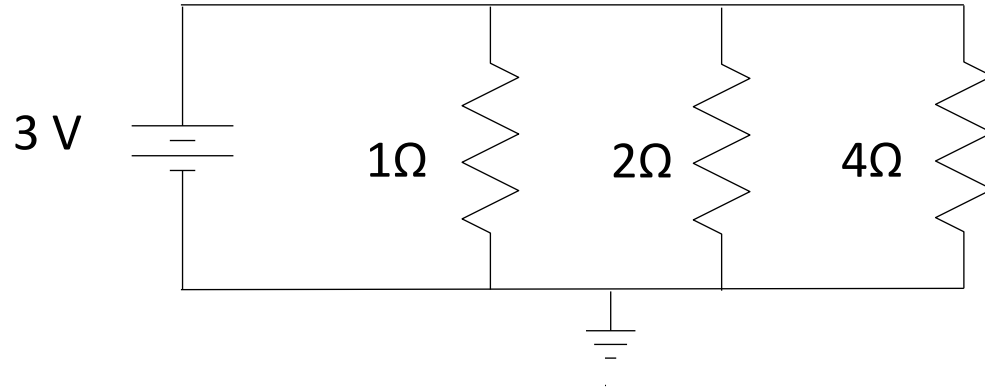

Find the current in each resistor and the total current drawn from the battery.


Combining KCL and KVL to solve more complicated circuits

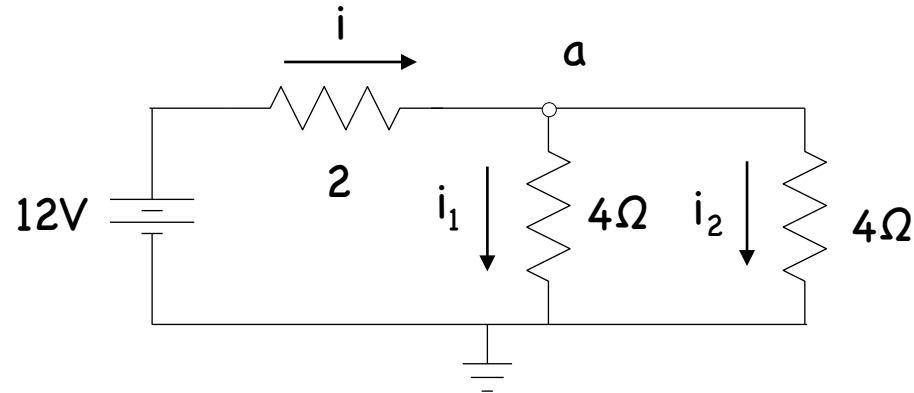Find all of the currents and then find the voltage at point a.



A more complicated circuit: the dc bridge

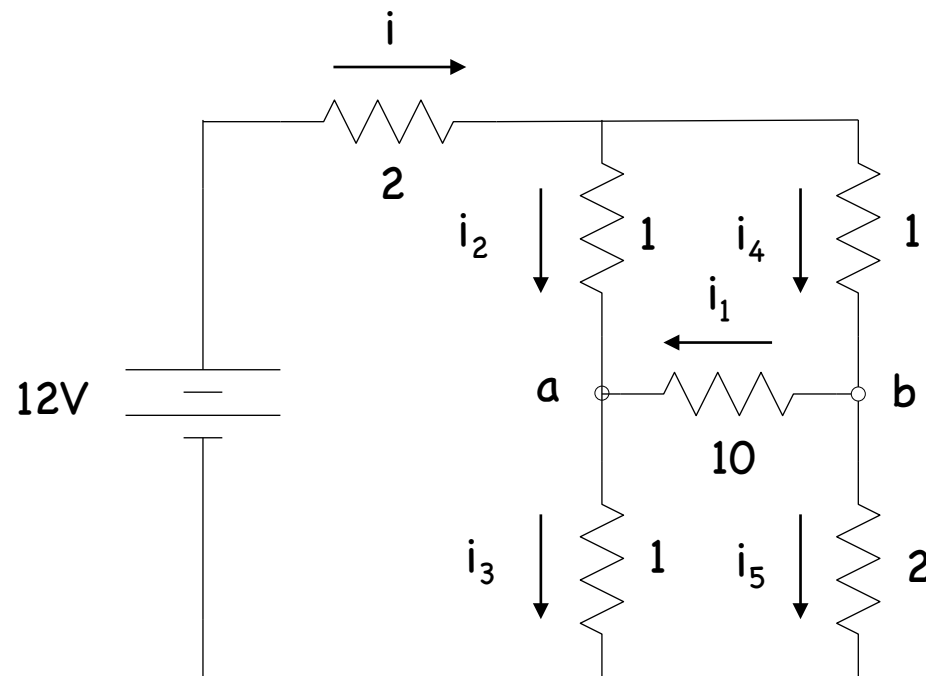Find all of the currents and then find the voltages at points a and b.



Energy and Power

Power \rightarrow Energy (Work) per unit time

Energy is measured in Joules.

(Force \times distance) \rightarrow $\text{kg m/sec}^2 \times \text{m}$



Power is measured in Watts.

1 Watt = 1 Joule/1 sec

Units: Force \times velocity \rightarrow $\text{kg m/sec}^2 \times \text{m/sec}$

Energy/time \rightarrow $\text{kg m}^2/\text{sec}^2 / \text{sec}$

Same amount of work (energy).

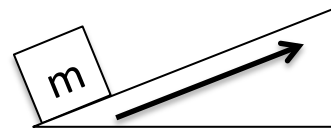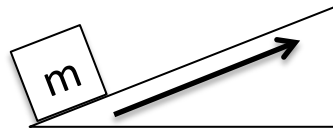

3X Power

... same energy delivered in 1/3 of the time

Laser Bay 2 of the National Ignition Facility


192 laser beams deliver
500 trillion Watts !!
(1000 x US Power consumption)

But only for 3.6×10^{-9} secs
 $(500 \times 10^{12}) \text{ W} \times (3.6 \times 10^{-9}) \text{ sec}$
 $= 1.8 \times 10^6 \text{ Joules}$
 $= 1.8 \text{ Mega Joules (MJ)}$



This sounds like a lot of energy but this is only the amount of energy in about 50 ml of gasoline!

Power in an electrical circuit

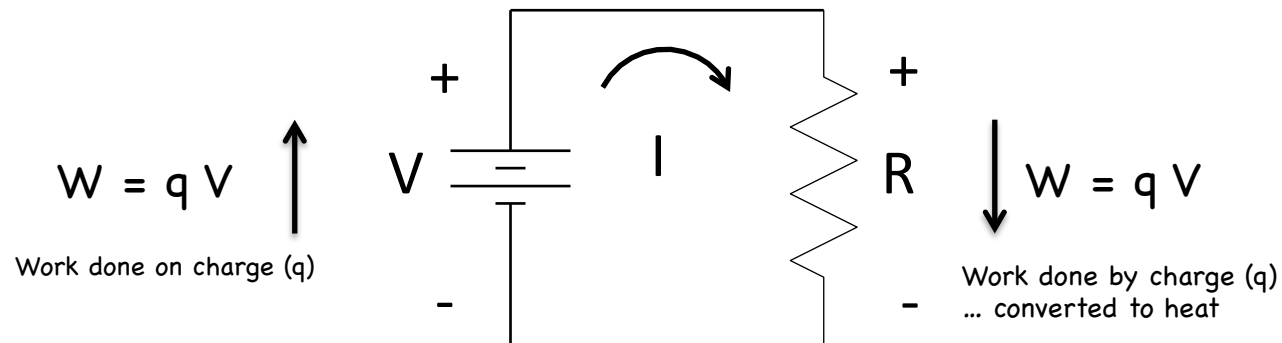

Energy is delivered by the battery and absorbed by the resistor.

Power is Work (Energy) per unit time: Energy/time

$$P = qV/t = I \times V$$

Combine this expression with Ohm's Law to find power dissipated in a resistor, $V = IR$, $I = V/R$



$$P = I \times V = V^2/R = I^2R$$

Note that it doesn't matter which direction the voltage is applied (or the current flows) through a resistor - the power dissipated is the same.

$$P = V^2/R = I^2R$$


Sign Convention: (To be consistent we really should make $P(\text{res})$ negative.)

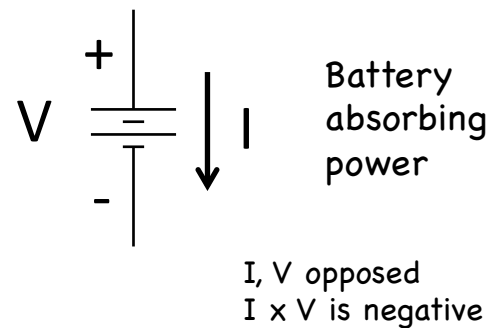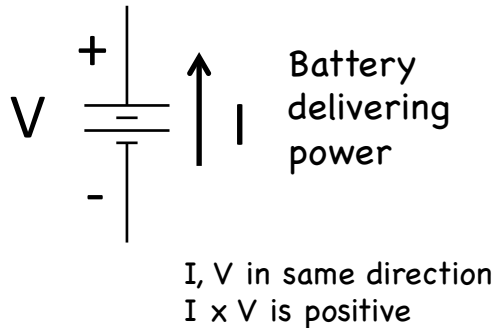$+P \rightarrow$ delivering power; $-P \rightarrow$ absorbing power



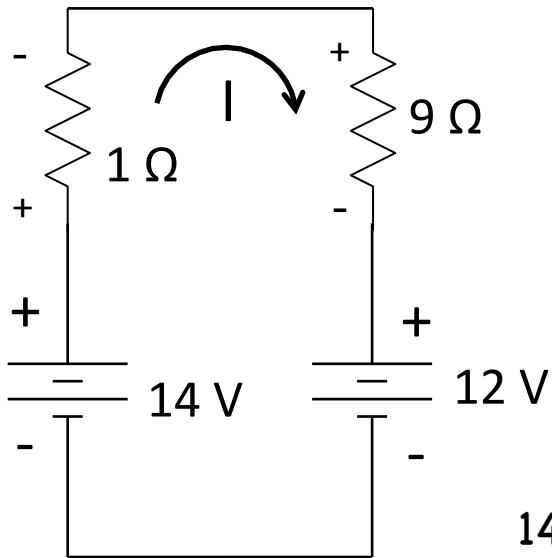Example: Battery Charging circuit

Find the Power absorbed or delivered by each element in the circuit.



$$\text{KVL: } 14 - 1 I - 9 I - 12 = 0$$

$$2 - 10 I = 0 \rightarrow I = 0.2 \text{ A}$$

$$14\text{V battery: } \begin{array}{c} + \\ \uparrow \\ - \end{array} I \quad 14 \times 0.2 = 2.8 \text{ Watts (delivered)}$$

$$12\text{V battery: } \begin{array}{c} + \\ \downarrow \\ - \end{array} I \quad 12 \times (-0.2) = -2.4 \text{ Watts (absorbed)}$$



$$1\Omega \text{ resistor: } \begin{array}{c} - \\ \uparrow \\ + \end{array} I \quad I^2 \times 1 = -0.04 \text{ Watts (absorbed)}$$

$$9\Omega \text{ resistor: } \begin{array}{c} + \\ \downarrow \\ - \end{array} I \quad I^2 \times 9 = -0.36 \text{ Watts (absorbed)}$$

$$\text{Total} = 0$$


Real Voltage and Current Sources

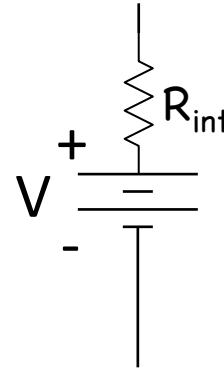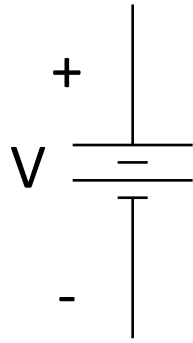Ideal voltage source:
Voltage remains fixed
no matter how much
current is drawn.



A real voltage source has
a small internal resistance.
(AA battery $\sim 0.1 \Omega$)

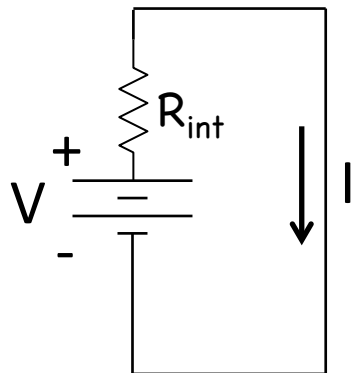
This limits the maximum
current available from the
source.



If we short circuit the source the current flow is limited.

(AA battery: $V = 1.5V$, $R_{int} = 0.1 \Omega$)
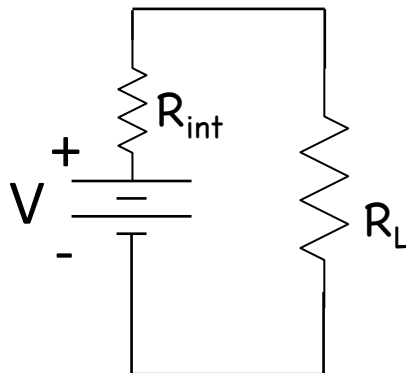
$$I = V/R_{int} = 1.5/0.1 = 15 \text{ Amps}$$




R_L and R_{int} form a voltage divider

Voltage developed across R_L :

$$V_L = V[R_L/(R_L + R_{int})]$$

Impedance Matching

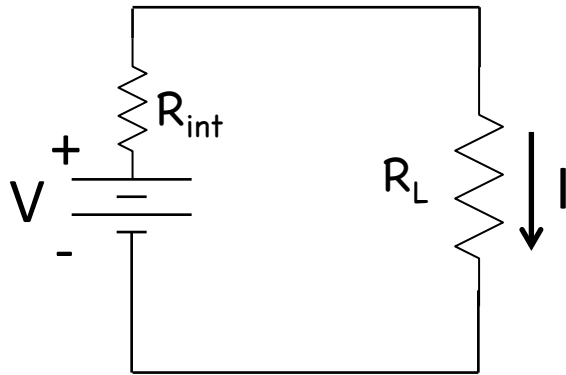

What is the value of R_L that gives maximum power transfer from source to load?


$$P = I \times V_L$$

$$I = V / (R_{int} + R_L)$$

$$V_L = I R_L = V R_L / (R_{int} + R_L)$$

$$\text{so ... } P = V^2 \frac{R_L}{(R_{int} + R_L)^2}$$

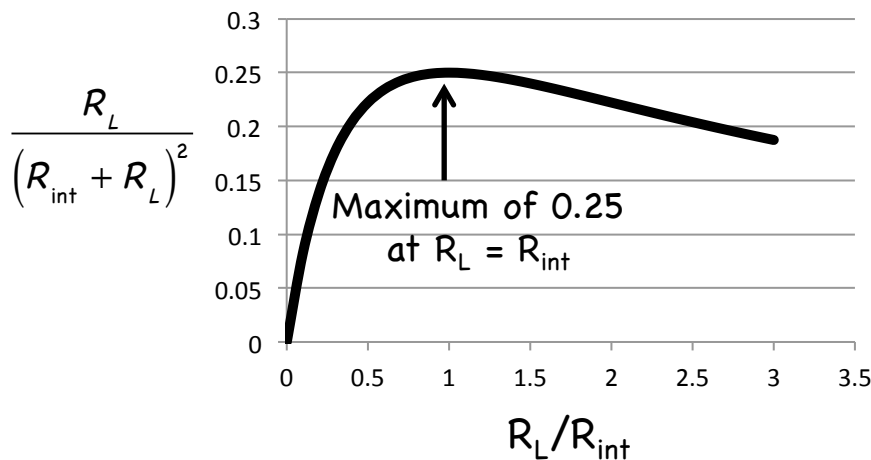Find the value of R_L that makes this expression a maximum.




We can use calculus to find the maximum.

$$\text{set } \frac{d}{dR_L} \left[\frac{R_L}{(R_{int} + R_L)^2} \right] = 0 \quad \text{and solve for } R_L$$


$$\text{sol'n, } R_L = R_{int} \quad P_{\max} = \frac{1}{4} \frac{V^2}{R_{int}}$$

Impedance "matched" for maximum power transfer.

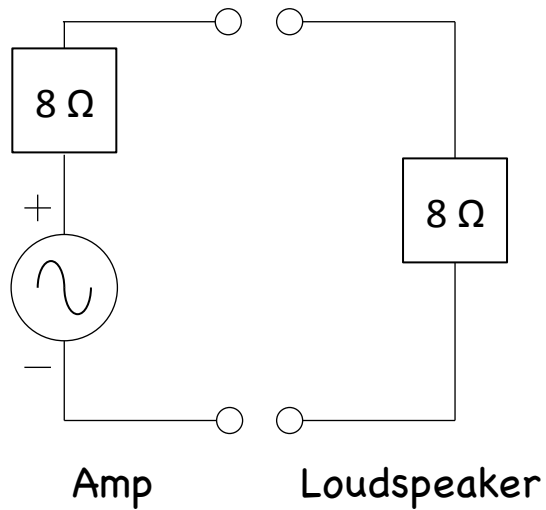Impedance matching: Amplifier & Loudspeaker



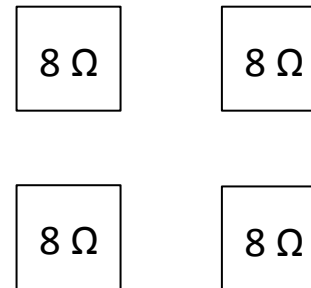
How to connect 4 speakers
(and maintain 8 Ohms)



Maximum power transfer when
loudspeaker and amplifier have the
same impedance

Operational Amplifier

Op-amp – dependent voltage source model

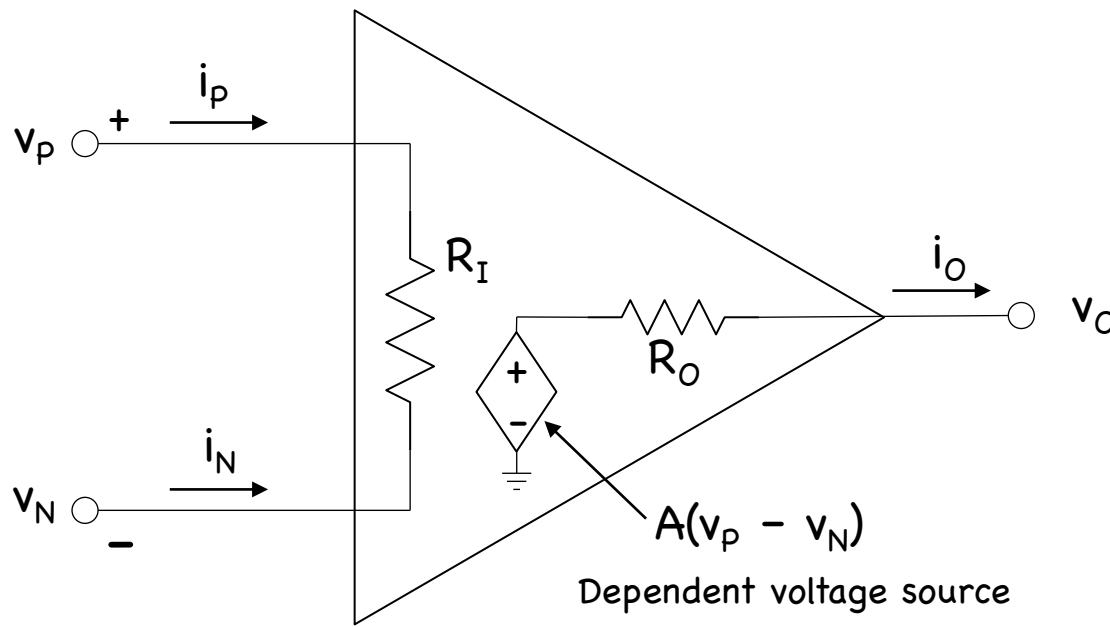

Typical Values

$$10^6 < R_I < 10^{12} \Omega$$

$$10 < R_O < 100 \Omega$$

$$10^5 < A < 10^8$$

Output voltage is limited to power supply voltage and A is large $\rightarrow v_p \approx v_N$


Ideal Op-Amp Model: $A \rightarrow \infty \rightarrow v_p = v_N$ & $i_p = i_N = 0$

The ideal model is adequate for analyzing many op-amp circuits.

Simple Op Amp Circuits

(Analyzed using the idealized op amp model)

Voltage Follower (buffer)

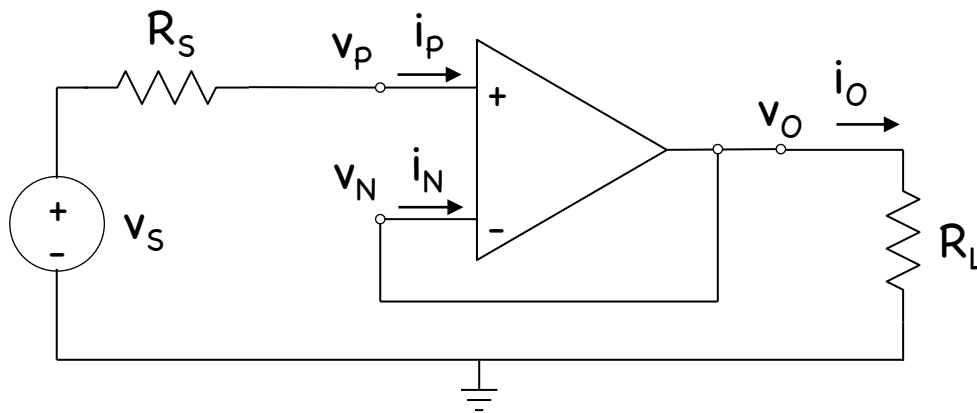

Feedback forces: $v_N = v_O$

$i_P = 0$, no voltage drop across R_S

then, $v_P = v_S$

ideal op amp model $\rightarrow v_P = v_N$

therefore $v_O = v_S$


The output voltage simply “follows” the input voltage.

However there is no current drawn from the source and the output voltage is independent of the source resistance. (The source is buffered.)

Why can't you plug headphones directly into an electric guitar ... and hear anything?

You need a buffer amplifier.

Inverting Amplifier

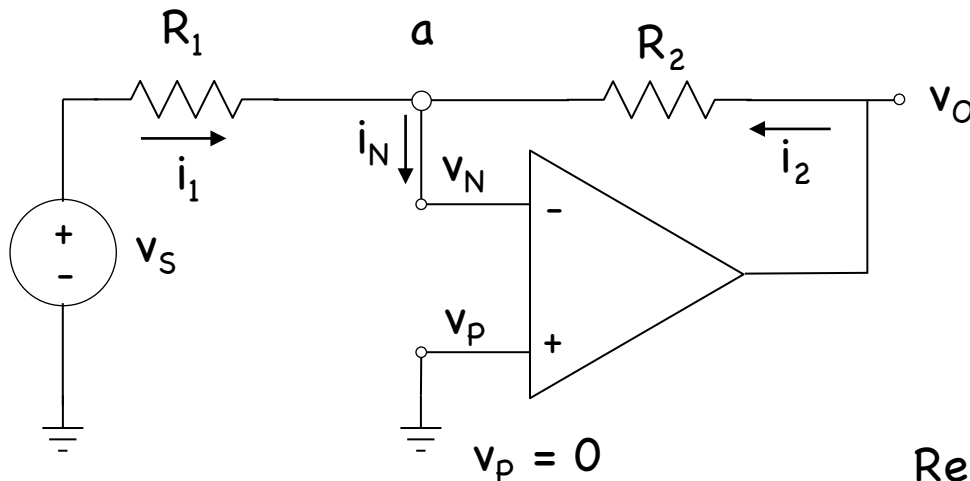

Apply KCL at node a:



$$i_1 + i_2 - i_N = 0$$

$$\Rightarrow \frac{v_s - v_N}{R_1} + \frac{v_o - v_N}{R_2} - i_N = 0$$

Remember that ... $v_p = v_N$ & $i_p = i_N = 0$

We made $v_p = 0$, and $v_p = v_N$ so $v_N = 0$
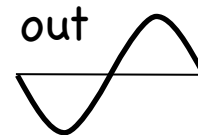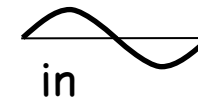
$$\frac{v_s}{R_1} + \frac{v_o}{R_2} = 0 \quad \text{so ...} \quad v_o = -\frac{R_2}{R_1} v_s$$



Control the gain by adjusting R_2/R_1 .